
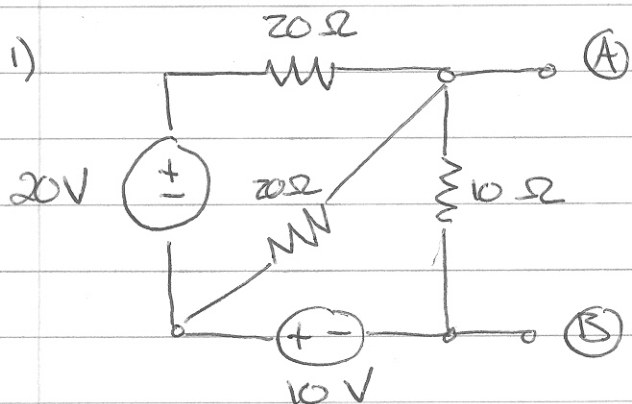


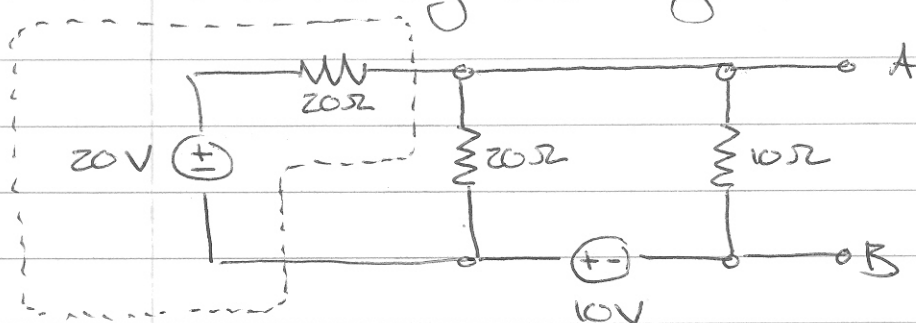


+1 point per
step, no need to
explicitly show each
w/ proper results!

ii) Redrawing the original circuit:




$V_{oc} = 20V$

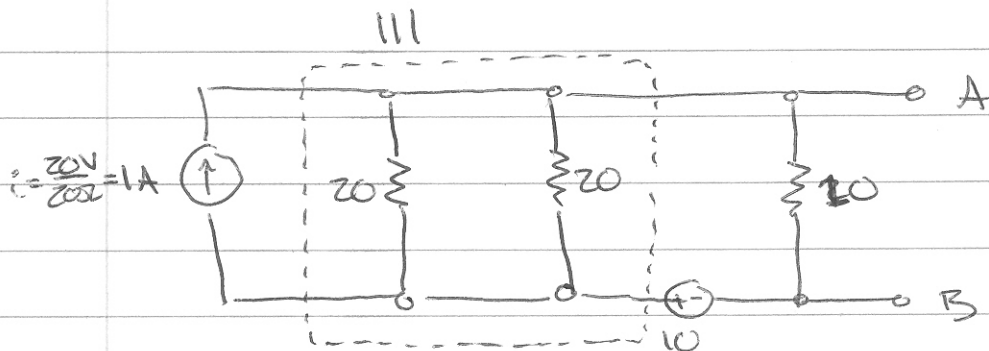




+1 (source
transform)
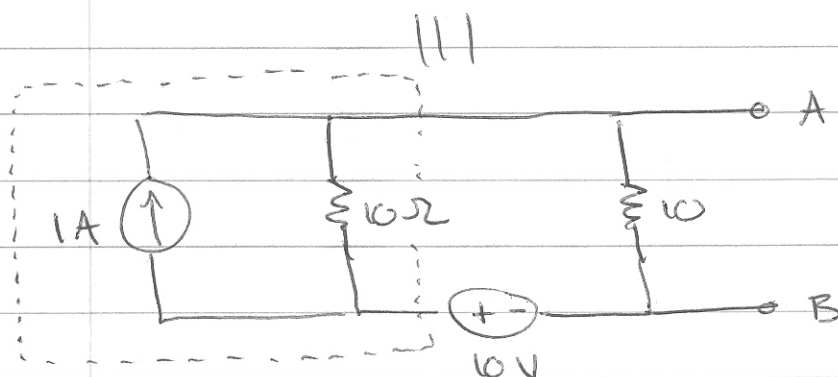
$$20\Omega \parallel 20\Omega = \frac{(20)(20)}{20+20} = \frac{400}{40} = 10\Omega$$




+1 (combining
R's)

1 cont.)

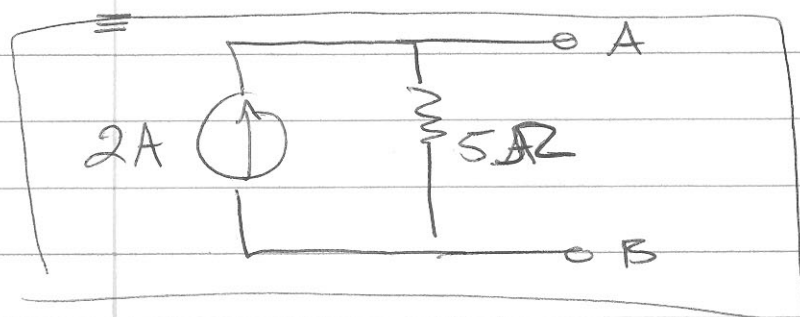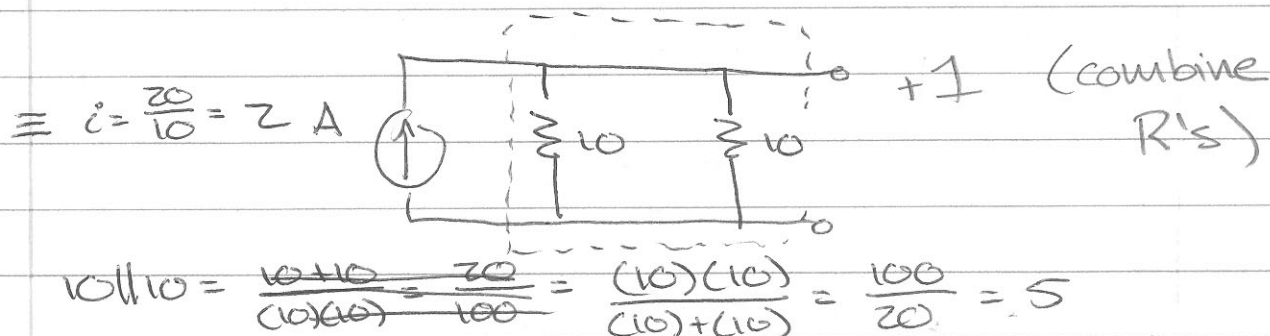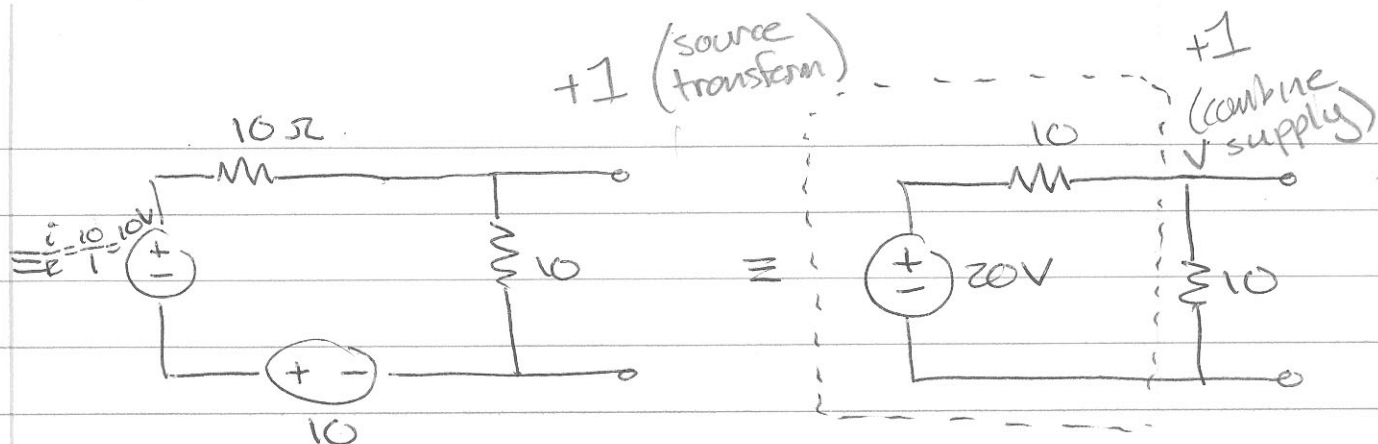

+1 (show N-equivalent circuit)

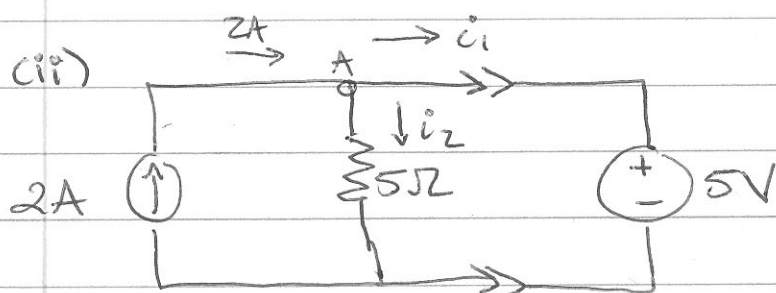


KCL @ A: $2A = i_1 + i_2$

$i_2 = \frac{5}{5} = 1A \Rightarrow 2A = 1A + i_2 \Rightarrow i_2 = 1A$

$P = iV \Rightarrow P = (1A)(5V) = \boxed{5W} +1$

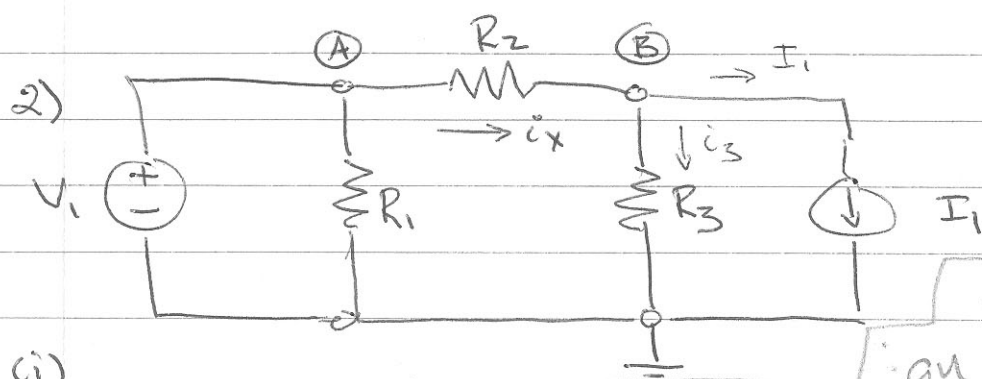$P_{is} (+) \Rightarrow$ the voltage supply absorbs power +1



Need to give each equation for the nodes (A)

then supply an explanation (+2)

(not necessarily an eq.) to get V_B .

(i)

$$V_A - 0 = V_1 \Rightarrow V_A = V_1 \quad +1$$

$$i_x - i_3 - I_1 = 0, \quad i_x = \frac{V_A - V_B}{R_2}, \quad i_3 = \frac{0 - V_B}{R_3}$$

$$\Rightarrow \frac{V_A - V_B}{R_2} - \frac{V_B}{R_3} - I_1 = 0 \quad +1$$

(subbing in $V_A = V_1$)


$$\Rightarrow \left[\frac{V_1 - V_B}{R_2} - \frac{V_B}{R_3} - I_1 = 0 \right] \text{ and we solve this for } V_B \quad +2$$

(ii) as noted $i_x = \frac{V_A - V_B}{R_2} \Rightarrow i_x = \frac{V_1 - V_B}{R_2}$

$$\therefore \frac{V_1 - V_B}{R_2} - \frac{V_B}{R_3} - I_1 = 0 \Rightarrow i_x - \frac{V_B}{R_3} - I_1 = 0$$

$$\Rightarrow \left[i_x = I_1 + \frac{V_B}{R_3} \right] \text{ \& } V_B \text{ found above!}$$

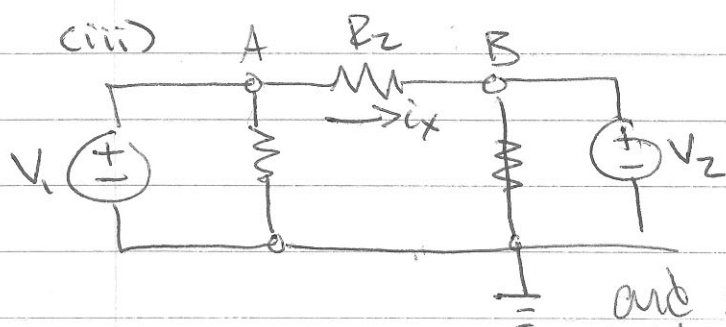Any approp. eq. for i_x w/ respect to work in (i) +2




$$V_B = V_2 \quad +1$$

$\Rightarrow$ we no longer need (i)

and simply solve Ohm's law
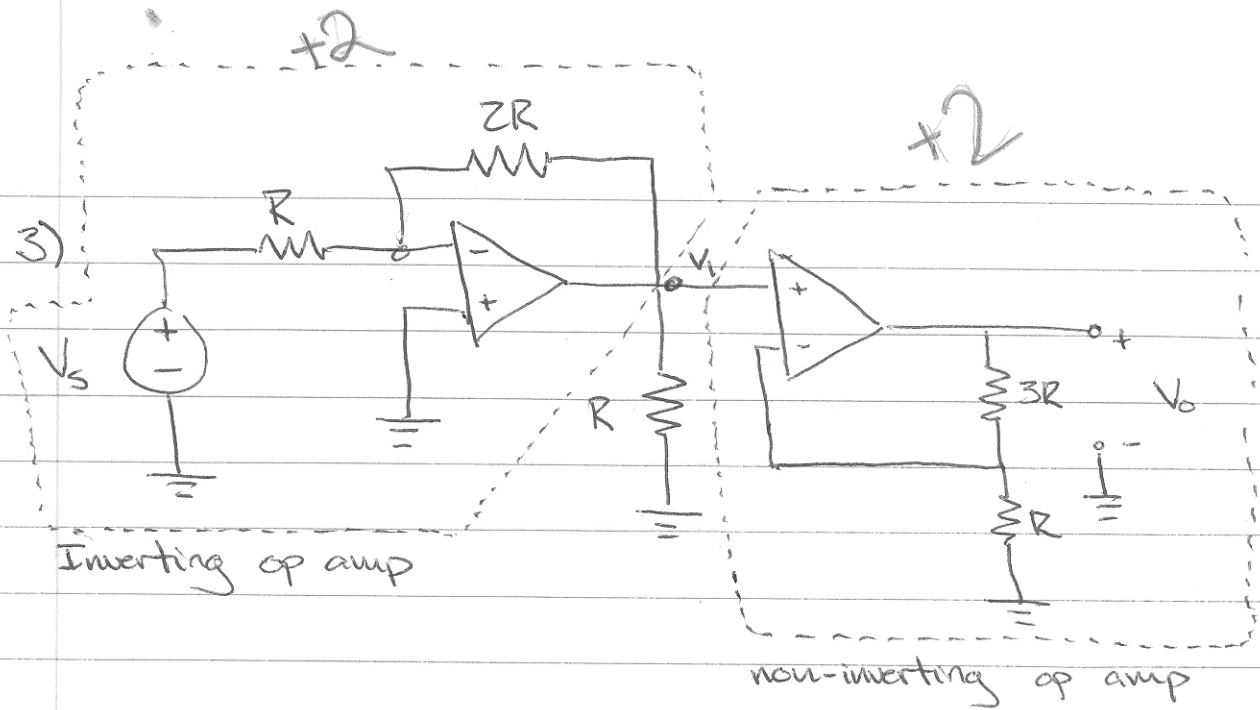
$$\frac{V_A - V_B}{R_2} = i_x = \frac{V_1 - V_2}{R_2} \quad +1$$



cii) inverting op amp: $+2$


$$\frac{V_1}{V_s} = -\left(\frac{2R}{R}\right) \Rightarrow \cancel{V_1 = -2V_s} \quad \text{(this is the input voltage to the next block!)}$$

$$V_1 = -2V_s$$

non-inverting op amp: $+2$

$$\frac{V_o}{V_1} = \frac{(3R + R)}{R} \Rightarrow V_o = 4V_1$$
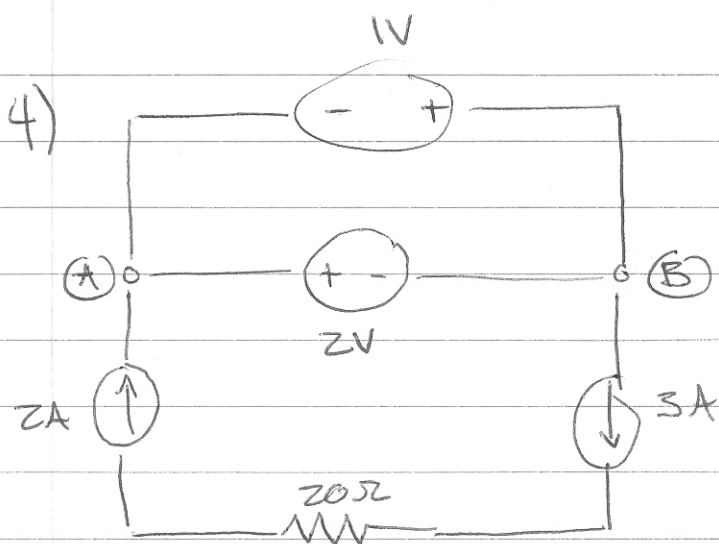
$$\therefore V_o = 4(-2)V_s = \boxed{-8V_s = V_o}$$



if note this
only +1

(Nodes A & B are both at 2V and 1V simultaneously!)

∴ KVL is violated! +1/+2 (if note this only +2)

(The resistor loop connecting A & B is at 3A and 2A at the same time.)

∴ KCL is violated! +1/+2

(if this only)
+2

if this only
+1