

MAE140 HW1 Solutions

1.16)

$$i(t) = 20 \sin(1000t) \text{ mA}, v(t) = 100 \sin(1000t) \text{ V}$$

$$\text{Power} = iv = (.02 * 100) \sin^2(1000t) \text{ Watts}$$

$$\text{Max} = 2 \text{ Watts}$$

$$\text{Min} = 0 \text{ Watts}$$

1.21)

a) $P = 11\text{V} * -1.1\text{A} = -12.1 \text{ Watts from A to B} = \mathbf{12.1 \text{ Watts from B to A}}$

b) $P = 80\text{V} * .02 \text{ A} = \mathbf{1.6 \text{ Watts from A to B}}$

c) $P = -120\text{V} * -.012 \text{ A} = \mathbf{1.44 \text{ Watts from A to B}}$

d) $P = -1.5\text{V} * -0.0006 \text{ A} = \mathbf{0.0009 \text{ Watts} = 900\mu\text{W from A to B}}$

MAE140 HW1 Solutions

1.23)

Method 1)

Power is Balanced (for convenience flip arrow on i_1 and label it +2A)

$$P_1 = 20V * 2A = 40W \text{ (Sourcing Power)}$$

$$P_1 - P_2 - P_3 - P_4 - P_5 - P_6 = 0 \text{ (All other elements are absorbing power)}$$

$$P_4 = 40 - 20 - 10 - 2.5 - 2.5$$

$$\mathbf{P_4 = 5 Watts Absorbing}$$
 (Absorbing because i_4 is >0 from v_{4+} to v_{4-})

Method 2)

$$P_2 = 20W = i_v = 2A * V \rightarrow v_2 = 10V$$

$$P_{5,6} \text{ in parallel absorb 5 Watts @ } 1A \rightarrow v_{5,6} = 5V$$

$$v_4 = v_2 - v_{5,6} = 5V$$

$$i_4 = 1A \text{ (given)}$$

$$P_4 = 5V * 1A = \mathbf{5W Absorbing}$$

MAE140 HW1 Solutions

2.3)

$$\text{Conductance} = 1\text{mS} = 1 \cdot 10^{-3} \text{ S}$$

$$\text{Resistance} = 1/\text{Conductance} = 1000\Omega = 1\text{k}\Omega$$

$$I = V/R = 9\text{V}/1\text{k}\Omega = .009\text{A} = 9\text{mA}$$

2.7)


$$10\text{ k}\Omega \text{ with } P_{\text{max}} = 1/8 \text{ W}$$

$$P_{\text{max}} = (V_{\text{max}})^2/R \rightarrow V_{\text{max}} = \sqrt{\frac{10\text{k}\Omega \text{W}}{8}} = 35.36\text{V}$$

MAE140 HW1 Solutions

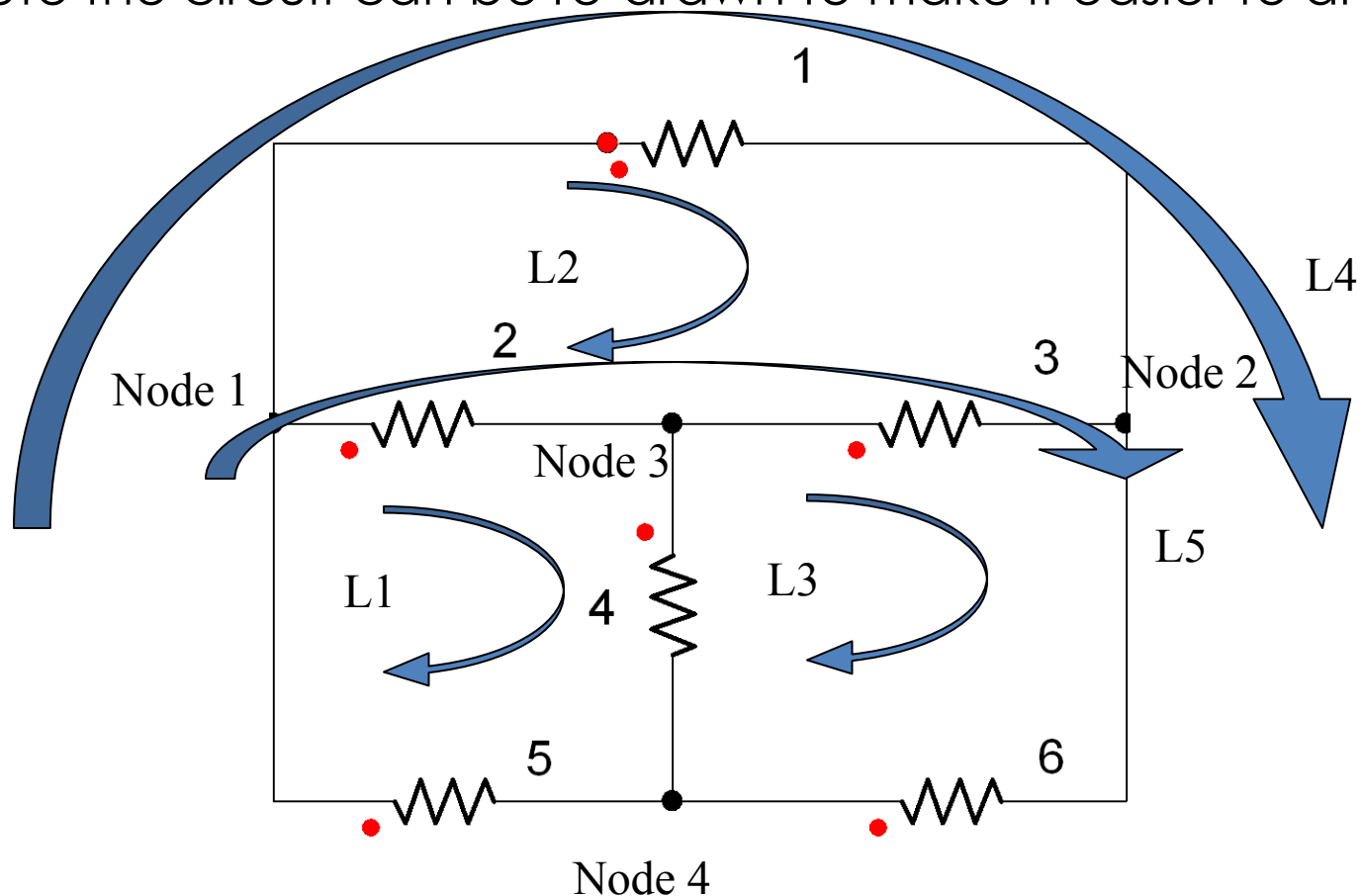2.13)

Note the circuit can be re-drawn to make it easier to analyze



MAE140 HW1 Solutions

2.13) Continued

B) No elements are in series or parallel

C) KVL

$$V_2 - V_3 - V_6 - V_5 = 0$$

$$V_1 + V_3 - V_2 = 0$$

$$V_3 - V_4 + V_6 = 0$$

$$V_2 - V_4 - V_5 = 0$$

$$V_1 - V_6 - V_5 = 0$$


KCL

$$i_1 + i_2 + i_5 = 0$$

$$i_2 + i_4 + i_3 = 0$$


$$i_1 - i_3 + i_6 = 0$$

$$i_5 - i_4 - i_6 = 0$$

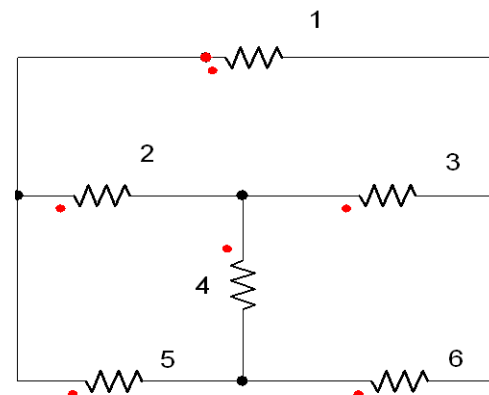

This is more equations than you will actually need to solve the circuit

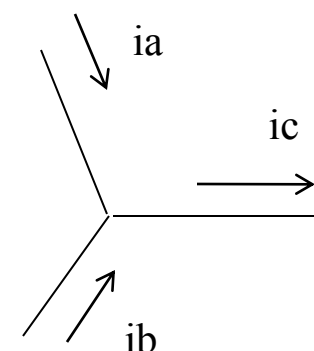
If you are having trouble with determining the signs, remember KCL is just saying charge is **conserved**! All current entering a node exits the node.



$$i_c = i_a + i_b$$

Problem

2-16

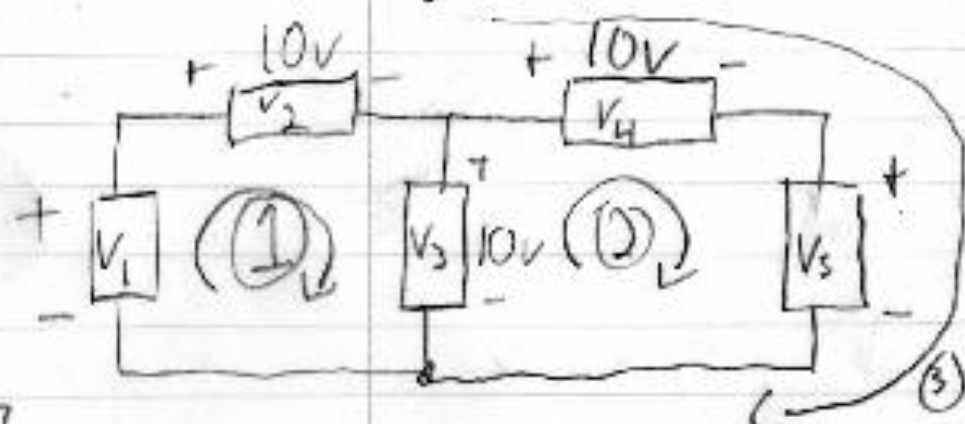

Note See
Slide 16 of Course
Slides

Loop 1

KVL Gives: $-V_1 + V_2 + V_3 = 0 \Rightarrow V_1 = 20 \text{ Volts}$

Loop 2

KVL Gives: $-V_3 + V_4 + V_5 = 0 \Rightarrow V_5 = V_3 - V_4 = 0 \text{ Volts}$

Use as a Check (optional)

Loop 3


KVL Gives: $-V_1 + V_2 + V_4 + V_5 = 0$
 $-20 + 10 + 10 + 0 = 0$



MAE140 HW1 Solutions

2.22)

A:

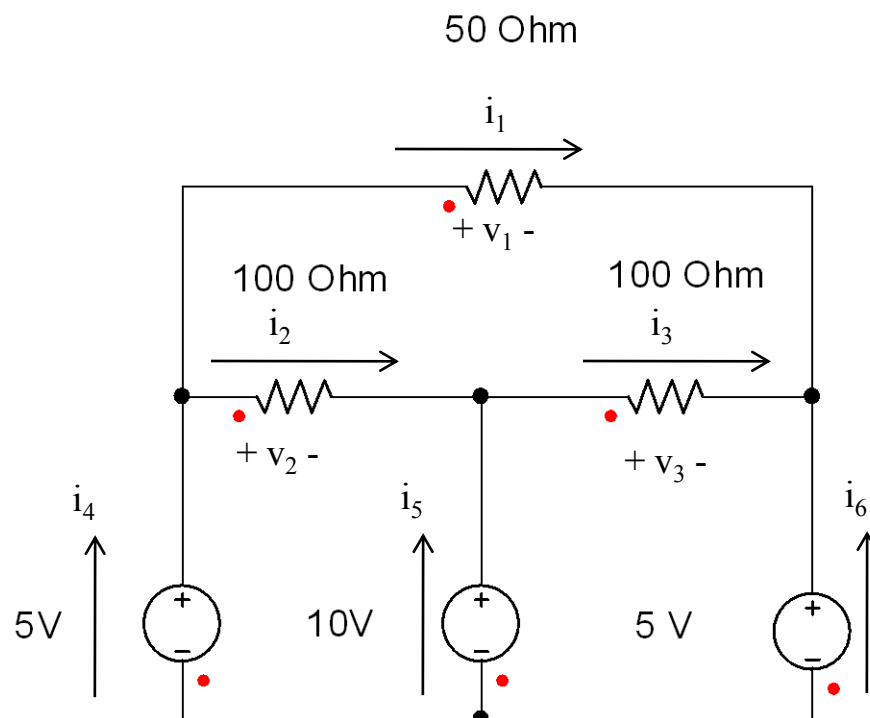

B: 1) $v_1 - v_2 - v_3 = 0$

2) $v_2 - 5V + 10V = 0$

3) $v_3 - 10V + 5V = 0$

$$\begin{bmatrix} 1 & -1 & -1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -5 \\ 5 \end{bmatrix} \rightarrow \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -5 \\ 5 \end{bmatrix}$$

*The fact that $b = x$ is a coincidence! (It means 1 is an eigenvalue)

MAE140 HW1 Solutions

2.22) continued

$$c: i_1 = v_1/50\Omega = 0A$$

$$i_2 = v_2/100\Omega = -50mA$$

$$i_3 = v_3/100\Omega = 50mA$$

d:

$$i_4 = i_2 + i_1 = -50mA$$

$$i_5 = i_3 - i_2 = 100mA$$

$$i_6 = -i_3 - i_1 = -50mA$$

CHECK! Sum All Currents: Should Equal Zero

$$0 + -50 + 50 - 50 + 100 - 50 = 0 \quad \boxed{\checkmark}$$

MAE140 HW1 Solutions

2.29)

a) $100 + (200 \parallel 50) + 50 = 100 + (200 \cdot 50) / (200 + 50) + 50 = \mathbf{190 \Omega}$

b) $100 + 50 = \mathbf{150 \Omega}$

2.34)

Remember, an **ideal** current source outputs the stated current no matter what! (Infinite power), so 5Ω resistor does nothing when looking at the voltage from A to B because 5 A always goes through R_{AB} . Therefore, $V_{AB} = 50V$

For completeness, look at the Thevenin equivalent

$$V_{oc} = 50V, I_{sc} = 5A, R_t = V_{oc} / I_{sc} = 10 \Omega$$

