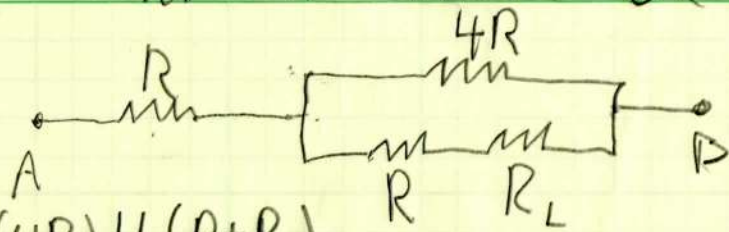


2.38 Redraw



$$\Rightarrow R_{AB} = R + (4R) \parallel (R + R_L)$$

$$= R + \frac{4R^2 + 4RR_L}{5R + R_L}$$

$$= \frac{5R^2 + RR_L + 4R^2 + 4RR_L}{5R + R_L}$$

$$R_{AB} = \frac{9R^2 + 5RR_L}{5R + R_L} = R_{AB} \cdot \frac{5R + R_L}{5R + R_L}$$


Now we have

$$5R_{AB}R + R_{AB}R_L = 9R^2 + 5RR_L$$

Let $R_{AB} = R_L$ and substitute in: $R_L^2 = 9R^2$

$$\Rightarrow \boxed{R = R_L/3} \quad \text{This } R \text{ value will make } R_L = R_{AB}$$

2.41.

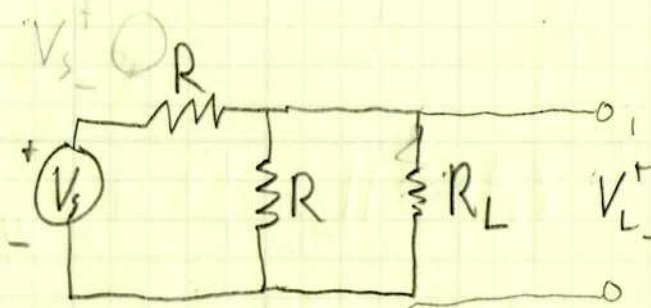
To use Voltage divider First find R_{eq} across V_L : $R_{eq} = \frac{R \cdot R_L}{R + R_L}$ rule!

Now apply Voltage divider rule!


$$V_L = \left(\frac{R_{eq}}{R + R_{eq}} \right) V_S$$

Substitute $R_{eq} = \frac{R R_L}{R + R_L}$ and do some algebra* to get!

$$\boxed{V_L = \left(\frac{R_L}{R + 2R_L} \right) V_S}$$

* you may want to investigate Matlabs Symbolic toolbox.

2.45

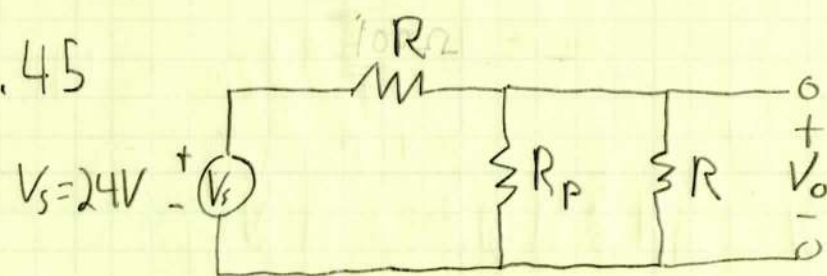

$R = 100\Omega$, R_p is a potentiometer

$$0 < R_p < 100\Omega$$

Trivial Solution: $R_p = 0$

$R_p = 0$, all current flows through R_p which now acts as a wire
 $\Rightarrow V_o = 0V$

Now let $R_p = 100\Omega$ Use voltage division to get


$$V_o = \left(\frac{R_p}{R + 2R_p} \right) V_s \quad (\text{see 2.41 solution})$$

Sub in values to get $V_o = 8V$

also notice if $R_p = 0$ then $V_o = 0V$

$$\Rightarrow 0V < V_o < 8V$$

2.49

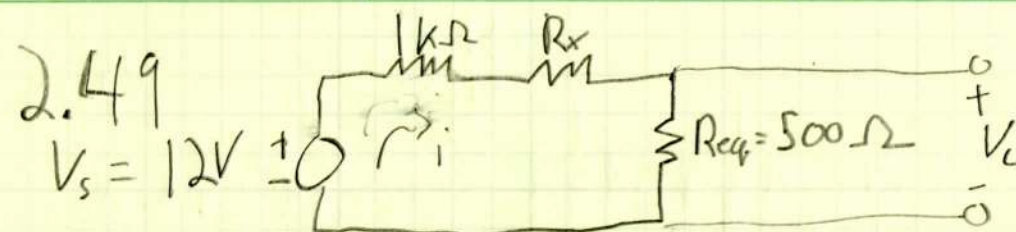


Simple Voltage Divider.

$$V_L = i R_{eq} = \left(\frac{R_{eq}}{1k\Omega + R_x + R_{eq}} \right) \cdot V_s$$

$$\text{Solve for } R_x = R_{eq} \cdot \frac{V_s}{V_L} - 1k\Omega - R_{eq}$$

$$R_x = 500\Omega$$

2.51

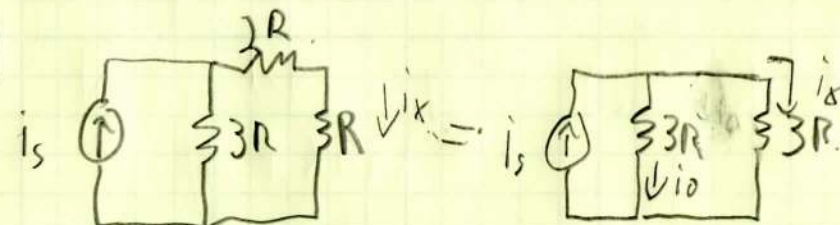




$$\text{KCL } i_s = i_o + i_x \text{ but } i_o = i_x \text{ so } i_x = i_s/2$$

Reduce circuit further to see

$$i_s \uparrow \left\{ \begin{array}{l} V_x \\ - \end{array} \right\} \frac{3R \cdot 3R}{3R + 3R} = \frac{3}{2} R \quad V_x = iR = \frac{3}{2} R i_s$$

$$\text{Alternatively } V_x = 3R \cdot i_x = 3R \cdot \frac{i_s}{2} = \frac{3}{2} R i_s$$

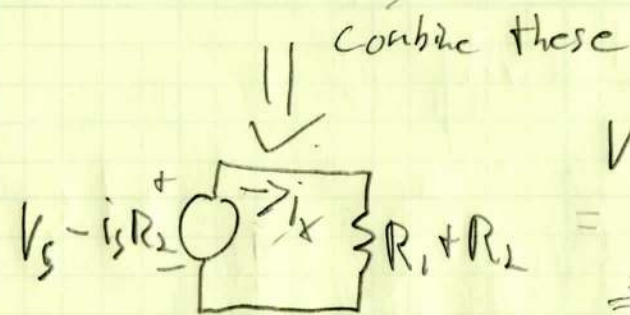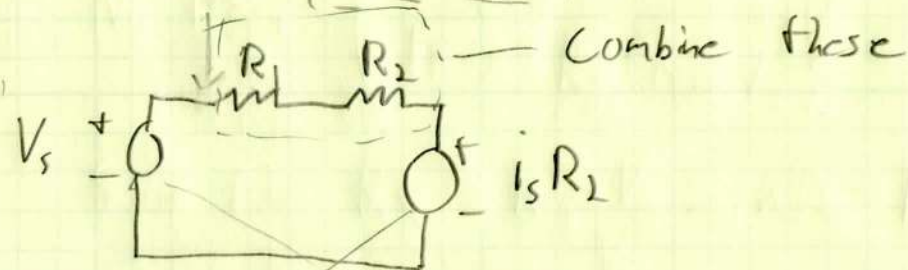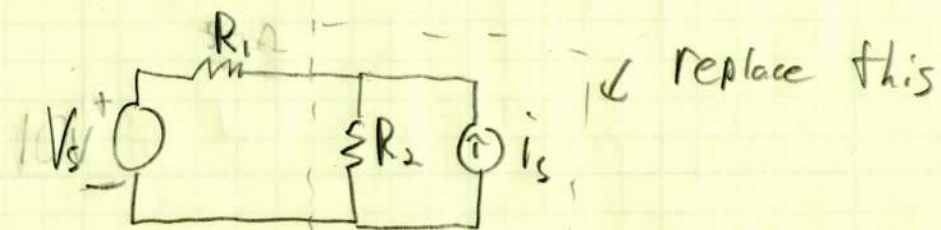
2.55 Note! (more than one way to go about this.)





$$V = iR \Rightarrow i = \frac{V}{R}$$

$$\Rightarrow i_x = \frac{V_s - i_s R_2}{R_1 + R_2} = 50 \text{ mA}$$


2.57

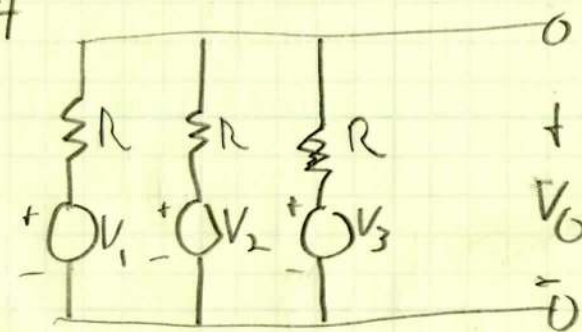


Replace With Current Source

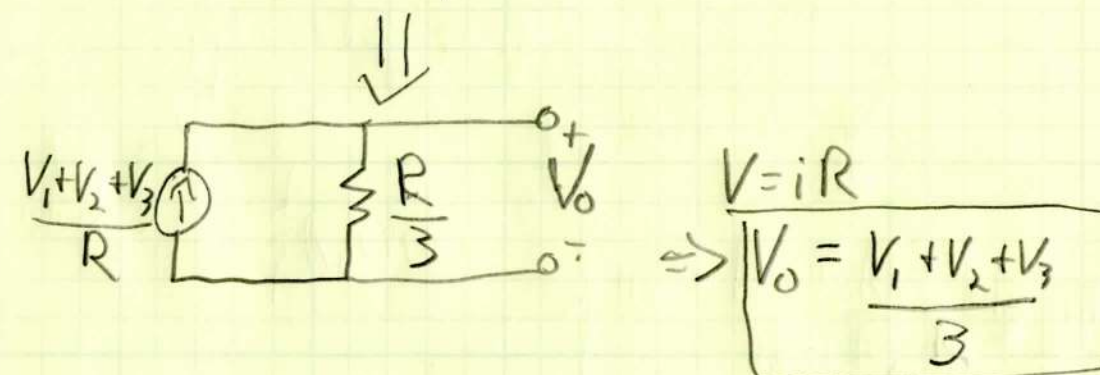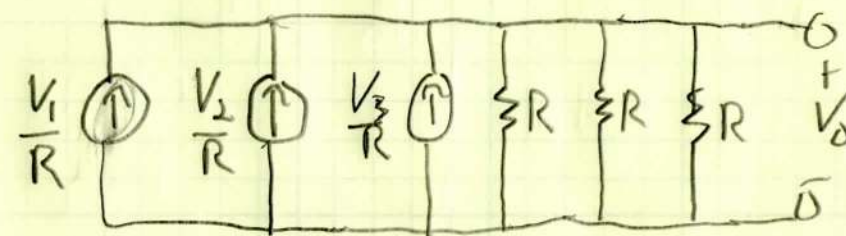

3.35 a. Open Circuit Voltage V_{oc} :

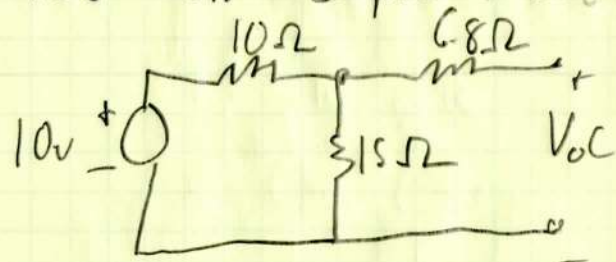

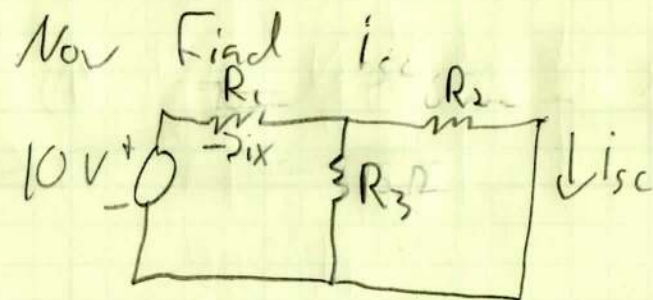
Use Voltage divider $V_{oc} = \left(\frac{15\Omega}{10\Omega + 15\Omega} \right) \cdot 10V = 6V$




$$i_x = \frac{10V}{\left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right)} = 0.681 \text{ mA}$$

$$i_{sc} = \frac{R_3}{R_2 + R_3} \cdot i_x = 0.469 \text{ mA}$$

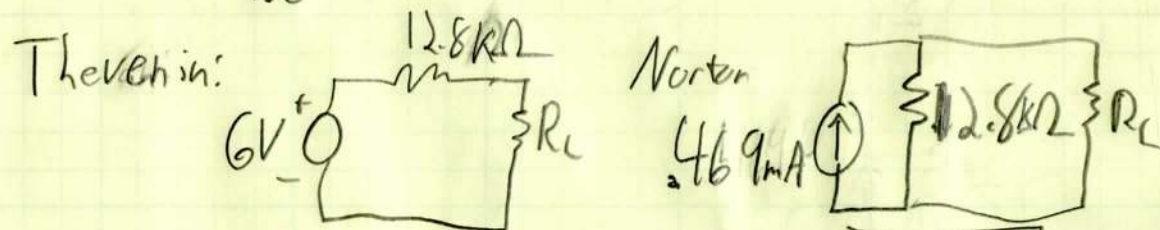
$$R_{TN} = \frac{V_{oc}}{i_{sc}} = 12.8 \text{ k}\Omega$$



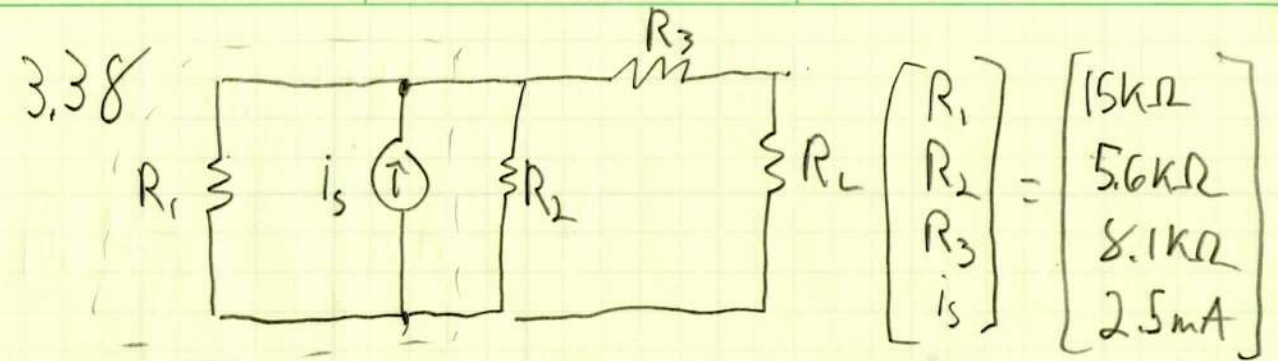b. Find i_L ; $i_L = \frac{V}{R} = \frac{6V}{12.8 \text{ k}\Omega + R_L} = 1 \text{ mA}$



Using Circuit Reduction from Chpt. 2:

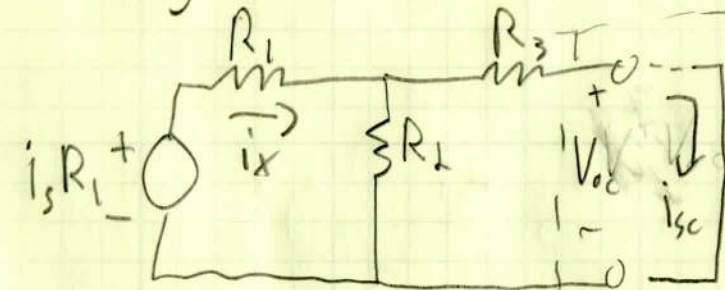

Doesn't this look a lot like the last problem. Maybe you could use the same Matlab Script!


$$V_{oc} = \left(\frac{R_2}{R_1 + R_2} \right) i_s R_1 = 10.19 \text{ V}$$

Now Short Circuit

$$i_x = \frac{i_s R_1}{\left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right)} = 2.05 \text{ mA}$$

$$i_{sc} = \left(\frac{R_2}{R_2 + R_3} \right) \cdot i_x = 0.837 \text{ mA}$$
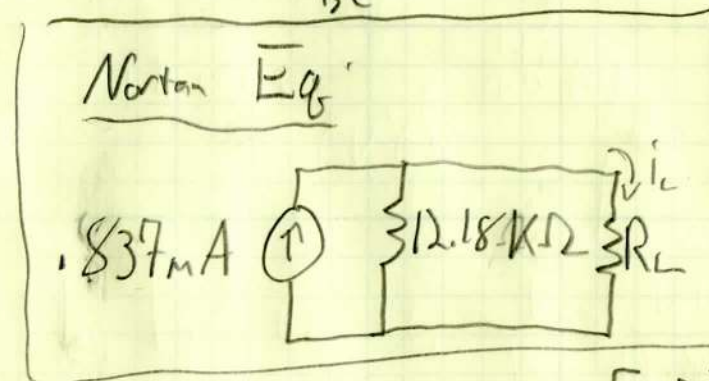
$$R_N = \frac{V_{oc}}{i_{sc}} = 12.18 \text{ k}\Omega$$




Current Division

$$i_L = \left[\frac{1/R_L}{1/R_L + 1/R_N} \right] i_{sc}$$

$$= \left[\frac{R_N}{R_N + R_L} \right] i_{sc}$$

For $R_L = \begin{bmatrix} 4.7 \\ 15 \\ 68 \end{bmatrix} \text{ k}\Omega$ $i_L = \begin{bmatrix} 0.64 \\ 0.38 \\ 0.13 \end{bmatrix} \text{ mA}$

3.42

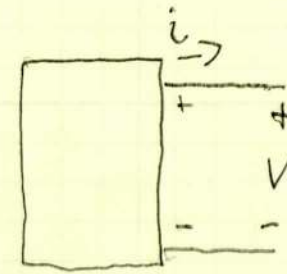


Solve by finding Thévenin equivalent! (Norton could be used too)

First, $V=0V$ gives us $i_{sc} \Rightarrow \underline{i_{sc}=1A}$

Now, we need V_T and R_T .

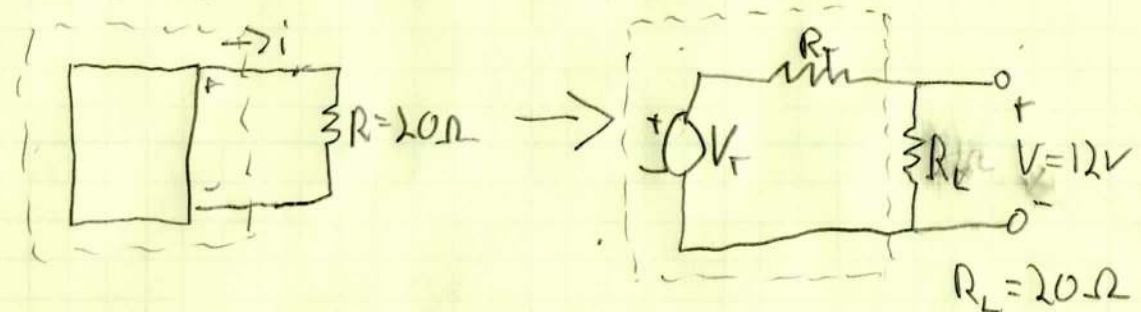Replace Car Port with Thévenin equivalent and connect to the 20Ω resistor!




We know $\frac{V_T}{R_T} = i_{sc} = 1A$ (1)

And we can write $V_T - iR_T - \underbrace{iR_L}_{=V=12V} = 0$; where $i = \frac{V}{R_L} = \frac{12V}{20\Omega}$

$\Rightarrow \frac{V_T - 12V}{R_T} = \frac{12}{20}$ (2)

Solve (1) and (2) to get $\underline{R_T=30\Omega}$; $V_T=30V$

Connect Battery

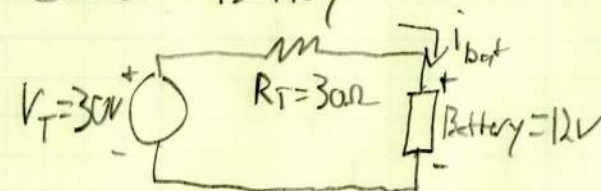

$$i_{bat} = \frac{V_T - V_{bat}}{R_T} = \frac{30V - 12V}{30\Omega} = 600mA$$