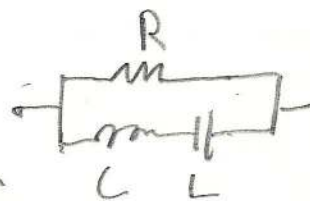


10. 3, 7, 9, 11, 13, 19, 21, 23, 30

10.3 Find Z_{eq} of

$$R = 2k\Omega, L = .4, C = 100nF$$

$$Z_{eq} = (Z_C + Z_L) \parallel R$$

$$= \left(\frac{1}{Cs} + Ls \right) \parallel R$$

$$= \frac{Cs + LCs^2}{Cs} \parallel R$$

$$= \frac{R(CLs^2 + 1)}{CLs^2 + CRs + 1}$$

$$CLs^2 + CRs + 1$$


$$= \frac{2,000(s^2 + 25 \times 10^6)}{s^2 + 5,000s + 25 \times 10^6}$$

$$s^2 + 5,000s + 25 \times 10^6$$

Zeros: $s = \sqrt{-25 \times 10^6} \Rightarrow s = \pm 5,000j$

Poles: $s = -2,500 \pm 4,330j$

10.7

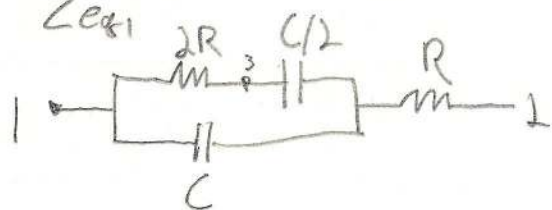For Z_{eq1} 

$$Z_{eq1} = \left(\frac{1}{Cs} \right) \parallel \left(2R + \frac{2}{Cs} \right) + R$$

$$= \frac{\frac{1}{Cs} \cdot \frac{2RCs+2}{Cs}}{\frac{1}{Cs} + \frac{2RCs+2}{Cs}} + R$$

$$= \frac{2RCs^{\cancel{2}} + 2\cancel{C}}{\cancel{Cs^{\cancel{2}}} + 2RC\cancel{s^{\cancel{2}}} + 2Cs^{\cancel{2}}} + R$$

$$= \frac{2RCs + 2}{Cs + 2RCs^2 + 2Cs} + \frac{CsR(2RCs + 3)}{Cs(2RCs + 3)}$$

$$= \frac{CRs(2CRs + 5) + 2}{Cs(2RCs + 3)}$$


$$= \frac{(2CRs+1)(CRs+2)}{Cs(2RCs+3)}$$

$$\text{Zeros: } s = -\frac{1}{2CR}, s = -\frac{2}{CR}$$

$$\text{Poles: } s = 0, s = -\frac{3}{2RC}$$

10.7 Cont.

Z_{eq2} :

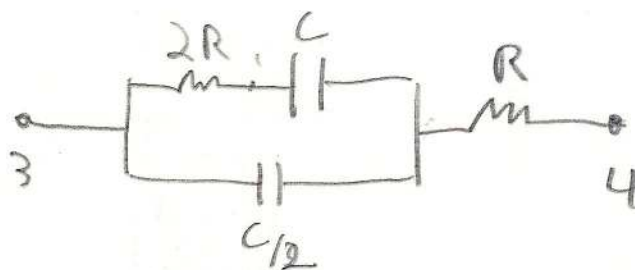

$$Z_{eq2} = \left(\frac{2RCs + 1}{Cs} \right) \parallel \frac{2}{Cs} + R$$


$$= \frac{Cs(4RCs + 2)}{Cs^2(2RCs + 3)} + \frac{CsR(2RCs + 3)}{Cs(2RCs + 3)}$$

$$= \frac{2R^2C^2s^2 + 7RCS + 2}{Cs(2RCs + 3)}$$

$$\text{Zeros: } s = \frac{-7RC \pm \sqrt{49R^2C^2 - 16R^2C^2}}{4}$$

$$s = \frac{-7RC \pm RC \cdot \sqrt{33}}{4}$$
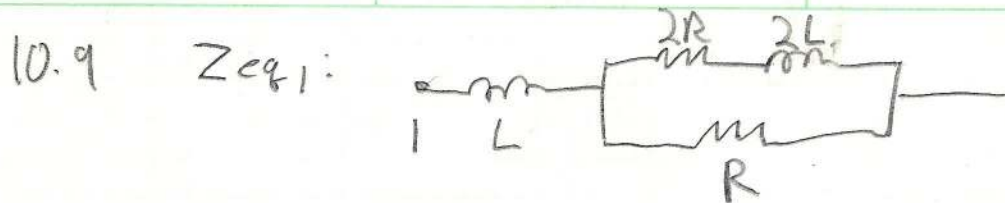
$$\text{poles } s=0, s = -\frac{3}{2RC}$$



$$Z_{eq1} = Ls + 2(R+Ls) \parallel R$$

$$= Ls + \frac{2R^2 + 2RLs}{3R + 2Ls}$$

$$= \frac{3RLs + L^2s^2 + 2R^2 + 2RLs}{3R + 2Ls}$$


$$= \frac{(2Ls + R)(Ls + 2R)}{3R + 2Ls}$$

$$\text{Zeros: } s = \frac{-R}{2L}, \frac{-2R}{L}$$

$$\text{poles: } s = \frac{-3R}{2L}$$

10.9 cont.

Z_{eqL} :

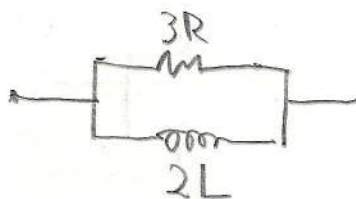


$$Z_{eqL} = 3R \parallel 2Ls =$$

$$\frac{6RLs}{3R + 2Ls}$$


Zeros: $s = 0$

Poles: $s = -\frac{3R}{2L}$

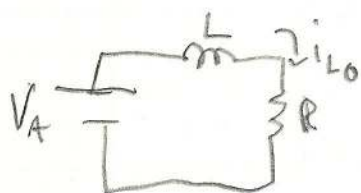10.11 When switch is at A for a long time


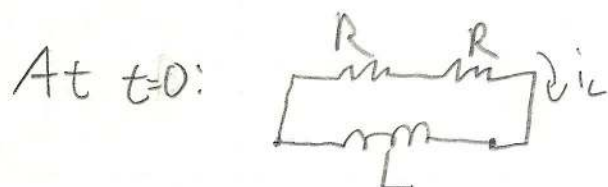
$$i_{L0} = \frac{V_A}{R} \leftarrow \text{this is your initial condition } i_L(0)$$



$$\text{KVL: } iR + iR + L \frac{di_L}{dt} = 0$$

$$\Rightarrow 0 = I_L(s) \cdot 2R + L(s I_L(s) - i_L(0))$$


$$0 = I_L(s)(2R + Ls) - L V_A / R$$

$$\Rightarrow \boxed{I_L(s) = \frac{L V_A}{L R s + 2 R^2}}$$


$$I_L(s) = \frac{L V_A}{L R} \cdot \left(\frac{1}{s + 2R/L} \right)$$

$$\boxed{i_L(t) = \mathcal{L}^{-1}[I_L(s)] = \frac{V_A}{R} \cdot e^{-(2R/L)t}$$

10.13 When switch is at A:

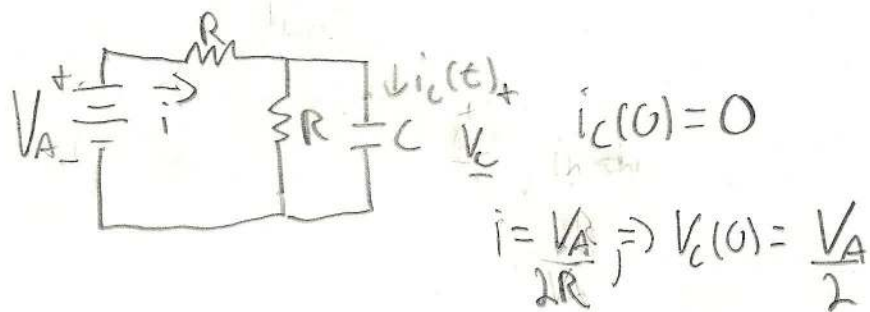


At $t=0$, Switched to B

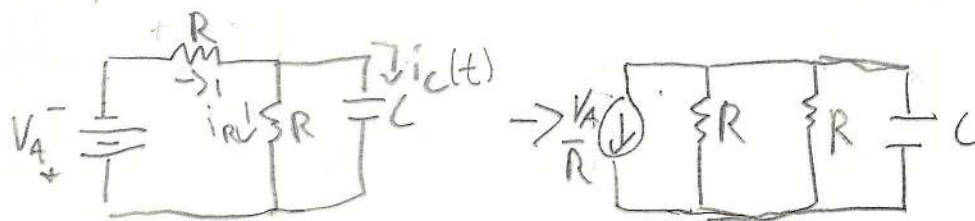

Use Superposition for Output / O state

In s domain

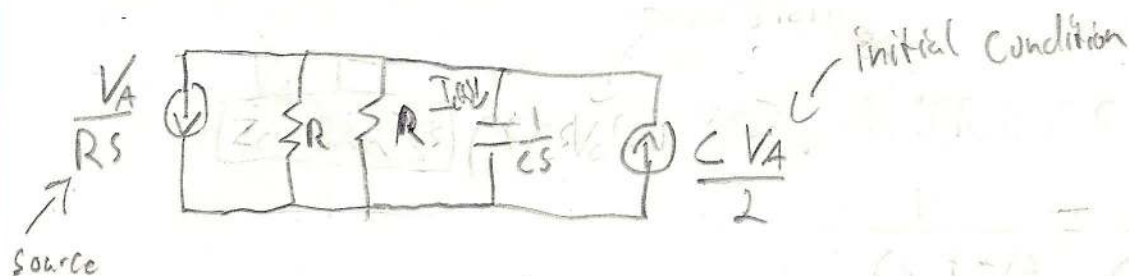

Zero Source,

$$I_{CZ}(s) = \frac{Cs}{Cs + \frac{1}{R} + \frac{1}{R}} \cdot \frac{CV_A}{2} = \frac{C^2 V_A R s}{2(CRs + 2)}$$

Zero Initial Condition

$$I_{CZI}(s) = \frac{-Cs}{Cs + \frac{1}{R} + \frac{1}{R}} \cdot \frac{V_A}{R \cdot s} = \frac{-CV_A}{CRs + 2}$$

10.13 cont. $I_c(s) = I_{c2s}(s) + I_{c2I}(s)$

$$= \frac{C^2 V_A R s - 2 C V_A}{2(CR s + 2)}$$

Note $I_c(s)$ is not proper so divide


$$\begin{array}{r} \frac{1}{2} C V_A \\ 2CRs + 4 \overline{) C^2 V_A R s - 2 C V_A} \\ - C^2 V_A R s + 2 C V_A \\ \hline -4 C V_A \end{array}$$

$$\Rightarrow I_c(s) = \frac{C V_A}{2} - \frac{2 C V_A}{CR s + 2}$$

$$\Rightarrow i_c(t) = \mathcal{L}^{-1}[I_c(s)] =$$

$$i_c(t) = \frac{C V_A}{2} \delta(t) - \frac{2 V_A}{R} \cdot e^{-(\frac{2}{CR})t}$$

10.19. In s domain

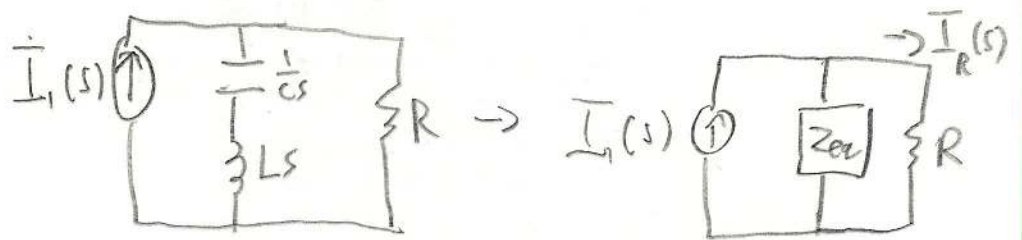

$$Z_{eq} = \frac{1}{Cs} + LS = \frac{CLS^2 + 1}{Cs}$$

Using Current Division!


$$\bar{I}_R(s) = \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{Z_{eq}}} \bar{I}_1(s)$$

$$\Rightarrow \frac{\bar{I}_R(s)}{\bar{I}_1(s)} = \frac{\frac{1}{R}}{\frac{1}{R} + \frac{Cs}{CLS^2 + 1}} = \frac{\frac{1}{R}}{\frac{CLS^2 + 1 + RCS}{R(CL S^2 + 1)}}$$

$$= \frac{R(CL S^2 + 1)}{R(CL S^2 + RCS + 1)}$$

10.21

In s domain

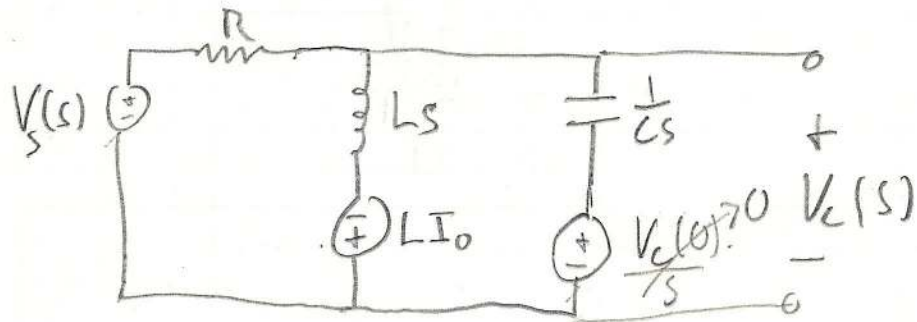

Zero State (inductor section is O.C.)

$$V_{CZS}(s) = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} V_s(s) = \frac{Cs}{Cs(RCs + 1)} V_s(s)$$

$$= \frac{1}{RCs + 1} V(s)$$


Zero Input (Source section is O.C.)

$$V_{CZI}(s) = - \frac{\frac{1}{Cs}}{\frac{1}{Cs} + Ls} = \frac{-Cs}{Cs(1 + LCs^2)}$$

$$= \frac{-1}{LCs^2 + 1}$$

10.23

In s Domain

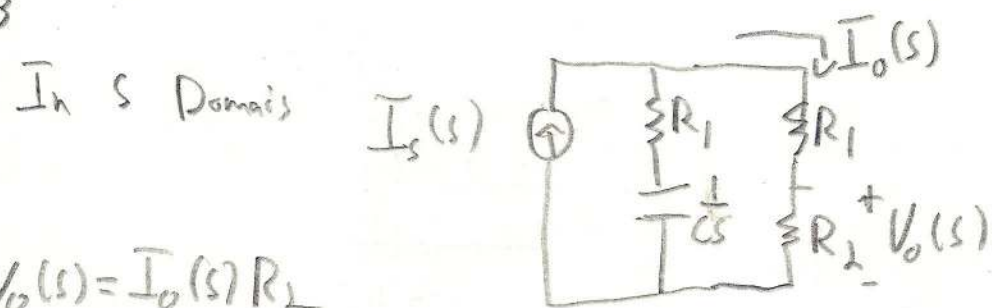

$$V_o(s) = I_o(s) R_2$$

$$\begin{aligned} I_o(s) &= \frac{\frac{1}{R_1 + R_2}}{\frac{1}{R_1 + R_2} + \frac{1}{R_1 + \frac{1}{Cs}}} \cdot I_s(s) = \frac{\frac{1}{R_1 + R_2}}{\frac{1}{R_1 + R_2} + \frac{Cs}{R_1 Cs + 1}} \cdot I_s(s) \\ &= \frac{\frac{1}{R_1 + R_2}}{\frac{R_1 Cs + 1 + Cs(R_1 + R_2)}{(R_1 + R_2)(R_1 Cs + 1)}} \cdot I_s(s) = \frac{(R_1 + R_2)(R_1 Cs + 1)}{(R_1 + R_2)(R_1 Cs + 1 + Cs(R_1 + R_2))} \cdot I_s(s) \end{aligned}$$

Sub in and Manipulate to get

$$I_o(s) = \frac{2(s + 1000)}{5(s + 400)} \cdot I_s(s) ; \quad I_s(s) = \frac{5}{2} \cdot \frac{1}{(s + 200)}$$

$$\Rightarrow I_o(s) = \frac{(s + 1000)}{(s + 400)(s + 200)}$$

$$\Rightarrow V_o(s) = 5k\Omega \cdot \frac{(s + 1000)}{(s + 400)(s + 200)}$$

Forced pole: $s = -200$ Natural pole: $s = -400$


10.23 cont. $I_0(s) = \frac{a}{s+400} + \frac{b}{s+200}$

$$a = \left. \frac{s+1000}{s+200} \right|_{s=-400} = -3$$

$$b = \left. \frac{s+1000}{s+400} \right|_{s=-200} = 4$$

$$\Rightarrow V(t) = 5,000 \cdot (4 \cdot e^{-200t} - 3e^{-400t})$$

10.30

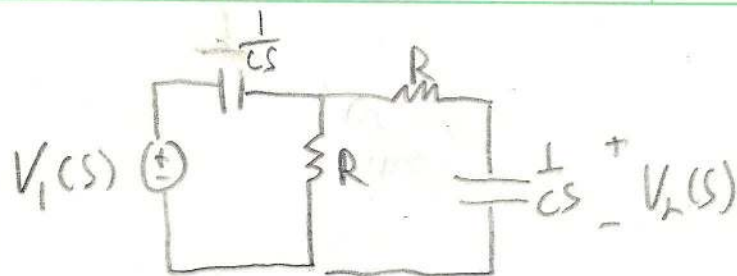

Z_{eq} (as seen from $V_1(s)$)

$$Z_{eq} = \frac{1}{Cs} + R \parallel \left(R + \frac{1}{Cs}\right)$$

$$= \frac{1}{Cs} + \frac{R(RCs + 1)}{Cs} \cdot \frac{RCs + 1}{Cs}$$

$$= \frac{1}{Cs} + \frac{R(RCs + 1)}{2RCs + 1} = \frac{2RCs + 1 + RCs(RCs + 1)}{2RCs^2 + Cs}$$

$$= \frac{1 + RCs(RCs + 3)}{2RCs^2 + Cs}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{1/Cs}{Z_{eq}} = \frac{2CRs + 1}{C^2R^2s^2 + 3 \cdot CRs + 1}$$

$$\text{poles } s = \frac{-3CR \pm \sqrt{9C^2R^2 - 4C^2R^2}}{2 \cdot C^2R^2}$$

$$= \frac{-3 \pm \sqrt{5}}{2 \cdot C \cdot R}$$

10.30 Cont.

$$\text{Want } \frac{-3 - \sqrt{5}}{2CR} = -2,618 \text{ rad/s}$$

$$\Rightarrow CR = \frac{+3 + \sqrt{5}}{2 \cdot 2,618}$$


$$\text{Also } \frac{-3 + \sqrt{5}}{2CR} = -382 \text{ rad/s}$$

$$\Rightarrow CR = \frac{3 - \sqrt{5}}{2 \cdot 382}$$

Either way $CR = .001$

For example $R = 1 \text{ k}\Omega$
 $C = 1 \mu\text{F}$

10.31 in s Domain

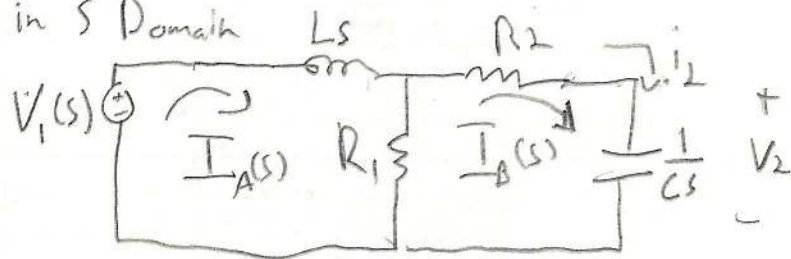

a. Mesh A: $-V_1(s) + Ls I_A(s) + R_1(I_A(s) - I_B(s)) = 0$

Mesh B: $R_1(I_B(s) - I_A(s)) + R_2 I_B(s) + \frac{I_B(s)}{Cs} = 0$

b. $I_2(s) = I_B(s)$

Solve
$$\begin{bmatrix} Ls + R_1 & -R_1 \\ -R_1 & R_1 + R_2 + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \end{bmatrix}$$

$$\Rightarrow I_2(s) = \frac{V_1(s) C R_1 s}{CL(R_1 + R_2)s^2 + (CR_1 R_2 + L)s + R_1}$$

Zeros: $s = 0$

Poles:
$$s = \frac{-(CR_1 R_2 + L) \pm \sqrt{(CR_1 R_2 + L)^2 - 4R_1 CL(R_1 + R_2)}}{2CL(R_1 + R_2)}$$

part C. $R_1 = 1k\Omega$, $R_2 = 2k\Omega$, $L = 2H$

$C = 500\mu F$, $V(t) = 50$

$\Rightarrow V_1(s) = 50/s$

$\Rightarrow$ poles s : $-500 \pm \frac{500\sqrt{3}}{3}j$

$\Rightarrow I_2(s) = \frac{a}{(s + 500 - \frac{500\sqrt{3}}{3}j)} + \frac{a^*}{(s + 500 + \frac{500\sqrt{3}}{3}j)}$

$a = I_2(s) \cdot (s + 500 - \frac{500\sqrt{3}}{3}j) \Big|_{s = -500 + \frac{500\sqrt{3}}{3}j}$

$= \frac{.025}{s + 500 + \frac{500\sqrt{3}}{3}j} \Big|_{s = -500 + \frac{500\sqrt{3}}{3}j} = -4.33 \times 10^{-5}j$

$|a| = 4.33 \times 10^{-5}$ $\angle a = -\pi/2$

$\Rightarrow i_2(t) = 2 \cdot |a| t e^{-500t} \cdot \cos\left(\frac{500\sqrt{3}}{3}t - \angle a\right)$

$i_2(t) = .0866 t e^{-500t} \cos\left(\frac{500\sqrt{3}}{3}t - \frac{\pi}{2}\right) \text{mA}$