


Solutions

HW 8

10: 55, 11: 5, 7, 9, 27, 56, 59, 12: 3, 15, 57

10.55 Note Zero States so $V_{C_1}(t=0) = V_{C_2}(t=0) = 0$

In s domain:

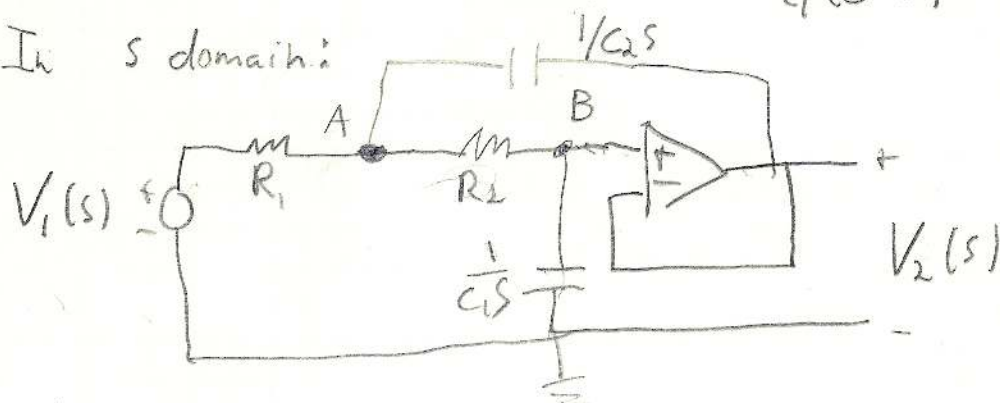

$$V_2(s) = V_B(s) \quad (1)$$

$$\frac{V_A(s) - V_B(s)}{R_2} = V_B(s) \cdot C_1 \cdot s \quad (2)$$

$$\frac{V_1(s) - V_A(s)}{R_1} = V_B(s) \cdot C_1 \cdot s + (V_A(s) - V_2(s)) C_2 \cdot s \quad (3)$$

Eq 2 gives $V_A(s) = R_2 C_1 V_2(s) \cdot s + V_2(s)$


$$= V_2(s) \cdot (R_2 C_1 s + 1)$$

Sub into eq 3

$$V_2(s) (R_2 C_1 s + 1 + R_1 C_1 s + R_1 R_2 C_1 s^2 \cdot C_2 - \cancel{C_2 R_1 s} + \cancel{R_1 C_1 s}) = V_1(s)$$

$$= V_1(s)$$
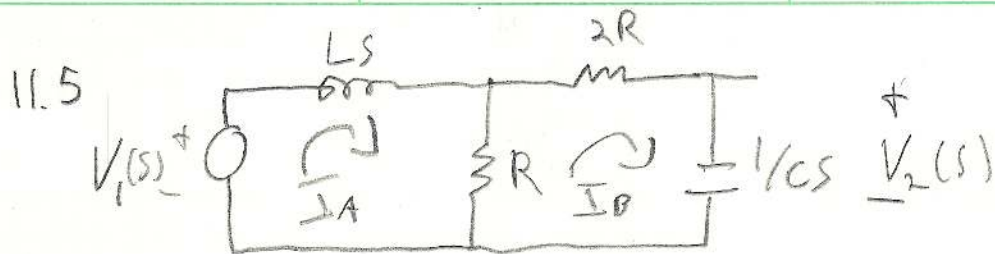
$$\Rightarrow \frac{V_2(s)}{V_1(s)} = \frac{1}{R_1 R_2 C_1 C_2 s^2 + C_1 (R_2 + R_1) s + 1}$$




$$\begin{bmatrix} LS + R & -R \\ -R & 3R + \frac{1}{cS} \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} V_1(s) \\ 0 \end{bmatrix}$$

$$I_B = \frac{C \cdot R \cdot V_1(s) \cdot s}{3CLR \cdot s^2 + (2CR^2 + L) \cdot s + R}$$

$$V_2(s) = I_B(s) \cdot \frac{1}{cS}$$

$$\Rightarrow \frac{V_2(s)}{V_1(s)} = \frac{R V_1(s)}{3CLR \cdot s^2 + (2CR^2 + L) \cdot s + R}$$

11.7.

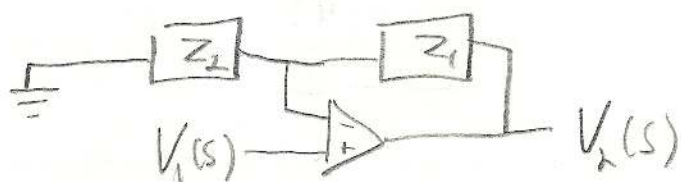

Noninverting Amp.

$$T_V = \frac{Z_1 + Z_2}{Z_2}, \quad Z_2 = R, \quad Z_1 = \frac{R/c s}{R + 1/c s}$$


$$\Rightarrow T_V = \frac{R + \frac{R}{R c s + 1}}{R} = \frac{R}{R c s + 1}$$

$$\Rightarrow \boxed{T_V(s) = \frac{C R s + 1}{C R s + 1}}$$

poles at $s = -1/CR$

$$\Rightarrow \boxed{C \cdot R = .001}$$

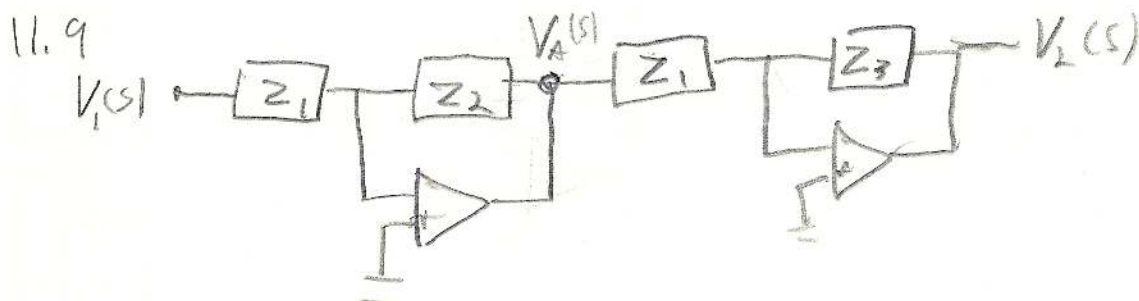Let $C = 1 \mu F$, $R = 1 k\Omega$ for example



2 - inverting Amps

$$\frac{V_A}{V_1} = -\frac{Z_2}{Z_1} ; \quad \frac{V_2}{V_A} = -\frac{Z_3}{Z_1}$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{Z_2 \cdot Z_3}{Z_1^2}$$

$$\Rightarrow T_V = \frac{V_2}{V_1} = \frac{10^6}{(s+100)(s+1000)}$$

$$\text{Poles: } s = -100, -1000$$

$$Z_1 = 10 \text{ k}\Omega$$

$$Z_2 = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega \cdot 100 \text{ nF} s + 1}$$

$$Z_3 = \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega \cdot 100 \text{ nF} s + 1}$$

11.27 Simple Voltage divider

So.

$$V_2(s) = \frac{Ls}{R + \frac{1}{Cs} + Ls} V_1(s) = \frac{CLs^2}{RCs + Lcs^2 + 1} V_1(s)$$

When $V_1(t) = 10 \cos(2000t)$, $V_1(s) = \frac{10s}{s^2 + 2000^2}$

Sub in $L = 5 \text{ mH}$, $C = 50 \text{ } \mu\text{F}$, $R = 10 \Omega$

and $V_1(s)$ to get

$$V_2(s) = \frac{10s^3}{(s^2 + 4 \times 10^6)(s^2 + 2000s + 4 \times 10^6)}$$

Poles: $s = \pm 2000j$, $-1000 \pm 1000\sqrt{3}j$

$$\Rightarrow V_2(s) = \frac{a}{(s + 2000j)} + \frac{a^*}{s - 2000j} + \frac{b}{s + 1000(1 - \sqrt{3}j)} + \frac{b^*}{s + 1000(1 + \sqrt{3}j)}$$


$$a = V_2(s)(s + 2000j) \Big|_{s = -2000j} = -5j$$

$$b = V_2(s)(s + 1000(1 - \sqrt{3}j)) \Big|_{s = -1000 + \sqrt{3}j} = 5 - \frac{5 \cdot j}{\sqrt{3}} = 5 - \frac{5\sqrt{3}}{3}j$$

$$\text{abs}(a) = 5, \angle a = -\frac{\pi}{2}; \text{abs}(b) = \frac{10\sqrt{3}}{3}; \angle b = -\frac{\pi}{6}$$

$$\Rightarrow V_2(t) = 10 \cdot \cos(2000t - \pi/2) + \frac{20\sqrt{3}}{3} \cdot \cos(1000\sqrt{3}t - \pi/6)$$

11.51 11.9 gives some help setting this up.

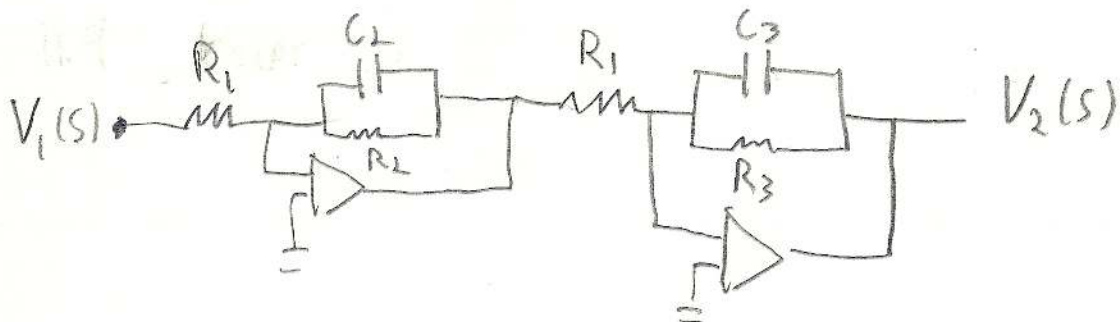

In 11.9 we see this is:

$$\frac{V_2}{V_1} = \frac{1}{R_1^2} \cdot \left(\frac{R_2}{R_2 C_2 s + 1} \right) \left(\frac{R_3}{R_3 C_3 s + 1} \right)$$

$$= \frac{1}{R_1^2} \cdot \left(\frac{1/C_2}{s + 1/(C_2 R_2)} \right) \left(\frac{1/C_3}{s + 1/(C_3 R_3)} \right)$$

let $\frac{1}{C_2 R_2} = 100$ so

$C_2 = 100 \text{ nF}, R_2 = 100 \text{ k}\Omega$

let $\frac{1}{C_3 R_3} = 10,000$ so

$C_3 = 10 \text{ nF}, R_3 = 10 \text{ k}\Omega$


Now $2 \times 10^5 = \frac{1}{R_1^2 C_2 C_3}$

$\Rightarrow R_1 = \sqrt{\frac{1}{2 \times 10^5 C_2 C_3}}$

$R_1 = 70.71 \text{ k}\Omega$

11.59

First Circuit look like:

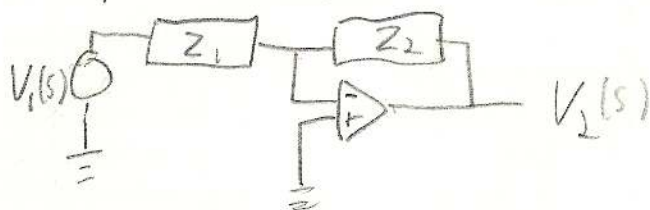


$$T_V = -\frac{Z_2}{Z_1}; \quad Z_1 = R_1 + \frac{1}{C_1 s} = \frac{C_1 R_1 s + 1}{C_1 s}$$

$$\Rightarrow T_V = -\frac{R_2 C_1 s}{(C_1 R_1 s + 1)(C_2 R_2 s + 1)} \quad Z_2 = \frac{R_2 / C_2 s}{R_2 + 1/C_2 s} = \frac{R_2}{C_2 R_2 s + 1}$$

$$= -\frac{(R_2 C_1 / (C_1 R_1 R_2 C_2)) \cdot s}{(s + 1/C_1 R_1)(s + 1/R_2 C_2)}$$

$$= -\frac{1000 s}{(s + 4000)(s + 1000)} \quad \checkmark$$

Second Circuit

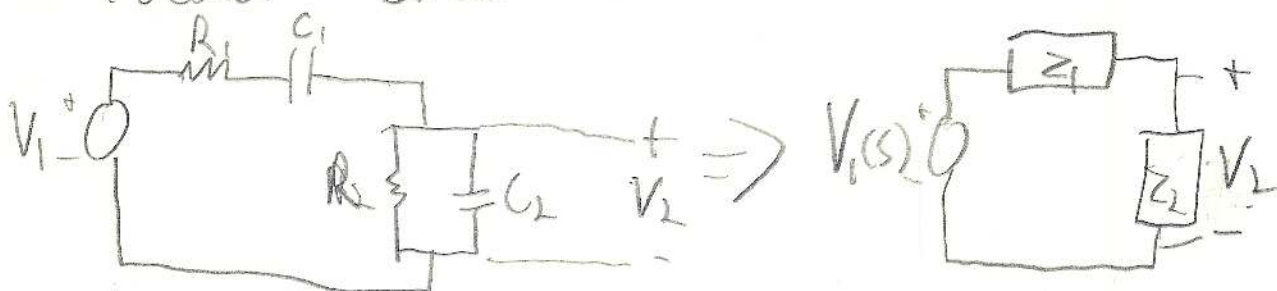

Voltage Division gives

$$T_V = \frac{V_2}{V_1} = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2 / (C_2 R_2 s + 1)}{\frac{C_1 R_1 s + 1}{C_1 s} + \frac{R_2}{C_2 R_2 s + 1}}$$

$$\begin{aligned}
 T_v &= \frac{C_1 R_2 s}{C_1 C_2 R_1 R_2 s^2 + (C_1 R_1 + C_1 R_2 + C_2 R_2) s + 1} \\
 &= \frac{(C_1 R_1) \cdot s}{C_1 C_2 R_1 R_2} \cdot \left(\frac{1}{s^2 + \frac{(C_1 R_1 + C_1 R_2 + C_2 R_2)}{C_1 C_2 R_1 R_2} s + \frac{1}{C_1 C_2 R_1 R_2}} \right) \\
 &= \frac{1000 s}{s^2 + 5000 s + 4000,000} \quad \checkmark
 \end{aligned}$$

b. The output impedance for circuit 1 is 0 so use circuit 1. If is 0 due to the op. amp.

So Use circuit 1. Impedance is 0.

C. Circuit 1 input impedance is

$$Z_1 = \frac{s + 1/(C_1 R_1)}{s} \cdot \left(\frac{C_1 R_1}{C_1} \right) = 10k\Omega \cdot \left(\frac{s + 4000}{s} \right)$$

$\Rightarrow$ 10K Gain


Circuit 2 has an input impedance of

$$Z_1 + Z_2 = \frac{(C_1 C_2 R_1 R_2) s^2 + (C_1 R_1 + C_1 R_2 + C_2 R_2) s + 1}{C_1 C_2 R_2 s^2 + C_1 s}$$

$$= 200 \cdot \left(\frac{(s + 1000)(s + 4000)}{s \cdot (s + 2000)} \right)$$


$\rightarrow$ Use Circuit 2. Circuit 1 has
a much higher input impedance

d. For C_2 followed by C_1 :

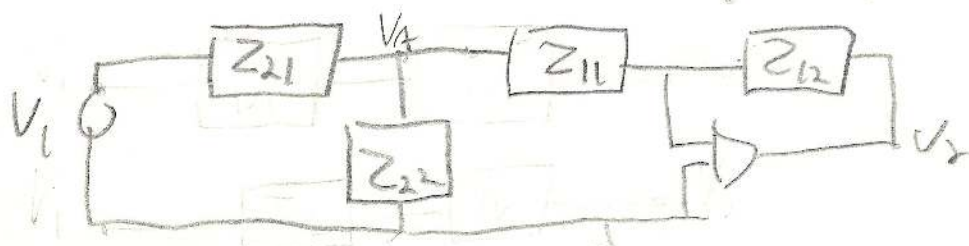

In this set up, $T_2 \left(\frac{V_A}{V_1} \right)$ is different
then before so it will not work
for this set up

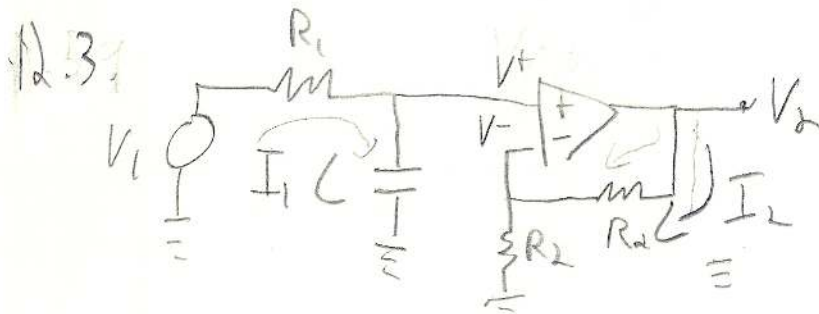However C_1 followed by C_2 is fine
since the op-amp comes first



$$V^+ = \frac{I_1}{C_1} \quad ; \quad I_1 = \frac{V_1}{(R_1 + \frac{1}{C_1 s})} = \frac{C_1 s V_1}{C_1 s + 1}$$

$$\Rightarrow V^+ = \frac{V_1}{C_1 s + 1} \quad , \quad V^+ = V^-$$

$$I_2 = \frac{V_2}{2R_2} \quad ; \quad V^- = I_2 R_2 = \frac{V_2}{2}$$

$$\Rightarrow \frac{V_1}{C_1 s + 1} = \frac{V_2}{2} \Rightarrow T_V = \frac{2}{C_1 s + 1}$$

a. $T_V(j\omega) = \frac{400}{j\omega + 200}$

DC gain $|T_V(0)| = 2 = 6.0 \text{ dB}$

Infinite Freq Gain:


$$|T_V(j\omega = \infty)| = 0$$

Cut off Freq
For $T(s) = \frac{12/C_1}{s + \frac{1}{C_1}}$

Standard low pass
form so $\omega_c = \alpha = \frac{1}{C_1}$
 $\Rightarrow \omega_c = 200 \text{ rad/s}$

12.3 cont.

a. Cont. This is a low pass filter.

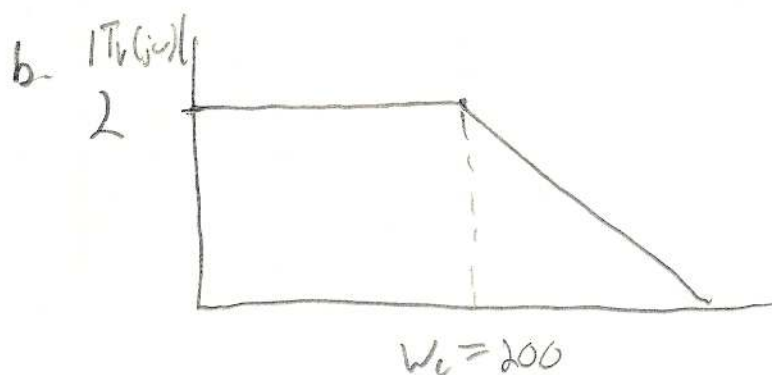


c. $|T_V(j\omega)|_{\omega = 0.5\omega_c} = \underline{5.05 \text{ dB}}$

$$|T_V(j\omega)|_{\omega = \omega_c} = \underline{3.01 \text{ dB}}$$

$$|T_V(j\omega)|_{\omega = 2\omega_c} = \underline{-1.97 \text{ dB.}}$$

d. Not Necessary but see next page.
Command in Matlab: $\text{sys} = \text{tf}([2], [CR, 1])$
 $\text{Bode}(\text{sys})$

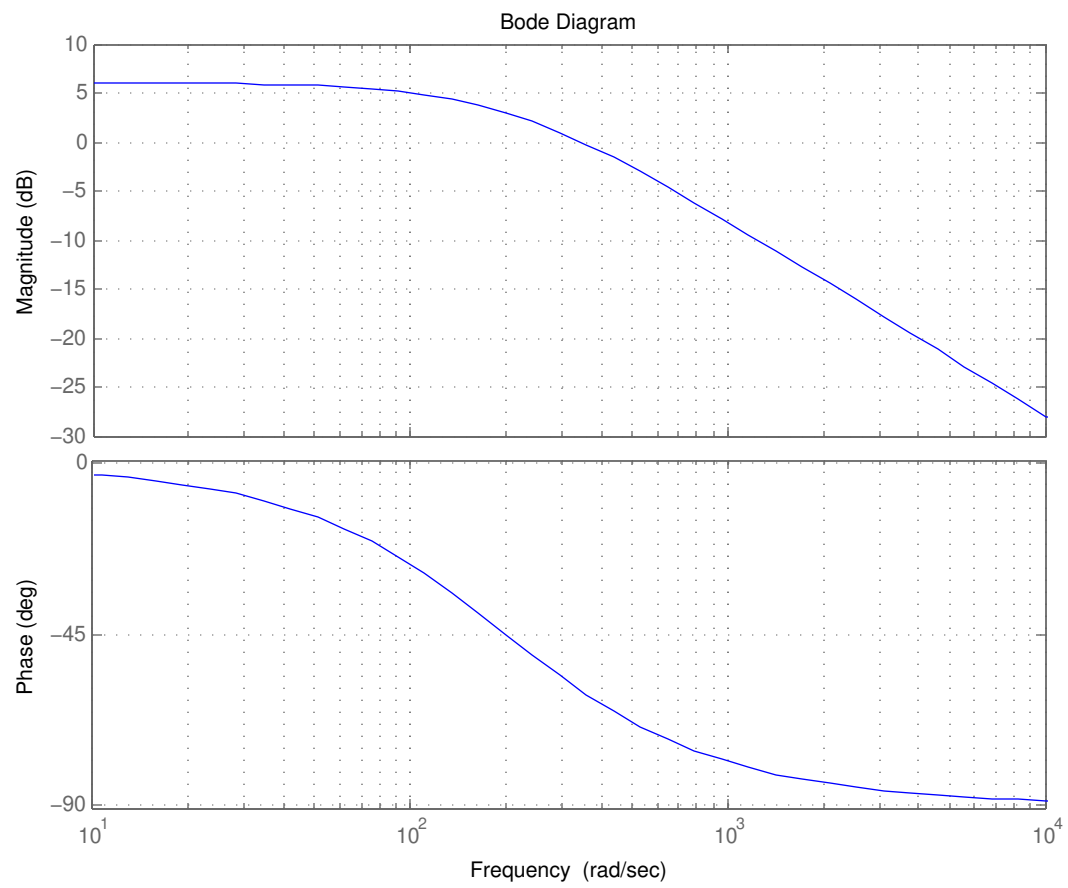e. Since ω_c is set by the $20 \text{ k}\Omega$ resistor and capacitor, you would adjust the gain by changing the two $30 \text{ k}\Omega$ res.



Q.15 For the first inverting Amp

$$T_1(s) = \frac{\frac{1}{C_1 s} \parallel R_2}{R_1} = - \frac{R_2}{R_1 (C_1 R_2 s + 1)}$$

And for the second

$$T_2(s) = \frac{R_4}{\frac{1}{C_2 s} + R_3} = - \frac{R_4 C_2 s}{C_2 R_3 s + 1}$$

For the 1st part, $\omega_c = \frac{1}{C_1 R_2}$, it is low pass

For the second part, $\omega_c = \frac{1}{C_2 R_3}$, it is high pass.

For high pass $\omega_{ch} = \frac{1}{C_2 R_3} = 100 \text{ rad/s}$

For low pass $\omega_{cl} = \frac{1}{C_1 R_2} = 2500 \text{ rad/s}$

The gain is $\frac{|K_1 K_2|}{\omega_{cl}} = \frac{1}{R_1 C_1} \cdot \frac{R_4}{R_3} \cdot C_1 R_2$

Let $C_2 = 100 \text{ nF}$, $R_3 = 100 \text{ k}\Omega$

Let $C_1 = 1 \text{ nF}$, $R_2 = 400 \text{ k}\Omega$


$$= \frac{R_4 R_2}{R_1 R_3} = 30$$

Then to meet the gain

$$R_1 = 10 \text{ k}\Omega$$

$$R_4 = 75 \text{ k}\Omega$$

12.57 For Vender 1:

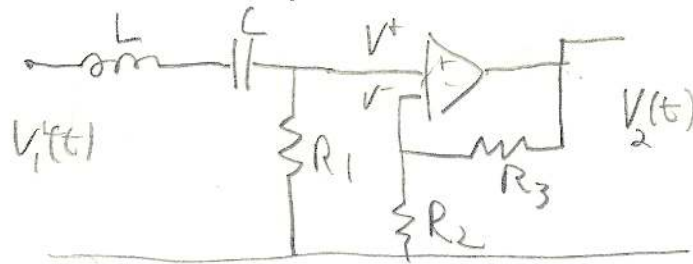


$$V^+ = \frac{R_1}{Ls + \frac{1}{Cs} + R_1} V_1(s) \quad (\text{Voltage Divider})$$

$$V^- = \frac{R_2}{R_3 + R_2} V_2(s) \quad (\text{Voltage Division})$$

$$V^+ = V^- \text{ gives: } T_1(s) = \frac{V_2}{V_1} = \frac{R_1(R_2 + R_3)C \cdot s}{R_2(LLs^2 + CR_1s + 1)}$$

Vender 2

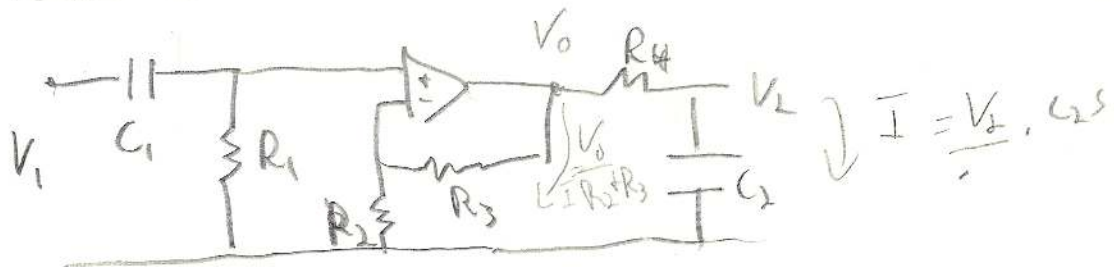

$$V^+ = \frac{R_1}{R_1 + \frac{1}{C_1s}} V_1$$

$$V^+ = V^-$$

Gives

$$T_2(s) = \frac{R_1 C_1 (R_2 + R_3) s}{R_2 (L R_1 s + 1) (C_2 R_4 s + 1)}$$

$$V_2 + V_2 C_2 s R_4 = V_0$$

$$\frac{V_0 - V^-}{R_3} = \frac{V^-}{R_2}$$

$$\Rightarrow V_0 = V^- \left(\frac{R_3}{R_2} + 1 \right)$$

$$\Rightarrow V^- = \frac{V_2 (1 + C_2 s R_4)}{\left(\frac{R_3}{R_2} + 1 \right)}$$

12.57 Cont: Both denominators can be written
in the form $s^2 + 2\beta\omega_0 s + \omega_0^2$

For T_1 $\omega_0 = \sqrt{1/L} = 5 \text{ Krad/s}$

T_2 $\omega_0 = \sqrt{1/C_1 R_1 C_2 R_4} = 5.0023 \text{ Krad/s}$

both meet requirements

B: for T_1 : $B = R/L = 10,000 \text{ rad/s}$

T_2 : $B = \frac{1}{C_2 R_4} - \frac{1}{C_1 R_1} = 10,074 \text{ rad/s}$

Passband Gain K

For T_1 : Non inverting Amp so $K = 1 + \frac{R_2}{R_1} = 10$

For T_2 : $\frac{K_1 \cdot K_2}{\rightarrow \omega_L} = \frac{R_1 C_1 (R_2 + R_3)}{R_2 (C_1 R_1) (C_2 R_4)} \cdot \frac{C_1 R_4}{\rightarrow} = 11.7$
low pass pole Not Good

For ω_{cl}

For T_1 $\omega_{cl} = -\frac{R_1}{2L} + \sqrt{\left(\frac{R_1}{2L}\right)^2 + \frac{1}{LC}} = 2,077 \text{ rad/s}$

T_2 $\omega_{cl} = \frac{1}{C_1 R_1} = 2,062 \text{ rad/s}$

Pick Circuit 1, it meets all criteria
Circuit 2 fails Passband Gain

