
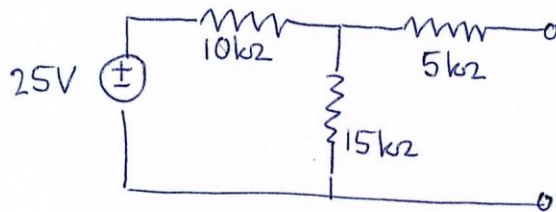


3.47, 3.52, 3.58, 3.1, 3.3, 3.4, 3.5, 3.13, 3.17b)+c), 3.22b)+d)

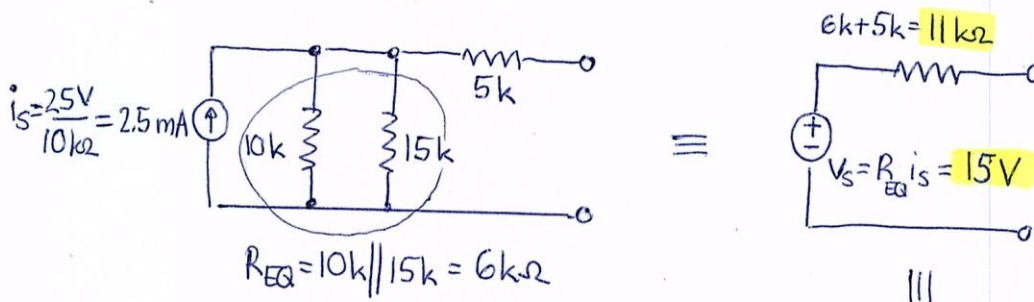
3.47 Find its Thévenin and Norton equivalent circuit



↓ source transformation






Thévenin
equivalent
circuit

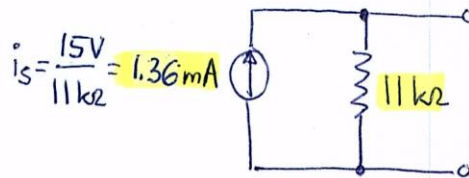


Norton
equivalent
circuit

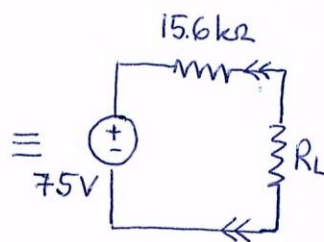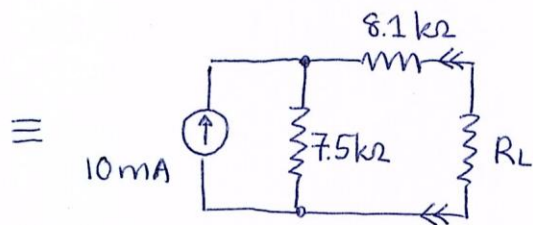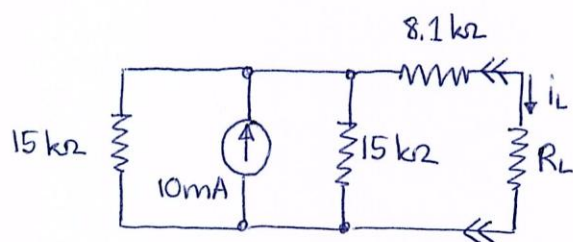3.52 Norton equivalent circuit and current i_L



Norton equivalent circuit

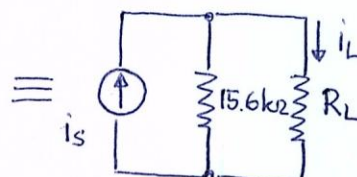

$$i_s = \frac{75V}{15.6k\Omega} = 4.8mA$$

Current i_L via current division


$$i_L = \frac{15.6k\Omega}{15.6k\Omega + R_L} i_s$$

$$i_L (R_L = 4.7k\Omega) = 3.69mA$$

$$i_L (R_L = 15k\Omega) = 2.45mA$$

$$i_L (R_L = 68k\Omega) = 0.99mA$$


3.58

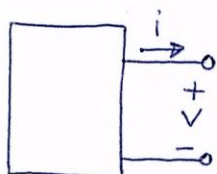


- $i = 1A$ for $V = 0V$ case A
- $V = 12V$ when connected to 20Ω resistor case B
- current when charging a 12V battery?

Use Thevenin equivalent circuit

case A:

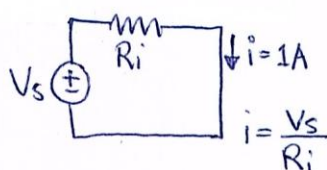

case B:

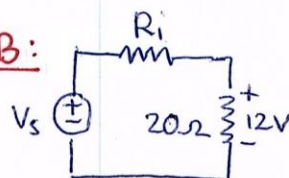

voltage division

$$12V = \frac{20\Omega}{20\Omega + R_i} \cdot V_s$$

$$\rightarrow 12V = \frac{20\Omega}{20\Omega + R_i} \cdot V_s$$

$$V_s = 1A \cdot R_i$$


$$12V \cdot 20 \frac{V}{A} + 12V \cdot R_i = 20 \frac{V}{A} \cdot 1A \cdot R_i$$

$$240 \frac{V^2}{A} = 8V \cdot R_i$$

$$R_i = 30\Omega \rightarrow V_s = 30V$$

$$i = \frac{V_s}{R_{total}} = \frac{30V}{30\Omega + 20\Omega} = \underline{\underline{\frac{3}{5}A}}$$


3.1 Node-voltage equations

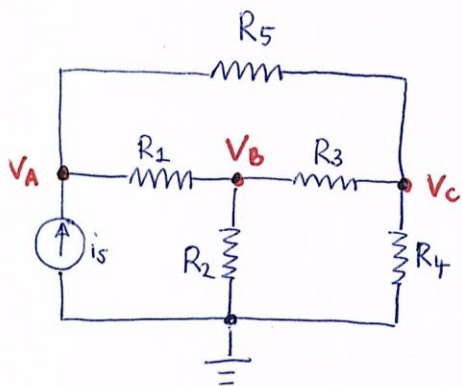

By inspection we can write

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_5} & -\frac{1}{R_1} & -\frac{1}{R_5} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_5} & -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{Bmatrix} V_A \\ V_B \\ V_C \end{Bmatrix} = \begin{Bmatrix} i_s \\ 0 \\ 0 \end{Bmatrix}$$

3.3 Node-voltage equations

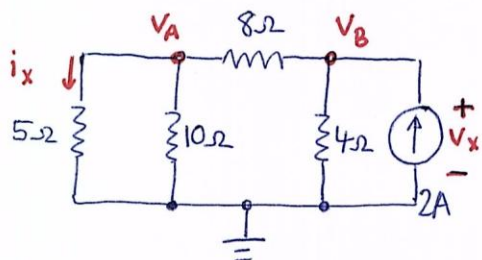

node A: $\left(\frac{1}{5\Omega} + \frac{1}{10\Omega}\right)V_A - \frac{1}{8\Omega}(V_A - V_B) = 0$

node B: $-\frac{1}{8\Omega}(V_B - V_A) - \frac{1}{4\Omega}V_B + 2A = 0$

By inspection we can write

$$\begin{bmatrix} \frac{1}{5\Omega} + \frac{1}{10\Omega} + \frac{1}{8\Omega} & -\frac{1}{8\Omega} \\ -\frac{1}{8\Omega} & \frac{1}{8\Omega} + \frac{1}{4\Omega} \end{bmatrix} \begin{Bmatrix} V_A \\ V_B \end{Bmatrix} = \begin{Bmatrix} 0 \\ 2A \end{Bmatrix}$$

$$V_A = \frac{\begin{vmatrix} 0 & -0.125 \\ 2 & 0.375 \end{vmatrix}}{|A|} = \frac{0.25}{0.14375} = \underline{\underline{1.74 \text{ V}}}$$

$$V_B = \frac{\begin{vmatrix} 0.425 & 0 \\ -0.125 & 2 \end{vmatrix}}{|A|} = \frac{0.85}{0.14375} = \underline{\underline{5.91 \text{ V}}}$$

$$\Leftrightarrow \begin{matrix} A & X & = & b \\ \begin{bmatrix} 0.425 & -0.125 \\ -0.125 & 0.375 \end{bmatrix} & \begin{Bmatrix} V_A \\ V_B \end{Bmatrix} & = & \begin{Bmatrix} 0 \\ 2 \end{Bmatrix} \end{matrix}$$

$$i_x = \frac{V_A}{5\Omega} = \underline{\underline{347.8 \text{ mA}}}$$

$$V_x = V_B = \underline{\underline{5.91 \text{ V}}}$$

3.4 Node voltage equations

$$\begin{bmatrix} \frac{1}{20\Omega} + \frac{1}{10\Omega} + \frac{1}{8\Omega} & -\frac{1}{8\Omega} \\ -\frac{1}{8\Omega} & \frac{1}{4\Omega} + \frac{1}{8\Omega} \end{bmatrix} \begin{Bmatrix} V_A \\ V_B \end{Bmatrix} = \begin{Bmatrix} 3A \\ -3A + 1A \end{Bmatrix} \Leftrightarrow \begin{bmatrix} 0.275 & -0.125 \\ -0.125 & 0.375 \end{bmatrix} \begin{Bmatrix} V_A \\ V_B \end{Bmatrix} = \begin{Bmatrix} 3 \\ -2 \end{Bmatrix}$$


$$A \times = b$$

$$V_A = \frac{\begin{vmatrix} 3 & -0.125 \\ -2 & 0.375 \end{vmatrix}}{|A|} = \frac{0.875}{0.0875} = \underline{\underline{10 \text{ V}}}$$

$$V_B = \frac{\begin{vmatrix} 0.275 & 3 \\ -0.125 & -2 \end{vmatrix}}{|A|} = \frac{-0.175}{0.0875} = \underline{\underline{-2 \text{ V}}}$$

$$i_x = \frac{V_A}{20\Omega} = \underline{\underline{0.5 \text{ A}}}$$

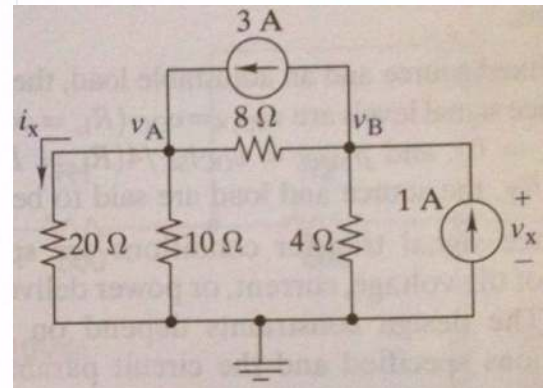
$$V_x = V_B = \underline{\underline{-2 \text{ V}}}$$



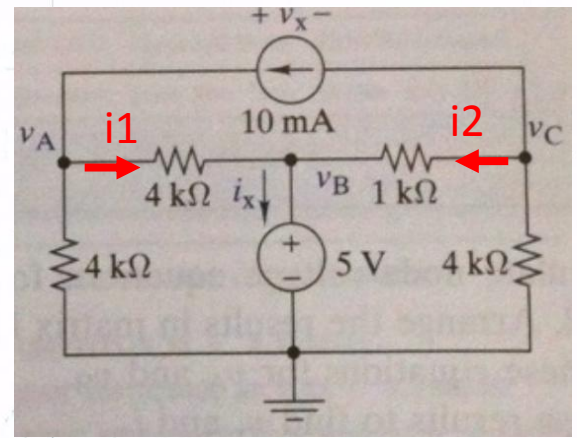3.5 Node-voltage analysis

The circuit contains a voltage source!
 Since one terminal of the source is connected to ground we know that
 $V_B = V_{\text{source}} = 5V$.

Using method 2 we can write by inspection



$$\begin{array}{c} \text{node A} \\ \text{node C} \end{array} \begin{array}{ccc} v_A & v_B & v_C \\ \left[\begin{array}{ccc} \frac{1}{4k\Omega} + \frac{1}{4k\Omega} & -\frac{1}{4k\Omega} & 0 \\ 0 & -\frac{1}{4k\Omega} & \frac{1}{1k\Omega} + \frac{1}{4k\Omega} \end{array} \right] \begin{Bmatrix} v_A \\ v_B \\ v_C \end{Bmatrix} = \begin{Bmatrix} 10\text{mA} \\ -10\text{mA} \end{Bmatrix}$$

Rearrange

$$\begin{bmatrix} \frac{1}{2k\Omega} & 0 \\ 0 & \frac{5}{4k\Omega} \end{bmatrix} \begin{Bmatrix} v_A \\ v_C \end{Bmatrix} = \begin{Bmatrix} 11.25\text{mA} \\ -5\text{mA} \end{Bmatrix} \rightarrow \begin{array}{l} v_A = \underline{\underline{22.5V}} \\ v_C = \underline{\underline{-4V}} \end{array}$$


$$V_x = V_A - V_C = \underline{\underline{26.5V}}$$

$$i_x = i_1 + i_2 = \frac{1}{4k\Omega} (V_A - V_B) + \frac{1}{1k\Omega} (V_C - V_B) = \frac{1}{4k\Omega} 17.5V + \frac{1}{1k\Omega} (-9V) = \underline{\underline{-4.625\text{mA}}}$$

3.13 Current voltage analysis

You can use method 1 or method 2.

Method 1: Source transformation

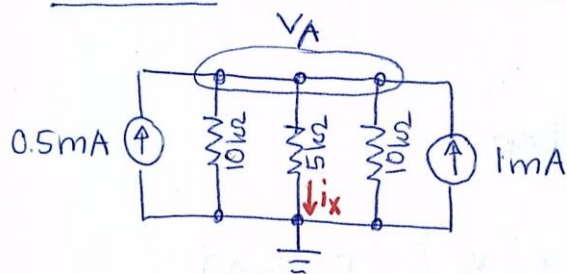

$$\left(\frac{1}{10k\Omega} + \frac{1}{5k\Omega} + \frac{1}{10k\Omega}\right) V_A = 0.5mA + 1mA$$

$$\frac{4}{10k\Omega} V_A = 1.5mA$$

$$V_A = \underline{\underline{3.75V}}$$


$$i_x = \frac{1}{5k\Omega} \cdot V_A = 0.75mA = \underline{\underline{750\mu A}}$$

$$V_x = 5V - V_A = 5V - 3.75V = \underline{\underline{1.25V}}$$

$$i_A = \frac{1}{10k\Omega} (V_B - V_A) = \frac{1}{10k\Omega} 1.25V = \underline{\underline{125\mu A}}$$

$$i_B = \frac{1}{10k\Omega} (V_A - V_C) = \frac{1}{10k\Omega} (-6.25V) = \underline{\underline{-625\mu A}}$$

Method 2:

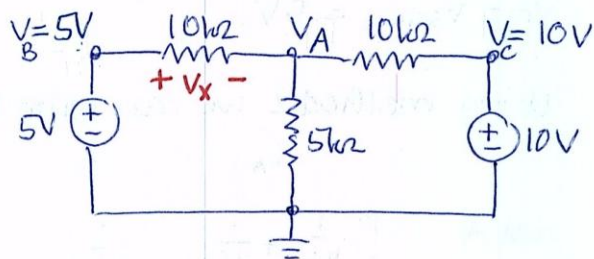

$$\left[\frac{1}{10k\Omega} + \frac{1}{5k\Omega} + \frac{1}{10k\Omega} \quad -\frac{1}{10k\Omega} \quad -\frac{1}{10k\Omega} \right] \begin{Bmatrix} V_A \\ V_B \\ V_C \end{Bmatrix} = 0$$

$$\Leftrightarrow \frac{4}{10k\Omega} V_A = 1.5mA$$

...

3.17 b) Select node D as the reference node $\rightarrow V_A = V_S$
By inspection we obtain


$$\begin{array}{l} \text{node B} \\ \text{node C} \end{array} \begin{bmatrix} -\frac{1}{R_A} & \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_E} & -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{bmatrix} \begin{Bmatrix} V_A \\ V_B \\ V_C \end{Bmatrix} = \begin{Bmatrix} 0 \\ 0 \\ 0 \end{Bmatrix} \quad V_A = V_S$$

Rarrange

$$\begin{bmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{bmatrix} \begin{Bmatrix} V_B \\ V_C \end{Bmatrix} = \begin{Bmatrix} \frac{V_S}{R_A} \\ \frac{V_S}{R_E} \end{Bmatrix}$$

$$e) V_x = V_B = \frac{\begin{vmatrix} \frac{V_S}{R_A} & -\frac{1}{R_C} \\ \frac{V_S}{R_E} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix}}{\begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix}}$$
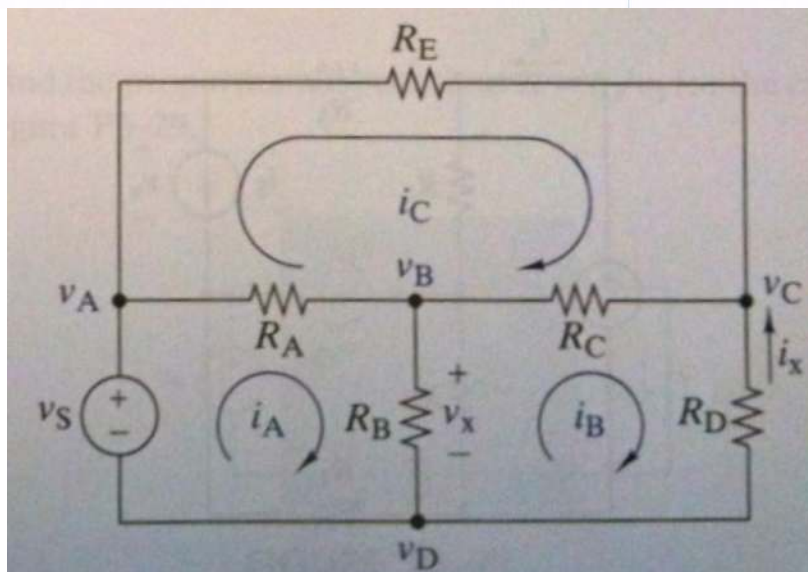
$$i_x = \frac{1}{R_D} \cdot (-V_C) = -\frac{1}{R_D} \cdot \frac{\begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & \frac{V_S}{R_A} \\ -\frac{1}{R_C} & \frac{V_S}{R_E} \end{vmatrix}}{\begin{vmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{vmatrix}}$$



3.22b) + d)

Node-voltage equation

b) NOTE: We only have to look at node B since v_A and v_C are determined by the voltage sources.

$$v_A = 20 \text{ V}$$

$$v_C = -15 \text{ V}$$

For node B we can write

$$3 \text{ mA} - \frac{1}{2 \text{ k}\Omega} (v_B - 20 \text{ V}) - \frac{1}{4 \text{ k}\Omega} v_B - \frac{1}{8 \text{ k}\Omega} (v_B + 15 \text{ V}) = 0$$

$$\left(\frac{1}{2 \text{ k}\Omega} + \frac{1}{4 \text{ k}\Omega} + \frac{1}{8 \text{ k}\Omega} \right) v_B = 3 \text{ mA} + 10 \text{ mA} - \frac{15}{8} \text{ mA}$$

$$\frac{0.875}{1000} v_B = 11.125 \text{ mA}$$

$$v_B = \underline{\underline{12.71 \text{ V}}}$$

$$d) i_x = \frac{1}{8 \text{ k}\Omega} (v_C - v_B) = \frac{1}{8 \text{ k}\Omega} (-27.71 \text{ V}) = \underline{\underline{-3.46 \text{ V}}}$$

$$v_x = v_B = \underline{\underline{12.71 \text{ V}}}$$

