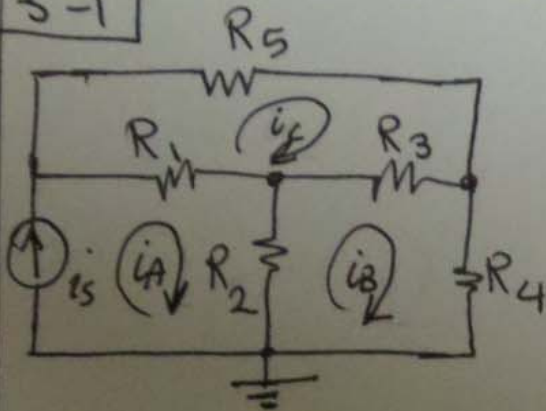


Homework #4 — Solutions

Page 1

3-1



We drop the row associated to loop (A) and write the equations for the other two loops by inspection:

$$\begin{pmatrix} \times & \times & \times \\ -R_2 & R_2+R_3+R_4 & -R_3 \\ -R_1 & -R_3 & R_1+R_3+R_5 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} \times \\ 0 \\ 0 \end{pmatrix}$$


for loop (A) we have:

$$i_A = i_s$$

We can also write $i_A = i_s$ in the matrix form $\begin{pmatrix} 1 & 0 & 0 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} i_s \\ 0 \\ 0 \end{pmatrix}$ and insert it into the matrix form above

$$\Rightarrow \underbrace{\begin{pmatrix} 1 & 0 & 0 \\ -R_2 & R_2+R_3+R_4 & -R_3 \\ -R_1 & -R_3 & R_1+R_3+R_5 \end{pmatrix}}_A \underbrace{\begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix}}_{\underline{x}} = \underbrace{\begin{pmatrix} i_s \\ 0 \\ 0 \end{pmatrix}}_{\underline{b}} \Rightarrow A\underline{x} = \underline{b}$$

3-3

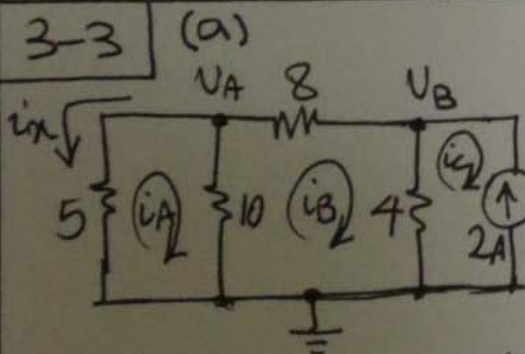

$$\textcircled{A} \begin{pmatrix} 5+10 & -10 & 0 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\textcircled{B} \begin{pmatrix} -10 & 10+8+4 & -4 \end{pmatrix}$$

$$\textcircled{C}: i_C = -2A$$

Gaussian Elimination: $\begin{pmatrix} 15 & -10 & 0 & 0 \\ -10 & 22 & -4 & 0 \end{pmatrix} \xrightarrow{\substack{2/3 \text{ row 1} \\ + \text{ row 2}}} \begin{pmatrix} 15 & -10 & 0 & 0 \\ 0 & \frac{46}{3} & -4 & 0 \end{pmatrix}$

$$\Rightarrow \frac{46}{3} i_B - 4 i_C = 0 \Rightarrow i_B = \frac{3 \times 4}{46} i_C = \frac{3 \times 4}{46} (-2) = -\frac{12}{23} A$$

$$15 i_A - 10 i_B = 0 \Rightarrow i_A = \frac{2}{3} i_B = -\frac{8}{23} A$$


$$(b) \quad v_A = 10(i_A - i_B) = 10\left(-\frac{8}{23} + \frac{18}{23}\right) = \frac{40}{23} = \underline{1.7391 V}$$

$$v_B = 4(i_B - i_C) = 4\left(-\frac{12}{23} + 2\right) = \frac{136}{23} = \underline{5.913 V}$$

$$(c) \quad v_n = v_B = 5.913 V$$

$$i_n = -i_A = \frac{8}{23} = 0.347826 A = \underline{347.826 mA}$$

3-4

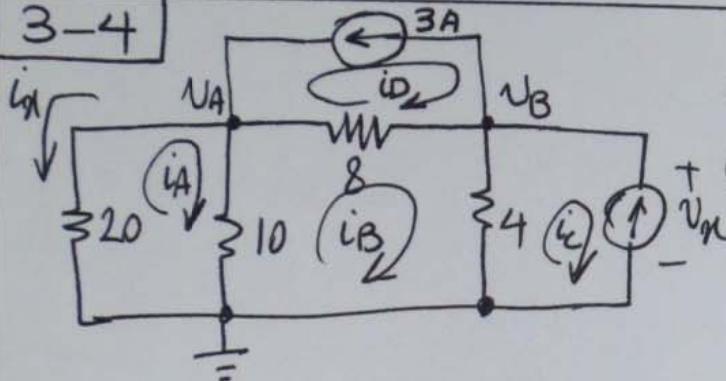

$$\begin{aligned} \textcircled{A} & \begin{pmatrix} 20+10 & -10 & 0 & 0 \\ -10 & 10+4+8 & -4 & -8 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \\ i_D \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \end{pmatrix} \\ \textcircled{B} & \quad i_C = -1 A \\ & \quad i_D = -3 A \end{aligned}$$

$$\text{Gaussian Elimination} \Rightarrow i_A = -0.5 A, \quad i_B = -1.5 A$$

$$(b) \quad v_A = -20 i_A = -20(-0.5) = \underline{10 V}$$


$$v_B = 4(i_B - i_C) = 4(-1.5 + 1) = \underline{-2 V}$$

$$(c) \quad v_n = v_B = \underline{-2 V}$$

$$i_n = -i_A = \underline{0.5 A}$$

3-5

(a)

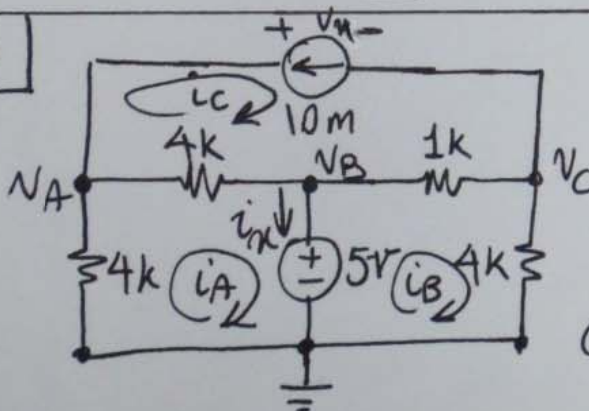

$$\begin{aligned} \textcircled{A} & \begin{pmatrix} 4+4 & 0 & -4 \\ 0 & 1+4 & -1 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} -5 \\ 5 \end{pmatrix} \\ \textcircled{B} & \quad i_C = -10 mA \end{aligned}$$

$$\text{G.E.} \Rightarrow i_A = -5.625 mA$$


$$i_B = -1 mA$$

$$(b) \quad v_A = -4 i_A = \underline{22.5 V}$$

$$v_C = 4 i_B = \underline{-4 V}$$

$$(c) \quad v_n = v_A - v_C = 22.5 + 4 = \underline{26.5 V}, \quad i_n = i_A - i_B = -4.625 mA$$

3-13

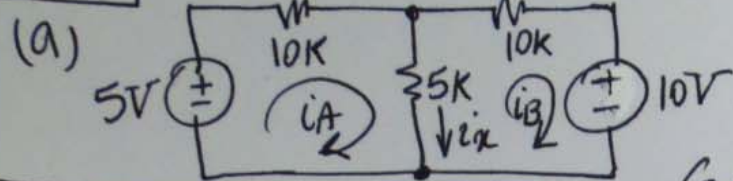

$$\begin{pmatrix} 10+5 & -5 \\ -5 & 10+5 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} 5 \\ -10 \end{pmatrix}$$

G.E. $\Rightarrow i_A = \frac{1}{8} \text{ mA}, i_B = -\frac{5}{8} \text{ mA}$
 $= 125 \mu\text{A} \quad = -625 \mu\text{A}$


(b)

(c) $v_x = 10 i_A = 10 \times \frac{1}{8} = \frac{5}{4} = 1.25 \text{ V}$

$i_x = i_A - i_B = \frac{1}{8} + \frac{5}{8} = \frac{3}{4} \text{ mA} = 750 \mu\text{A}$

3-17

(a)

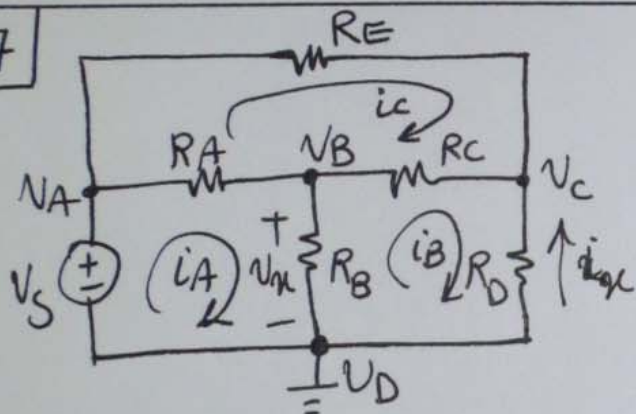

$$\begin{pmatrix} R_A+R_B & -R_B & -R_A \\ -R_B & R_B+R_C+R_D & -R_C \\ -R_A & -R_C & R_A+R_C+R_D \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} V_S \\ 0 \\ 0 \end{pmatrix}$$

(b) (B) $\begin{pmatrix} -\frac{1}{R_A} & \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_E} & -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{pmatrix} \begin{pmatrix} v_A \\ v_B \\ v_C \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \end{pmatrix}$

$v_A = V_S$

(c) Node-Voltage Analysis:

number of nodes (excluding ground) = 3

number of voltage sources = 1

$\Rightarrow 3-1=2$ unknowns $\rightarrow$ 2 equations required

Mesh-Current Analysis:

number of meshes = 3


number of current sources = 0

$\Rightarrow 3-0=3$ unknowns $\rightarrow$ 3 equations required

$\Rightarrow$ Node-voltage analysis is easier to solve because there are fewer unknowns/equations

3-20

(a)

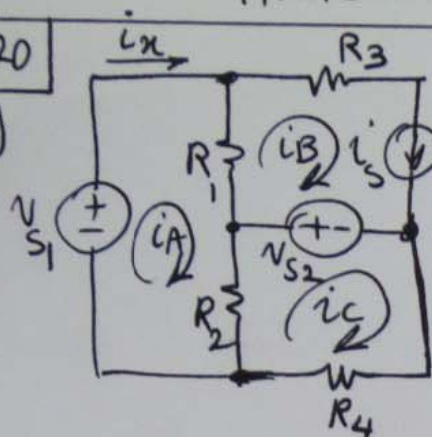

$$\textcircled{A} \begin{pmatrix} R_1 + R_2 & -R_1 & -R_2 \\ -R_2 & 0 & R_2 + R_4 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} V_{S1} \\ -V_{S2} \\ 0 \end{pmatrix}$$

$i_B = i_C$

(b) Note: It is easier to solve this problem by node-voltage analysis, because there is only one unknown.

(c) $R_1 = R_2 = 5.6k, R_3 = 2.2k, R_4 = 1.5k,$

$i_s = 3mA, V_{S1} = 15V, V_S = 5V$

G.E. $\Rightarrow i_A = 4.11mA, i_B = 3mA, i_C = 2.53mA$


$i_x = i_A = 4.11mA$

$V_x = V_{S2} - R_1(i_B - i_A) - R_3 i_B = 5 - 5.6(3 - 4.11) - 2.2 \times 3 = 4.6V$

(d) $p = V_{S1} \cdot i_x = 15 \times 4.11 = 61.6W$

3-22

(a)

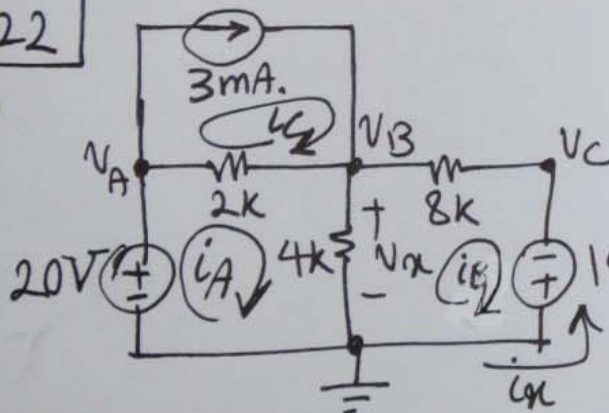

$$\textcircled{A} \begin{pmatrix} 2+4 & -4 & -2 \\ -4 & 4+8 & 0 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \\ i_C \end{pmatrix} = \begin{pmatrix} 20 \\ 15 \end{pmatrix}$$

$i_C = 3mA$

(b) $\textcircled{B} \begin{pmatrix} -\frac{1}{2} & \frac{1}{2} + \frac{1}{4} + \frac{1}{8} & -\frac{1}{8} \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = (3)$

$V_A = 20V$

$V_C = -15V$

(c) Node-Voltage:

number of nodes (excluding ground) = 3

number of voltage sources = 2

 $\Rightarrow$ number of unknown/equations = $3 - 2 = 1$

mesh-current:

number of meshes = 3

number of current sources = 1

 $\Rightarrow$ number of unknowns/equations = $3 - 1 = 2$ $\Rightarrow$ Node-Voltage equations are easier to solve

(d) Part (b): $-\frac{1}{2}V_A + (\frac{1}{2} + \frac{1}{4} + \frac{1}{8})V_B - \frac{1}{8}V_C = 3$




$\Rightarrow -\frac{1}{2}(20) + \frac{7}{8}V_B - \frac{1}{8}(-15) = 3$

$\Rightarrow V_B = \frac{89}{7} = \underline{12.71 \text{ V}}$

$V_A = V_B = \underline{12.71 \text{ V}}$

$i_n = \frac{V_C - V_B}{8} = \frac{-15 - \frac{89}{7}}{8} = -\frac{194}{7 \times 8} = \underline{-3.46 \text{ mA}}$

3-37

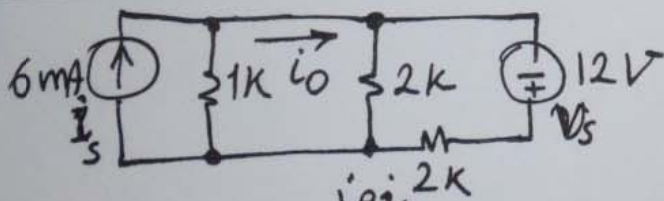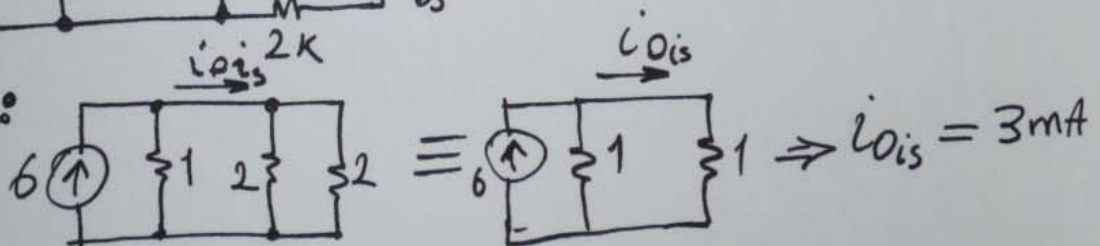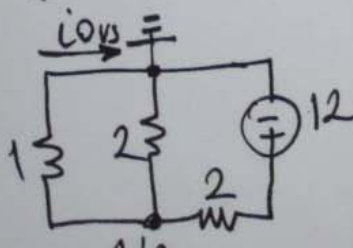response to i_s :(turn off V_s)response to V_s :(turn off i_s)


KCL at (A): $\frac{V_A - 12}{2} + \frac{V_A}{2} + \frac{V_A}{1} = 0$

$\Rightarrow V_A = 3$


$\Rightarrow i_{o_{V_s}} = \frac{V_A}{1} = 3 \text{ mA}$

$$\Rightarrow i_0 = i_{0is} + i_{0vs} = 3 + 3 = \underline{6 \text{ mA}}$$

3-39

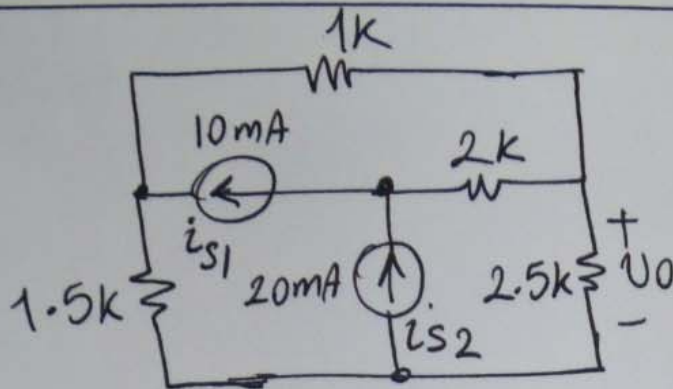

response to i_{s1} :
(turn off i_{s2})

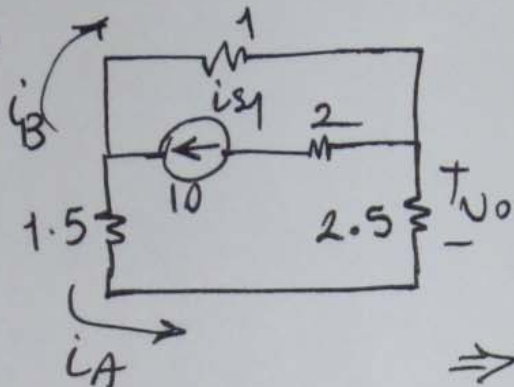


current division rule:

$$i_A = 10 \frac{1}{1.5 + 2.5 + 1} = 2 \text{ mA}$$

$$\Rightarrow v_{0is_1} = -i_A \times 2.5 = -5 \text{ V}$$

response to i_{s2} :
(turn off i_{s1})

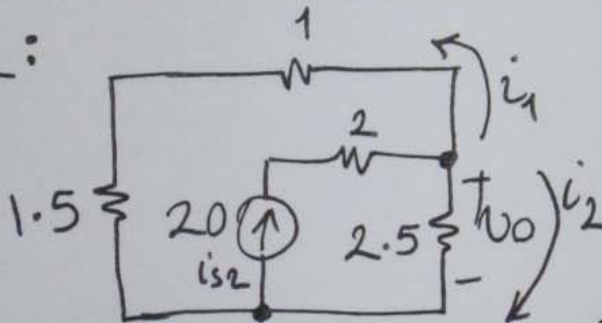

current division rule:

$$i_2 = 20 \frac{1 + 1.5}{1 + 1.5 + 2.5} = 10 \text{ mA}$$

$$\Rightarrow v_{0is_2} = 2.5 i_2 = 25 \text{ V}$$

$$\Rightarrow v_0 = v_{0is_1} + v_{0is_2} = -5 + 25 = \underline{20 \text{ V}}$$

End