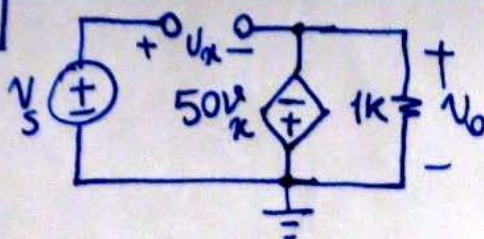



4-5



$$v_x = V_s - (-50v_x) = V_s + 50v_x \Rightarrow v_x = -\frac{V_s}{49}$$

$$v_o = -50v_x = -50\left(-\frac{V_s}{49}\right) = \frac{50}{49}V_s \Rightarrow \frac{v_o}{V_s} = \frac{50}{49}$$

4-6

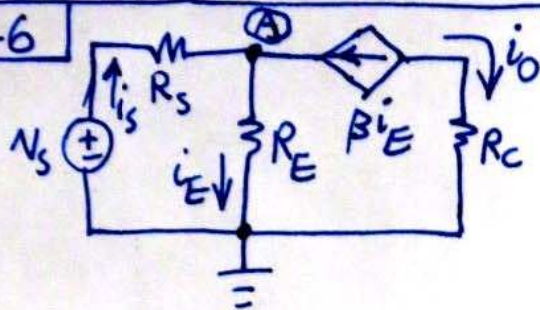


$$\text{KCL at } \textcircled{A}: i_E - \beta i_E - i_s = 0$$

$$\Rightarrow \frac{i_E}{i_s} = \frac{1}{1-\beta}$$

$$i_o = -\beta i_E \Rightarrow \frac{i_o}{i_s} = \frac{-\beta i_E}{i_s} = \frac{-\beta}{1-\beta} = \frac{\beta}{\beta-1}$$

4-23

(a)

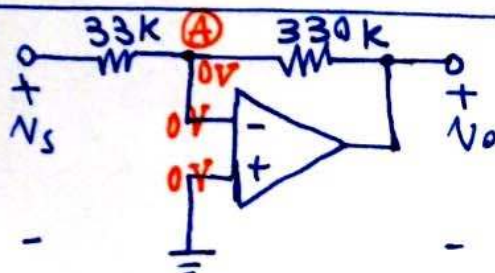


$V_A = 0$ due to the virtual short-circuit between op-amp input terminals

$$\text{KCL at } \textcircled{A}: \frac{0-V_s}{33} + \frac{0-v_o}{330} = 0$$

$$\Rightarrow \frac{v_o}{V_s} = -\frac{330}{33} = -10$$


(b)

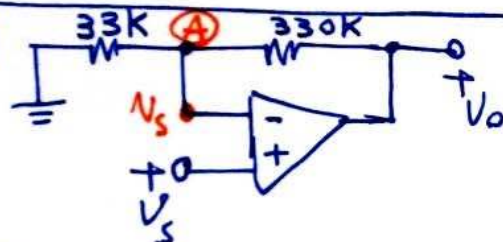

$$V_A = V_s$$

$$\text{KCL at } \textcircled{A}: \frac{V_s}{33} + \frac{V_s - v_o}{330} = 0 \Rightarrow \frac{v_o}{V_s} = 11$$

4-27

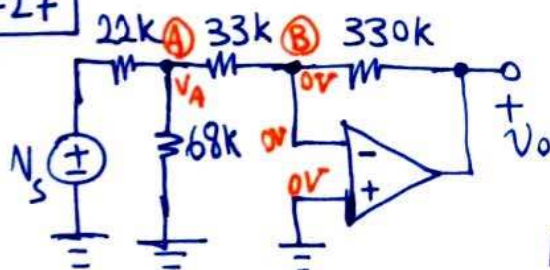

$$V_B = 0V$$


$$\text{KCL at } \textcircled{A}: \frac{V_A}{68} + \frac{V_A - V_s}{22} + \frac{V_A - 0}{33} = 0$$

$$\Rightarrow V_A = 0.5025V_s$$

$$\text{KCL at } \textcircled{B}: \frac{0 - V_A}{33} + \frac{0 - v_o}{330} = 0 \Rightarrow v_o = -10V_A$$

$$\Rightarrow \frac{v_o}{V_s} = -10 \frac{V_A}{V_s} = -5.025$$

4-28

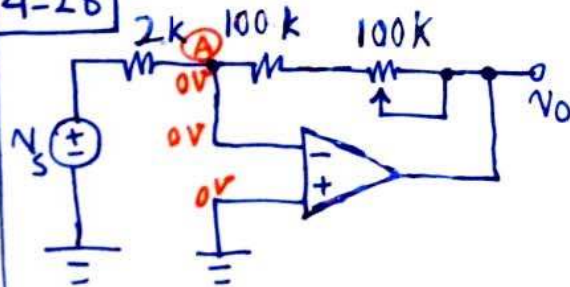

$$V_A = 0$$


$$\text{KCL at } \textcircled{A}: \frac{0 - V_s}{2} + \frac{0 - v_o}{100+R} = 0 \Rightarrow \frac{v_o}{V_s} = -\frac{100+R}{2}$$

$$0 \leq R \leq 100k \Rightarrow \frac{100+0}{2} \leq -\frac{v_o}{V_s} \leq \frac{100+100}{2}$$

$$\Rightarrow 50 \leq -\frac{v_o}{V_s} \leq 100$$

4-31

(a)

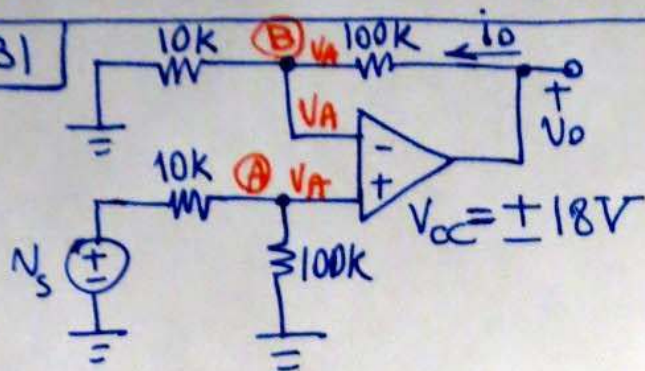

$$V_A = V_B$$

Voltage division rule: $V_A = V_s \frac{100}{100+10}$
 $= \frac{10}{11} V_s$

KCL at (B): $\frac{V_A}{10} + \frac{V_A - V_o}{100} = 0 \Rightarrow V_o = 11 V_A$

$$\Rightarrow V_o = 11 \left(\frac{10}{11} V_s \right) = 10 V_s$$

Note: $V_o = 10 V_s$ provided the OpAmp is not saturated, i.e., $-V_{cc} \leq V_o \leq V_{cc}$

$$\Rightarrow -V_{cc} \leq 10 V_s \leq V_{cc} \Rightarrow -18 \leq 10 V_s \leq 18 \Rightarrow -1.8 \leq V_s \leq 1.8$$

$$\Rightarrow V_o = \begin{cases} -18V, & V_s < -1.8 \\ 10 V_s, & -1.8 \leq V_s \leq 1.8 \\ 18V, & 1.8 < V_s \end{cases}$$

range of values V_s without saturating the OpAmp

(b) $V_s = 0.5V \Rightarrow -1.8 \leq V_s \leq 1.8 \rightarrow$ OpAmp is not saturated


$$i_o = \frac{V_o - V_A}{100} = \frac{10 V_s - \frac{10}{11} V_s}{100} = \frac{1}{11} V_s = \frac{1}{11} (0.5) \text{ mA} = 45.45 \mu\text{A}$$

$V_s = 2V \Rightarrow V_s > 1.8 \rightarrow$ OpAmp is saturated $\rightarrow V_o = 18V$

$$i_o = \frac{V_o - V_A}{100} = \frac{18 - \frac{10}{11} V_s}{100} = \frac{18 - \frac{10}{11} \times 2}{100} = 0.161818 \text{ mA} = 161.818 \mu\text{A}$$

4.34

(a)

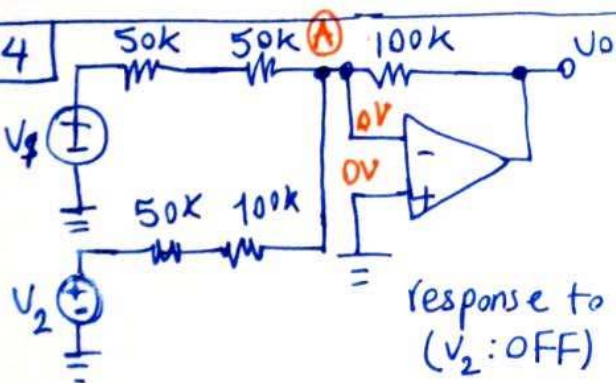

We can find V_o in terms of V_1 and V_2 by writing a KCL at (A). However, it is easier to find using superposition principle.

response to V_1 : Inverting Amp $\rightarrow V_{o1} = -\frac{100}{50+50} V_1$
 $= -V_1$ (V_2 : OFF)


response to V_2 : Inverting Amp $\rightarrow V_{o2} = -\frac{100}{100+50} V_2$
 $= -\frac{2}{3} V_2$

$$\Rightarrow V_o = V_{o1} + V_{o2} = -V_1 - \frac{2}{3} V_2$$

$$(b) -V_{CC} \leq V_0 \leq V_{CC} \Rightarrow -15 \leq -V_1 - \frac{2}{3}V_2 \leq 15$$

$$V_1 = 1V \Rightarrow -14 \leq -\frac{2}{3}V_2 \leq 16 \Rightarrow \boxed{-24 \leq V_2 \leq 21}$$

4.37

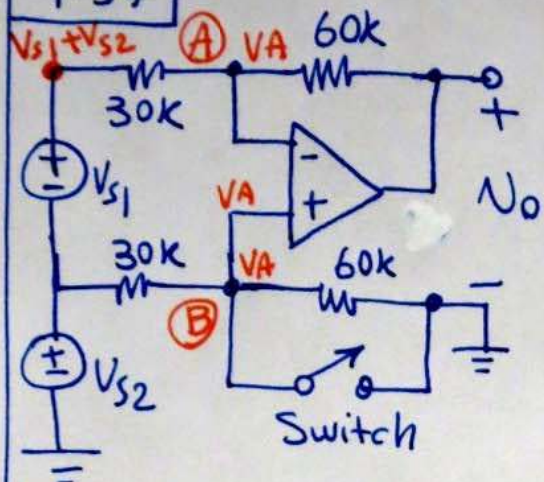

Switch open:

$$\text{KCL at } \textcircled{A}: \frac{V_A - (V_{s1} + V_{s2})}{30} + \frac{V_A - V_0}{60} = 0$$

$$\text{KCL at } \textcircled{B}: \frac{V_A - V_{s2}}{30} + \frac{V_A - 0}{60} = 0$$

$$\Rightarrow V_A = \frac{2}{3}V_{s2}$$


$$\text{Substituting } V_A \text{ in KCL } \textcircled{A} \Rightarrow \boxed{V_0 = -2V_{s1}}$$

Switch closed: $\Rightarrow V_A = 0$

$$\text{KCL at } \textcircled{A}: \frac{0 - (V_{s1} + V_{s2})}{30} + \frac{0 - V_0}{60} = 0$$

$$\Rightarrow \boxed{V_0 = -2(V_{s1} + V_{s2})}$$

4.39

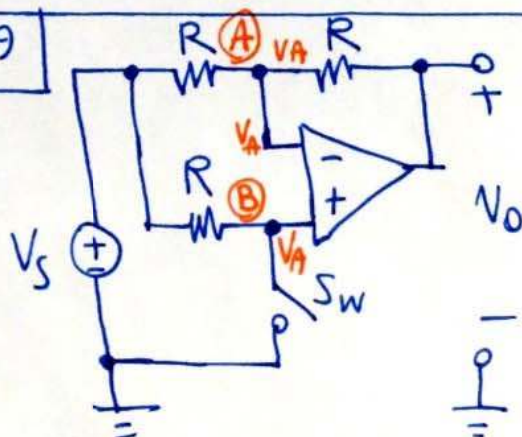

Switch open:

$$\text{KCL at } \textcircled{A}: \frac{V_A - V_s}{R} + \frac{V_A - V_0}{R} = 0$$

$$\Rightarrow V_0 = 2V_A - V_s$$


$$\text{KCL at } \textcircled{B}: \frac{V_B - V_s}{R} = 0 \Rightarrow V_A = V_s$$

$$\text{Substituting } V_A \text{ in KCL } \textcircled{A} \Rightarrow \boxed{V_0 = V_s}$$

Switch closed: $V_A = 0$

$$\text{KCL at } \textcircled{A}: \frac{0 - V_s}{R} + \frac{0 - V_0}{R} = 0 \Rightarrow \boxed{V_0 = -V_s} \rightarrow \text{The claim is false}$$

4.42

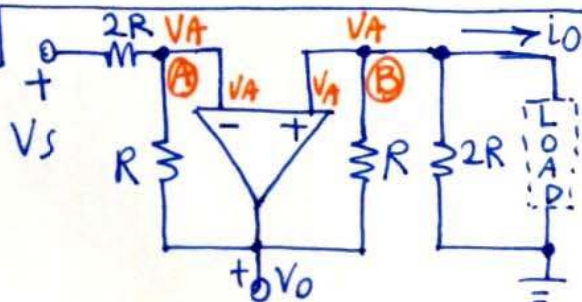

$$V_B = V_A$$

$$\text{KCL at } \textcircled{A}: \frac{V_A - V_s}{2R} + \frac{V_A - V_0}{R} = 0$$

$$\text{KCL at } \textcircled{B}: \frac{V_A - V_0}{R} + \frac{V_A}{2R} + i_0 = 0$$

$$\textcircled{B} - \textcircled{A} \Rightarrow \frac{V_s}{2R} + i_0 = 0 \Rightarrow \boxed{i_0 = -\frac{V_s}{2R}}$$