

MAE140 - Linear Circuits - Fall 2012
Midterm, November 1st

Instructions

1. This exam is open book. You may use whatever written materials you choose, including your class notes and textbook. You may use a hand calculator with no communication capabilities
2. You have 70 minutes
3. Write your answers on your “Blue Book”
4. Do not forget to write your name, student number, and instructor

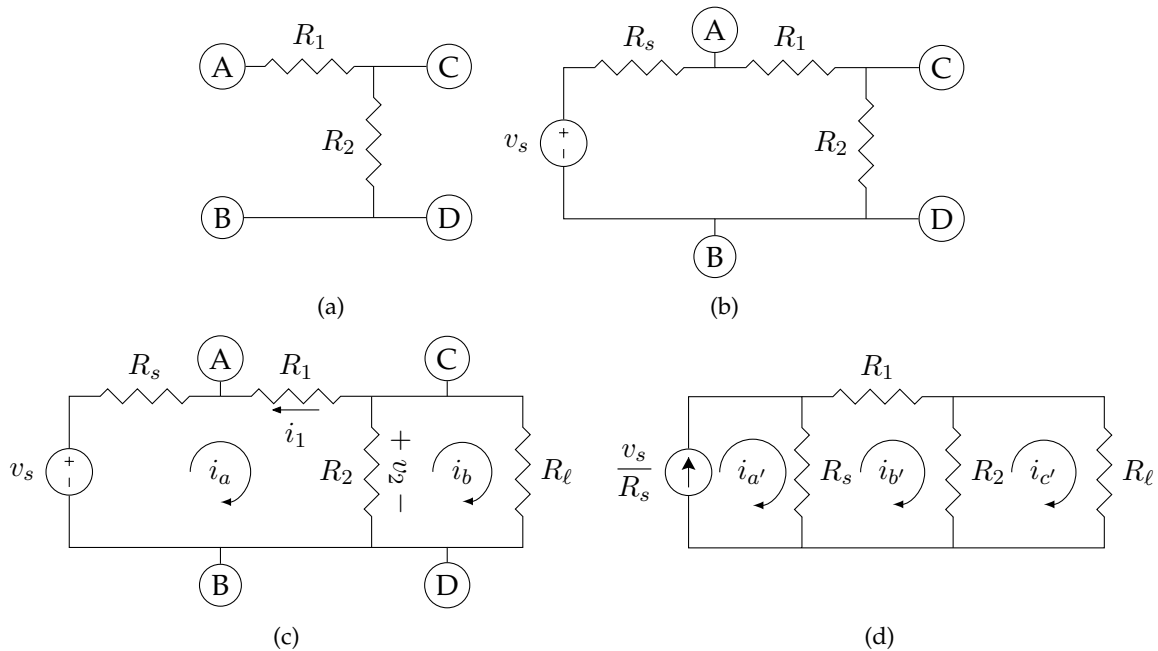


Figure 1: Circuits for Questions 1 and 2.


1. Equivalent Circuits

The circuit in Fig. 1(a) is an *L-Pad Attenuator*. Answer the following questions:

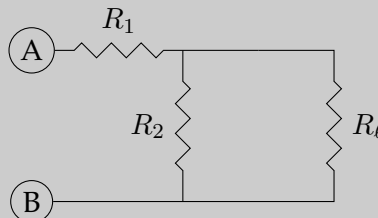- (a) (3 points) Show that when a (load) resistance R_ℓ is connected to terminals (C) and (D) the equivalent resistance as seen from terminals (A) and (B) is equal to

$$R_{AB} = \frac{R_1(R_2 + R_\ell) + R_2R_\ell}{R_2 + R_\ell}.$$

Solution: After connecting the load resistance R_ℓ we obtain the circuit



in which R_2 is in parallel with R_ℓ . (+1 point)

The parallel association of R_2 and R_ℓ is then in series with R_1 . (+1 point)


Hence

$$R_{AB} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_\ell}} = R_1 + \frac{R_2 R_\ell}{R_2 + R_\ell} = \frac{R_1(R_2 + R_\ell) + R_2 R_\ell}{R_2 + R_\ell}. \quad (+1 \text{ point})$$

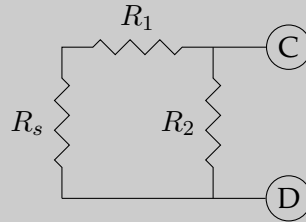- (b) (3 points) Show that when a (source) resistance R_s is connected to terminals (A) and (B) the equivalent resistance as seen from terminals (C) and (D) is equal to

$$R_{CD} = \frac{R_2(R_1 + R_s)}{R_2 + R_1 + R_s}.$$

Solution: After connecting the source resistance R_s we obtain the circuit



in which R_1 is in series with R_s . (+1 point)

The series association of R_1 and R_s is then in parallel with R_2 . (+1 point)

Hence

$$R_{CD} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_1 + R_s}} = \frac{R_2(R_1 + R_s)}{R_2 + R_1 + R_s}. \quad (+1 \text{ point})$$

- (c) (2 points (bonus)) Verify that when a (source) resistance R_s is connected to terminals (A) and (B) and

$$R_2 = \frac{R_\ell(R_1 + R_s)}{R_1 + R_s - R_\ell}, \quad R_1 \geq R_\ell - R_s, \quad R_1 \geq 0$$

then $R_{CD} = R_\ell$.

Solution: Substitute the given formula for R_2 into R_{CD} calculated in part (b):

$$\begin{aligned} R_{CD} &= \frac{\frac{R_\ell(R_1 + R_s)^2}{R_1 + R_s - R_\ell}}{\frac{R_\ell(R_1 + R_s)}{R_1 + R_s - R_\ell} + R_1 + R_s} \quad (+1 \text{ point}) \\ &= \frac{R_\ell(R_1 + R_s)^2}{R_\ell(R_1 + R_s) + (R_1 + R_s)(R_1 + R_s - R_\ell)} \\ &= \frac{R_\ell(R_1 + R_s)}{R_\ell + R_1 + R_s - R_\ell} = R_\ell \end{aligned}$$

Plus one point for correct conclusion. (+1 point)

2. Thévenin Equivalence and Voltage Division

Connect a voltage source v_s with resistance R_s to terminals (A) and (B) as shown in Fig. 1(b). Answer the following questions:

- (a) (2 points) Use voltage division to show that the Thévenin equivalent circuit as seen from terminals (C) and (D) has resistance and voltage

$$R_T = \frac{R_2(R_1 + R_s)}{R_1 + R_2 + R_s}, \quad v_T = K v_s, \quad K = \frac{R_T}{R_1 + R_s}.$$

K is the circuit's *voltage attenuation*.

Hint: Use the answers to Question 1.

Solution: When the voltage source is $v_s = 0$ we obtain the circuit of Question 1 part (b). Hence

$$R_T = R_{CD} = \frac{R_2(R_1 + R_s)}{R_1 + R_2 + R_s}. \quad (+0.5 \text{ point})$$

The Thévenin voltage is obtained from the open-circuit as in Fig. 1(b) through voltage-division as

$$v_T = \frac{R_2}{R_1 + R_2 + R_s} v_s. \quad (+1 \text{ point})$$

Note that

$$v_T = \frac{R_2(R_1 + R_s)}{R_1 + R_2 + R_s} \frac{1}{R_1 + R_s} v_s = \frac{R_T}{R_1 + R_s} v_s = K v_s. \quad (+0.5 \text{ point})$$

NOTE TO GRADERS: Students may also derive the equivalence through open-circuit and short-circuit calculations.

- (b) (2 points) When R_1 and R_2 are selected as in part (c) of Question 1, that is

$$R_2 = \frac{R_\ell(R_1 + R_s)}{R_1 + R_s - R_\ell}, \quad R_1 \geq R_\ell - R_s, \quad R_1 \geq 0,$$

then

$$R_T = R_\ell, \quad K = \frac{R_\ell}{R_1 + R_s}.$$


With such values of R_1 and R_2 , connect a load resistance R_ℓ to terminals (C) and (D) as shown in Fig. 1(c). Show that the power absorbed by the load is

$$p_\ell = \frac{K^2}{4} p_0, \quad p_0 = \frac{v_s^2}{R_\ell}.$$

K^2 is the circuit's *power attenuation*.

Hint: Use part (a) and voltage division.

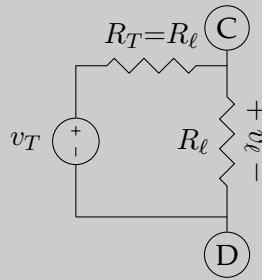Solution: After connecting the load R_ℓ and substituting the circuit on the left of the terminals (C) and (D) by its Thévenin equivalent we obtain the voltage divider:



(+1 point)

The voltage across the load resistance R_ℓ can be computed recalling that $R_T = R_\ell$ and using voltage division:

$$v_\ell = \frac{R_\ell}{R_\ell + R_\ell} v_T = \frac{1}{2} v_T = \frac{K}{2} v_s. \quad (+0.5 \text{ point})$$

The power absorbed by the load is then

$$p_\ell = \frac{v_\ell^2}{R_\ell} = \frac{K^2}{4} \frac{v_s^2}{R_\ell} = \frac{K^2}{4} p_0. \quad (+0.5 \text{ point})$$

- (c) (2 points) Calculate values for the resistors $R_1 \geq 0$ and $R_2 \geq 0$ to design an L-Pad Attenuator in which $R_T = R_\ell = 50\Omega$ (as in a coaxial input connector) is connected to a voltage source with resistance $R_s = 300\Omega$ (as in a VHF or FM radio antenna) and achieve a voltage attenuation $K = 0.1$. *Hint: Use the expressions in part (b).*

Solution: From $K = 1/10$, $R_\ell = 50\Omega$, $R_s = 300\Omega$ we determine

$$\frac{1}{10} = \frac{50}{R_1 + 300} \quad \Rightarrow \quad R_1 = 500 - 300 = 200\Omega \quad (+1 \text{ point})$$

and then

$$R_2 = \frac{50(200 + 300)}{200 + 300 - 50} = \frac{2500}{45} \approx 56\Omega. \quad (+1 \text{ point})$$

- (d) (2 points (bonus)) Use the resistances R_1 and R_2 you calculated in part (c) to compute the L-Pad input resistance R_{AB} and output resistance R_{CD} as in Question 1 when $R_\ell = 50\Omega$ and $R_s = 300\Omega$. In which way does the circuit match the source and load resistances?

Solution: Substituting R_1 and R_2 we obtain

$$R_{AB} = 200 + \frac{56 \times 50}{56 + 50} \approx 226\Omega, \quad R_{CD} = \frac{56(200 + 300)}{56 + 200 + 300} \approx 50\Omega. \quad (+1 \text{ point})$$

The circuit makes the Thévenin resistance $R_T = R_{CD} \approx 50\Omega$ as seen from (C) and (D) be very close to the load 50Ω resistance. It makes the resistance $R_{AB} \approx 226\Omega$ as seen from (A) and (B) be close but not equal to the source 300Ω resistance. (+1 point)

3. Mesh Current Analysis

Consider the circuits in Fig. 1(c) and Fig. 1(d).

- (a) (3 points) Formulate mesh-current equations for the circuit in Fig. 1(c). Use the mesh currents and labels provided in the figure and clearly indicate the final equations and circuit variable unknowns.

Solution: Writing the KVL equations by inspection in terms of the mesh currents we obtain the current equations:

$$\begin{bmatrix} R_s + R_1 + R_2 & -R_2 \\ -R_2 & R_\ell + R_2 \end{bmatrix} \begin{pmatrix} i_a \\ i_b \end{pmatrix} = \begin{pmatrix} v_s \\ 0 \end{pmatrix} \quad (+2 \text{ points})$$

which need to be solved in terms of the mesh currents i_a and i_b . (+1 point)

- (b) (2 points) Show how the current i_1 and the voltage v_2 are related to the mesh currents.

Solution: The current i_1 is obtained directly from the mesh current i_a as

$$i_1 = -i_a. \quad (+1 \text{ point})$$

The voltage v_2 is obtained after using Ohm's law

$$v_2 = R_2(i_a - i_b). \quad (+1 \text{ point})$$

- (c) (1 point) Without writing any equations, show how the mesh currents in the circuit in Fig. 1(d) are related to the mesh currents in the circuit in Fig. 1(c). Calculate $i_{a'}$, $i_{b'}$ and $i_{c'}$ as a function of i_a and i_b .

Solution: The circuits are equivalent because the current source is obtained from the voltage source through a source transformation. As a results of this equivalence

$$i_{b'} = i_a, \quad i_{c'} = i_b, \quad i_{a'} = \frac{v_s}{R_s}. \quad (+1 \text{ point})$$