

1-10/

- $V = 9.6V$
- 50mA fuse
- 1.5W charger.

Need to determine current flowing through the fuse. If it exceeds 50mA then the fuse will blow.

$$P = VI$$

$$\Rightarrow I = \frac{P}{V} = \frac{1.5}{9.6} = 0.15625 \text{ Amps} = \underline{\underline{156.25 \text{ mA}}}$$

$$156.25 > 50$$

HENCE THE FUSE WILL BLOW

OR:

$$P = VI$$

$$= 9.6 \times 50 \times 10^{-3}$$

$$= 0.48W < 1.5W$$

so the fuse will

blow.

1-16/

- 5A fuse
- 25 bulbs per string
- Each bulb rated at 7W

Need to determine the maximum number of strings that can be connected without blowing the fuse.


How much power consumed per string? $7 \times 25 = \underline{\underline{175W}}$

Maximum power able to be delivered before fuse blows? $120 \times 5 = 600W$.

So, maximum number of strings is $\frac{600}{175} = \underline{\underline{3.43}}$

We need to round down to 3 strings, 4 strings will blow the fuse.

1-22

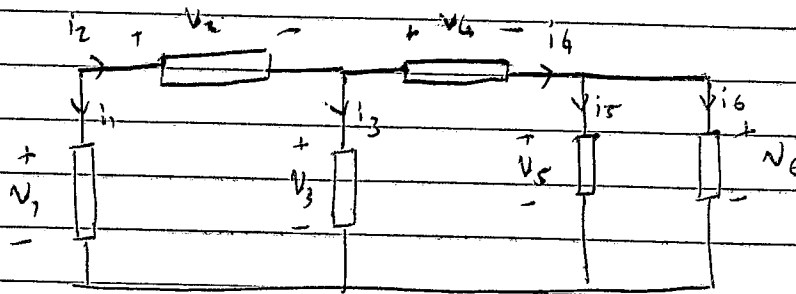

DEVICE	V	I	P	Absorb/Deliver?
#1	15	-1	-15	DELIVER
#2	5	1	5 W	ABSORB
#3	10	2	20 W	ABSORB
#4	-10	-1	10 W	ABSORB
#5	20	-3	-60 W	DELIVER
#6	20	2	40	ABSORB

check balance:

$\sum \text{absorbing} + \sum \text{delivering}$

$$= -15 + 5 + 20 + 10 - 60 + 40$$

$$= 0$$

0

$$V = 15V,$$

$$P_R = 25mW$$

Find the resistance.

$$P = VI, \quad V = IR$$

$$I = \frac{V}{R}$$

$$\Rightarrow P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$$

$$= \frac{15^2}{(25 \times 10^{-3})} = \frac{9000 \Omega}{1} = \underline{900 \Omega}$$

2-10/

Maximum power rating of resistors: 500V, 0.25W.

Let us first compute case for $R > 1M\Omega$

$$P = \frac{V^2}{R}$$

Given $V = 500V$, we see the power absorbed by the resistor is maximum when the resistance takes its lowest possible value.

Therefore

$$P = \frac{500^2}{1 \times 10^6} = \underline{0.25W}$$

Increasing the resistance above $1M\Omega$ with a constant voltage will reduce the absorbed power below $0.25W$, so

Voltage is the controlling limit.

Now for $R < 1M\Omega$

We have $V = \sqrt{PR}$

Given $P = 6.25W$, we see that the voltage across the resistor is $500V$ when $R = 1 \times 10^6 \Omega$ and decreases with the resistance. Therefore for $R < 1M\Omega$, the power rating of the resistor is the controlling limit.

2-12

Resistance of $5k\Omega$ at $25^\circ C$

Resistance of 340Ω at $100^\circ C$

Formulate two linear equations:

$$(1) \quad 5000 = m(25) + c$$

$$(2) \quad 340 = m(100) + c$$

Rearrange equation 2,

$$c = 340 - 100m$$

sub into (1)

$$5000 = 25m + (340 - 100m)$$

$$4660 = -75m$$

$$m = -62.13$$

$$c = 340 - 100m$$

$$= \underline{6553.3}$$


so, we have a relationship

$$\underline{R = -62.13 T + 6553.3}$$

the

$$1000 = -62.13 T + 6553.3$$
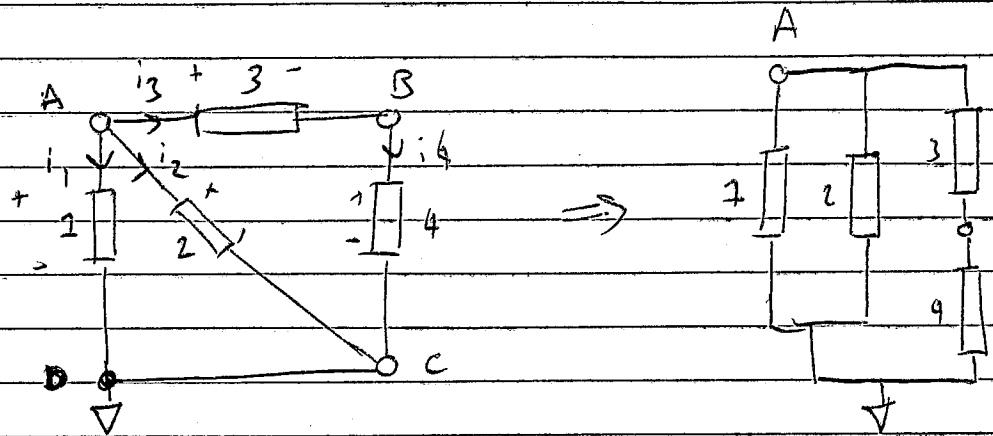
$$\Rightarrow \underline{T = 89.38^\circ C}$$



(a) Nodes: A, B, C.

We note that the connection labelled D is not a node as it is connected by short circuit to node C.

Loops: D-A-C
A-B-C
A-B-C-D

- (b)
- 1 & 2 are connected in parallel
 - 3 & 4 are connected in series
 - ~~The same resistor as of B and C~~ The sum of 3 & 4 are in parallel with 1 & 2.

(c) KCL


Node	Equation
A	$i_1 + i_2 + i_3 = 0$
B	$i_3 = i_4$
C	$i_1 + i_2 + i_4 = 0$

NVL

$$V_1 - V_2 = 0$$

$$V_2 - V_3 - V_4 = 0$$

2-17

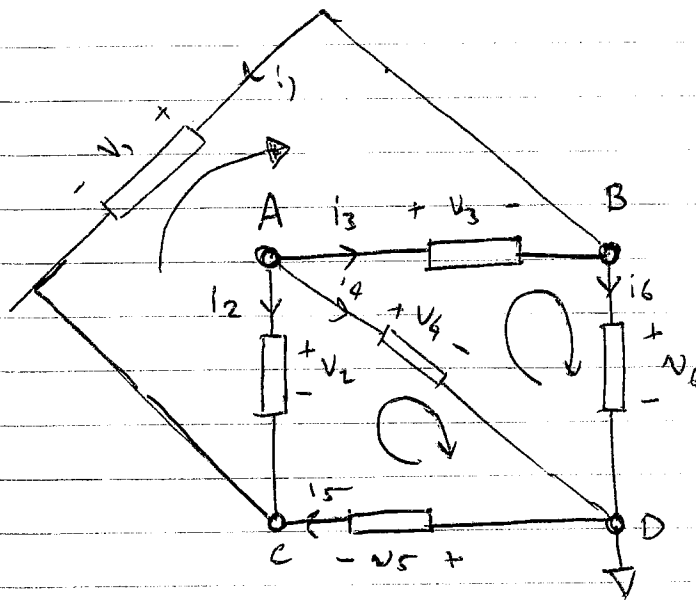

(a) CURRENT NODES : A, B, C, D

VOLTAGE LOOPS : A-D-C , A-B-D , B-D-C , A-B-C

(b) No elements in series or parallel

(c) CURRENT NODES

NODE A : $i_2 + i_3 + i_4 = 0$

NODE B : $i_3 = i_1 + i_6$

NODE C : $i_2 + i_5 = 0$

NODE D : $i_4 + i_6 = i_5$

VOLTAGE LOOPS

$$v_5 - v_2 + v_4 = 0$$


$$v_6 - v_4 + v_3 = 0$$

$$v_2 - v_1 - v_3 = 0$$


2-19

FOR THIS QUESTION, ACTUAL VOLTAGES DO NOT NEED TO BE COMPUTED.

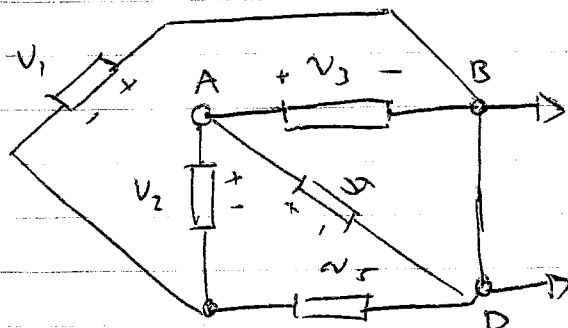Let us redraw the circuit when node B touches ground



This is the same as:

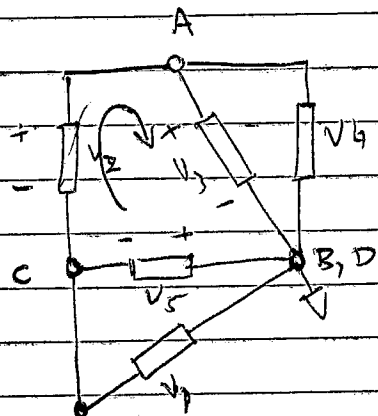

We see that:

$$V_3 = V_4$$


$$V_5 = V_1$$

$$V_5 - V_2 + V_3 = 0$$

$$V_6 = 0$$

2-23

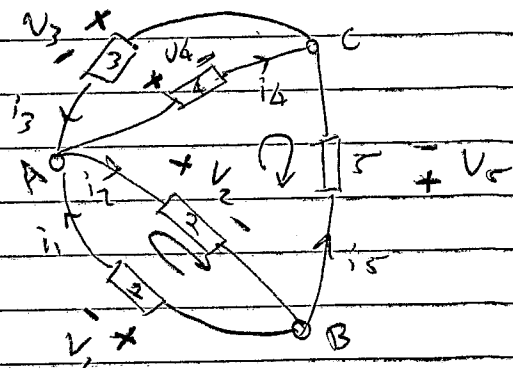(a) With the passive sign convention, the reference direction of current points toward positive terminal. so:



We get the following voltage loops (others may be possible):

$$V_1 + V_2 = 0$$

$$V_5 + V_2 - V_4 = 0$$

$$V_3 + V_4 = 0$$

(b) $V_3 = 0$

$$V_5 = -V_2$$

$$V_1 = -V_2$$

$$V_5 = V_1$$

