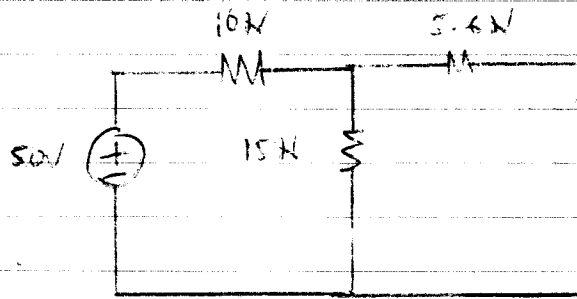



HW3 SOLUTIONS

(i)

3.49




Find V_{th}

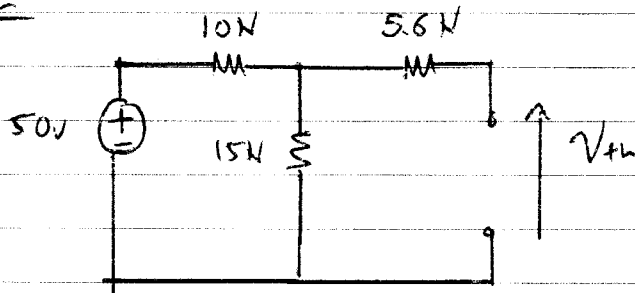


$$V_{th} = \left(\frac{50}{15k + 10k} \right) 15k = \underline{\underline{30V}}$$

Find R_{th}

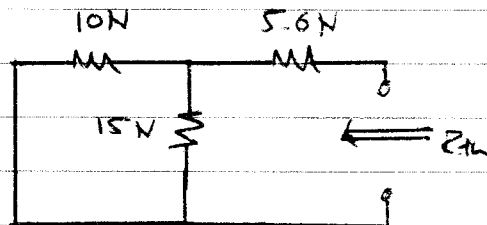


$$R_{th} = 5.6k + \frac{10k \times 15k}{10k + 15k} = \underline{\underline{11.6k}}$$

Find I_{sc}

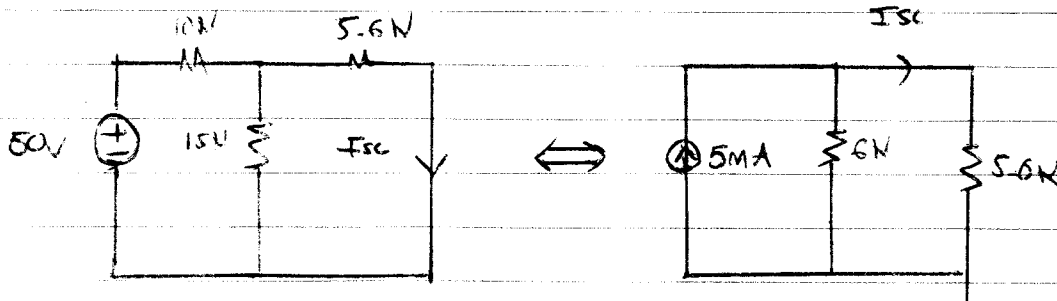


$$I_{sc} = 5mA \times \left(\frac{6k \times 5.6k}{6k + 5.6k} \right) = \underline{\underline{2.585mA}}$$

Thevenin's

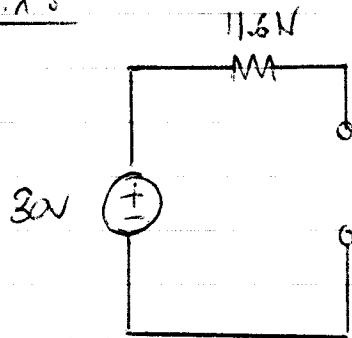


Norton's

(2)

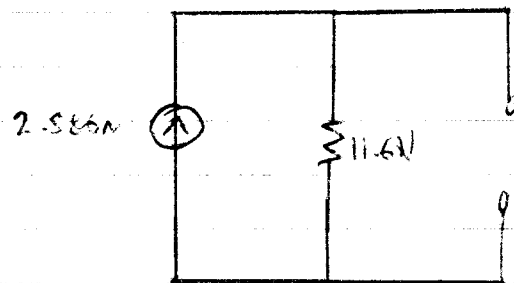

(b) $R_L = 22k\Omega$,

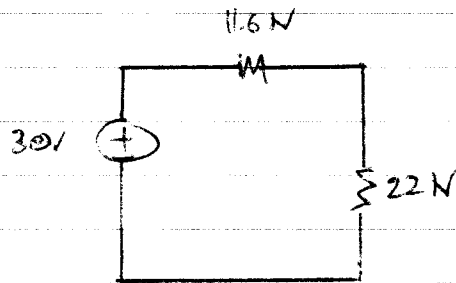


$$I_L = \frac{30}{11.6k + 22k}$$

$$= \underline{0.8929 \text{ mA}}$$

3.50

(c)

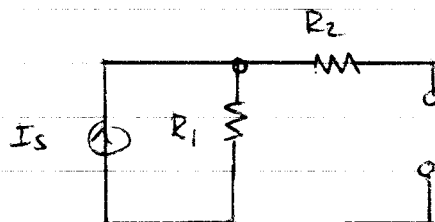

$$R_{th} = R_1 + R_2$$

$$V_{th} =$$


~~$$I_s \times \frac{R_1 R_2}{R_1 + R_2}$$~~

$$I_s \cdot R_1$$


$$I_{sc} = \frac{I_s - \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right)}{R_2} = \frac{I_s \cdot R_1}{R_1 + R_2}$$

3


Thevenin circuit :

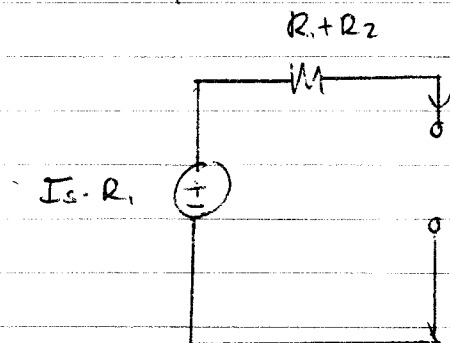

Norton :

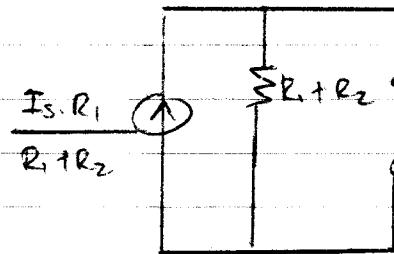

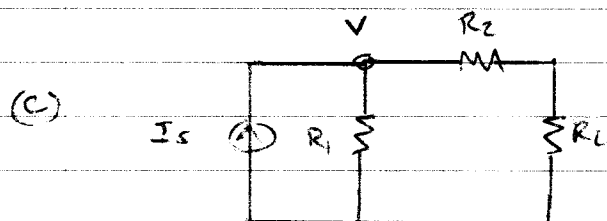(b)
$$I_L = \frac{I_s \cdot R_1}{R_1 + R_2 + R_L}$$




By current division :

$$I_L = \frac{I_s \times (R_2 + R_L) \times R_1}{(R_2 + R_L + R_1)(R_2 + R_L)}$$


$$= \frac{I_s \cdot R_1}{R_2 + R_L + R_1}$$

3.62


(4)

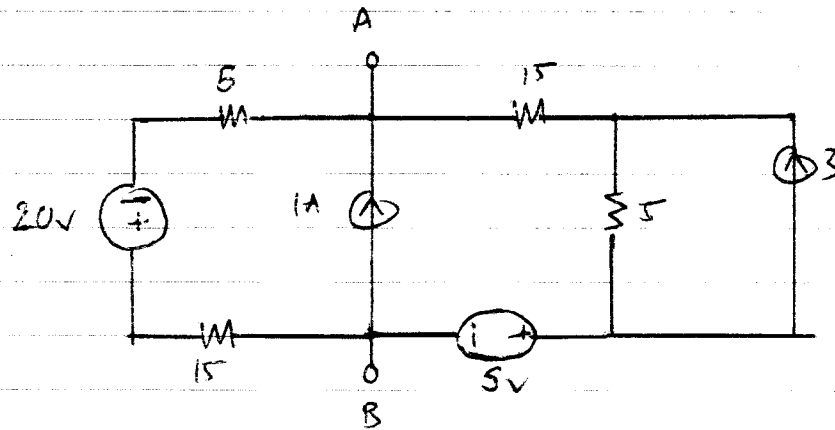

↕

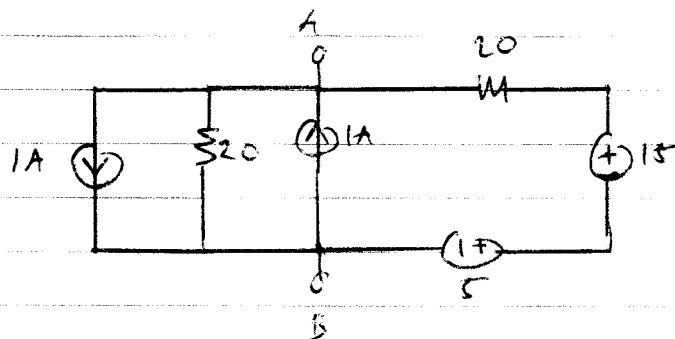

↕

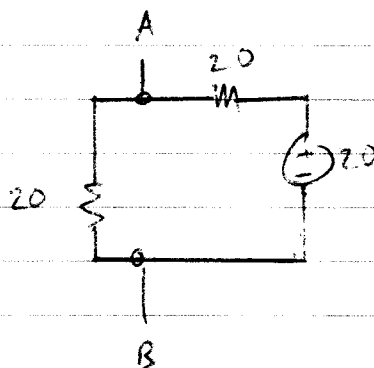

so


$$V_{th} = \left(\frac{20}{20+20} \right) 20$$

$$= 10V$$

$$I_{sc} = \frac{20}{20} = 1A$$

$$R_{th} = 10\Omega$$

Which resistor?

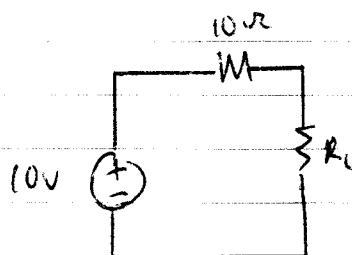


$$5 = \left(\frac{10}{10+R_L} \right) R_L$$

$$50 + 5R_L = 10R_L$$

$$R_L = 10\Omega$$

8.1

5

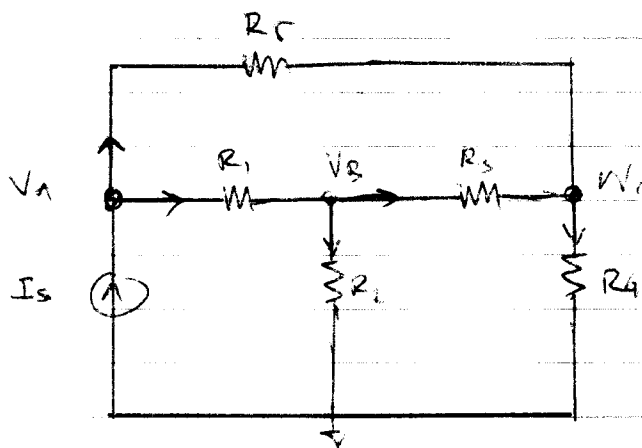

AT NODE A

$$I_s + \frac{V_A - V_C}{R_5} = \frac{V_A - V_B}{R_1}, \quad I_s = \frac{V_A}{R_1} - \frac{V_B}{R_1} + \frac{V_A}{R_5} - \frac{V_C}{R_5}$$

AT NODE B

$$\frac{V_B}{R_2} + \frac{V_B - V_C}{R_3} = \frac{V_A - V_B}{R_1}, \quad 0 = \frac{V_B}{R_1} + \frac{V_B}{R_3} - \frac{V_C}{R_3} - \frac{V_A}{R_1} + \frac{V_B}{R_1}$$


AT NODE C

$$\frac{V_C}{R_4} = \frac{V_B - V_C}{R_3} + \frac{V_A - V_C}{R_5}, \quad \frac{V_C}{R_4} + \frac{V_C}{R_3} + \frac{V_C}{R_5} - \frac{V_B}{R_3} - \frac{V_A}{R_5} = 0$$

COMBINE INTO SYSTEM

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_5} & -\frac{1}{R_1} & -\frac{1}{R_5} \\ -\frac{1}{R_1} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_1} & -\frac{1}{R_3} \\ -\frac{1}{R_5} & -\frac{1}{R_3} & \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} I_s \\ 0 \\ 0 \end{bmatrix}$$

3.4

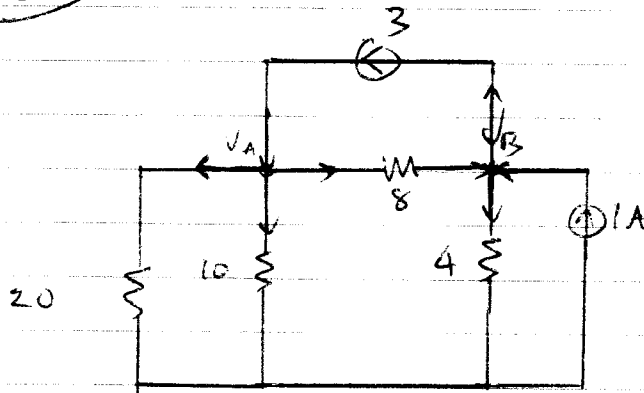

AT NODE A

$$\frac{V_A}{20} + \frac{V_A}{10} + \frac{V_A - V_B}{8} = 3$$

AT NODE B

$$1 + \frac{V_A - V_B}{8} = 3 + \frac{V_B}{4}$$

COMBINING INTO SYSTEM OF EQUATIONS

$$\begin{bmatrix} 1/40 & -1/8 \\ -1/8 & 3/8 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 3 \\ -2 \end{bmatrix}$$

Solving this gives us

$$V_A = 10V$$


$$V_B = -2V$$

$$V_x = V_B = \underline{\underline{-2V}}$$

$$I_s = \frac{10}{20} = \underline{\underline{0.5A}}$$

3.5

(7)

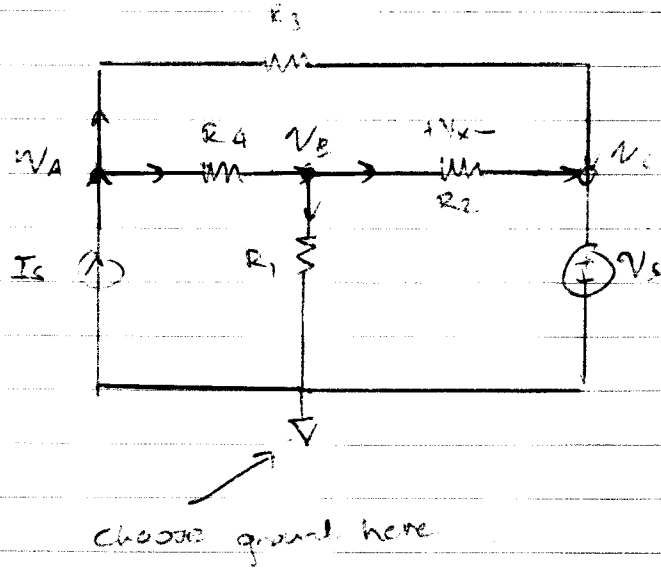

AT NODE A

$$I_s = \frac{V_A - V_S}{R_1} + \frac{V_A - V_B}{R_4}$$

AT NODE B

$$\frac{V_B}{R_1} + \frac{V_B - V_S}{R_2} = \frac{V_A - V_B}{R_4}$$

SYSTEM OF EQUATIONS

$$\begin{bmatrix} \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_4} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} I_s + V_S/R_3 \\ V_S/R_2 \end{bmatrix}$$

(b) Solving gives us

$$\begin{bmatrix} \frac{1}{10k} + \frac{1}{10k} & -\frac{1}{10k} \\ -\frac{1}{10k} & \frac{1}{10k} + \frac{1}{10k} + \frac{1}{10k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 1 + 25/10k \\ 25/10k \end{bmatrix}$$

$$\Rightarrow \begin{aligned} V_A &= 26 \\ V_B &= 17 \end{aligned}$$

$$\begin{aligned} V_x &= -8V \\ I_x &= -0.1mA \end{aligned}$$


9.7

$$V_A = V_S$$


$$\frac{V_B - V_A}{R_1} + \frac{V_B - V_C}{R_2} - I_S = 0$$

$$\frac{V_C - V_A}{R_3} + \frac{V_C - V_B}{R_2} + \frac{V_C}{R_4} = 0$$

$$V_B = 0$$

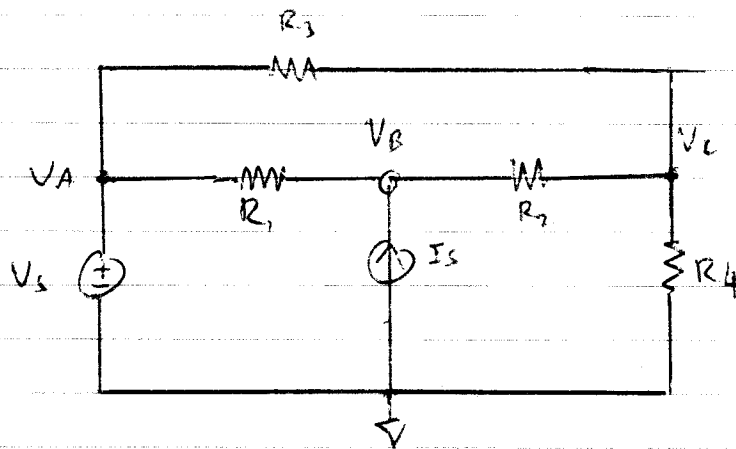

8.16

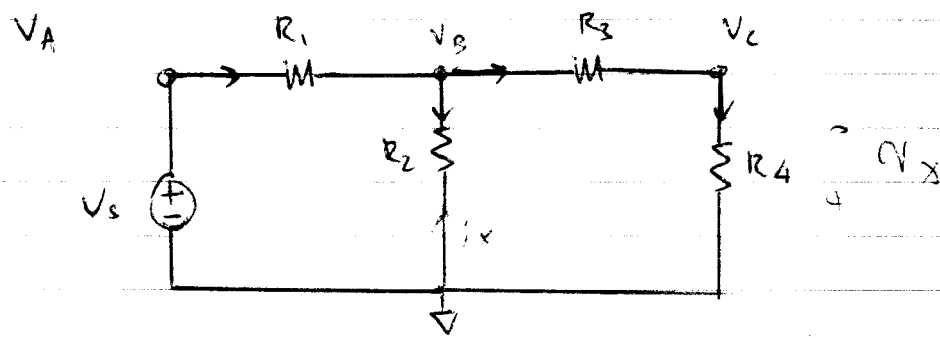

$$V_A = V_s$$

$$\frac{V_A - V_B}{R_1} = \frac{V_B}{R_2} + \frac{V_B - V_C}{R_3}$$

$$\frac{V_C}{R_4} = \frac{V_B - V_C}{R_3}, \quad \left(\frac{1}{R_3} + \frac{1}{R_4} \right) V_C = \frac{V_B}{R_3}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{V_s}{R_1} \\ 0 \end{bmatrix}$$

we $V_x = -V_C$


~~$i_x = \frac{V_B}{R_2}$~~

$$i_x = -\frac{V_B}{R_2}$$

$$i_A = -i_x$$

$$i_B = \frac{V_C}{R_4}$$

3/8

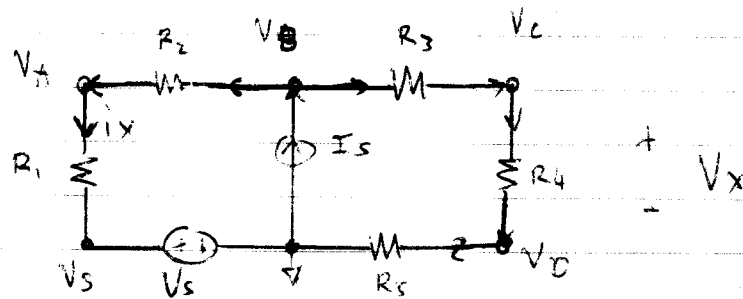

$$\frac{V_A - V_S}{R_1} = \frac{V_A - V_B}{R_2}$$

$$I_S = \frac{V_B - V_A}{R_2} + \frac{V_B - V_C}{R_3}$$

$$\frac{V_B - V_C}{R_3} = \frac{V_C - V_D}{R_4}$$

$$\frac{V_C - V_D}{R_4} = \frac{V_D}{R_5}$$

$$\begin{bmatrix} 1/R_1 + 1/R_2 & -1/R_2 & 0 & 0 \\ -1/R_2 & 1/R_2 + 1/R_3 & -1/R_3 & 0 \\ 0 & -1/R_3 & 1/R_3 + 1/R_4 & -1/R_4 \\ 0 & 0 & -1/R_4 & 1/R_4 + 1/R_5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} V_S/R_1 \\ I_S \\ 0 \\ 0 \end{bmatrix}$$

Substitute values and solve,

$$V_A = 29.2V$$

$$V_B = 37V$$

$$V_C = 33.3V$$

$$V_D = 17.8V$$


$$\begin{aligned} V_x &= V_c - V_D \\ &= \underline{18.5V} \end{aligned}$$

$$i_x = \frac{V_B - V_S}{R_1 + R_2} = \underline{2.6mA}$$

(c) Power dissipation

$$\begin{aligned} &= \frac{(V_B)^2}{(R_3 + R_4 + R_5)} + \frac{(V_B - V_S)^2}{R_1 + R_2} \\ &= \underline{0.3076W} \end{aligned}$$

3.1a

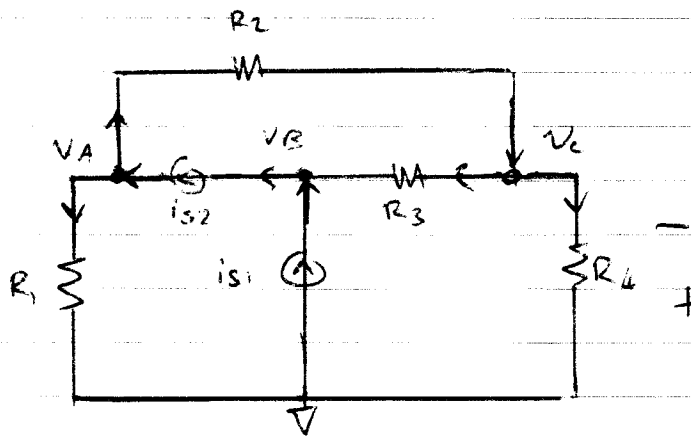

$$\frac{V_A}{R_1} + \frac{V_A - V_C}{R_2} = i_{s2}$$


$$-i_{s2} + \frac{V_C - V_B}{R_3} + i_{s1} = 0$$

$$\frac{V_A - V_C}{R_2} + \frac{V_C}{R_4} = \frac{V_C - V_B}{R_3}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & 0 & -\frac{1}{R_2} \\ 0 & \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_2} & -\frac{1}{R_3} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_{s2} \\ i_{s1} - i_{s2} \\ 0 \end{bmatrix}$$

$$\underline{\underline{V_x = -V_C}}$$

3.24

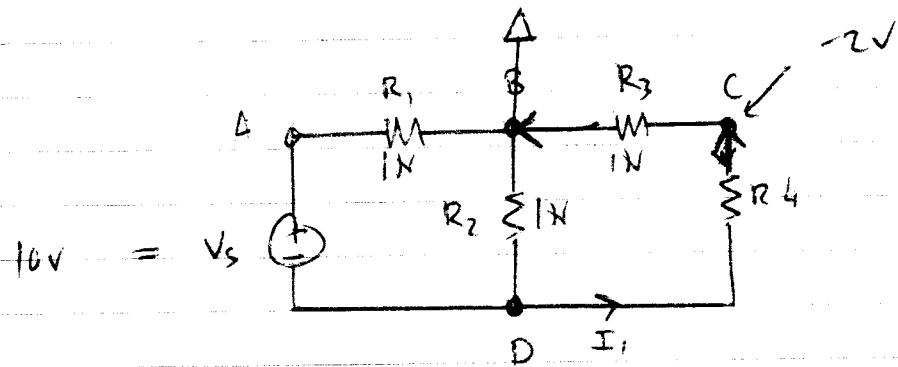

$$V_C = -2V$$

$$V_D = -2V + R_4 \cdot I_1$$

$$= -2V + 1k \left(\frac{2}{1k} \right)$$

$$= \underline{\underline{-4V}}$$

$$V_A = V_D + V_S$$

$$= \underline{\underline{6V}}$$