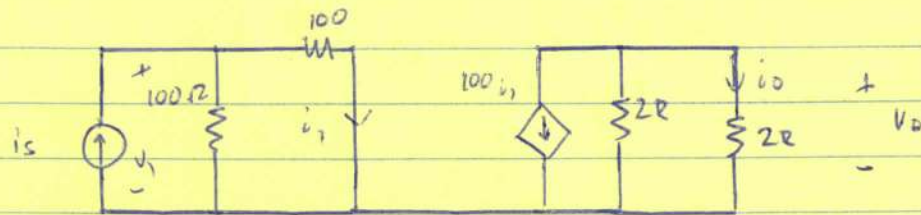


# HW#5 SOLUTIONS,

AMIT PANDAY

4.2.




① Find an expression for  $i_1$ .

→ We have a current divider between two equal valued

resistors, so 
$$i_1 = \frac{i_s}{2}$$

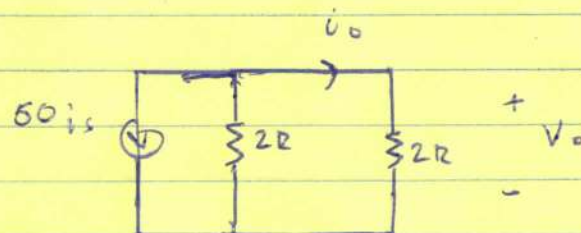Redraw second half of circuit with value of current source



We have another current divider with two equal valued resistances.  $\Rightarrow$

$$i_o = \frac{-50i_s}{2}, \quad \frac{i_o}{i_s} = \underline{\underline{-25}}$$

Now we want to find the Voltage gain.

$$V_s = i_s \cdot 50$$

$$V_o = 2R i_o$$

$$\frac{V_o}{V_s} = \frac{2R i_o}{50 i_s}$$

$$= \frac{2R}{50} (-25)$$

$$= \underline{\underline{-1000}}$$

Now for  $i_s = 5\text{mA}$ , we want to find the power supplied and the power delivered.


Power supplied

$$\begin{aligned} P &= I^2 R \\ &= 50 \times (5 \times 10^{-3})^2 \\ &= \underline{\underline{1.25\text{mW}}} \end{aligned}$$

Power delivered

$$\begin{aligned} P &= V \cdot I \\ &= 2k i_o - \frac{50 i_s}{2} \\ &= 2k \left( \frac{-50 i_s}{2} \right)^2 \\ &= \underline{\underline{31.25\text{W}}} \end{aligned}$$

4.6

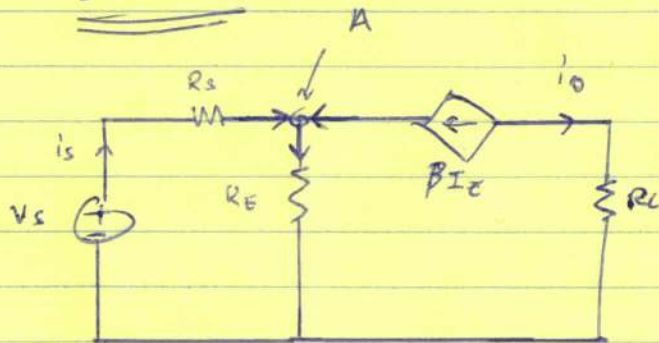

$$\begin{aligned} \frac{V_A - V_s}{R_s} + \beta I_E &= \frac{V_A}{R_E} && \text{nodal analysis at A.} \\ \underbrace{i_s}_{\text{is}} + \beta I_E &= I_E && \text{Convert to currents because we want to find the current gain.} \end{aligned}$$

$$i_s = I_E(1 - \beta)$$

$$\begin{aligned} i_o &= -\beta I_E \\ I_E &= \frac{-i_o}{\beta} \end{aligned}$$


$$\Rightarrow i_s = \frac{-i_o(1 - \beta)}{\beta}$$

$$\frac{i_o}{i_s} = \frac{-\beta}{1 - \beta}$$

$$= \left( \frac{\beta}{\beta - 1} \right)$$



4.9)

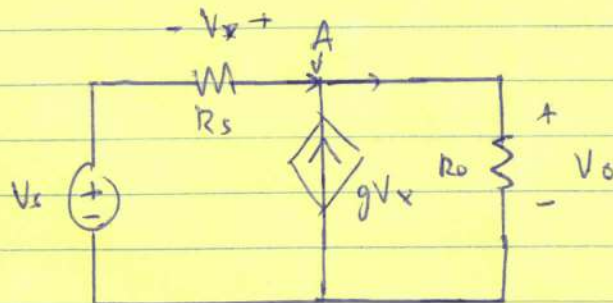Find an expression for the voltage gain  $V_o/V_s$ .

Nodal Analysis at A:

$$\frac{V_s - V_A}{R_s} + gV_x = \frac{V_A}{R_o}$$

$$V_A = V_o$$

$$V_x = V_o - V_s$$

$$\Rightarrow \frac{V_s - V_o}{R_s} + g(V_o - V_s) = \frac{V_o}{R_o}$$

$$V_s \left( \frac{1}{R_s} - g \right) = V_o \left( \frac{1}{R_o} + \frac{1}{R_s} - g \right)$$


$$\frac{V_o}{V_s} = \frac{1 - gR_s}{R_s} \div \left( \frac{1}{R_o} + \frac{1}{R_s} - g \right)$$

$$= \frac{1 - gR_s}{R_s} \div \left( \frac{R_s + R_o - gR_oR_s}{R_oR_s} \right)$$

$$= \frac{(1 - gR_s) R_o}{R_s + R_o - gR_oR_s}$$

4.23


OPAMP #1

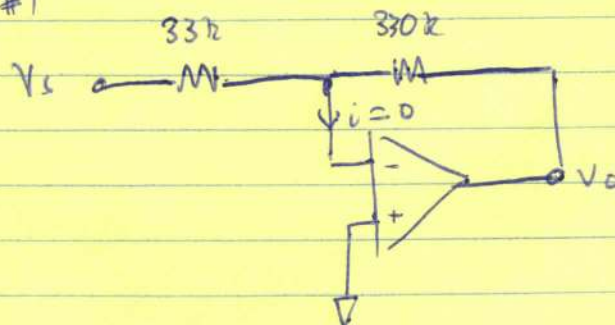

$$V_+ = V_- = 0$$

$$\frac{V_s}{33k} = -\frac{V_o}{330k}, \quad \frac{V_o}{V_s} = \underline{\underline{-10}}$$

OPAMP #2

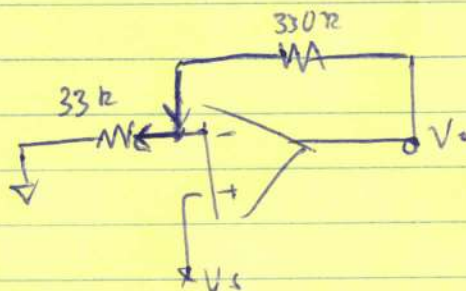


$$\frac{V_s}{33k} = \left( \frac{V_s - V_o}{330k} \right), \Rightarrow V_s \left( \frac{1}{33k} + \frac{1}{330k} \right) = \frac{+V_o}{330k}$$

$$\frac{V_o}{V_s} = 330k \left( \frac{1}{33k} + \frac{1}{330k} \right)$$

$$\frac{V_o}{V_s} = \underline{\underline{11}}$$



4.27)

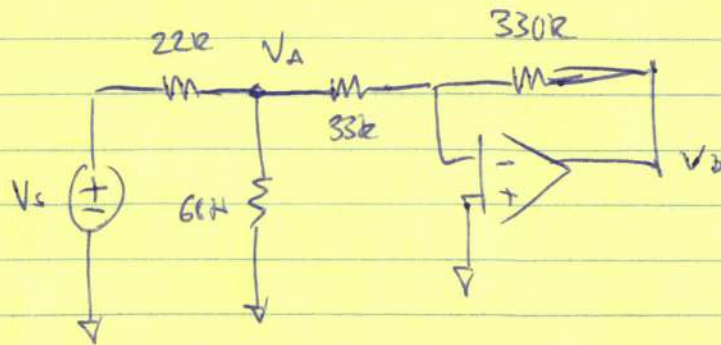

Find expression for  $\frac{V_o}{V_s}$ .

Nodal analysis at A:

$$\frac{V_s - V_A}{22k} = \left( \frac{1}{68k} + \frac{1}{33k} \right) V_A$$

$$\frac{V_s}{22k} = V_A \left( \frac{1}{68k} + \frac{1}{33k} + \frac{1}{22k} \right)$$

$$\frac{V_A}{V_s} = \frac{1}{22k} \div \left( \frac{1}{68k} + \frac{1}{33k} + \frac{1}{22k} \right)$$


$$\frac{V_A}{33k} = - \frac{V_o}{330k}$$

$$V_o = -10 V_A, \quad V_A = -\frac{V_o}{10}$$


$$\Rightarrow \frac{V_o}{V_s} = \frac{-10}{22k} \div \left( \frac{1}{68k} + \frac{1}{33k} + \frac{1}{22k} \right)$$

$$\approx \underline{\underline{-5.02}}$$

Q.28)

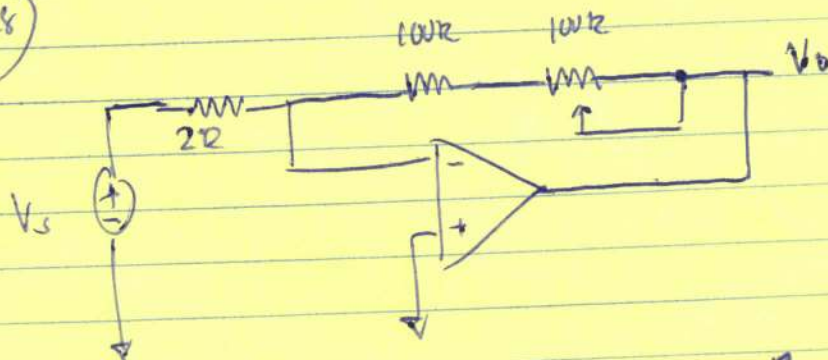

We can rewrite this circuit as

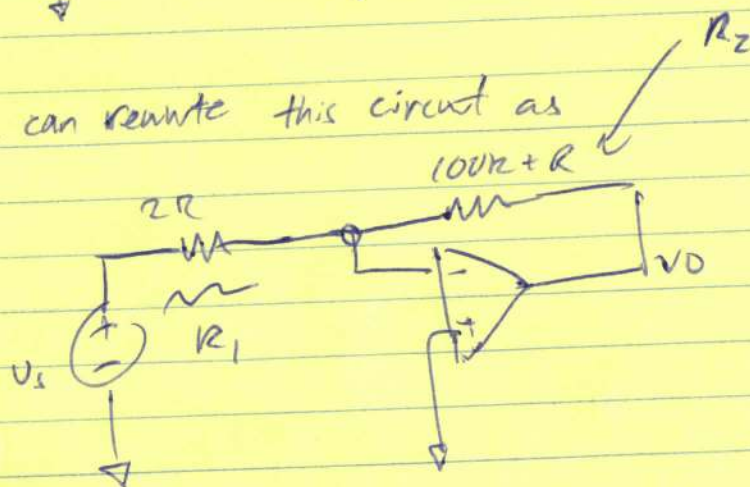

$$0 \leq R \leq 100k$$

This is now an inverting amplifier gain:  $-\frac{R_2}{R_1}$

$$G = \frac{-100k + R}{2k}$$

~~So gain can vary between~~

So gain can vary between

$$-50, \rightarrow -100$$


$$-100 \leq \frac{V_o}{V_s} \leq -50$$



4.32)

When gain = 10, output voltage = 20V but  $V_{CC} = 15V$ , so the amplifier saturates.  
Fix would be to increase  $V_{CC}$  to above  $20 \times 10 = 20V$ .

4.34)

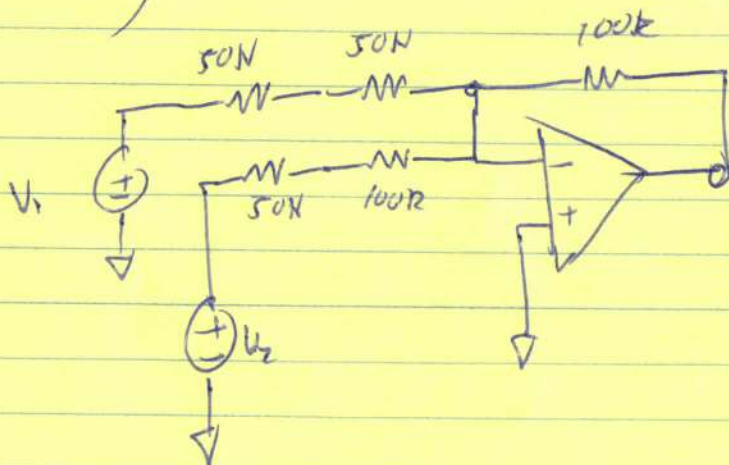

This is an inverting summer:

$$\frac{V_0}{100k} = -\frac{V_1}{50k} - \frac{100k}{150k} V_2$$

(a) 
$$V_0 = -\left(V_1 + \frac{2}{3}V_2\right)$$

(b) 
$$V_0 = -1 - \frac{2}{3}V_2$$

Max rail:

$$15 = -1 - \frac{2}{3}V_2$$

$$16 = -\frac{2}{3}V_2 \quad V_2 = -24V$$

Min rail

$$-15 = -1 - \frac{2}{3}V_2$$


$$V_2 = 21V$$

So:

$$\underline{\underline{-24V \leq V_2 \leq 21V}}$$



437)

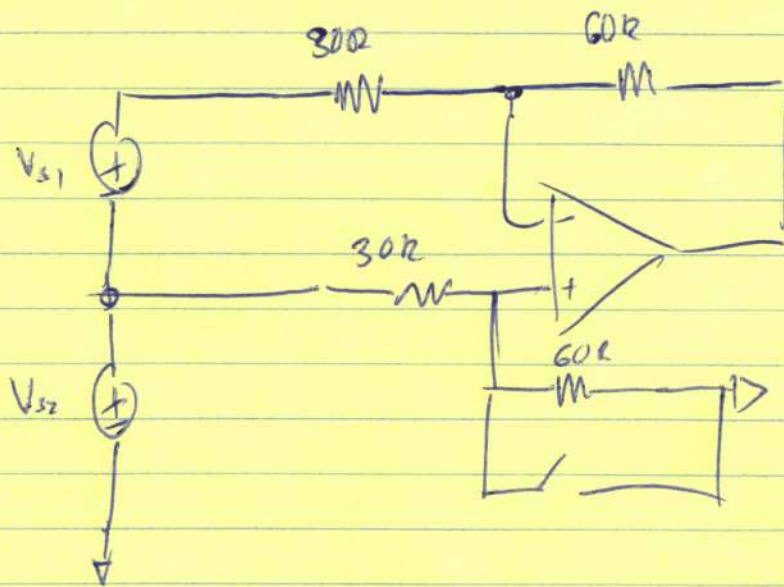

Switch open:

$$V_+ = \frac{V_{s2} - 60k}{90k} = \frac{2}{3} V_{s2} = V_-$$

$$\frac{V_{s1} + V_{s2} - \frac{2}{3} V_{s2}}{30k} = \frac{\frac{2}{3} V_{s1} - V_o}{60k}$$

$$\frac{V_{s1}}{30k} + \frac{V_{s2}}{30k} - \frac{2V_{s2}}{90k} = \frac{2V_{s1}}{180k} - \frac{V_o}{60k}$$

$$\Rightarrow \frac{V_{s1}}{30k} = \frac{-V_o}{60k} \Rightarrow V_o = -2V_{s1}$$

Switch closed:

$$V_+ = 0 = V_-$$


$$\frac{V_{s1} + V_{s2}}{30k} = -\frac{V_o}{60k}$$

$$V_o = -2(V_{s1} + V_{s2})$$

---



4.47

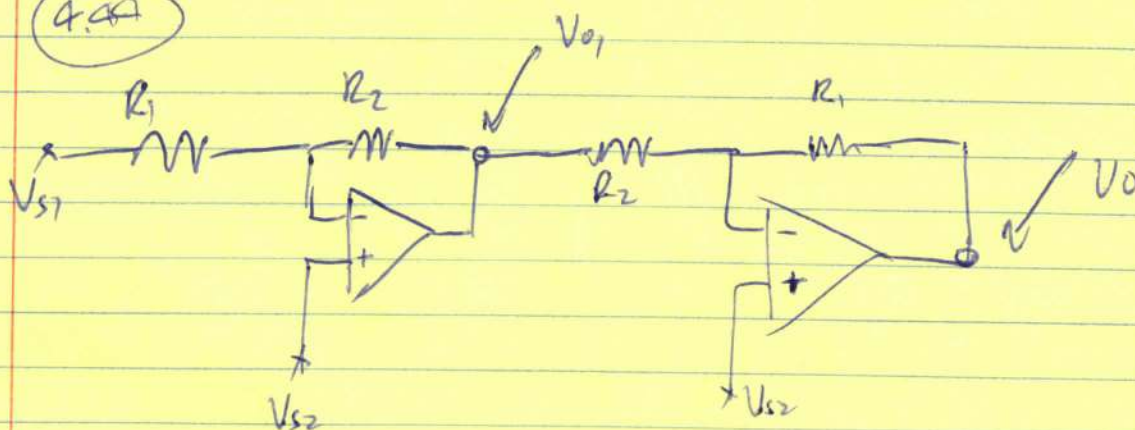

$$(1) \quad \frac{V_{s1} - V_{s2}}{R_1} = \frac{V_{s2} - V_{o1}}{R_2}$$

$$-R_2 \left[ \frac{V_{s1}}{R_1} - \frac{V_{s2}}{R_1} - \frac{V_{s2}}{R_2} \right] = V_{o1}$$

$$(2) \quad \frac{V_{o1} - V_{s2}}{R_2} = \frac{V_{s2} - V_o}{R_1}$$

$$V_o = -R_1 \left[ \frac{V_{o1}}{R_2} - \frac{V_{s2}}{R_2} - \frac{V_{s2}}{R_1} \right]$$

$$= -R_1 \left[ \frac{V_{s1}}{R_1} + \frac{V_{s2}}{R_1} + \frac{V_{s2}}{R_2} - \frac{V_{s2}}{R_2} - \frac{V_{s2}}{R_1} \right]$$

$$= -R_1 \left[ \frac{V_{s1}}{R_1} \right]$$

$$= \underline{\underline{-V_{s1}}}$$