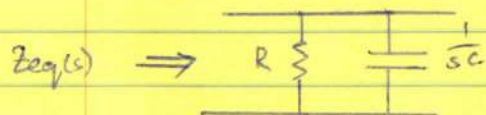


HW #7 SOLUTIONS
AMST PANDAY

(10-2) For a parallel RC circuit, find $Z_{eq}(s)$ and then select R & C so that there is a pole at -10krad/s .



$$Z_{eq}(s) = \frac{R \left(\frac{1}{sC} \right)}{R + \frac{1}{sC}}$$

$$Z_{eq}(s) = \frac{R}{1 + sRC}$$

Pole is the root of the denominator:

$$1 + sRC = 0$$

$$1 = -sRC$$


$$s = \frac{-1}{RC}$$

To achieve pole at -10krad/s , select, $R = 10\text{k}\Omega$ and $C = 10\text{nF}$


(or any other standard value of R, C which gives the correct location).

(10-4) (a) Find and express $Z_{eq}(s)$ as a rational transfer function and find its poles and zeros

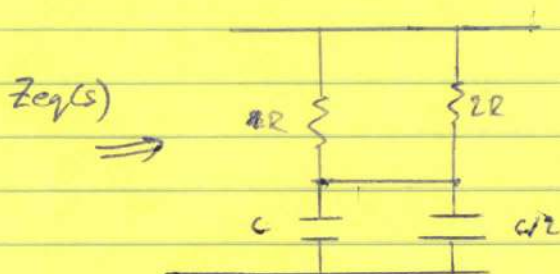(b) Select R & C to locate ~~pole~~^{zero} at ~~33k rad/s~~^{-33k rad/s}. What is the resulting ~~zero~~^{pole}?



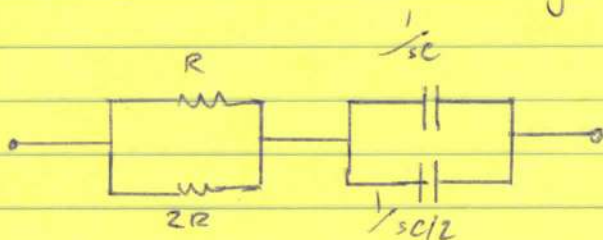This circuit is equivalent to the following:



$$R_{eq} = \frac{2R}{3},$$

$$C_{eq} = \frac{2}{3Cs} \quad (\text{capacitance adds in parallel})$$

$$Z_{eq}(s) = \frac{2R}{3} + \frac{2}{3Cs} = \frac{2}{3} \left(R + \frac{1}{Cs} \right)$$


$$= \frac{2}{3} \left(\frac{RCs + 1}{Cs} \right)$$

Location of pole = 0 rad/s

Location of zero = $\frac{-1}{RC} \text{ rad/s}$

(b) $\frac{1}{RC} = 33k$, so $R = 10 \Omega$, $C = 3 \mu F$ (or otherwise)

(10-14)

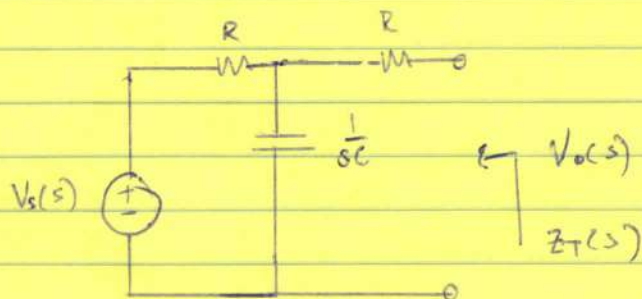


$$\begin{aligned} \text{(a)} \quad V_o(s) &= \frac{V_s(s)}{\left(R + \frac{1}{sC}\right)} \cdot \frac{1}{sC} \\ &= \frac{V_s(s)}{1 + RCs} \end{aligned}$$

(b) Short out voltage source,

$$\begin{aligned} Z_T(s) &= R \parallel \frac{1}{sC} + R \\ &= \frac{\frac{R}{sC}}{R + \frac{1}{sC}} + R = \frac{R(2 + RCs)}{1 + RCs} \end{aligned}$$

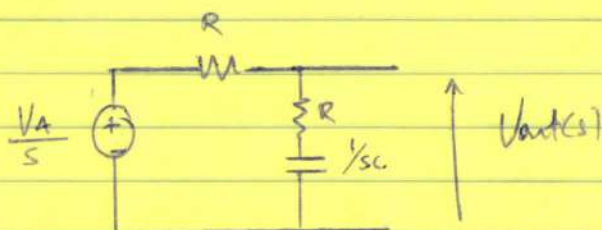(10-16)

$$V_{oc}(s) = \frac{V_A (RCs + 1)}{s(2RCs + 1)}$$




$$V_{oc}(s) = \frac{V_A}{s} \cdot \frac{1}{2R + \frac{1}{sC}} \left(R + \frac{1}{sC} \right)$$

$$= \frac{V_A}{s} \cdot \frac{1}{\frac{2RCs + 1}{sC}} \cdot \frac{RCs + 1}{sC}$$

$$= \underline{\underline{\frac{V_A}{s} \frac{(RCs + 1)}{(2RCs + 1)}}}$$

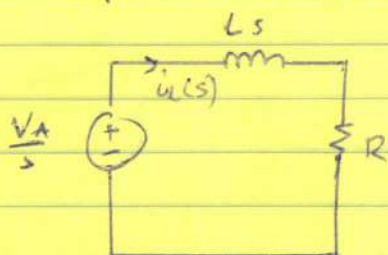(10-20)

Switch in position (B) allows us to determine initial current through the inductor. There is no energy source, so $i_L(0) = 0$. Now, let us draw the s-domain representation of the switch in position - A.



$$I_L(s) = \frac{V_A}{s} \cdot \frac{1}{Ls + R}$$

~~$$I_L(s) = \frac{V_A}{s} \cdot \frac{1}{Ls + R}$$~~

$$I_L(s) = \frac{V_A}{s(Ls + R)}$$

Now, we want to find $I_L(t)$. Need to take the inverse Laplace transform. We do this with a partial fraction expansion

$$I_L(s) = \frac{A}{s} + \frac{B}{s + R/L} = \frac{V_A/L}{s(s + R/L)}$$

$$\Rightarrow A\left(s + \frac{R}{L}\right) + Bs = \frac{V_A}{L}$$

evaluate @ $s = -R/L$

$$\Rightarrow B = \frac{-V_A}{R}$$


evaluate @ $s = 0$

$$A = \frac{V_A}{R}$$

$$\Rightarrow I_L(s) = \frac{V_A/R}{s} + \frac{\left(\frac{-V_A}{R}\right)}{s + R/L}$$

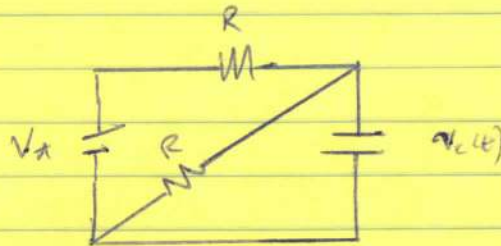
(10-21)

Determine initial condition by analysing circuit in position (A).



$$v_C(0) = \frac{V_A}{2} \quad (\text{voltage divider, capacitor acts as open circuit as } t \rightarrow \infty)$$

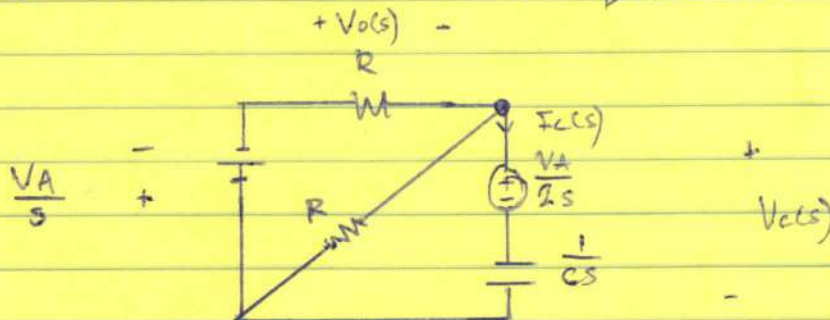Now, we look at the s-domain circuit in position B.



Now, we find our unknown quantities:

$$\frac{v_C(s) + \frac{V_A}{s}}{R} + \frac{v_C(s)}{R} + \frac{v_C(s) - \frac{V_A}{2s}}{1/Cs} = 0$$

$$v_C(s) = \frac{V_A}{2s} \frac{(RCs - 2)}{2 + RCs}$$

$$I_C(s) = \frac{v_C(s) - \frac{V_A}{2s}}{1/Cs}$$

$$I_C(s) = 2V_A \cdot C \cdot \left[\frac{-1}{2 + RCs} \right]$$

Now, we can take the inverse Laplace transform.

$$I_L(s) = \mathcal{L}^{-1}\left(\frac{V_A}{R} s\right) + \mathcal{L}^{-1}\left(\frac{-V_A/R}{s + R/L}\right)$$

$$= \frac{V_A}{R} - \frac{V_A}{R} e^{-R/L t}$$

$$I_L(t) = \frac{V_A}{R} \left(1 - e^{-R/L t}\right) u(t)$$

Now, we want an expression for $V_c(t)$.

We can take a KCL expression about the outer loop.

$$\frac{+V_A(s)}{s} + V_o(s) + V_c(s) = 0$$

$$\Rightarrow V_o(s) = -V_c(s) - \frac{V_A}{s}$$

$$= -\frac{V_A}{2s} \frac{(RCs - 2)}{(2 + RCs)} - \frac{V_A}{s}$$

$$= -\frac{V_A}{s} \left(\frac{\frac{1}{RC} + \frac{3}{2}s}{s(s + \frac{2}{RC})} \right)$$

~~using partial fractions:~~

~~$$-\frac{V_A}{s} \left(\frac{1}{RC} + \frac{3}{2}s \right) = A \left(s + \frac{2}{RC} \right) + Bs$$~~

~~$$\Rightarrow A = -\frac{V_A}{2}, B = -V_A$$~~

~~$$-\frac{V_A}{s} \left(\frac{1}{RC} + \frac{3}{2}s \right) = \frac{N_1}{s} + \frac{N_2}{s + \frac{2}{RC}}$$~~

~~computing partial fractions: $N_1 = -\frac{V_A}{2}$~~

$$V_o(s) = -V_A \left(\frac{\frac{1}{RC} + \frac{2}{2}s}{s(s + \frac{2}{RC})} \right)$$

Take partial fractions


$$\frac{-V_A \left(\frac{1}{RC} + \frac{2}{2}s \right)}{s \left(s + \frac{2}{RC} \right)} = \frac{A}{s} + \frac{B}{s + \frac{2}{RC}}$$

$$\Rightarrow A = -\frac{V_A}{2}, \quad B = -V_A$$


$$\Rightarrow V_o(s) = -\frac{V_A/2}{s} - \frac{V_A}{s + \frac{2}{RC}}$$

$$\Rightarrow \underline{\underline{V_o(t) = - \left[\frac{V_A}{2} + V_A e^{-\frac{2t}{RC}} \right] u(t)}}$$

10-41)

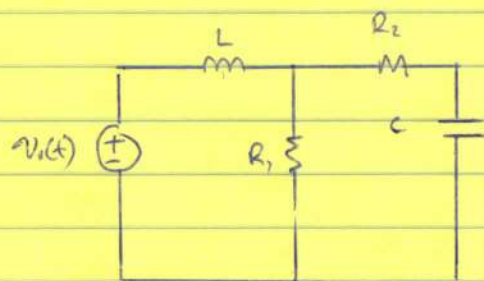

(a)

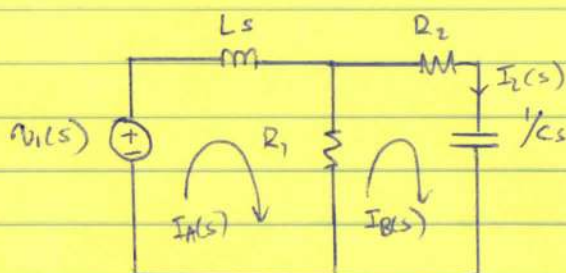

Express the current in the
s-domain with no initial
energy

Let us formulate the mesh current equations:

$$① \quad -v_i(s) + I_A(s)Ls + R_1(I_A(s) - I_B(s)) = 0$$

$$v_i(s) = I_A(s)(Ls + R_1) - I_B(s)R_1$$

$$② \quad 0 = (R_1 + R_2 + \frac{1}{cs})I_B(s) - R_1 I_A(s) = 0$$

$$①^* \quad I_A(s) = \frac{v_i(s) + I_B(s)R_1}{Ls + R_1}$$

$$I_B(s) = \frac{R_1 I_A(s)}{cs(R_1 + R_2) + 1} = \frac{R_1 cs}{cs(R_1 + R_2) + 1} \left[\frac{v_i(s) + I_B(s)R_1}{Ls + R_1} \right]$$

$$I_B(s) \left[1 - \frac{R_1^2 cs}{(cs(R_1 + R_2) + 1)(Ls + R_1)} \right] = \frac{v_i(s) \cdot R_1 cs}{(cs(R_1 + R_2) + 1)(Ls + R_1)}$$

$$I_B(s) \left[(cs(R_1 + R_2) + 1)(Ls + R_1) - R_1^2 cs \right] = v_i(s) \cdot R_1 cs$$

$$\Rightarrow I_2(s) = \frac{R_1 cs v_i(s)}{(R_1 + R_2) Lcs^2 + (R_1 R_2 c + L)s + R_1}$$

(c) Single zero of system located at $s = 0$.

Poles of system are roots of :

$$s^2(R_1 + R_2)LC + (R_1 R_2 C + L)s + R_1 = 0$$

By the quadratic formula

$$p = \frac{-(R_1 R_2 C + L) \pm \sqrt{(R_1 R_2 C + L)^2 - 4(R_1 + R_2)LC R_1}}{2(R_1 + R_2)LC}$$

(d) $v_i(t) = 10u(t)$, $R_1 = 1k$, $R_2 = 2k$, $L = 2$, $C = 0.5 \mu F$

$$I_2(s) = \frac{1k \times 0.5 \mu s \cdot 10/s}{s[3k]1\mu s^2 + (2k \cdot 1k \cdot 0.5 \mu + 2)s + 1k}$$

$$= \frac{5 \times 10^{-3}}{(3 \times 10^{-3})s^2 + 3s + 1000} = \frac{5 \times 10^{-3}}{(3 \times 10^{-3})s^2 + 3s + 1000}$$


$$I_2(s) = \frac{5/3}{s^2 + 1000s + (\frac{1}{3}) \times 10^6} = \frac{5/3}{(s+500)^2 + (\frac{500}{\sqrt{3}})^2}$$

~~Now use table partial fractions~~ Taking the inverse Laplace transform,

$$\frac{\sqrt{3}}{300} e^{-500t} \cdot \sin\left(\frac{500}{\sqrt{3}}t\right) u(t)$$

(10-42)

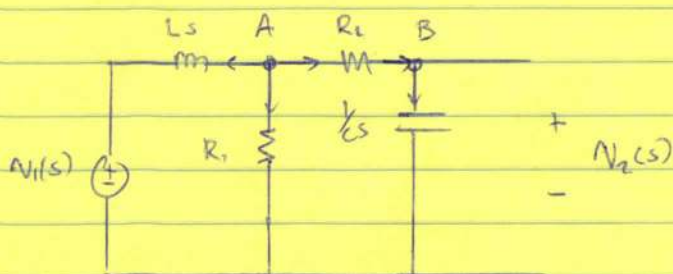(a) Transform circuit into s domain and formulate node-voltage equations



Node voltage equations:

$$(1) \quad \frac{V_A(s) - V_1(s)}{sL} + \frac{V_A(s)}{R_1} + \frac{V_A(s) - V_B(s)}{R_2} = 0$$

$$(2) \quad V_B(s) \cdot sC + \frac{V_B(s) - V_A(s)}{R_2} = 0$$

(b) Solving for $V_B(s)$ gives

$$V_B(s) = V_2(s) = \frac{R_1 V_1(s)}{(R_1 + R_2)LCs^2 + (R_1 R_2 C + L)s + R_1}$$

(c) Natural ~~poles~~ poles are the poles caused by circuit elements, not in response to external stimulus:

$$p = \frac{-(R_1 R_2 C + L) \pm \sqrt{(R_1 R_2 C + L)^2 - 4(R_1 + R_2)LC}}{2(R_1 + R_2)LC}$$

Forced poles are unknown without knowing what $V_1(s)$ is.

(d) $V_1(t) = 25 \text{ mV}$, $R_1 = R_2 = 500$, $L = 0.5$, $C = 2 \mu\text{F}$.

$$N_2(s) = \frac{500 \times \frac{25}{s}}{(500+500)0.5 \times 2 \mu\text{F} s^2 + (500 \times 500 \times 2 \mu + 0.5)s + 500}$$

$$= \frac{1.25 \times 10^7}{s(s^2 + 1000s + 0.5 \times 10^6)} = \frac{12.5 \times 10^6}{s((s+500)^2 + 500^2)}$$

$$= \frac{N_1}{s} + \frac{N_2 s + N_3}{(s+500)^2 + 500^2}$$

$$\Rightarrow 12.5 \times 10^7 = N_1((s+500)^2 + 500^2) + (N_2 s + N_3)s$$

at $s=0$
 $N_1 = \underline{25}$

Now for N_1 & N_2 :

$$N_1 s^2 + N_2 s^2 = 0 \quad (\text{compare coefficients of } s^2)$$

$$\Rightarrow N_1 + N_2 = 0$$

$$\Rightarrow \underline{N_2 = -25}$$

Compare coefficients of s

$$1000N_1 + N_3 = 0$$


$$\Rightarrow \underline{N_3 = -25000}$$

$$V_2(s) = \frac{25}{s} + \frac{(-25)s - 25000}{(s+500)^2 + 500^2}$$

$$= \frac{25}{s} - 25 \left(\frac{s+500}{(s+500)^2 + 500^2} + \frac{500}{(s+500)^2 + 500^2} \right)$$

$$\Rightarrow V_2(t) = (25 - 25e^{-500t} \cos(500t) - 25e^{-500t} \sin(500t)) \text{ mV}$$

10-61 //

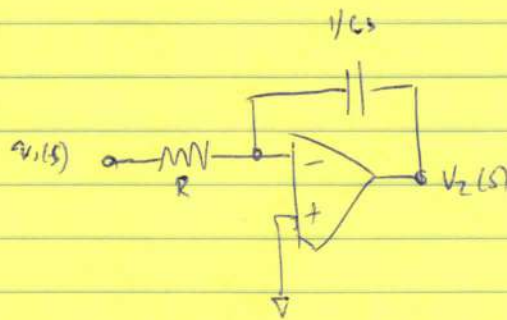

$$v_1(t) = \cos(1000t)$$

$$v_2(t) = -\sin(1000t)$$

This is an inverting amplifier with a gain of $\frac{-R_2}{R_1} = \frac{-1}{CRs}$

$$\text{So, } \frac{v_2(s)}{v_1(s)} = \frac{-1}{CRs}$$

$$v_2(s) = \frac{-1}{CRs} \cdot v_1(s)$$

$$v_1(s) = \mathcal{L}(\cos(1000t)) = \frac{s}{s^2 + 1000^2}$$

$$v_2(s) = \frac{-1}{CRs} \cdot \frac{s}{s^2 + 1000^2}$$

$$v_2(s) = \frac{-1}{RC} \cdot \frac{1}{s^2 + 1000^2}$$

∴ The Laplace transform of ~~-1000~~ $-\sin(1000t)$ is $\frac{-1000}{s^2 + 1000^2}$.


$$\text{So we require } \frac{1}{RC} = 1000 \Rightarrow \underline{R = 1\text{ k}\Omega, C = 1\text{ }\mu\text{F}}$$

or similar.


What if capacitor had 10V across it initially?

By superposition we can conclude that the output voltage will decrease by 10V.

10-68/

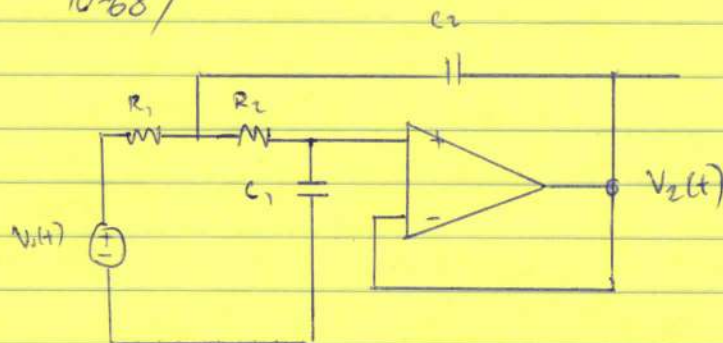

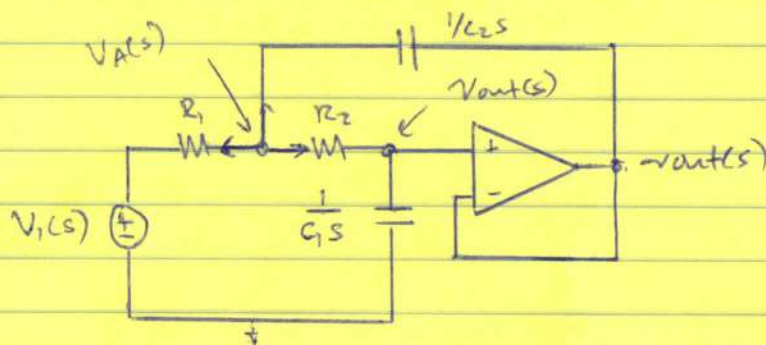First, we find the s -domain representation:



We have: $V_-(s) = V_+(s) = V_{out}(s)$.

So,

$$\frac{V_A(s) - V_1(s)}{R_1} + \frac{V_A(s) - V_{out}(s)}{R_2} + (V_A(s) - V_{out}(s))(C_2 s) = 0$$

$$(1) \quad V_A(s) \left[\frac{1}{R_1} + \frac{1}{R_2} + C_2 s \right] = \frac{V_1(s)}{R_1} + \frac{V_{out}(s)}{R_2} + V_{out}(s) C_2 s$$

$$(2) \quad V_{out}(s) = \frac{V_A(s)}{R_2 + \frac{1}{C_1 s}} \cdot \frac{1}{C_1 s} = \frac{V_A(s)}{1 + R_2 C_1 s}$$

$$\Rightarrow V_A(s) = V_{out}(s) (1 + R_2 C_1 s)$$

$$\Rightarrow V_{out}(s) (1 + R_2 C_1 s) \left[\frac{1}{R_1} + \frac{1}{R_2} + C_2 s \right] = \frac{V_1(s)}{R_1} + V_{out}(s) \left[\frac{1}{R_2} + C_2 s \right]$$

From (1)

$$V_A(s) [R_1 + R_2 + R_1 R_2 C_2 s] = V_1(s) R_2 + V_{out}(s) (R_1 + R_1 R_2 C_2 s)$$

$$\Rightarrow V_{out}(s) [(1 + R_2 C_1 s)(R_1 + R_2 + R_1 R_2 C_2 s) - R_1 - R_1 R_2 C_2 s] = V_1(s) R_2$$

$$\Rightarrow \frac{V_{out}(s)}{V_1(s)} = \frac{R_2}{(1 + R_2 C_1 s)(R_1 + R_2 + R_1 R_2 C_2 s) - R_1 - R_1 R_2 C_2 s}$$

$$= \frac{R_2}{R_1 R_2^2 C_1 C_2 s^2 + (R_1 R_2 C_1 + R_2^2 C_1) s + R_2}$$
