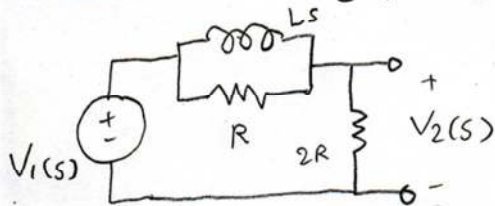


MAE 140 HW 8 Solution

11-2 Find driving point impedance and TF $T_V(s) = V_2(s)/V_1(s)$



$$Z_1 = \left(\frac{1}{R} + \frac{1}{Ls} \right)^{-1} = \frac{RLs}{R+Ls}$$


$$Z_2 = 2R$$

Driving pt impedance $\rightarrow Z_d = Z_1 + Z_2$

$$Z_d = \frac{RLs}{R+Ls} + 2R$$


$$V_2(s) = \frac{Z_2}{Z_1 + Z_2} V_1(s) = \frac{2R}{2R + \frac{RLs}{R+Ls}} V_1(s)$$
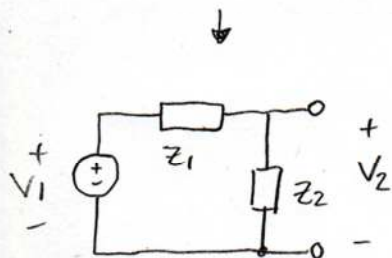
$$T_V(s) = (R+Ls) \frac{2R}{2R^2 + 3RLs}$$



Volt Divider

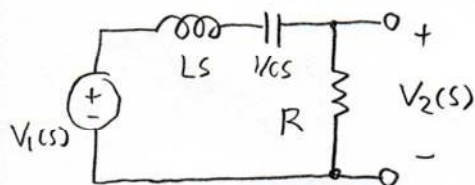11-3 Find driving point impedance and $T_V(s) = V_2(s)/V_1(s)$




$$Z_1 = Ls + \frac{1}{cs} = \frac{1+Lcs^2}{cs}$$

$$Z_2 = R$$


$$Z_d = Z_1 + Z_2 = R + Ls + \frac{1}{cs} = \frac{1+Rcs + Lcs^2}{cs}$$
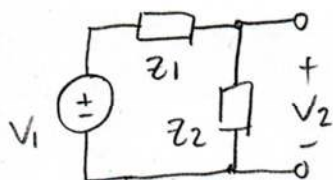
$$V_2(s) = \frac{Z_2}{Z_1 + Z_2} V_1(s) = \frac{R}{R + Ls + \frac{1}{cs}} V_1(s)$$




$$T_V(s) = \frac{Rcs}{1+Rcs + Lcs^2}$$

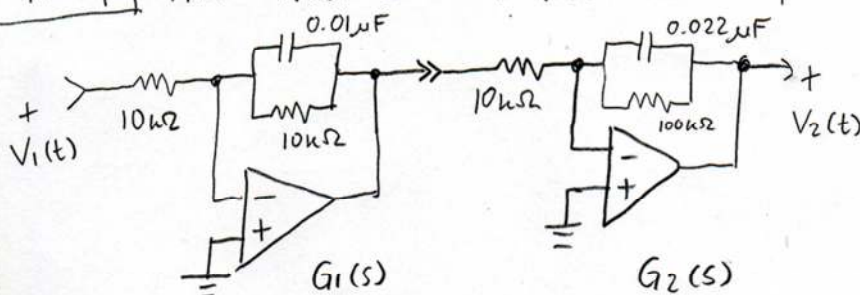11-14 Find $T_V(s) = V_2(s)/V_1(s)$ and its poles and zeros.



Cascade of 2 inverting OP Amps.

$$T_V(s) = G_1(s) \cdot G_2(s)$$

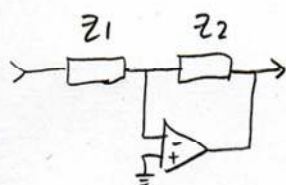

$$TF = -\frac{Z_2}{Z_1}$$

$$G_1(s) = \frac{-(10k\Omega \parallel \frac{1}{0.01\mu F s})}{10k\Omega} = -\frac{(\frac{1}{10^4\Omega} + 10^{-8}\mu F \cdot s)^{-1}}{10^4\Omega}$$

$$= -\frac{\frac{10^4}{1 + 10^{-4}s}}{10^4} = -\frac{1}{1 + 10^{-4}s} = -\frac{10000}{s + 10000}$$

$$G_2(s) = -\frac{(100k\Omega \parallel 0.022\mu F)}{10k\Omega} = -\frac{(\frac{1}{10^5} + 22 \cdot 10^{-9}s)^{-1}}{10^4}$$

$$= -\frac{10^5}{10^4} \left(\frac{1}{1 + 22 \cdot 10^{-4}s} \right) = -\frac{4545}{s + 454.5}$$


$$T_V(s) = G_1(s) \cdot G_2(s)$$

$$T_V(s) = 4.545 \cdot 10^7 \left(\frac{1}{s + 10000} \right) \left(\frac{1}{s + 454.5} \right)$$

$$\text{zeros} = \{ \}$$

$$\text{poles} = \{ -10^4, -454.5 \}$$

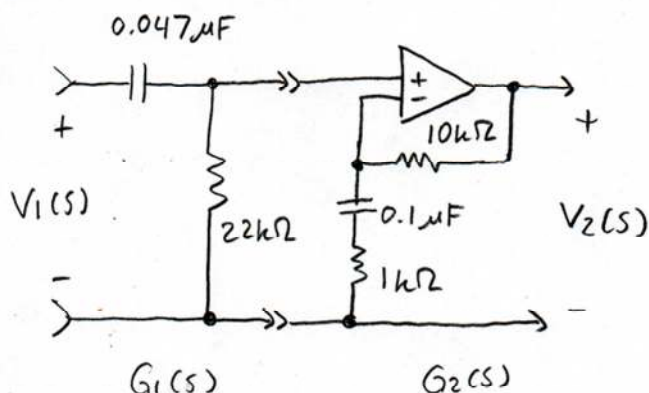11-15 Find $T_V(s) = V_2(s)/V_1(s)$ and its poles and zeros.



Cascade of Volt. divider and non-inverting OP Amp.

It's non-loading, so

$$T_V(s) = G_1(s) \cdot G_2(s)$$

$$G_1(s) = \frac{22k\Omega}{22k\Omega + \frac{1}{47 \cdot 10^{-9} \text{F} \cdot s}} = \frac{22k\Omega \cdot 47 \cdot 10^{-9} \text{F} \cdot s}{1 + 22k\Omega \cdot 47 \cdot 10^{-9} \text{F} \cdot s} = \frac{1.034 \cdot 10^{-3} s}{1 + 1.034 \cdot 10^{-3} s}$$

$$G_1(s) = \frac{s}{s + 967.12}$$

$$G_2(s) = 1 + \frac{10k\Omega}{1k\Omega + \frac{1}{0.1 \cdot 10^{-6} \text{F} \cdot s}} = 1 + \frac{10^4 \cdot 0.1 \cdot 10^{-6} s}{1 + 10^3 \cdot 0.1 \cdot 10^{-6} s} = 1 + \frac{10^{-3} s}{1 + 10^{-4} s}$$


$$G_2(s) = 1 + \frac{10s}{s + 10000} = \frac{11s + 10000}{s + 10000} \rightarrow G_2(s) = 11 \left(\frac{s + 909.1}{s + 10000} \right)$$

$$T_V(s) = G_1(s) \cdot G_2(s) \rightarrow T_V(s) = 11 \frac{s(s + 909.1)}{(s + 967.12)(s + 10000)}$$

$$\text{zeros} = \{-909.1, 0\} \quad \text{poles} = \{-967.12, -10000\}$$

11-34

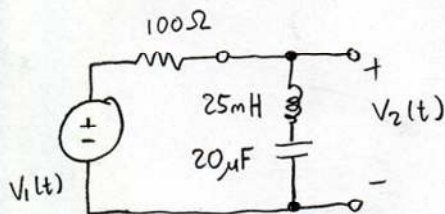Find $V_{2ss}(t)$ for $v_1(t) = 5 \cos(1414.21t) \text{V}$, $v_1(t) = 5 \cos(1kt) \text{V}$ and $v_1(t) = 5t$



Volt. Divider

Find the transfer function.

$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{(25 \text{mH} \cdot s + \frac{1}{20 \mu\text{F} \cdot s})}{100 \Omega + (25 \text{mH} \cdot s + \frac{1}{20 \mu\text{F} \cdot s})}$$

$$= \frac{5 \cdot 10^{-7} s^2 + 1}{5 \cdot 10^{-7} s^2 + 0.0025 s + 1}$$

$$T_V(s) = \frac{s^2 + 2 \cdot 10^6}{s^2 + 4000s + 2 \cdot 10^6}$$

Find magnitude and phase of $T_V(j\omega)$ at the ω of the sinusoidal input.

$$T_V(j \cdot 1414.21) = \frac{(1414.21)^2 j^2 + 2 \cdot 10^6}{(1414.21)^2 j^2 + 4000 \cdot 1414.21 j + 2 \cdot 10^6} = \frac{10.0759}{10.0759 + j 5.657 \cdot 10^6}$$

$$T_v(j1414.21) = \frac{10.076}{10.076 + j5.657 \cdot 10^6} \left(\frac{10.076 - j5.657 \cdot 10^6}{10.076 - j5.657 \cdot 10^6} \right)$$

$$= \frac{101.526 - j5.7 \cdot 10^7}{3.2 \cdot 10^{13}}$$

$$|T_v(j1414.21)| = \frac{\sqrt{101.526^2 + (5.7 \cdot 10^7)^2}}{3.2 \cdot 10^{13}} = 1.7813 \cdot 10^{-6}$$

$$\angle T_v(j1414.21) = \tan^{-1} \left(\frac{-5.7 \cdot 10^7}{101.526} \right) = -1.5708 \text{ rad or } -90^\circ$$

For $V_1(t) = 5 \cdot \cos(1414.12t) \text{ V}$

$$\hookrightarrow V_{2ss}(t) = (5 \cdot 1.7813 \cdot 10^{-6}) \cos(1414.12t - 1.5708) \text{ V}$$

$$\boxed{V_{2ss}(t) = 8.906 \cdot 10^{-6} \cos(1414.21t - 1.5708) \text{ V}}$$

Similarly for $V_1(t) = 5 \cos(1kt) \text{ V}$, find magnitude and phase of $T_v(j1000)$.

$$T_v(j1000) = \frac{-10^6 + 2 \cdot 10^6}{-10^6 + j4 \cdot 10^6 + 2 \cdot 10^6} = \frac{10^6}{10^6 + j4 \cdot 10^6} = \frac{10^{12} (1 - 4j)}{17 \cdot 10^{12}} = \frac{1 - 4j}{17}$$

$$|T_v(j1000)| = \frac{\sqrt{1+16}}{17} = 0.2425$$

$$\angle T_v(1000j) = \tan^{-1} \left(\frac{-4}{1} \right) = -1.3258$$

$$\hookrightarrow V_{2ss}(t) = (5 \cdot 0.2425) \cos(1kt - 1.3258) \text{ V}$$


$$\hookrightarrow \boxed{V_{2ss}(t) = 1.2620 \cdot \cos(1kt - 1.3258) \text{ V}}$$

For $V_1(t) = 5 \text{ V}$, use $V_1(t) = 5 \text{ V} \cdot \cos(0 \cdot t) \rightarrow \omega = 0$

$$T_v(0) = 1 \rightarrow \boxed{V_{2ss}(t) = 5 \text{ V}}$$

11-37

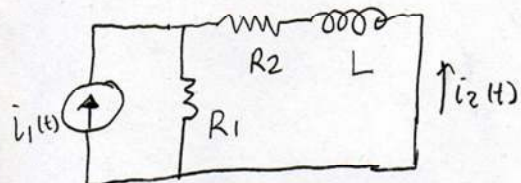Find $i_{2ss}(t)$ w/ $i_1(t) = 10 \cos(50kt) \text{ mA}$, $i_2(t) = 10 \cos(5kt) \text{ mA}$.
Where is the pole? $R_1 = 100 \Omega$, $R_2 = 400 \Omega$, $L = 100 \text{ mH}$.



Current Divider

Find the transfer function $G(s) = \frac{I_2(s)}{I_1(s)}$

$$G(s) = \frac{-R_1}{R_1 + R_2 + Ls} = \frac{-100}{500 + 0.1s}$$

$$G(s) = \frac{-1000}{s + 5000} \rightarrow \text{Pole} = -5000$$

$$\hookrightarrow \tilde{i}_1(t) = 10 \cos(50kt) \text{ mA}$$


$$G(j50k) = \frac{-1000}{50000j + 5000} = \frac{-1}{2525} (5 - 50j) = \frac{-1 + 10j}{505} \quad 95.7^\circ$$

$$|G(j50k)| = \frac{\sqrt{100+1}}{505} = 0.02$$

$$\angle G(j50k) = \tan^{-1}\left(\frac{10}{-1}\right) = 1.6705 \text{ rad}$$

$$\tan^{-1}(-10) = -84.3^\circ, \text{ but we want } 95.7^\circ$$

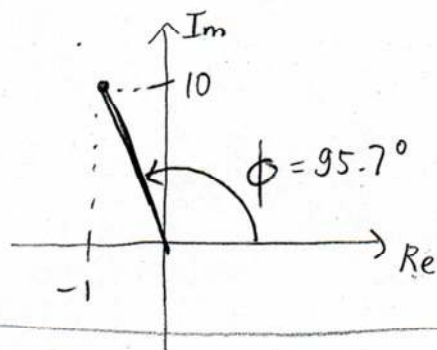!! Always check the complex plane diagram.
Use atan2 or phase in Matlab.



$$i_{2ss}(t) = (10 \cdot 0.02) \cos(50kt + 1.6705) \text{ mA} = 0.2 \cos(50kt + 1.6705) \text{ mA}$$

$$\hookrightarrow \tilde{i}_1(t) = 10 \cos(5kt) \text{ mA}$$


$$G(j5k) = \frac{-1000}{5000j + 5000} = \frac{-1}{50} (5 - 5j) = \frac{-1 + j}{10} \quad 135^\circ$$

$$|G(j5k)| = \frac{\sqrt{2}}{10} = 0.1414$$

$$\angle G(j5k) = \tan^{-1}\left(\frac{1}{-1}\right) = 2.3562 \text{ rad}$$

$$i_{2ss}(t) = 1.414 \cos(5kt + 2.3562) \text{ mA}$$

12-6

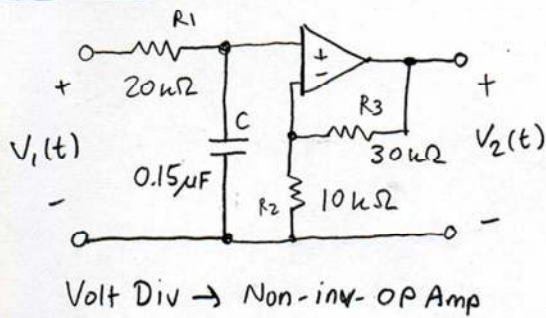Find $T_V(s) = V_2(s)/V_1(s)$!

$$T_V(s) = G_1(s) \cdot G_2(s) = \left(\frac{1/s}{R_1 + 1/s} \right) \left(1 + \frac{R_3}{R_2} \right)$$

$$= \frac{1}{1 + (20k\Omega)(0.15\mu F)s} \left(\frac{40k\Omega}{10k\Omega} \right) = \frac{4}{1 + 0.003s}$$

$$T_V(s) = \frac{1333}{s + 333.3}$$


a) DC Gain $\rightarrow |T_V(0)| = 4$

$\infty\omega$ gain $\rightarrow |T_V(j\infty)| = 0$

cutoff $\omega \rightarrow \omega_c = 333.3 \text{ rad/s}$

Response type: Low-pass filter
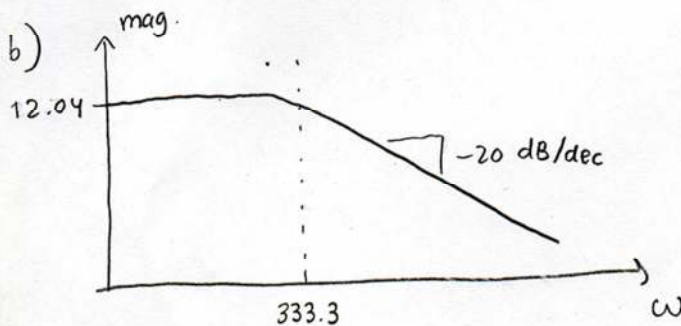
$$20 \cdot \log_{10}(4) = 12.04 \text{ dB}$$



d) on other page

c) $|T_V(0.1\omega_c)| = \text{DC Gain} = 4$

$|T_V(\omega_c)| = \text{DC Gain} / \sqrt{2} = 2.8284$

$|T_V(10\omega_c)| = \text{DC Gain} / 10 = 0.4$

Actual values:

3.98

2.8284


0.398

e) Should change the OP Amp's gain. Find R_3 such that $G_2(s) = 1 + \frac{R_3}{R_2} = 10$

$\rightarrow R_3 = 9R_2 = \underline{\underline{90k\Omega}}$

f) About -20 dB

12.7 Find $T_V(s) = V_2(s)/V_1(s)$

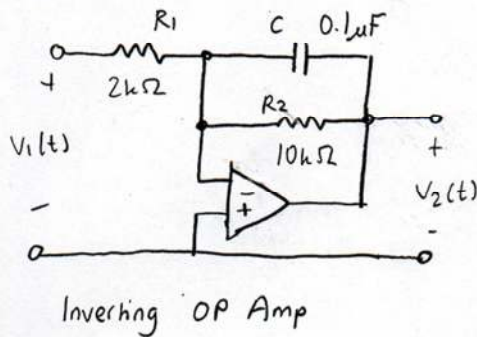

$$T_V(s) = - \frac{\left(\frac{1}{R_2} + cs\right)^{-1}}{R_1} = - \frac{R_2}{R_1} (1 + R_2 C s)^{-1}$$

$$= - \frac{10k\Omega}{2k\Omega} \frac{1}{(1 + 10k\Omega \cdot 0.1\mu F \cdot s)} = \frac{-5}{1 + 0.001s}$$

$$T_V(s) = \frac{-5000}{s + 1000}$$


a) DC Gain = $|T_V(0)| = \underline{+5}$

ω gain = $|T_V(j\omega)| = \underline{0}$

$\omega_c = \underline{1000 \text{ rad/s}}$

Type = low pass filter
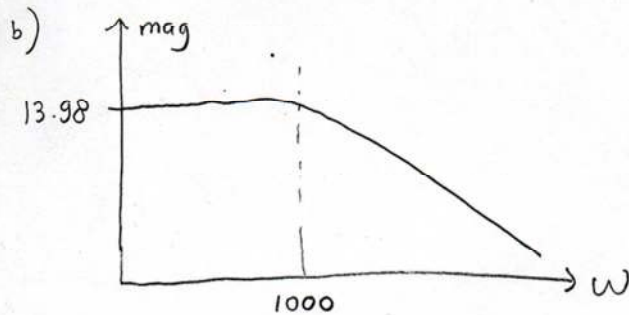
$$20 \cdot \log_{10}(5) = 13.98 \text{ dB}$$



d) on other page.

c) Gain at $\omega = 0.1 \omega_c \rightarrow |T_V(j0.1 \omega_c)| = \text{DC Gain} = \underline{5}$

Gain at $\omega = \omega_c \rightarrow |T_V(j\omega_c)| = \text{DC Gain}/\sqrt{2} = \underline{3.536}$

Gain at $\omega = 10 \omega_c \rightarrow |T_V(j10 \omega_c)| = \text{DC Gain}/10 = \underline{0.5}$

Actual value :-

$$4.9752$$

$$3.5355$$


$$0.4975$$

e) Double the passband gain

$\rightarrow$ make $\frac{R_2}{R_1} = 10$ instead of 5 $\rightarrow$ $R_1 = 1k\Omega$


Can't change R_2 because it affects the ω_c .

12-8

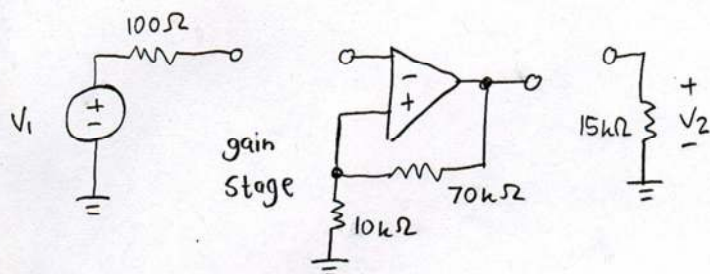Connect to make a $T_V(s)$ w/ gain 4, $\omega_c = 500 \text{ rad/s}$.Repeat if $\omega_c = 625 \text{ rad/s}$ and gain doesn't matter.

3 options:

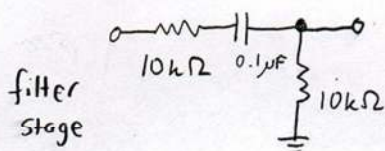1. Just the filter stage
2. Filter stage $\rightarrow$ gain stage
3. Gain stage $\rightarrow$ filter stage.



$\rightarrow$ Only the filter stage affects the ω_c .
OP Amp always have the same gain.

$$\text{OP Amp gain} = 1 + \frac{70\text{k}\Omega}{10\text{k}\Omega} = 8$$

Just the filter: $T_V(s) = \frac{(10\text{k}\Omega \parallel 15\text{k}\Omega)}{100\Omega + 10\text{k}\Omega + \frac{1}{0.1\mu\text{F}s} + (10\text{k}\Omega \parallel 15\text{k}\Omega)}$

$$= \frac{6\text{k}\Omega \cdot 0.1\mu\text{F} \cdot s}{16.1\text{k}\Omega \cdot 0.1\mu\text{F} \cdot s + 1} = \frac{0.0006 \cdot s}{1 + 0.00161s} = \frac{0.3727 \cdot s}{s + 621}$$

Filter $\rightarrow$ gain $T_V(s) = \left(\frac{10\text{k}\Omega \cdot 8}{100\Omega + 10\text{k}\Omega + \frac{1}{0.1\mu\text{F}s} + 10\text{k}\Omega} \right) = \frac{10\text{k}\Omega \cdot 0.1\mu\text{F} \cdot s \cdot 8}{20.1\text{k}\Omega \cdot 0.1\mu\text{F} \cdot s + 1}$

$$= \frac{0.001 \cdot 8 \cdot s}{1 + 0.00201s} = \frac{3.98 \cdot s}{s + 497.5}$$


gain $\rightarrow$ filter $T_V(s) = 8 \left(\frac{(10\text{k}\Omega \parallel 15\text{k}\Omega)}{10\text{k}\Omega + \frac{1}{0.1\mu\text{F}s} + (10\text{k}\Omega \parallel 15\text{k}\Omega)} \right) = \frac{8 \cdot 6\text{k}\Omega \cdot 0.1\mu\text{F} \cdot s}{1 + 16\text{k}\Omega \cdot 0.1\mu\text{F} \cdot s}$

$$= \frac{8 \cdot 0.0006 \cdot s}{1 + 0.0016s} = \frac{0.3 \cdot s}{s + 625}$$

So, use filter stage $\rightarrow$ gain stage for T_V with gain 4 and $\omega_c = 500 \text{ rad/s}$



use gain stage $\rightarrow$ filter stage for T_V w/ $\omega_c = 625 \text{ rad/s}$

12-44 Find $T_V(s) = V_2(s)/V_1(s)$

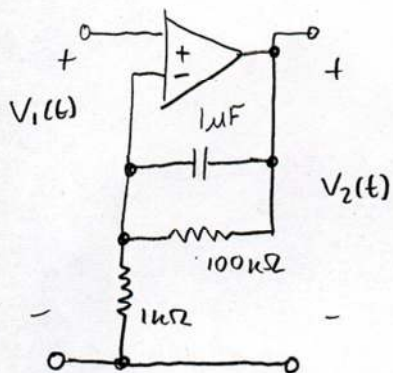

Non-inverting amp.
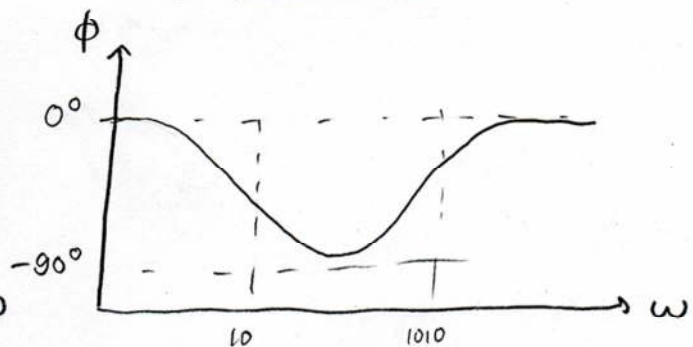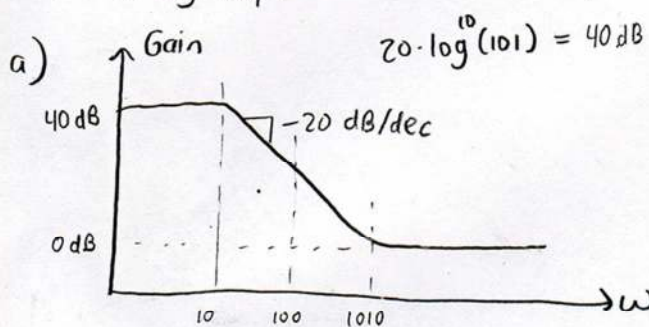
$$\begin{aligned}
 T_V(s) &= 1 + \frac{(100\text{k}\Omega \parallel \frac{1}{s\mu\text{F}})}{1\text{k}\Omega} = 1 + \frac{(\frac{1}{100\text{k}\Omega} + s\mu\text{F})^{-1}}{1\text{k}\Omega} \\
 &= 1 + \frac{\frac{100\text{k}\Omega}{1 + 100\text{k}\Omega s\mu\text{F}}}{1\text{k}\Omega} = 1 + \frac{100}{1 + 0.1s} \\
 &= 1 + \frac{1000}{s+10} = \frac{s+1010}{s+10}
 \end{aligned}$$



For $V_1(t) = 10 \sin(100t)\text{ V}$, gain $\approx 20\text{ dB}$, phase $\approx -90^\circ = -\pi/2$
 $= 10$

$$\rightarrow V_2(t) \approx 100 \sin(100t - \pi/2)$$

b) Actual gain and phase:


$$\begin{aligned}
 T_V(100j) &= \frac{100j + 1010}{100j + 10} = \frac{(1010 + 100j)(10 - 100j)}{100^2 + 10^2} \\
 &= \frac{10100 + 100^2 + 1000j - 101000j}{10100} = \frac{201 - 1000j}{101}
 \end{aligned}$$

$$|T_V(100j)| = \frac{\sqrt{201^2 + 1000^2}}{101} = \underline{\underline{10.099}}$$


$$\angle T(100j) = \underline{\underline{-1.3724\text{ rad}}}$$

c) on other page.

12.6) d

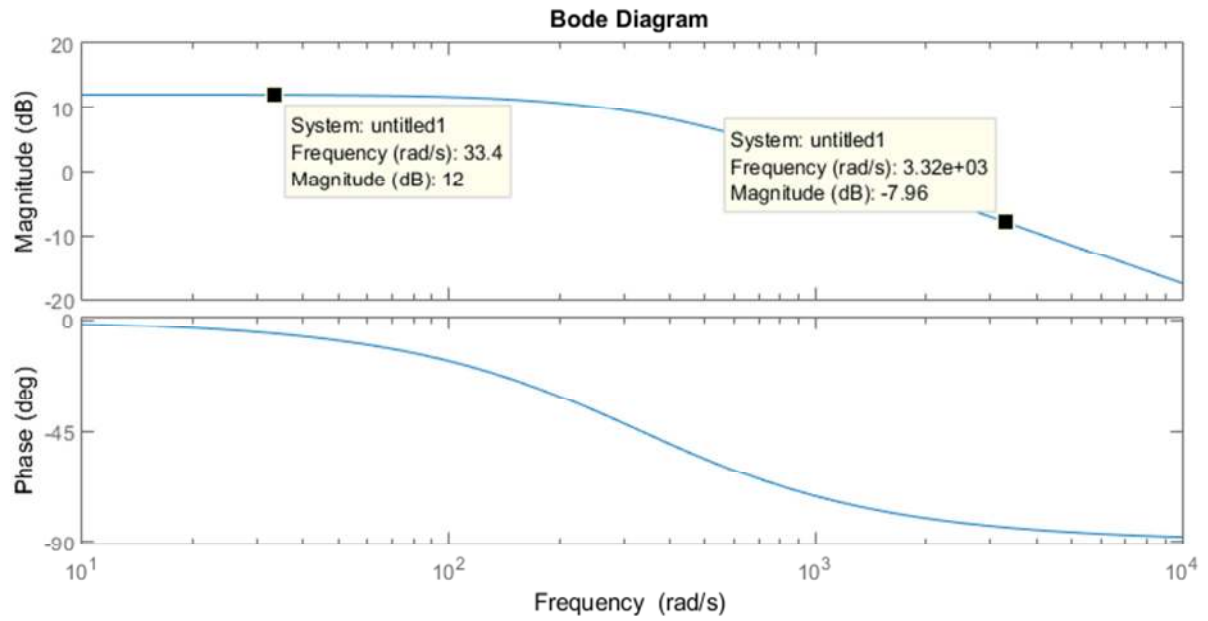

12.7) d

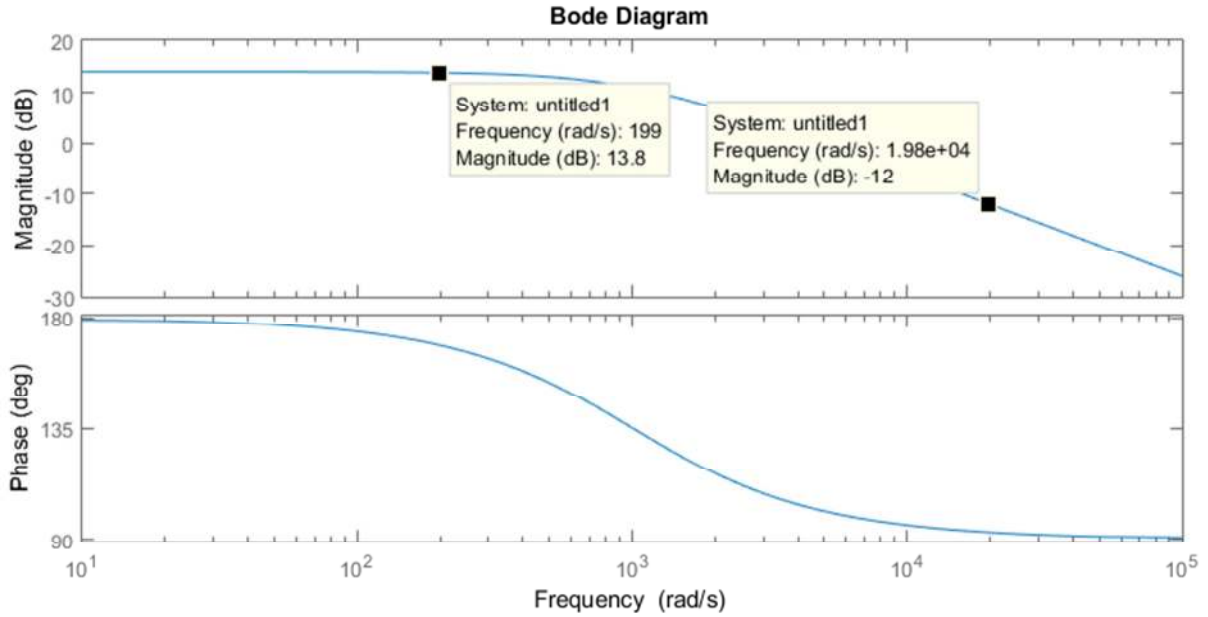

12.44) c

