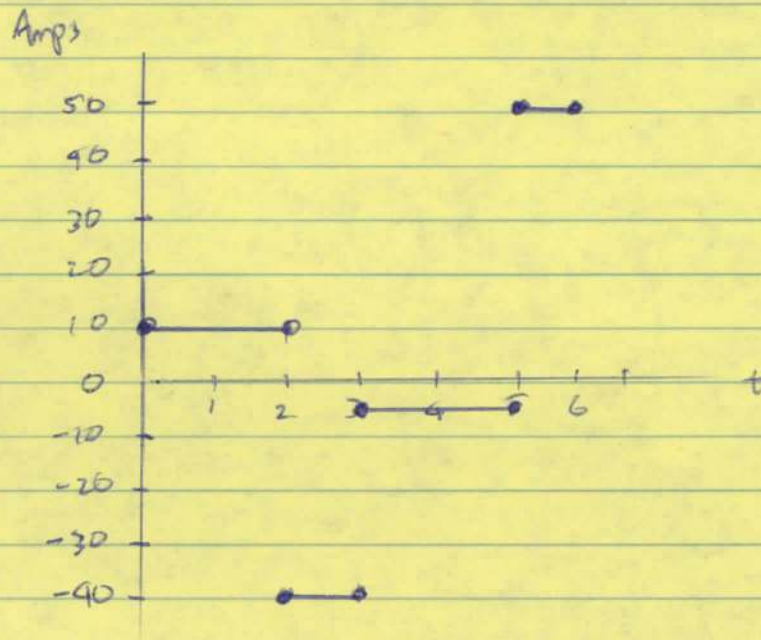


1-9

We have that $I = \frac{dy}{dt}$, so we get the following graph

(45)

$$I(t) = \begin{cases} 10A & 0 \leq t \leq 2 \\ -40A & 2 \leq t \leq 3 \\ -5A & 3 \leq t \leq 5 \\ 50A & 5 \leq t \leq 6 \end{cases}$$



(45)

NOTE: SUBTRACT 0.5 POINTS WHEN THERE IS NO UNIT GIVEN OR UNIT IS INCORRECT.

1.11

A cellphone charger outputs 9.6V and is protected by a 50mA fuse.
A 2W cellphone is connected to it. Will the fuse blow?

$$P = VI$$

$$I = \frac{P}{V} = \frac{2}{9.6} = 0.2083 \text{ amps}$$
$$= 208.3 \text{ mA}$$

(+8) Calculating current.

Since 208.3mA exceeds 50mA, the fuse will blow.

(+2) Stating that fuse will blow.

1.14

12V automobile battery has an output capacity of 100Ah when connected to a lamp that absorbs 200W of power.

(a) Find the current supplied by the battery and determine how long the battery can power the headlight for.

$$P = VI,$$

$$I = \frac{P}{V} = \frac{200}{12} = 16.67 \text{ A}$$

(+3)

To find how long battery can power the lamp-

$$t = \frac{100}{(200/12)} = \underline{\underline{6 \text{ hours}}} \quad (+3)$$


(b) A 100W device is connected through the utility port. How long can the battery power both the device and the headlight?

$$P_{\text{tot}} = 200 + 100 = 300 \text{ W}$$

$$I = \frac{300}{12} = \underline{\underline{25 \text{ A}}} \quad \sim$$

$$t = \frac{100}{25} = \underline{\underline{4 \text{ hours}}} \quad (+4)$$

1.23

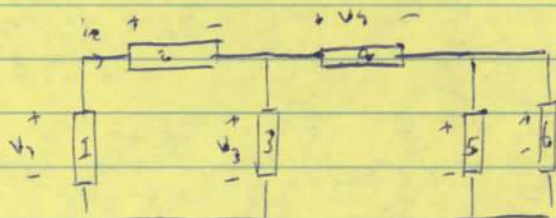

Use the power balance to find v_4 when $v_1 = 20V$, $i_1 = -2A$, $P_2 = 20W$,
 $P_3 = 10W$, $i_4 = 1A$, $P_5 = P_6 = 2.5W$

$$P_1 = -40W$$

$$P_1 + P_2 + P_3 + P_4 + P_5 + P_6 = 0$$

$$\Rightarrow P_4 = \underline{5W}$$

} As $P_4 > 0$, it is absorbing power. (+2)

$$P = VI$$

$$\Rightarrow v_4 = \underline{5V} \quad (+8)$$

2.7

$V = 15V$, $P_x = 25mW$. Find R_x

$$P = VI, \quad V = IR,$$

$$\Rightarrow I = \frac{V}{R}$$

$$\Rightarrow P = \frac{V^2}{R}, \quad R = \frac{V^2}{P} = \frac{15^2}{25m} = \underline{9000\Omega} \quad (+10)$$

2.81

$I = 10 \text{ mA}$, $V = 100 \text{ V}$, Find R_x and the power supplied by the source


$$P = VI = 100 \times 10 \text{ m} = 1 \text{ W} \quad (+5)$$

$$R = \frac{V}{I} = \frac{100}{10 \text{ m}} = 10000 \text{ } \Omega \quad (+5)$$

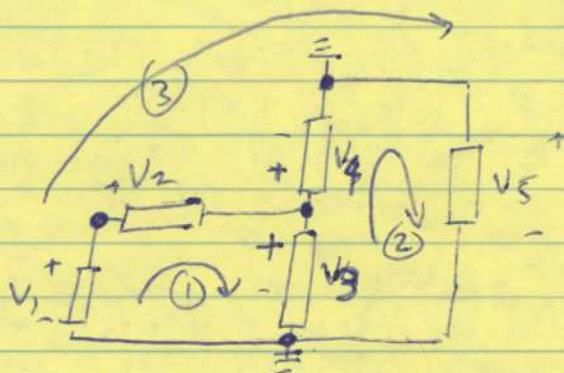2.16

Determine which elements are in series or parallel or neither, how many different nodes and loops are there in the circuit?

If $V_2 = 3 \text{ V}$, and $V_3 = 5 \text{ V}$, find V_1 , V_4 and V_5 .



• Elements V_1 & V_2 are in series. (+1)

• Elements V_3 & V_4 are in parallel with each other. (+1)

• There are 3 loops (indicated) (+1)

• There are 4 nodes (indicated by circles) (+1)

$$-V_1 + V_2 + V_3 = 0,$$

$$V_5 = 0 \quad (\text{connected between two grounds})$$


$$V_3 = +V_4$$

$$V_5 = 0 \text{ V}$$

$$V_4 = +5 \text{ V}$$

$$V_1 = 8 \text{ V}$$

2.18]

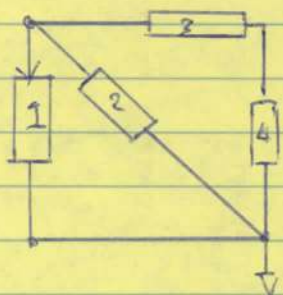

$i_2 = -30\text{mA}$, $i_4 = 20\text{mA}$, find i_1 & i_3 .


$$i_3 = i_4 \Rightarrow i_3 = 20\text{mA}$$

(+4)

$$i_1 + i_2 + i_3 = 0$$

$$\begin{aligned} i_1 &= -i_2 - i_3 \\ &= 30\text{m} - 20\text{m} \\ &= \underline{\underline{10\text{m}}} \end{aligned}$$

2.24]

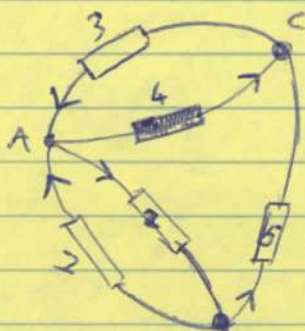

Are any of the elements in series or parallel? $i_1 = -3\text{mA}$, $i_2 = 10\text{mA}$, $i_3 = -15\text{mA}$, verify i_4 and i_5 .

3 & 4 and 1 & 2 are in parallel.

(+2)

Perform a nodal analysis at point A

Perform a nodal analysis at point C

$$\begin{aligned} i_1 + i_3 &= i_2 + i_4 \\ i_4 &= i_1 + i_3 - i_2 \\ &= -3\text{m} - 15\text{m} - 10\text{m} \\ &= \underline{\underline{-30\text{mA}}} \end{aligned}$$

(+4)

$$\begin{aligned} i_4 + i_5 &= i_3 \\ i_5 &= i_3 - i_4 \\ &= -15\text{m} + 30\text{m} \\ &= \underline{\underline{15\text{mA}}} \end{aligned}$$

(+4)

2.26

+5

If a wire is connected across (B) and (C) then $V_5 = 0$, so the voltage across elements 1, 2, 3, 4 will all be the same

+5