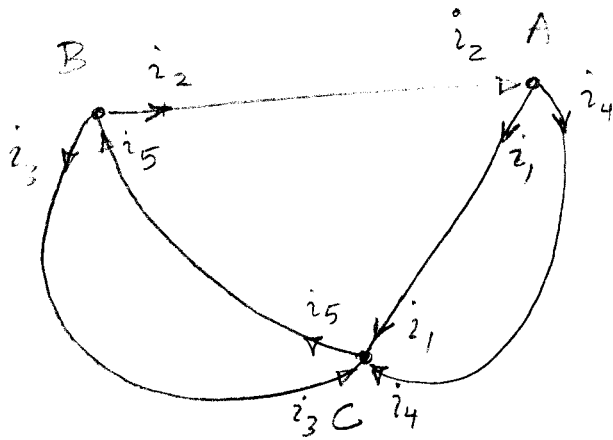


Problem 2.27



Problem 2-31

$$R_{eq} = \left(\underbrace{\frac{1}{R} + \dots + \frac{1}{R}}_n \right)^{-1} = \left(\underbrace{\frac{1}{50} + \dots + \frac{1}{50}}_n \right)^{-1} = \frac{50}{n} \Rightarrow$$


$$R_{eq} = \frac{50}{n} \text{ k}\Omega, \quad V = R_{eq} \cdot i \Rightarrow$$

$$\text{but we know } (1.5 + 1.5) = \frac{50}{n} \cdot i \Rightarrow$$

$$3 \text{ V} = \left(\frac{50}{n} \right) \text{ k}\Omega \cdot (500 \times 10^{-6}) \text{ A} \rightarrow 3 = \frac{50 \times 10^3}{n} \cdot 5 \times 10^{-4} \text{ A}$$

$$n = \frac{25}{3} = 8.33 \rightarrow \boxed{n = 8}$$

Problem 2.32

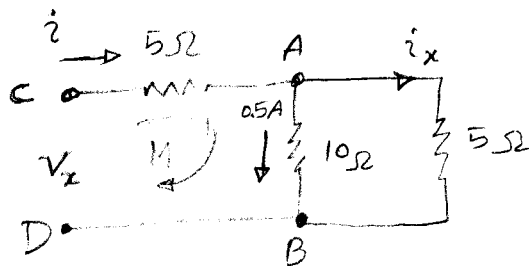

$$V_{AB} = 0.5 \text{ A} \cdot 10 \Omega = 5 \text{ V}$$

$$V_{AB} = 5 \Omega \cdot i_x \rightarrow i_x = \frac{5}{5} = 1 \text{ A} \rightarrow \boxed{i_x = 1 \text{ A}}$$



$$\text{KCL at node A: } i = 0.5 + i_x \rightarrow$$

$$\boxed{i = 1.5 \text{ A}} \rightarrow V_{CA} = 5 \cdot i = 7.5 \text{ V}$$



$$\text{KVL for loop M: } V_x = V_{CA} + V_{BA} = 7.5 + 5 = 12.5 \text{ V}$$

problem
2.42

R_{eq1}

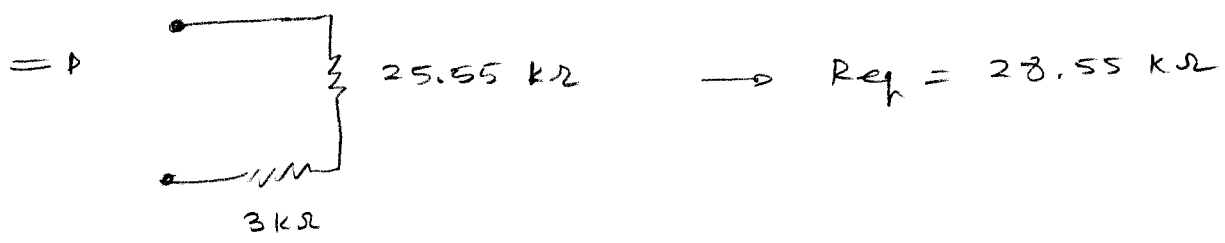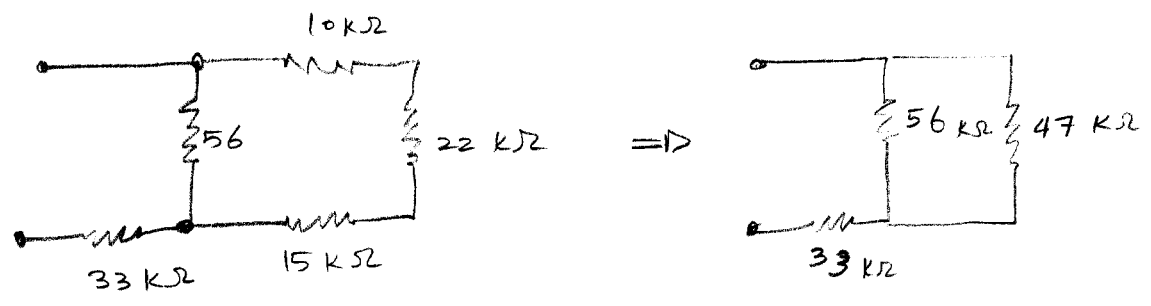


R_{eq2} :

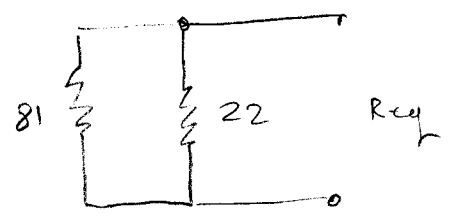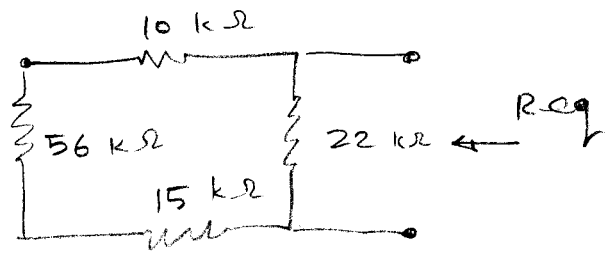


$$R_{eq} = \left(\frac{1}{81} + \frac{1}{22} \right)^{-1} = 17.3 \text{ k}\Omega$$

problem 2-45

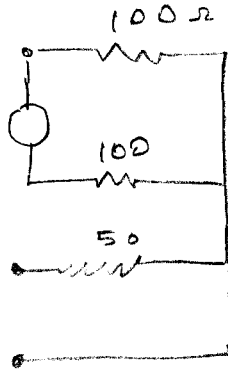


$$Req = 200 \Omega$$

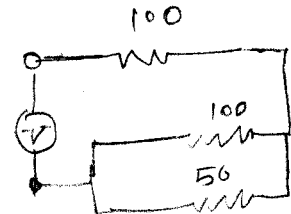


$$Req = \left(\frac{1}{100} + \frac{1}{50} \right)^{-1} + 100$$


$$Req = 133 \Omega$$

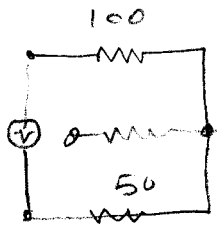


$$Req = 100 + 50 = 150$$

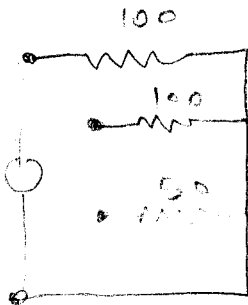


$$Req = 100 \Omega$$

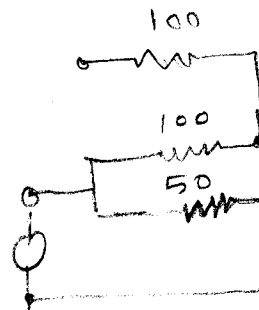
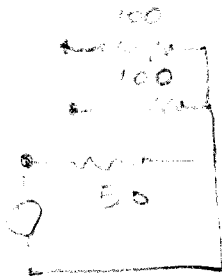
$$Req = \left(\frac{1}{50} + \frac{1}{100} \right)^{-1} = 33.3 \Omega$$




$$Req = 50$$

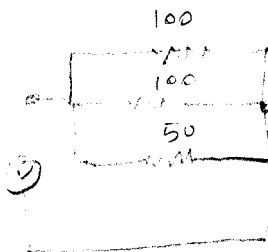

$$Req = \left(\frac{1}{100} + \frac{1}{100} + \frac{1}{50} \right)^{-1} = 25$$



2.51

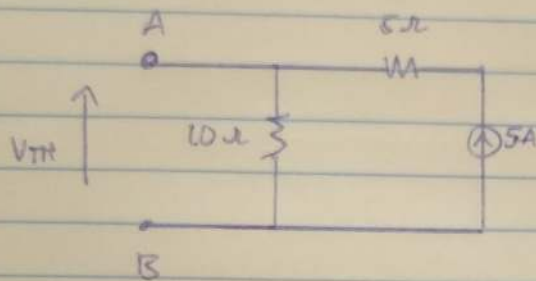

$$R_{eq} = 10\Omega$$


$$V_{TH} = 50V$$

, so we get

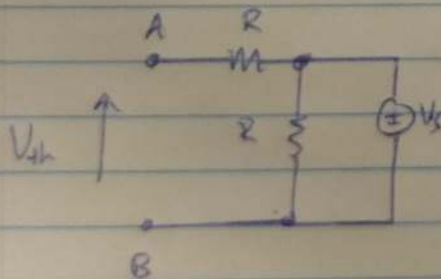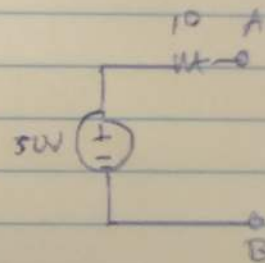

$$R_{eq} = R$$

$$V_{th} = V_s$$

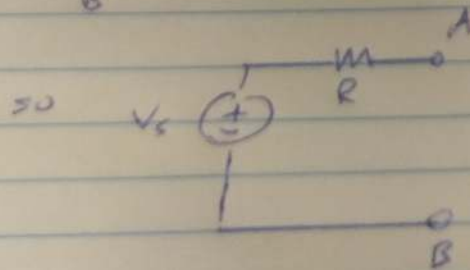

Problem 2.58

Voltage division for V_x :

$$\frac{V_x}{R_x} = \frac{V_{total}}{R_{eq}} \rightarrow V_x = R_x \cdot \frac{V_T}{R_{eq}} = 2 \cdot \frac{24}{14}$$

$$V_x = 3.42 \text{ V}$$

$$V_y = R_y \cdot \frac{V_T}{R_{eq}} = 8 \cdot \frac{24}{14} = 13.71 \text{ V}$$


$$V_y = 13.71 \text{ V}$$

$$V_z = R_z \cdot \frac{V_T}{R_{eq}} = 4 \cdot \frac{24}{14} = 6.85 \text{ V}, \quad V_x + V_y + V_z = V_T = 24 \text{ V}$$

Problem 2.61

$$\frac{i_k}{\frac{1}{R_k}} = \frac{i_{total}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

Let us find current for R_L , so we have

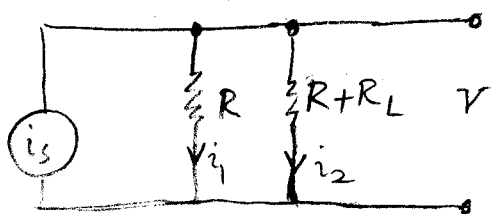

$$i_2 = \frac{\left(\frac{1}{R+R_L}\right) i_s}{\frac{1}{R} + \frac{1}{R+R_L}}$$

$$\text{We know that } V_L = i_2 \cdot R_L = \frac{\left(\frac{1}{R+R_L}\right) i_s R_L}{\frac{1}{R} + \frac{1}{R+R_L}}$$


Problem 2.75

$$(1 \parallel 1) \rightarrow R_1 = \frac{1}{1+1} = 0.5 \text{ k}\Omega$$

$$0.5, 1.5 \text{ in series } R_2 = 0.5 + 1.5 = 2 \text{ k}\Omega$$

$$(2 \parallel 2) \rightarrow R_3 = \frac{2 \times 2}{2+2} = 1 \text{ k}\Omega$$
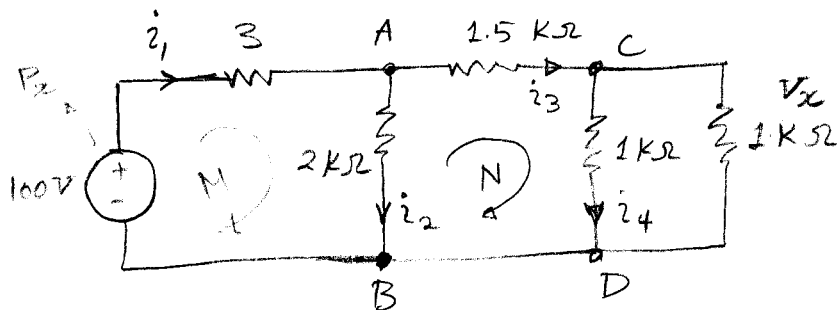
$$1, 3 \text{ series } R_{eq} = 4 \rightarrow$$



$$i_1 = \frac{V}{R_{eq}} = \frac{100}{4000} = 0.025 \text{ A}$$

$$\text{KVL for loop M: } 100 = 0.025 \times 3000 + V_{AB} \rightarrow V_{AB} = 25 \text{ V}$$

$$i_2 = \frac{V_{AB}}{2000} = \frac{25}{2000} = 0.0125 \text{ A} \rightarrow i_x = -i_2 = -0.0125 \text{ A}$$

$$\text{KCL at A} \rightarrow i_3 = i_1 - i_2 = 0.025 - 0.0125 = 0.0125 \text{ A}$$


$$\text{KVL for loop N: } V_{AC} + V_{CD} + V_{BA} = 0 \rightarrow$$

$$1500 \times 0.0125 + V_{CD} - 2000 \times 0.0125 = 0 \rightarrow V_{CD} = 6.25 \text{ V}$$

$$V_{CD} = V_x = 6.25 \text{ V}$$

$$P_x = 100 \times 0.025 = 25 \text{ W}$$

Problem 2.79

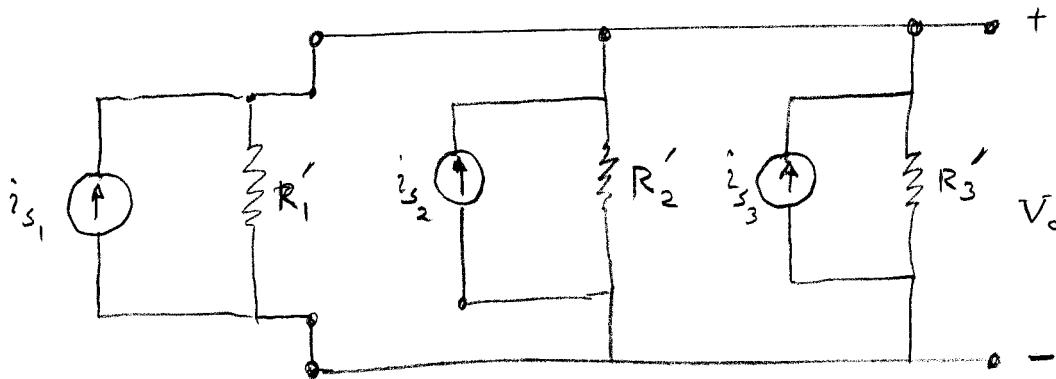

$$i_{s1} = \frac{v_1}{R}$$

$$i_{s2} = \frac{v_2}{R}$$

$$i_{s3} = \frac{v_3}{R}$$

$$R'_1 = \frac{v_1}{i_{s1}}$$

$$R'_2 = \frac{v_2}{i_{s2}}$$

$$R'_3 = \frac{v_3}{i_{s3}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R'_1} + \frac{1}{R'_2} + \frac{1}{R'_3} \rightarrow R_{eq} = \left(\frac{1}{R'_1} + \frac{1}{R'_2} + \frac{1}{R'_3} \right)^{-1} \rightarrow$$

$$V_o = (i_{s1} + i_{s2} + i_{s3}) R_{eq}$$