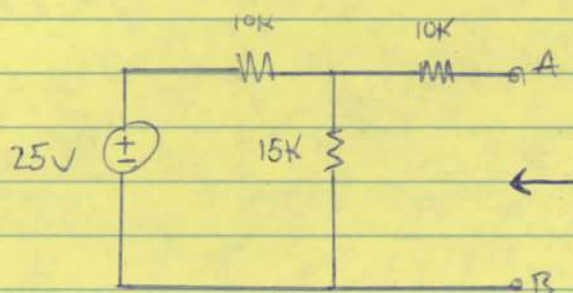
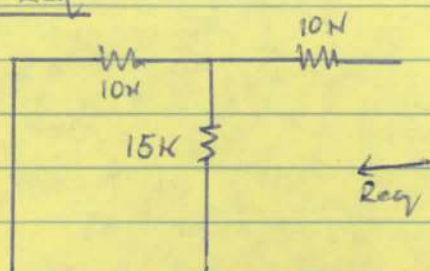


①

MAE140 HW#8 SOLUTIONS

3.51Let us start by finding V_{th}


$$V_{th} = \frac{25}{10k + 15k} \cdot 15k = 15V$$

Now we can find R_{eq} 

$$R_{eq} = 10k + 10k \parallel 15k$$

$$= 16k$$

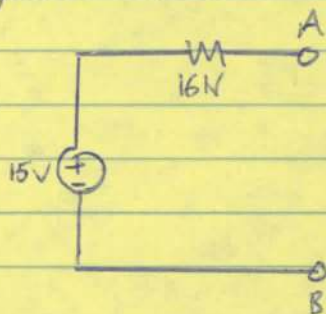
So, this gives us the Thevenin eq circuit



+5

To get the Norton circuit, we can do a source transformation

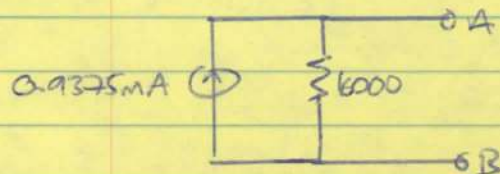
$$I_N = \frac{V_{th}}{R_{th}} = \frac{15}{16k} = 0.9375mA$$



+5

(Award full points if they have both circuits correct. There are other ways to compute.)

(2)

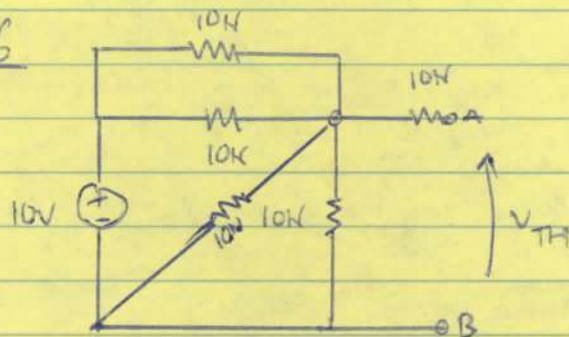3-56


We will find the Thevenin eq. circuit between terminals A & B. Note that when we do this, we do not consider R_L .

 V_{TH}

$$V_{TH} = \left(\frac{10V}{10k \parallel 10k + 10k \parallel 10k} \right) 10k \parallel 10k = \underline{\underline{5V}}$$

(+3)


(We see that we have a voltage divider between two sets of $10k \parallel 10k$ resistances)

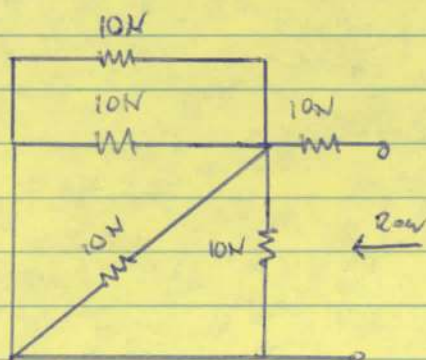 R_{eq} 

$$R_{eq} = 10k + 10k \parallel 10k \parallel 10k \parallel 10k = \underline{\underline{12.5k}}$$

(+3)

That gives us:

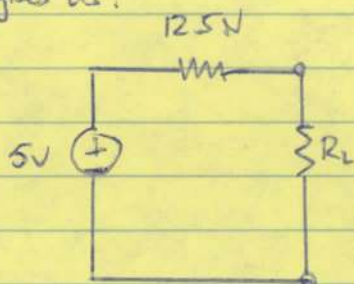

Now, we can compute the voltage across R_L

$$V_{RL} = \frac{5V}{12.5k + R_L} \cdot R_L$$


R_L	V_{RL}
5k	1.429
10k	2.22
20k	3.077

(+4)


NOTE: I ACCIDENTLY THOUGHT THE RESISTANCES WERE IN $k\Omega$, THE ANSWERS ARE ALL THE SAME THOUGH.

361

(3)

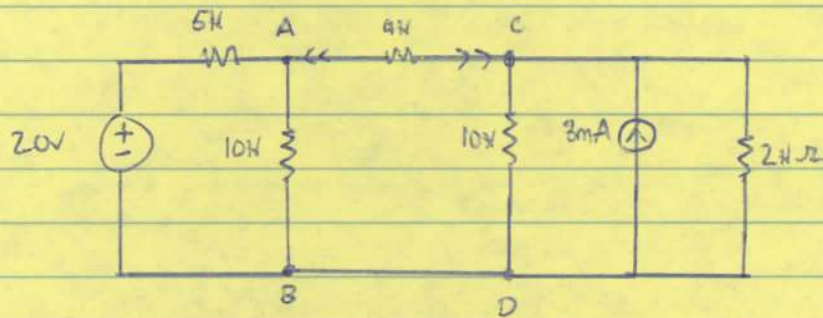

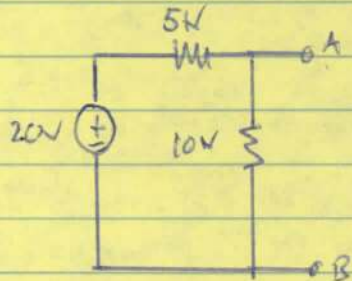Let's find the current between nodes A & B.



$$V_{TH} = \frac{20V \cdot 10k}{15k}$$

$$= 13.3V$$

(+2)

$$R_{eq} = 10k \parallel 5k = 3.33k$$

And now the eq. circuit between C & D.



$$V_{TH} = 3mA \times (10k \parallel 2k)$$


$$= 5V$$

(+2)

$$R_{eq} = 10k \parallel 2k$$

$$= 1.666.67$$

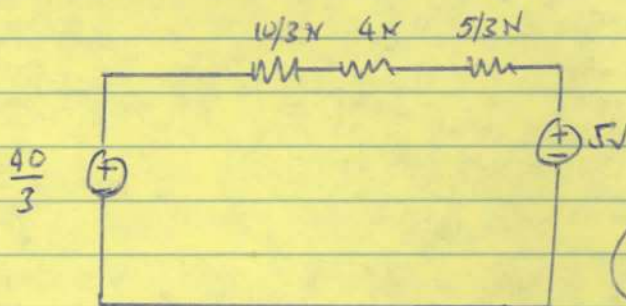Now we can combine both circuits together and add the load resistance



$$I_L = \frac{40}{3} - 5$$


$$\frac{10k + 4k + \frac{5}{3}k}{3}$$

(+6)

$$= \frac{25}{27} mA \quad (0.926 mA)$$

32

(4)

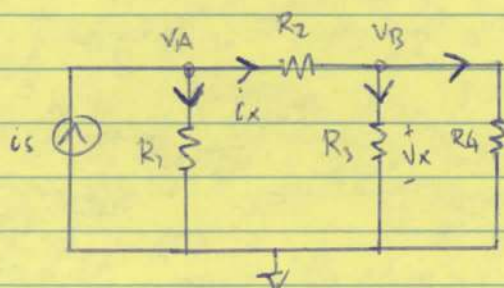

- (1) Assign current directions
- (2) Formulate node-voltage equations at V_A & V_B .

A
$$i_s = \frac{V_A}{R_1} + \frac{V_A - V_B}{R_2}, \quad i_s = \frac{V_A}{R_1} + \frac{V_A}{R_2} - \frac{V_B}{R_2}$$

B
$$\frac{V_A - V_B}{R_2} = \frac{V_B}{R_3} + \frac{V_B}{R_4} \quad \frac{V_B}{R_2} + \frac{V_B}{R_4} + \frac{V_B}{R_3} - \frac{V_A}{R_2} = 0$$

- (3) Write these equations in the form $Ax = b$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

(+6)

$$A = \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix}$$


$$A^{-1} = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) - \left(-\frac{1}{R_2}\right)^2} \begin{bmatrix} \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & +\frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_1} \end{bmatrix}$$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = A^{-1} \cdot \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

$$i_x = \frac{V_A - V_B}{R_2}, \quad V_x = V_B \quad (+4)$$

3.4

(5)

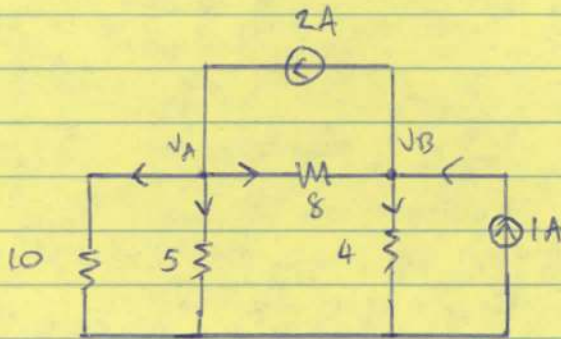

① Assign current directions

② Formulate node-voltage equations at V_A & V_B A

$$\frac{V_A}{10} + \frac{V_A}{5} + \frac{V_A - V_B}{8} = 2, \quad \frac{V_A}{10} + \frac{V_A}{5} + \frac{V_A}{8} - \frac{V_B}{8} = 2$$

B

$$\frac{V_B}{4} + 2 = \frac{V_A - V_B}{8} + 1, \quad \frac{V_B}{4} + \frac{V_B}{8} - \frac{V_A}{8} = -1$$

③ Formulate equations in form $Ax = b$

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{5} + \frac{1}{8} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{1}{4} + \frac{1}{8} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 2 \\ -1 \end{bmatrix} \quad (+4)$$


$$\Rightarrow \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} \frac{1}{10} + \frac{1}{5} + \frac{1}{8} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{1}{4} + \frac{1}{8} \end{bmatrix}^{-1} \begin{bmatrix} 2 \\ -1 \end{bmatrix}$$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4.3478 \\ -1.2174 \end{bmatrix} V \quad (+4)$$

$$V_x = V_b$$

$$I_x = \frac{V_A}{10} = 0.43478 A \quad (+2)$$

26

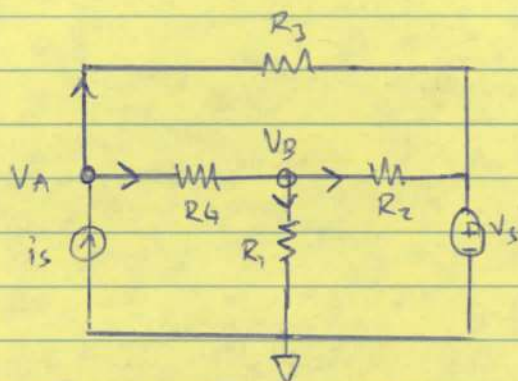

- ① Choose ground
- ② Assign current directions
- ③ Formulate node-voltage equations at V_A & V_B .

A

$$i_s = \frac{V_A - V_C}{R_3} + \frac{V_A - V_B}{R_4}, \quad i_s + \frac{V_C}{R_3} = \frac{V_A}{R_3} + \frac{V_A}{R_4} - \frac{V_B}{R_4}$$

B

$$\frac{V_B}{R_1} + \frac{V_B - V_s}{R_2} = \frac{V_A - V_B}{R_4}, \quad \frac{V_B}{R_1} + \frac{V_B}{R_2} + \frac{V_B}{R_4} - \frac{V_A}{R_4} = \frac{V_s}{R_2}$$

④

Formulate Matrix

$$\begin{bmatrix} \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_4} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} i_s + V_s/R_3 \\ V_s/R_2 \end{bmatrix} \quad (+4)$$

⑤ Solve when $R_1 = R_2 = R_3 = R_4 = 5k$, $V_s = 12V$, $i_s = 2mA$

$$\begin{bmatrix} \frac{1}{5k} + \frac{1}{5k} & -\frac{1}{5k} \\ -\frac{1}{5k} & \frac{1}{5k} + \frac{1}{5k} + \frac{1}{5k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 2mA + 12/5k \\ 12/5k \end{bmatrix}$$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 15.6 \\ 9.2 \end{bmatrix} V \quad (+3)$$

$$V_x = \frac{15.6 - 12}{5k} = 3.6V$$

$$i_x = \frac{9.2}{5k} = 1.84mA \quad (+3)$$


37

$$V_A = V_S$$


$$\frac{V_B - V_A}{R_1} + \frac{V_B - V_C}{R_2} - i_s = 0$$

$$\frac{V_C - V_A}{R_3} + \frac{V_C - V_B}{R_2} + \frac{V_C}{R_4} = 0$$

$$V_D = 0$$

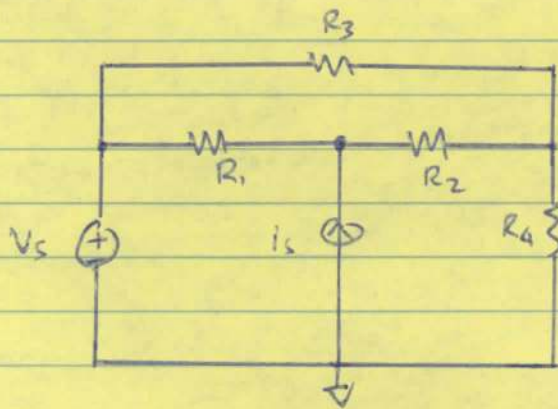

3/2

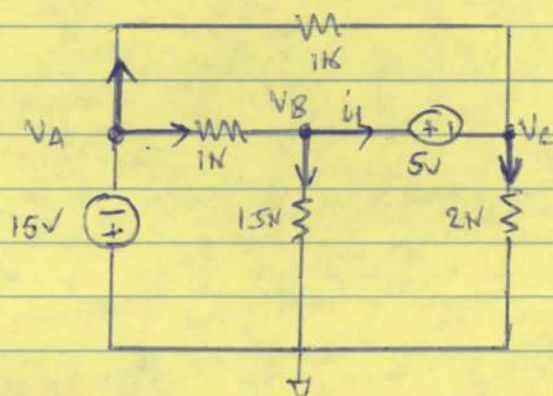

$$V_A = -15V$$

Formulate node voltage equation at B.

$$(1) \quad \frac{V_B}{1.5k} + i_1 = \frac{V_A - V_B}{1k}$$

Formulate node voltage equation at C.

$$(2) \quad \frac{V_C}{2k} = i_1 + \frac{V_A - V_C}{1k}$$

(1) - (2)

$$\frac{V_B}{1.5k} + \cancel{i_1} - \cancel{i_1} - \frac{V_A - V_C}{1k} = \frac{V_A - V_B}{1k} - \frac{V_C}{2k}$$

$$\Rightarrow \frac{V_B}{1.5k} - \frac{V_A - V_C}{1k} = \frac{V_A - V_B}{1k} - \frac{V_C}{2k}$$

$$\Rightarrow \frac{V_B}{1.5k} + \frac{V_C}{1k} + \frac{V_B}{1k} + \frac{V_C}{2k} = \frac{V_A}{1k} + \frac{V_A}{1k}$$

$$V_B - 5 = V_C$$

Combine equations at B & C to eliminate i_1 .

Super node equation

$$V_B \left(\frac{1}{1.5k} + \frac{1}{1k} \right) + V_C \left(\frac{1}{1k} + \frac{1}{2k} \right) = \frac{2V_A}{1k}$$

$$V_B \left(\frac{1}{1.5k} + \frac{1}{1k} \right) + (V_R - 5) \left(\frac{1}{1k} + \frac{1}{2k} \right) = \frac{-30}{1k}$$

$$V_B \left(\frac{1}{1.5k} + \frac{1}{1k} \right) + V_B \left(\frac{1}{1k} + \frac{1}{2k} \right) = \frac{-30}{1k} + 5 \left(\frac{1}{1k} + \frac{1}{2k} \right)$$


$$V_B \left(\frac{1}{1.5k} + \frac{1}{1k} + \frac{1}{1k} + \frac{1}{2k} \right) = -0.6225$$

$$\begin{array}{rcl} V_B & = & \underline{-7.105V} \quad + (4) \\ V_C & = & \underline{-12.105V} \quad + (4) \end{array}$$

$$V_x = V_C$$

$$I_x = \frac{V_C + 15}{1k} = \underline{\underline{2.8947mA}} \quad (2)$$

3.15

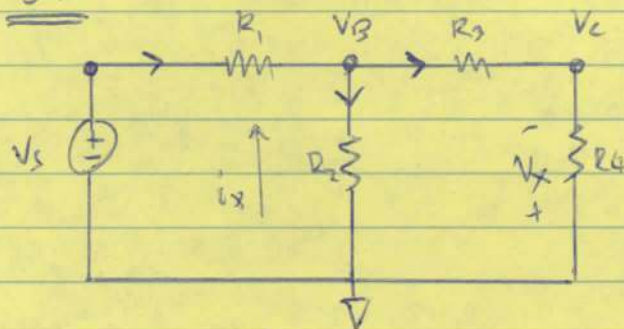

- (1) Assign circuit ground
- (2) Formulate nodal equation at V_B ,

$$\frac{V_s - V_B}{R_1} = \frac{V_B}{R_2} + \frac{V_B}{R_3 + R_4}$$


$$\frac{V_s}{R_1} = V_B \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3 + R_4} \right), \quad V_B = \frac{V_s}{R_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3 + R_4} \right)} \quad (+5)$$

$$i_x = -\frac{V_B}{R_2} \quad (+2) \quad V_x = -\frac{V_B}{R_3 + R_4} \cdot R_4 \quad (+3)$$

(Negative sign because directions of voltage/current opposite to what we have assigned)

• Other solutions possible.

3.4

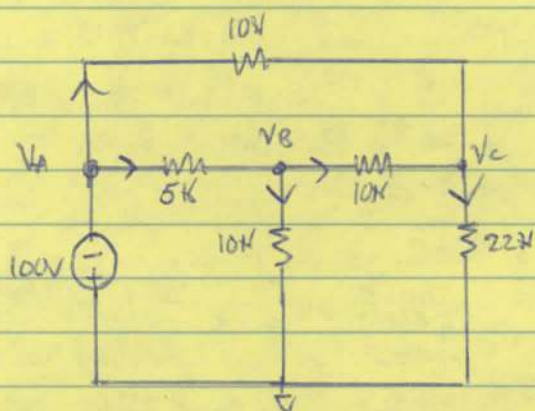

- (1) Assign ground and current directions
- (2) Formulate node-voltage equations

(B)

$$\frac{V_A - V_B}{5k} = \frac{V_B}{10k} + \frac{V_B - V_C}{10k}$$

(C)

$$\frac{V_A - V_C}{10k} + \frac{V_B - V_C}{10k} = \frac{V_C}{22k}$$

- (3) Combine into matrix form


$$\begin{bmatrix} \frac{1}{5k} + \frac{1}{10k} + \frac{1}{10k} & -\frac{1}{10k} \\ -\frac{1}{10k} & \frac{1}{10k} + \frac{1}{10k} + \frac{1}{22k} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{100}{5k} \\ -\frac{100}{10k} \end{bmatrix}$$

- (4) Solve for V_B & V_C

$$\begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -67.0103 \\ -68.0412 \end{bmatrix} V$$

$$V_x = V_C - V_B = \underline{-1.0309V} \quad (+5)$$

$$i_x = \frac{-100 - V_C}{10k} = \underline{3.2mA} \quad (+5)$$

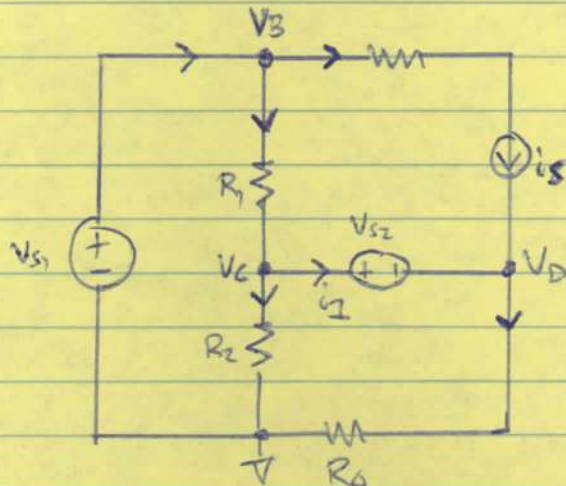3.20

- (1) Assign a ground and current directions
- (2) Formulate nodal equations

$$B/ \quad V_B = V_{SL}$$

$$c) \quad \frac{V_c}{R_2} + i_I = \frac{V_{s1} - V_c}{R_1} \quad (1)$$

$$\text{D/ } i_s + i_1 = \frac{V_D}{R_4} \quad (2)$$

① - ② To eliminate iz term from our expression

$$\frac{V_c}{R_2} + i_2 - i_5 - i_1 = \frac{V_{S1} - V_c}{R_1} - \frac{V_D}{R_6}$$

$$\Rightarrow \frac{V_c}{R_2} + \frac{V_c}{R_1} + \frac{V_D}{R_4} = \frac{V_{S1}}{R_1} + i_{is}$$

$$V_c - V_{s2} = V_D$$

These are our nodal equations

(c) $R_1 = R_2 = 8.2k$, $R_3 = 2.2k$, $R_4 = 3.3k$, $i_s = 2.5mA$,
 $V_{s1} = 15V$, $V_{s2} = 5V$

$$V_c \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + (V_c - V_{s2}) \frac{1}{R_4} = \frac{V_{s1}}{R_1} + i_s$$

$$V_c \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) = \frac{V_{s1}}{R_1} + i_s + \frac{V_{s2}}{R_4}$$

$$V_c \left(\frac{1}{8.2k} + \frac{1}{8.2k} + \frac{1}{3.3k} \right) = \frac{15}{8.2k} + 2.5m + \frac{5}{3.3k}$$

$$V_c = 10.6858V$$

$$V_D = 5.6858V$$

Now we want to find i_x and V_x

$$i_x = \frac{V_B - V_c}{8.2k} + i_s$$

$$= \underline{\underline{3.026mA}}$$

(+5)

$$V_x = V_B - R_3 \cdot i_s - V_D$$

$$= 15 - 2.2k \times 2.5m$$

$$= 9.5 - 5.6858$$

$$= \underline{\underline{3.8142V}}$$

(+5)