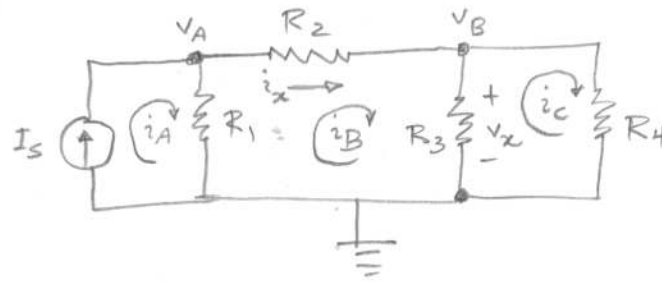


3.2



Sum of voltages around mesh B is

$$\boxed{R_1(i_B - i_A) + R_2 i_B + R_3(i_B - i_C) = 0} \quad (*)$$

sum of voltage around mesh C is

$$\boxed{R_3(i_C - i_B) + R_4 i_C = 0} \quad (**)$$

and also $I_s = i_A$

$$i_x = i_B$$

we substitute $I_s = i_A$ in then we get

$$R_1(i_B - I_s) + R_2 i_B + R_3(i_B - i_C) = 0$$

$$R_3(i_C - i_B) + R_4 i_C = 0$$

$$\Rightarrow \begin{cases} (R_1 + R_2 + R_3) i_B + (-R_3) i_C = R_1 I_s \\ (-R_3) i_B + (R_3 + R_4) i_C = 0 \end{cases} \rightarrow i_C = \frac{R_3}{R_3 + R_4} i_B$$

$$\left(R_1 + R_2 + R_3 - \frac{R_3^2}{R_3 + R_4} \right) i_B = R_1 I_s \rightarrow i_B = \frac{(R_3 + R_4) R_1 I_s}{(R_1 + R_2 + R_3)(R_3 + R_4) - R_3^2}$$

(1)

3.2

$$\dot{i}_L = \frac{R_3 R_1 I_s}{(R_1 + R_2 + R_3)(R_3 + R_4) - R_3^2}$$


$$V_A = (i_A - i_B) R_1 = \left[I_s - \frac{(R_3 + R_4) R_1 I_s}{(R_1 + R_2 + R_3)(R_3 + R_4) - R_3^2} \right] R_1$$

$$V_z = V_B = (i_B - i_L) R_3 = \frac{R_4 R_1 I_s R_3}{(R_1 + R_2 + R_3)(R_3 + R_4) - R_3^2}$$

$$\dot{i}_B = \frac{\begin{vmatrix} R_1 I_s & -R_3 \\ 0 & R_3 + R_4 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 \end{vmatrix}} = \frac{R_1 I_s (R_3 + R_4)}{(R_3 + R_4)(R_1 + R_2 + R_3) - R_3^2}$$

$$\dot{i}_L = \frac{\begin{vmatrix} R_1 + R_2 + R_3 & R_1 I_s \\ -R_3 & 0 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 \end{vmatrix}} = \frac{R_1 R_3 I_s}{(R_3 + R_4)(R_1 + R_2 + R_3) - R_3^2}$$

3-4

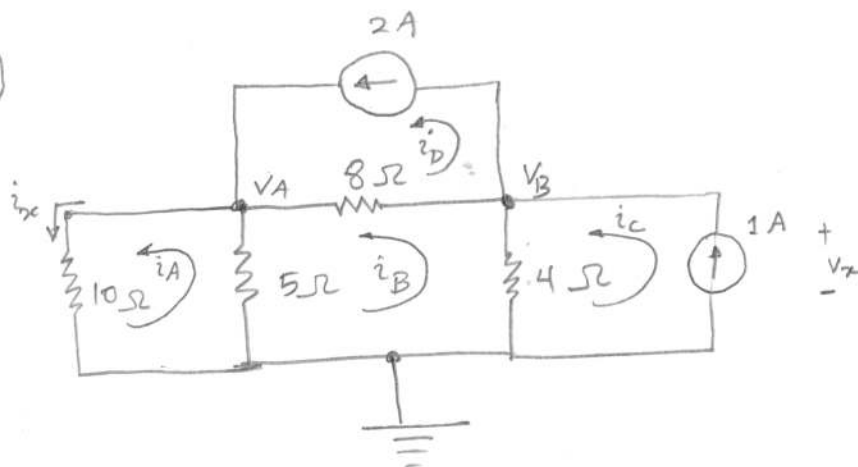

A: $5(i_A - i_B) + 10i_x = 0$ ($i_x = i_A$)

B: $4(i_B - i_C) + 8(i_B - i_D) + 5(i_B - i_A) = 0$

C: $i_C = 1 \text{ A}$

D: $i_D = 2 \text{ A}$

now substitute i_C, i_D in
above equations

$5(i_A - i_B) + 10i_A = 0 \rightarrow 15i_A - 5i_B = 0 \rightarrow i_B = 3i_A$

$4(i_B - 1) + 8(i_B - 2) + 5(i_B - i_A) = 0 \Rightarrow$

$17i_B - 5i_A - 4 - 16 = 0 \rightarrow 17i_B - 5i_A = 20$

$\Rightarrow 51i_A - 5i_A = 20 \rightarrow i_A = \frac{20}{46} \approx 0.43 \text{ A}$ ✓


$i_A = i_x = 0.43$

$i_B = 1.3 \text{ A}$ ✓

$V_B = 4(-i_B + i_C) = 4 \times 0.3 = -1.2 \text{ V}$

$V_A = 10i_x = 4.3 \text{ A}$

3.6

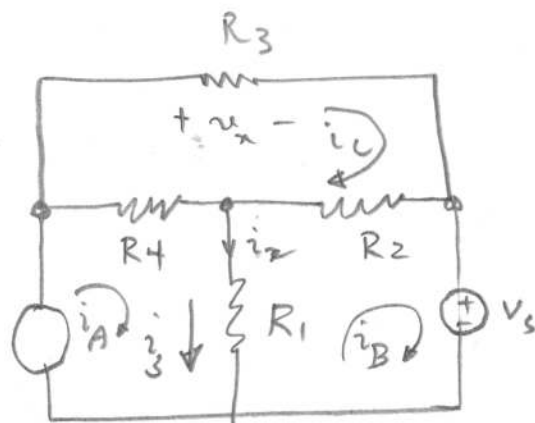

$$R_1 = R_2 = R_4 = 5\text{ k}\Omega$$

$$i_A = i_s = 2$$

mesh A:

$$i_A = i_s$$

mesh B:

$$i_B (R_1 + R_2) - i_A R_1 - i_C R_2 + V_s = 0$$

mesh C:

$$i_C (R_2 + R_3 + R_4) - i_A R_4 - i_B R_2 = 0$$

$$\begin{bmatrix} 1 & 0 & 0 \\ -R_1 & R_1 + R_2 & -R_2 \\ -R_4 & -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} i_s \\ -V_s \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & 0 \\ -5 & +10 & -5 \\ -5 & -5 & +15 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 2 \\ -12 \\ 0 \end{bmatrix}$$

$$i_A = 2\text{ mA}$$


$$i_B = 0.16\text{ mA}$$

$$i_C = 0.72\text{ mA}$$

$$u_x = i_C R_3 = 0.72 \times 5 = 3.6\text{ V}$$

$$i_z = i_A - i_B = 2 - 0.16 = 1.84\text{ mA}$$

3.13

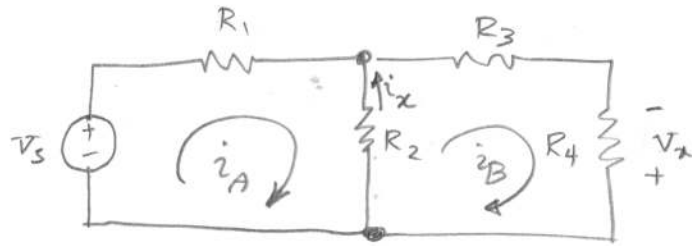

$$A: -v_s + R_1 i_A + R_2 (i_A - i_B) = 0$$

$$B: R_2 (i_B - i_A) + R_3 i_B + R_4 i_B = 0$$

$$i_x = i_B - i_A$$

$$\Rightarrow (R_1 + R_2) i_A + (-R_2) i_B = +v_s$$

$$(-R_2) i_A + (R_2 + R_3 + R_4) i_B = 0 \quad \rightarrow \quad i_A = \frac{R_2 + R_3 + R_4}{R_2} i_B$$

$$\left[\frac{(R_1 + R_2)(R_2 + R_3 + R_4)}{R_2} - R_2 \right] i_B = +v_s \quad \rightarrow$$

$$i_B = \frac{R_2 v_s}{-R_2^2 + (R_1 + R_2)(R_2 + R_3 + R_4)}$$

$$i_A = \frac{(R_2 + R_3 + R_4) v_s}{-R_2^2 + (R_1 + R_2)(R_2 + R_3 + R_4)}$$

$$\Rightarrow i_x = i_B - i_A = \frac{(R_3 + R_4) v_s}{-R_2^2 + (R_1 + R_2)(R_2 + R_3 + R_4) + R_2^2}$$

$$v_x = -i_B R_4 = \frac{R_4 R_2 v_s}{-(R_1 + R_2)(R_2 + R_3 + R_4) + R_2^2}$$

3.14

$$C: 10 i_c + 10 (i_c - i_B) + 5 (i_c - i_A) = 0$$

$$B: 10 (i_B - i_c) + 22 i_B + 10 (i_B - i_A) = 0$$

$$A: 5 (i_A - i_c) + 10 (i_A - i_B) + 100 = 0$$

$$\Rightarrow 25 i_c - 10 i_B - 5 i_A = 0$$

$$-10 i_c + 42 i_B - 10 i_A = 0$$

$$-5 i_c - 10 i_B + 15 i_A = -100$$

$$i_c = \frac{\begin{vmatrix} 0 & -10 & -5 \\ 0 & 42 & -10 \\ -100 & -10 & +15 \end{vmatrix}}{\begin{vmatrix} +25 & -10 & -5 \\ -10 & 42 & -10 \\ -5 & -10 & +15 \end{vmatrix}} = \frac{-31000}{9700} = -3.19 \text{ mA}$$

$$\boxed{i_c = -3.19 \text{ mA}}$$

$$i_B = \frac{\begin{vmatrix} 25 & 0 & -5 \\ -10 & 0 & -10 \\ -5 & -100 & 15 \end{vmatrix}}{|A|} = \frac{-30000}{9700}$$

$$\boxed{i_B = -3.09 \text{ mA}}$$


$$i_A = \frac{\begin{vmatrix} 25 & -10 & 0 \\ -10 & 42 & 0 \\ -5 & -10 & -100 \end{vmatrix}}{|A|} = \frac{-95000}{9700} = -9.79 \text{ mA}$$

$$\boxed{i_A = -9.79 \text{ mA}}$$

$$v_x = 10 (i_c - i_B) = -1.03 \text{ V}$$

$$i_x = i_c = -3.19 \text{ mA}$$

3.20

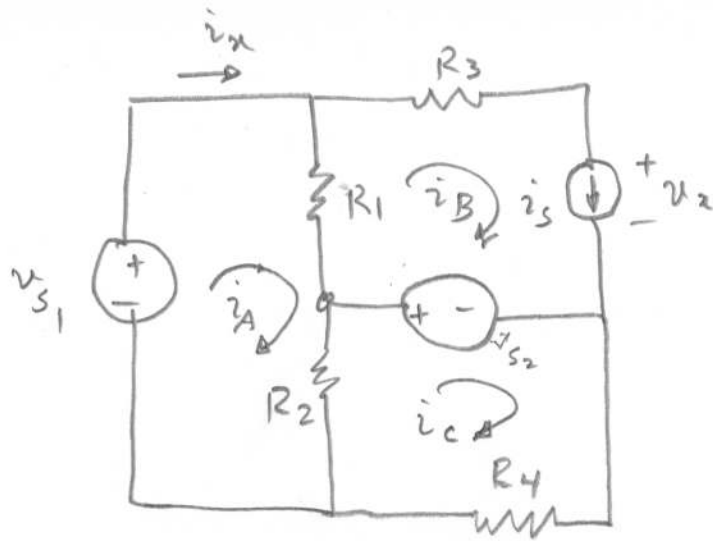

$$A: (R_1 + R_2) i_A - R_1 i_B - R_2 i_C = V_{S1}$$

$$C: -R_2 i_A + (R_2 + R_4) i_C = -V_{S2}$$

$$i_B = 2.5 \text{ mA}$$

$$\begin{bmatrix} 16.4 & -8.2 & -8.2 \\ -8.2 & 8.2 & 11.5 \\ 0 & 1 & 6 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 15 \\ -5 \\ 2.5 \end{bmatrix}$$

$$i_A = 3.02 \text{ mA}$$

$$i_B = 2.5 \text{ mA}$$

$$i_C = 1.72 \text{ mA}$$

now we write KVL for $\square B$

$$R_3 i_B + u_x - V_{S2} + R_1 i_B - R_1 i_A = 0 \rightarrow$$


$$2.2 (2.5) + u_x - 5 + 8.2 (2.5) - 8.2 (3.02) = 0$$

$$u_x = 3.76 \text{ V}$$

$$i_x = i_A = 3.02 \text{ mA}$$

$$\rightarrow P = u_{S1} \cdot i_x = 15 \times 3.02 = 45.3 \text{ mW}$$

3.41

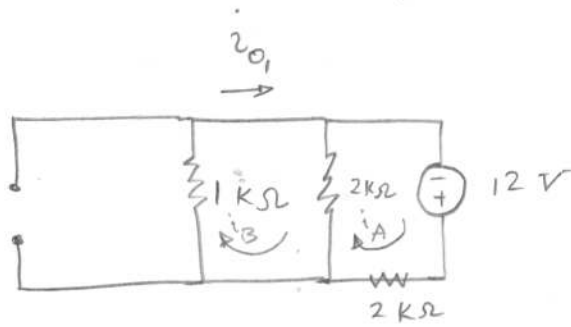


$$B: i_B + 2(i_B - i_A) = 0 \rightarrow 3i_B = 2i_A$$

$$A: 2i_A + 2(i_A - i_B) - 12 = 0 \rightarrow 4i_A - 2i_B = 12$$

$$6i_B - 2i_B = 12 \rightarrow i_B = 3 \text{ mA} \rightarrow i_A = 4.5 \text{ mA}$$

$$i_{o1} = i_B = 3 \rightarrow \boxed{i_{o1} = 3 \text{ mA}}$$
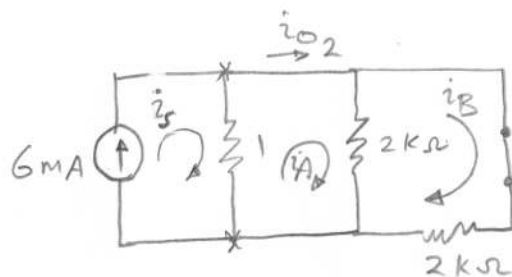
$$\boxed{v_{o1} = 1 \cdot i_B = 3 \text{ V}}$$



$$A: 1(i_A - i_s) + 2(i_A - i_B) = 0$$

$$i_{o2} = i_A \quad i_s = 6 \text{ mA}$$

$$B: 2(i_B - i_A) + 2i_B = 0$$

$$\Rightarrow 3i_A - 2i_B = 6$$

$$\rightarrow 4i_B = 6 \rightarrow$$

$$4i_B - 2i_A = 0 \rightarrow i_A = 2i_B$$

3.41

$$i_B = 1.5 \text{ mA}$$

$$i_A = 3 \text{ mA}$$

$$i_{o2} = i_A = 3 \text{ mA}$$


$$v_{o2} = 1(3 - 6) = -3$$

$\Rightarrow$

$$i_o = i_{o2} + i_{o1} = 3 + 3 = 6 \text{ mA}$$

$$v_o = v_{o1} + v_{o2} = 0$$

3.43

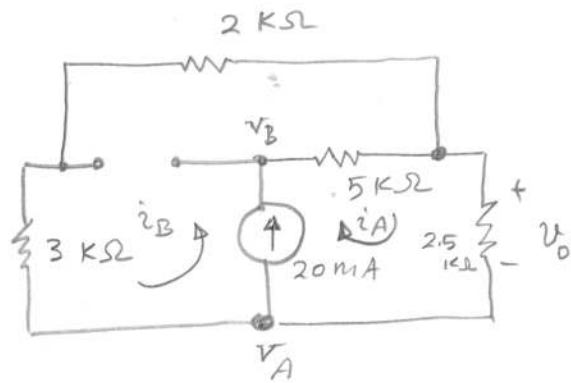

$$A: (V_A - V_B) + 5(20) + 2.5 i_A = 0$$

$$B: (V_A - V_B) + 5(20) + 2 i_B + 3 i_B = 0$$

$$\Rightarrow 2.5 i_A = 5 i_B$$

$$i_A = 2 i_B$$

$$20 = i_A + i_B$$


$$\Rightarrow 20 = 3 i_B$$

$$i_B = 6.67 \text{ mA}$$

$$i_A = 13.33 \text{ mA}$$

$$\Rightarrow v_{o1} = 2.5 i_A$$

$$v_{o1} = 33.32 \text{ V}$$

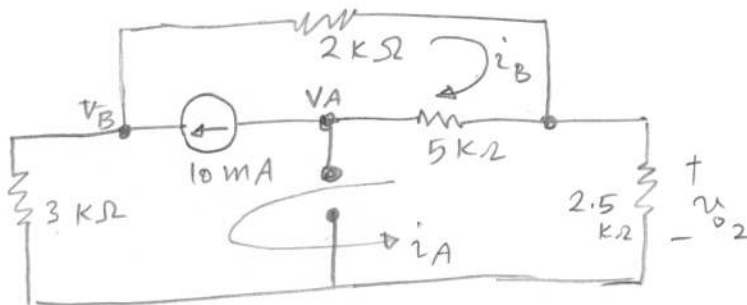

$$B: 2(i_B) + 5(i_B + i_A) + V_A - V_B = 0$$

$$A: 5(i_B + i_A) + V_A - V_B + 3 i_A + 2.5 i_A = 0$$


$$\Rightarrow 2 i_B = 5.5 i_A$$

$$i_B = 2.75 i_A$$

$$i_A + i_B = 10 \text{ mA} \Rightarrow i_A = 2.66 \text{ mA}$$

$$v_{o2} = -6.65 \text{ V}$$

$$v_o = 33.32 - 6.65 = 26.67 \text{ V}$$

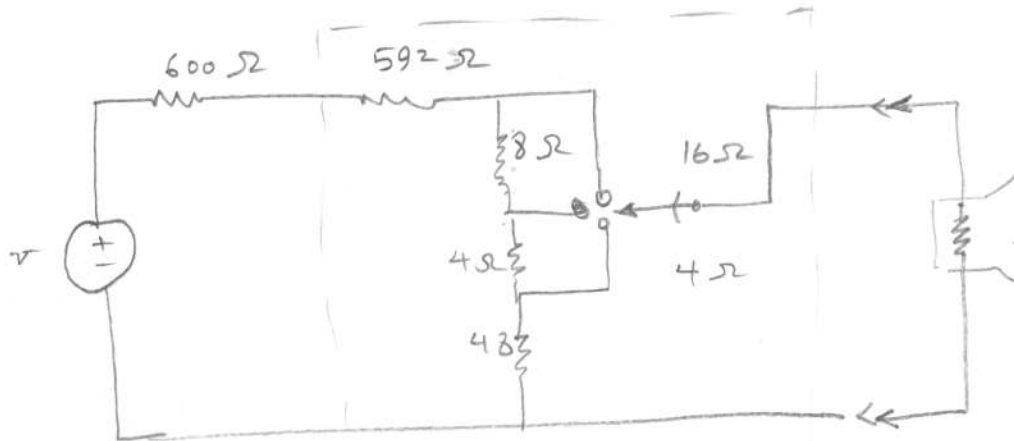

I If switch $16\ \Omega$ is connected

$$R_{in} = 592 + 16 \parallel (8 + 4 + 4) = 600\ \Omega$$

$$R_{out} = (4 + 4 + 8) \parallel (592 + 600) = 15.79\ \Omega$$

II If switch $8\ \Omega$ is connected

$$R_{in} = (592 + 8) + (4 + 4) \parallel 8 = 604\ \Omega$$

$$R_{out} = (4 + 4) \parallel (8 + 592 + 600) = 7.94\ \Omega$$

III If switch $4\ \Omega$ is connected


$$R_{in} = (592 + 8 + 4) + (4 \parallel 14) = 606\ \Omega$$

$$R_{out} = 4 \parallel (4 + 8 + 592 + 600) = 3.99\ \Omega$$

So, the claim is true


3-102

Let us try

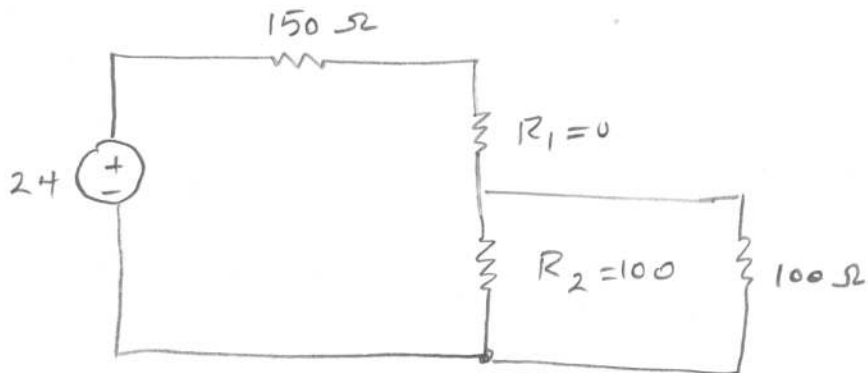

$$R_{eq} = 250 \longrightarrow i = \frac{24}{250} = 0.096\text{ A} \quad \checkmark$$


but now

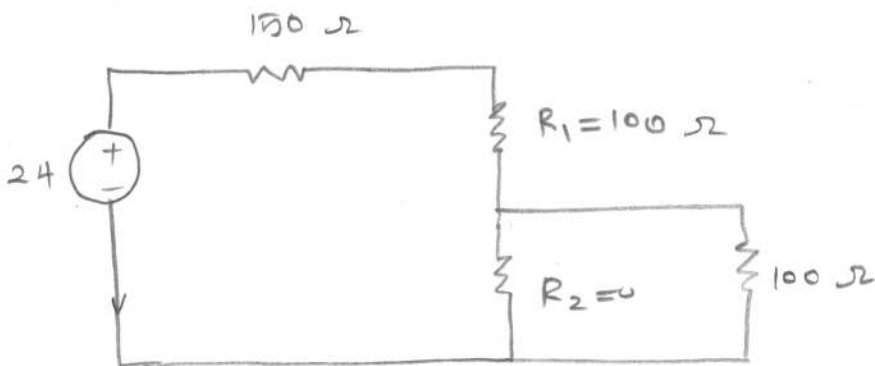

$$i = \frac{24}{350} = 0.06$$


3-102

Let put $R=0$ then we have

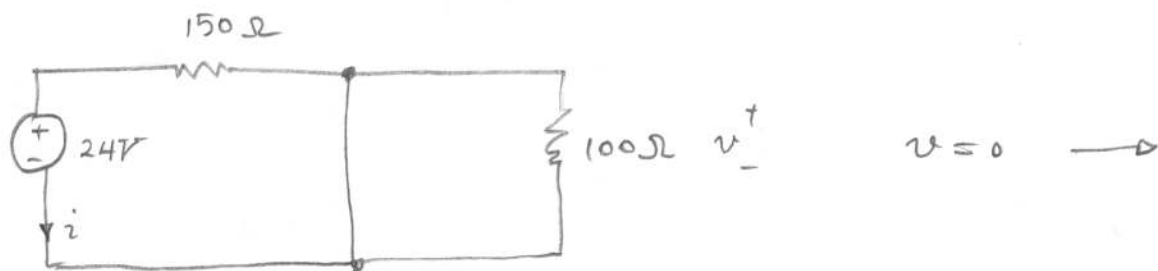

$i = \frac{24}{150} = 0.16$ too high more than maximum!
we need

but now

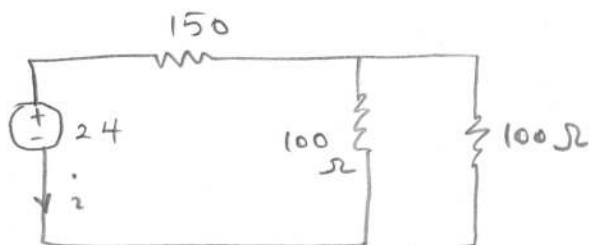

$$R_{eq} = 150 + 50 = 200$$

$$i = \frac{24}{200} = 0.12 \text{ A}$$

acceptable!