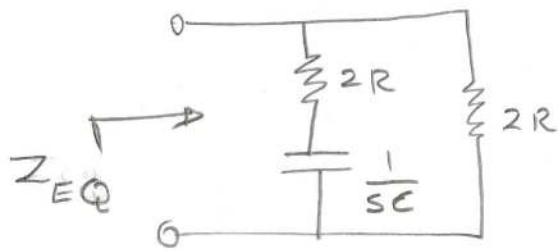


10.3

Let us consider in s-domain



$$Z_{EQ} = \left(2R + \frac{1}{sC}\right) \parallel 2R$$
$$= \left(\frac{2RCs + 1}{sC}\right) \parallel 2R$$

$$Z_{EQ} = \frac{\frac{2RCs + 1}{sC} \times 2R}{\frac{2RCs + 1}{sC} + 2R} = \frac{(2RCs + 1) 2R}{2RCs + 1 + 2RCs} = \frac{(2RCs + 1) 2R}{4RCs + 1}$$

Zeros : $2RCs + 1 = 0 \rightarrow s = \frac{-1}{2RC}$ (Zero)

Poles : $4RCs + 1 = 0 \rightarrow s = \frac{-1}{4RC}$ (Pole)


(b) $\frac{-1}{4RC} = -22 \Rightarrow RC = \frac{1}{88}$

Let $R = 12 \text{ k}\Omega \rightarrow C = 5.6 \text{ }\mu\text{F}$

Zero $\Rightarrow s = \frac{-1}{2\left(\frac{1}{88}\right)} = -44 \text{ rad/s}$

10.3

Let us consider in s-domain

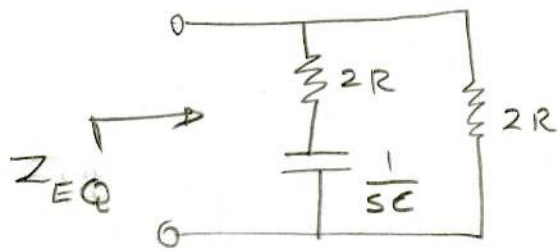

$$Z_{EQ} = \left(2R + \frac{1}{sC} \right) \parallel 2R$$

$$= \left(\frac{2RCs + 1}{sC} \right) \parallel 2R$$

$$Z_{EQ} = \frac{\frac{2RCs + 1}{sC} \times 2R}{\frac{2RCs + 1}{sC} + 2R} = \frac{(2RCs + 1) 2R}{2RCs + 1 + 2RCs} = \frac{(2RCs + 1) 2R}{4RCs + 1}$$

Zeros : $2RCs + 1 = 0 \rightarrow s = \frac{-1}{2RC}$ (Zero)


Poles : $4RCs + 1 = 0 \rightarrow s = \frac{-1}{4RC}$ (Pole)

(b) $\frac{-1}{4RC} = -22 \Rightarrow RC = \frac{1}{88}$


Let $R = 12 \text{ k}\Omega \rightarrow C = 5.6 \text{ }\mu\text{F}$

Zero $\Rightarrow s = \frac{-1}{2 \left(\frac{1}{88} \right)} = -44 \text{ rad/s}$

10.7

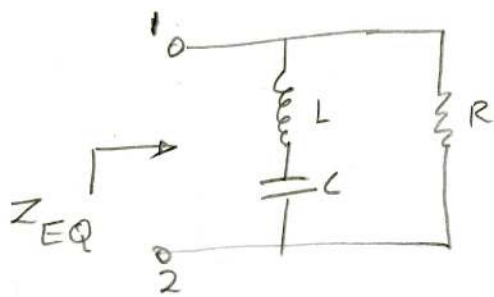

S-domain
→

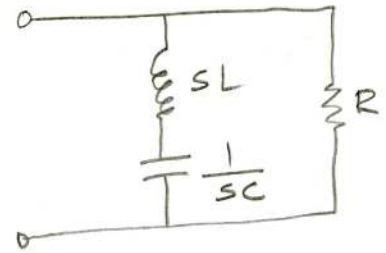

$$(a) \quad Z_{EQ} = \left(sL + \frac{1}{sC} \right) \parallel R = \left(\frac{s^2 LC + 1}{sC} \right) \parallel R$$

$$Z_{EQ} = \frac{R + s^2 LCR}{1 + sRC + s^2 LC}$$

$$\text{Zeros: } R + s^2 LCR = 0 \rightarrow s = \pm j \sqrt{\frac{1}{LC}} \quad (\text{Zeros})$$

$$\text{Poles: } 1 + sRC + s^2 LC = 0 \rightarrow s = \frac{-RC \pm \sqrt{R^2 C^2 - 4LC}}{2LC} \quad (\text{Poles})$$

$$[b] \quad R = 1 \text{ k}\Omega, \quad C = 0.1 \text{ }\mu\text{F}$$

$$\text{if zeros at } \pm j 10 \text{ krad/s} = \pm 10^4 \text{ rad/s}$$


$$\sqrt{\frac{1}{LC}} = 10^4 \rightarrow L = \frac{1}{C (10^4)^2} = \frac{1}{0.1 \times 10^{-6} \times 10^8} = \frac{1}{10}$$

$$\rightarrow \boxed{L = 0.1 \text{ H}}$$

$$[c] \quad s = \frac{-R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} = \frac{-1000}{2 \times 0.1} \pm \sqrt{\frac{10^6}{4 (0.01)} - 10^8}$$

$$s = -5000 \pm j 8660 \text{ rad/s}$$

10. 21

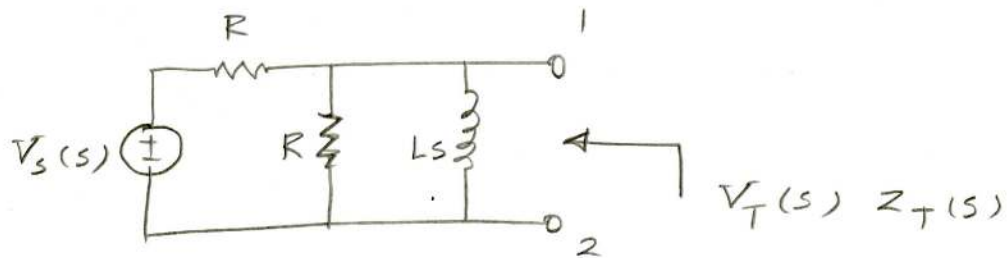


$V_T(s)$ = voltage across $R \parallel Ls$

$$V_T(s) = \frac{(R \parallel Ls)}{(R + R \parallel Ls)} V_S(s) = \frac{\frac{RLs}{R+Ls}}{\frac{RLs}{R+Ls} + R} \times V_S(s)$$

$$V_T(s) = \frac{Ls}{R + 2Ls} V_S(s)$$

By short circuiting 1, 2 we get,

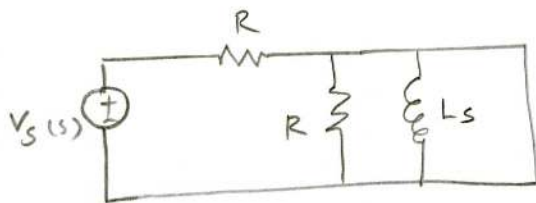

$$I_{sc}(s) = \frac{V_S(s)}{R}$$

$$Z_T(s) = \frac{V_T(s)}{I_{sc}(s)} = \frac{RLs}{R + 2Ls}$$


Pole at $s = \frac{-R}{2L} = -24 \text{ krad/s} \rightarrow$

Choose $R = 6 \text{ k}\Omega \rightarrow L = 125 \text{ mH}$

X 10.25

solve for $I_L(s)$, $i_L(t)$, $V_o(s)$, $v_o(t)$

Let move switch to position B at $t=0$

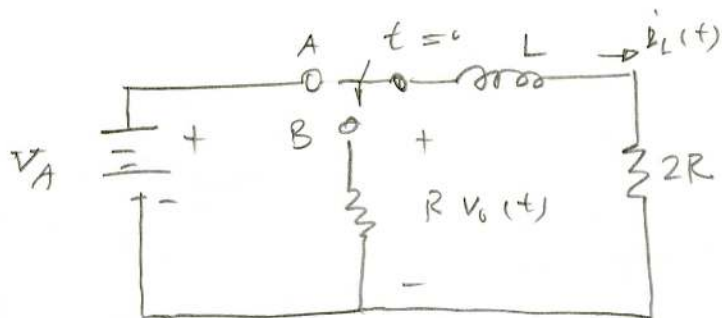


initial condition:

For $t < 0$ circuit is in a DC steady state condition acts like a short circuit



$$\text{So } i_L(t) = \frac{V_A}{2R}$$

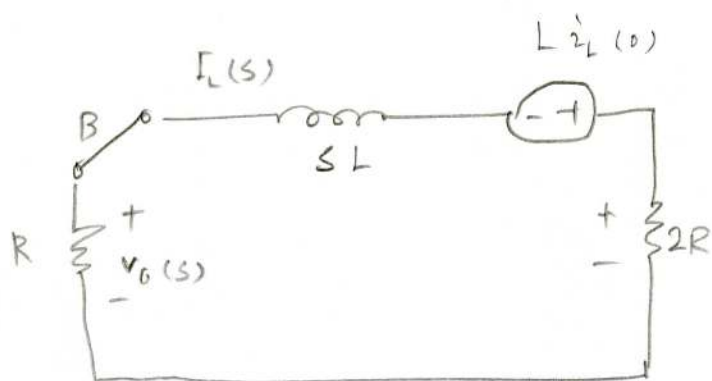

① using KVL we get

$$sL I_L(s) - L i_L(0) + 2R I_L(s) = 0$$

$$+ R I_L(s) = 0$$

$$(sL + 3R) I_L(s) = L i_L(0) = L \frac{V_A}{2R}$$

$$I_L(s) = \frac{L \frac{V_A}{2R}}{sL + 3R} = \frac{1/R}{s + \frac{3R}{L}} V_A$$

②

$$V_o(s) = -R I_L(s) = -\frac{V_A}{s + \frac{3R}{L}}$$


$$V_o(t) = \left\{ -V_A e^{-\frac{3R}{L}t} \right\} u(t)$$

$$I_L(s) = \frac{1/R}{s + \frac{3R}{L}} V_A$$

$$i_L(t) = \left\{ \frac{V_A}{R} e^{-\frac{3R}{L}t} \right\} u(t)$$

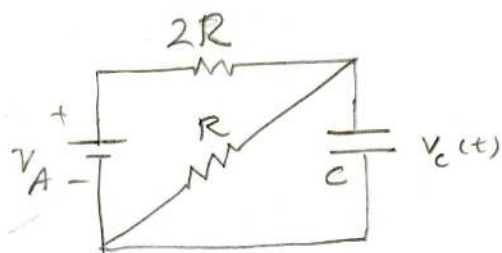problem 27


Determine initial condition by analysing circuit in position



- voltage divider, Capacitor acts as open circuit as $t \rightarrow \infty$

$$\frac{V_C(0)}{R} = \frac{V_A}{3R} \rightarrow V_C(0) = \frac{V_A}{3}$$

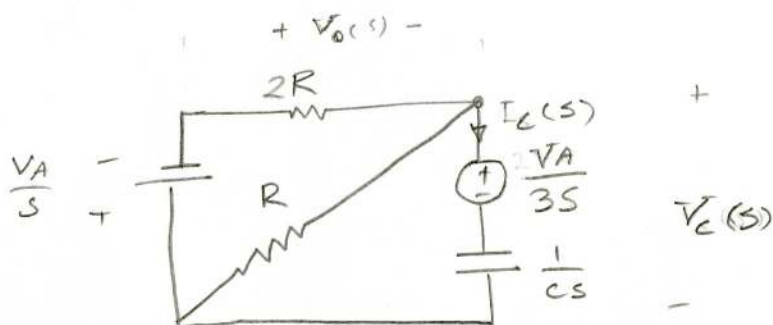Now we look at the s-domain circuit in position B.



So we have

$$\frac{V_C(s) + \frac{V_A}{s}}{2R} + \frac{V_C(s)}{R} + \frac{V_C(s) - \frac{V_A}{3s}}{1/cs} = 0$$

$$\left(\frac{3}{2R} + cs\right)V_C(s) = \left(\frac{c}{3} - \frac{1}{2Rs}\right)V_A \Rightarrow V_C(s) = \frac{2R}{3+2Rcs} \times \frac{2Rcs-3}{6Rs} V_A$$

$$V_C(s) = \frac{V_A}{3s} \left(\frac{2Rcs-3}{3+2Rcs} \right), \quad I_C(s) = \frac{V_C(s) - \frac{V_A}{3s}}{1/cs} = cs \cdot V_C(s) - \frac{c}{3} V_A$$

Now let take the inverse Laplace transform.

$$I_C(s) = \frac{cV_A}{3} \left(\frac{2Rcs-3}{3+2Rcs} \right) - \frac{c}{3} V_A = \frac{cV_A}{3} \frac{2Rcs-3-3-2Rcs}{3+2Rcs}$$

$$I_C(s) = \frac{cV_A}{3} \left(\frac{-6}{3+2Rcs} \right) = \frac{-2cV_A}{3+2Rcs}$$


$$I_C(s) = \frac{-6}{3+2Rcs} \frac{cV_A}{3} = \frac{-2cV_A}{3+2Rcs} \Rightarrow I_C(s) = -\frac{2cV_A}{3+2Rcs}$$

Now we have for output loop

$$V_A + V_C(s) - V_C(s) = 0 \Rightarrow V_C(s) = -V_C(s) - \frac{V_A}{s}$$

s-domain

Q.51

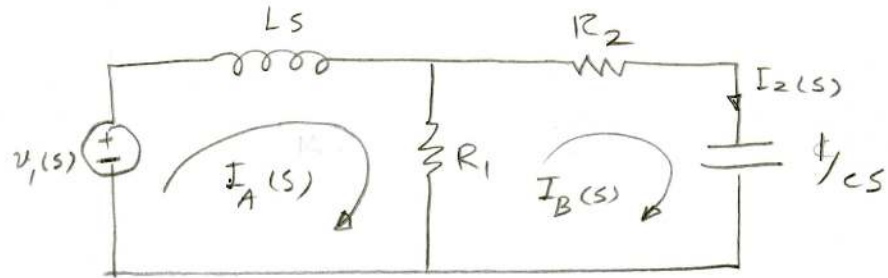

Let us formulate the mesh current equation.

$$(1) -v_1(s) + I_A(s)LS + R_1(I_A(s) - I_B(s)) = 0$$

$$v_1(s) = I_A(s)(LS + R_1) - I_B(s)R_1$$

$$(2) 0 = (R_1 + R_2 + \frac{1}{cS})I_B(s) - R_1 I_A(s) = 0$$

$$\text{from (1)} \quad I_A(s) = \frac{v_1(s) + I_B(s)R_1}{LS + R_1}$$

$$I_B = \frac{R_1 I_A(s)}{\frac{cS(R_1 + R_2) + 1}{cS}} = \frac{R_1 cS}{cS(R_1 + R_2) + 1} \left[\frac{v_1(s) + I_B(s)R_1}{LS + R_1} \right]$$

$$I_2(s) = I_B(s) = \frac{R_1 v_1(s) cS}{(R_1 + R_2)LCs^2 + (R_1 R_2 C + L)s + R_1}$$

(E) single zero of system located at $s=0$

$$\text{Poles: } s^2(R_1 + R_2)LC + (R_1 R_2 C + L)s + R_1 = 0$$

$$P = \frac{-(R_1 R_2 C + L) \pm \sqrt{(R_1 R_2 C + L)^2 - 4(R_1 + R_2)LCR_1}}{2(R_1 + R_2)LC}$$


10.51

$$(d) \quad v_1(t) = 20 u(t) \quad R_1 = 2 \text{ k}\Omega \quad R_2 = 1 \text{ k}\Omega \\ L = 1 \text{ H} \quad C = 0.5 \text{ }\mu\text{F}$$

$$I_2(s) = \frac{2 \cdot (20) \cdot 0.5 \text{ MF} \cdot s}{(2+1)1(0.5 \text{ MF})s^2 + (2 \times 0.5 + 1) + 2}$$

* prob.

10.53

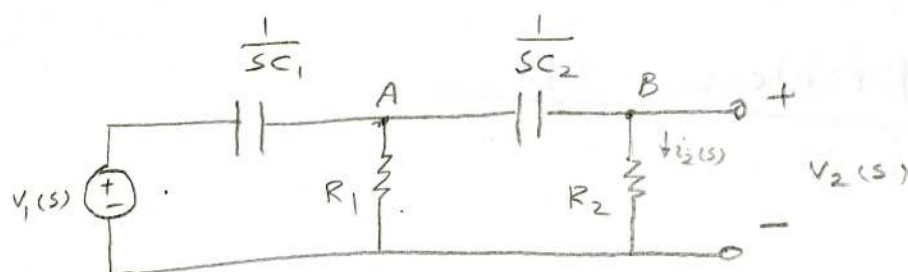

Let consider the node voltage equations at A, B are

$$A: \left(\frac{1}{1/sC_1} + \frac{1}{1/sC_2} + \frac{1}{R_1} \right) V_A - \left(\frac{1}{1/sC_2} \right) V_B = \frac{1}{1/sC_1} V_1(s)$$

$$\Rightarrow (sC_1 + sC_2 + \frac{1}{R_1}) V_A - sC_2 V_B = sC_1 V_1(s) \quad (i)$$

$$B: \left(-\frac{1}{1/sC_2} \right) V_A + \left(\frac{1}{1/sC_2} + \frac{1}{R_2} \right) V_B = 0 \Rightarrow$$

$$-sC_2 V_A + (sC_2 + \frac{1}{R_2}) V_B = 0 \quad (ii)$$

Solving $V_2(s)$ ($V_2(s) = V(B)$)

$$V_A = \frac{sC_1 V_1(s) + sC_2 V_2(s)}{sC_1 + sC_2 + \frac{1}{R_1}}$$


Substituting in (ii) we

$$\text{get } -sC_2 \frac{sC_1 V_1(s) + sC_2 V_2(s)}{sC_1 + sC_2 + \frac{1}{R_1}} + (sC_2 + \frac{1}{R_2}) V_2(s) = 0 \rightarrow$$

$$V_2(s) = \frac{s^2 C_1 C_2 R_1 R_2 V_1(s)}{s^2 R_1 R_2 C_1 C_2 + s(R_1 C_1 + R_2 C_2 + R_1 C_2) + 1}$$

10.53

c)

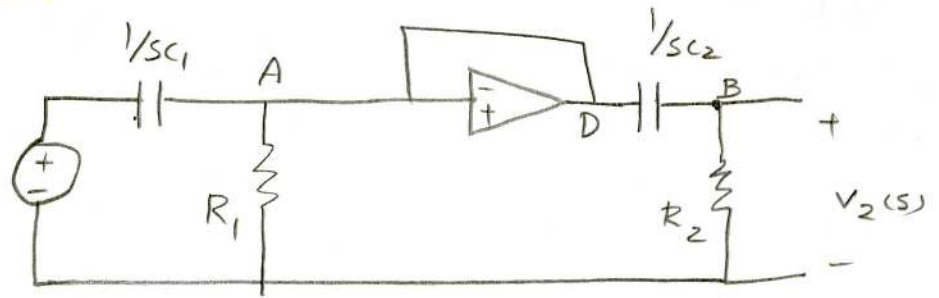

as the output impedance of opamp is very low

$$V_A = V_D$$

at Node A: $(\frac{1}{R_1} + sC_1) V_A = V_1(s) \times sC_1$

at Node B: $(-sC_2) V_A + (sC_2 + \frac{1}{R_2}) V_2(s) = 0$

$$(-sC_2) \left(\frac{V_1(s) sC_1}{sC_1 + \frac{1}{R_1}} \right) + \left(sC_2 + \frac{1}{R_2} \right) V_2(s) = 0 \Rightarrow$$

$$V_2(s) = \frac{s^2 C_1 C_2 R_1 R_2 V_1(s)}{(sC_1 R_1 + 1)(sC_2 R_2 + 1)} = \frac{s^2 V_1(s)}{(s + \frac{1}{C_1 R_1})(s + \frac{1}{C_2 R_2})}$$

(d) Poles are $s = \frac{-1}{C_1 R_1}$ $s = \frac{-1}{C_2 R_2}$

$$\left\{ \begin{array}{l} \text{if } R_1 = 1 \text{ k}\Omega \rightarrow C_1 = 0.01 \text{ }\mu\text{F} \\ \frac{1}{C_1 R_1} = 10^4 \end{array} \right.$$

$$\left\{ \begin{array}{l} \text{if } R_2 = 1 \text{ k}\Omega \\ \frac{1}{C_2 R_2} = 10^5 \end{array} \right. \rightarrow C_2 = 0.1 \text{ }\mu\text{F}$$


10.72

$$V_1(t) = \cos 2000t$$

desired output $V_2(t) = -\sin 2000t$

$$V_1(s) = \frac{s}{s^2 + (2000)^2}$$
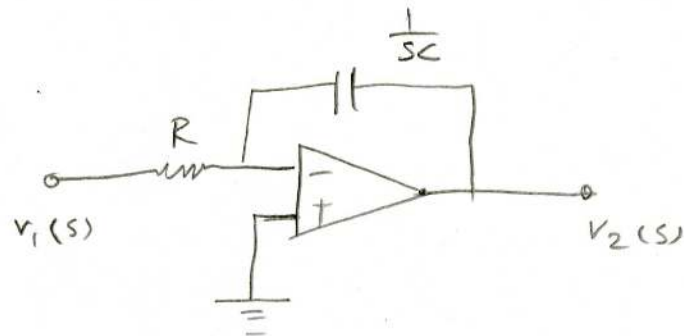
$$V_2(s) = \frac{-2000}{s^2 + (2000)^2}$$



this is an inverting amplifier and know that

$$V_2(s) = K V_1(s) = -\frac{1}{sCR} V_1(s) = -\frac{1}{sCR} V_1(s) \quad \text{So}$$


$$V_2(s) = -\frac{1}{sCR} V_1(s)$$

$$-\frac{2000}{s^2 + (2000)^2} = -\frac{1}{sCR} \frac{s}{s^2 + (2000)^2} \rightarrow \frac{1}{CR} = 2000 \rightarrow$$

$$C = \frac{1}{2000R}$$

Let select $R = 0.5 \text{ k}\Omega \rightarrow C = 1 \mu\text{F}$

what happens if $V_2(0) = 5 \text{ V}$

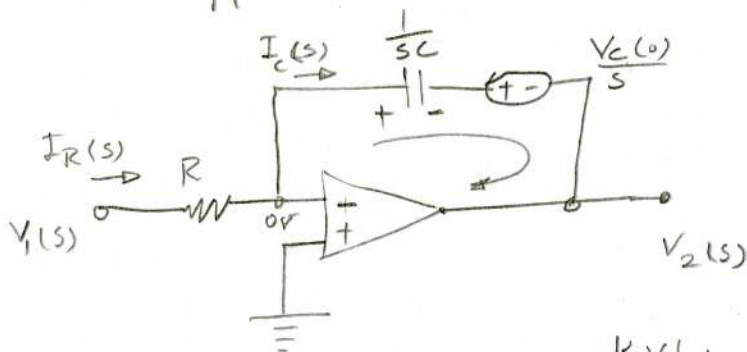

We know that

$$i_N = i_P = 0 \quad \text{so}$$

$$I_C(s) = I_R(s) = I(s)$$

$$V^+ = V^- = 0$$

$$\text{KVL: } -V_2(s) = \frac{1}{sC} I(s) + \frac{V_C(0)}{s}, \quad I(s) = \frac{V_1(s)}{R}$$


$$-V_2(s) = \frac{1}{sC} \frac{V_1(s)}{R} + \frac{V_C(0)}{s}$$

$$V_2(s) = -\frac{V_1(s)}{sCR} - \frac{V_C(0)}{s}$$

step function in time domain

output is shifted by $V_C(0) = 5 \text{ V}$

10-12

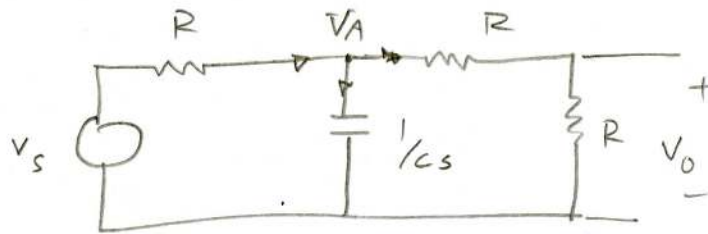

node Analysis at (A)

$$\frac{V_s - V_A}{R} = \frac{V_A}{1/s_c} + \frac{V_A}{2R} \rightarrow \frac{V_s}{R} = \frac{3V_A}{2R} + s_c V_A = \left(\frac{3 + 2R s_c}{2R} \right) V_A$$


Voltage divider

$$\frac{V_o}{R} = \frac{V_A}{2R} \rightarrow V_o = \frac{V_A}{2}$$

$$V_s = \frac{3 + 2R s_c}{2} V_A$$


$$V_o = \frac{V_A}{2} \rightarrow \frac{V_o}{V_s} = \frac{1}{3 + 2R s_c}$$

10-83

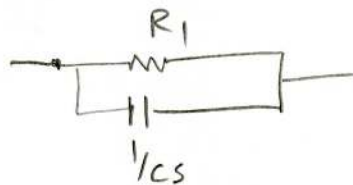

$$R_{eq} = \frac{R_1 \frac{1}{s_c}}{R_1 + \frac{1}{s_c}} = \frac{R_1}{R_1 s_c + 1}$$

inverting Amp

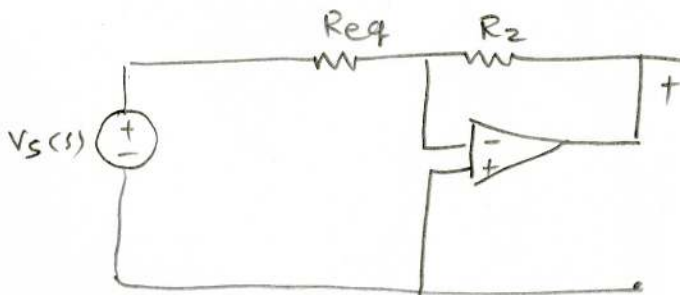

$$K = -\frac{R_2}{R_1} = -\frac{R_2}{R_{eq}}$$

$$\frac{V_o}{V_s} = -\frac{R_2}{\frac{R_1}{R_1 s_c + 1}} = -\frac{R_2 (R_1 s_c + 1)}{R_1}$$

if a pole get and cancel

$$\text{zero } s = -\frac{1}{R_1 C} \quad \text{then}$$

zero at

$$R_1 s_c + 1 = 0$$

$$\rightarrow s = -\frac{1}{R_1 C}$$