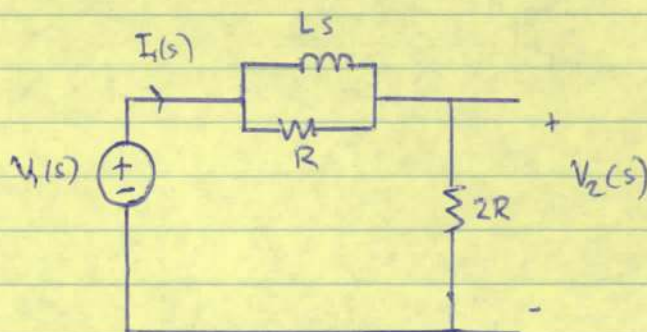


(a) 11.2



We want to find the voltage transfer function. Let us first find the parallel resistance of the inductor and resistor

$$Ls \parallel R = \frac{1}{\frac{1}{R} + \frac{1}{Ls}} = \frac{1}{\frac{Ls + R}{RLs}} = \frac{SLR}{Ls + R}$$

Now,

$$I_1(s) = \frac{V_1(s)}{\frac{SLR}{Ls + R} + 2R} = \frac{V_1(s) \cdot (Ls + R)}{SLR + 2R(Ls + R)}$$

$$V_2(s) = I_1(s) \cdot 2R$$

$$= \frac{V_1(s) \cdot (Ls + R) \cdot 2R}{SLR + 2R(Ls + R)} = \frac{V_1(s) \cdot (2RLs + 2R^2)}{S(LR + 2RL) + 2R^2}$$

so,

$$T(s) = \frac{2RLs + 2R^2}{3RLs + 2R^2}$$

The driving point impedance is $Z(s) = \frac{SLR}{Ls + R} + 2R$

$$= \frac{SLR + 2R(Ls + R)}{Ls + R}$$

(b) Select value of R & L such that transfer function has a zero at $s = -120 \text{ rad/s}$ and a pole at $s = -80 \text{ rad/s}$.

The value of the zero is

$$2RLs + 2R^2 = 0$$

$$2RLs = -2R^2$$

$$s = \frac{-2R^2}{2RL} = \frac{-2R}{2L} = \underline{\underline{-\frac{R}{L}}}$$

and the value of the pole is

$$3RLs + 2R^2 = 0$$

$$3RLs = -2R^2$$


$$s = \frac{-2R^2}{3RL}$$

$$= -\frac{2}{3} \cdot \frac{R}{L}$$

so, we select

$$\underline{\underline{R = 12, L = 0.1 \text{ H}}}$$

11.3

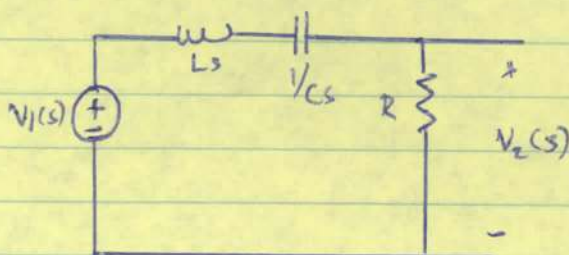

Let's first compute the driving point impedance $Z(s) = Ls + \frac{1}{Cs} + R$

$$= \frac{s^2 LC + 1 + sCR}{Cs}$$

$$= \frac{s^2 LC + sCR + 1}{Cs}$$

Now let us compute the transfer function.

$$I_1(s) = \frac{V_1(s)}{Z} = \frac{V_1(s) \cdot Cs}{s^2 LC + sCR + 1}$$

$$V_2(s) = I_1(s) \cdot R$$

$$= V_1(s) \cdot \frac{sCR}{s^2 LC + sCR + 1}$$

$$T(s) = \frac{sCR}{s^2 LC + sCR + 1} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{R}{L} \cdot \frac{s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

There is a single zero at $s=0$. For the poles we require

$$(s+1000)(s+1000) = s^2 + \frac{R}{L}s + \frac{1}{LC}$$

$$s^2 + 2000s + 1000000 = s^2 + \frac{R}{L}s + \frac{1}{LC}$$

$$\frac{R}{L} = 2000,$$

$$\omega = 6283$$

$$R = 200$$


$$L =$$

$$R = 2K$$

$$L = 1H$$

$$C = 1 \times 10^{-6} F$$

12.32

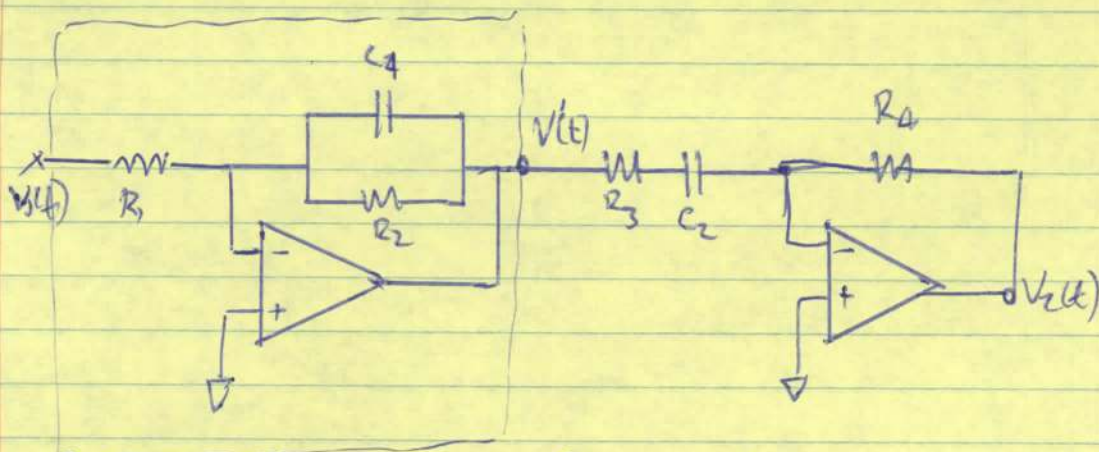

Low pass filter (we know this from before)

The transfer function of the first stage circuit is

$$T(s) = \frac{-R_2}{R_1} \cdot \frac{1}{1 + R_2 C_1 s}$$

We can also find the transfer function of the second stage which is also an inverting amplifier.

$$T(s) = \frac{-R_4}{R_3 + \frac{1}{sC_2}} = \frac{-R_4}{\frac{sR_3C_2 + 1}{sC_2}} = \frac{-sC_2R_4}{1 + sR_3C_2}$$


which we see is a high pass response.

Let us select the low pass filter cutoff frequency

$$\omega_{c1} = \frac{1}{R_2 C_1} = 40000, \quad R_2 = 10\text{N}, \quad C_1 = 2.5\text{nF}$$

$$\omega_{c2} = \frac{1}{R_3 C_2} = 1000, \quad R_3 = 10\text{N}, \quad C_2 = 0.1\mu\text{F}$$

Box

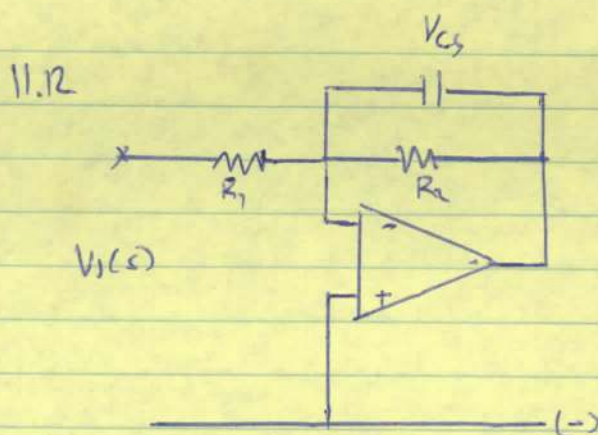

This is an inverting amplifier with $H(s) = -\frac{Z_2}{Z_1}$ where $Z_1 = R_1$ and

$$Z_2 = \frac{1}{\frac{1}{R_2} + Cs} = \frac{1}{\frac{1 + R_2Cs}{R_2}} = \frac{R_2}{1 + R_2Cs}$$

so, $H(s) = T(s) = -\frac{R_2}{1 + R_2Cs} \cdot \frac{1}{R_1} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + R_2Cs}$

We can see immediately that the input impedance is equal to R_1 , so select $R_1 = 1.5k$.

We can then select $R_2 = 150k$.


Finally, we need to determine the location of the pole

$$R_1 + R_1 R_2 Cs = 0$$

$$s = -\frac{R_1}{R_1 R_2 C} = -500$$

$$C = \frac{+R_1}{(100 R_1 R_2)} = \frac{1}{500 R_2} = \underline{\underline{13.3 \text{ pF}}}$$

11.14

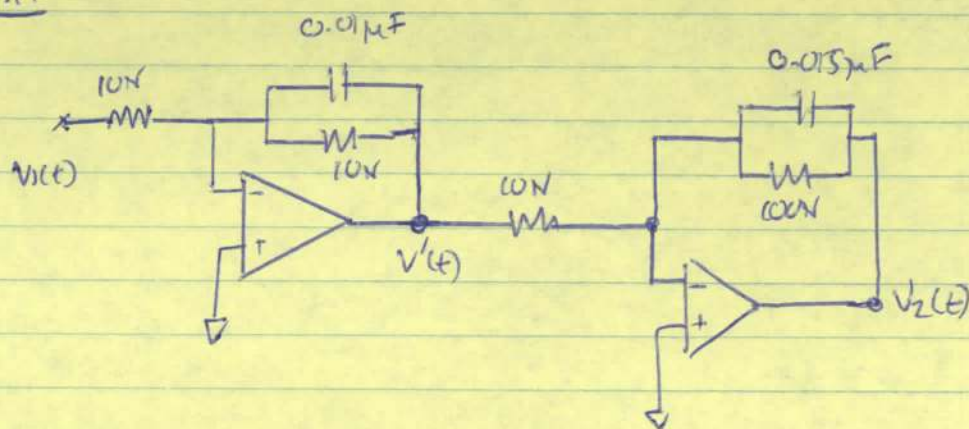

This is two inverting amplifiers cascaded together, so

$$T(s) = T_1(s) \cdot T_2(s)$$


$$= \frac{-10k}{10k} \cdot \frac{1}{1 + 10k \cdot 0.01\mu s} \cdot \frac{-100k}{10k} \cdot \frac{1}{1 + 100k \cdot 0.015\mu s}$$

$$= \frac{-10}{(1 + 1 \times 10^{-4}s)(1 + 1.5 \times 10^{-3}s)}$$

$$s = -\frac{1}{10^{-4}} = -10^4, \quad \frac{1}{1.5 \times 10^{-3}} = -\underline{\underline{666.67}}$$

There are no zeros.

11.36

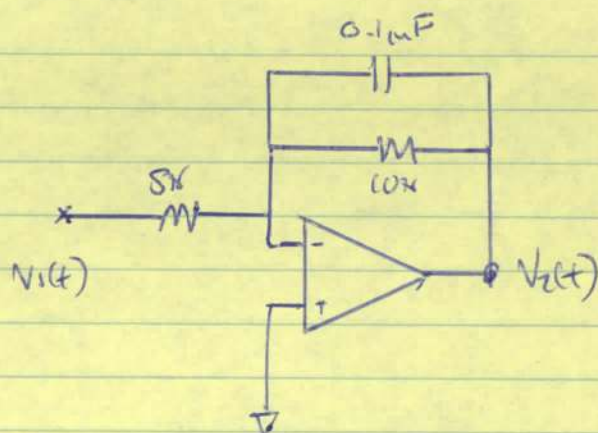

We have another inverting amplifier, so the transfer function is

$$T(s) = \frac{-R_2}{R_1} \cdot \frac{1}{1 + R_2 C s} = \frac{-10k}{5k} \cdot \frac{1}{1 + 10k \cdot 0.1\mu s}$$

$$= \frac{-2}{1 + 1 \times 10^{-3} s}$$

The pole is located at $s = -\frac{1}{1 \times 10^{-3}} = -1000$

$$T(s) = \frac{-2000}{s + 1000}, \quad T(j\omega) = \frac{-2000}{j\omega + 1000}$$

$$V_1(t) = 5 \cos(500t) \text{ V}, \quad \omega = 500$$

$$T(j500) = -1.6 + 0.8j$$

$$|T(j500)| = 1.78885$$

$$\angle T(j500) = 153.435^\circ$$


$$\text{so, } V_2(t) = 5 \cdot 1.78885 \cos(500t + 153.4^\circ)$$

$$= 8.9442719 \cos(500t + 153.4^\circ)$$

$$V_1(t) = 5 \cos(1000t), \quad V_2(t) = 7.07 \cos(1000t + 135^\circ)$$

$$V_1(t) = 5 \cos(1071t), \quad V_2(t) = 0.945 \cos(10000t + 95.7^\circ)$$

11.40

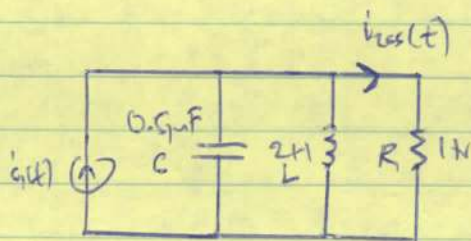

$$I_1(s) = V sL + \frac{V}{sL} + \frac{V}{R}$$

$$I_1(s) = V \left(sC + \frac{1}{sL} + \frac{1}{R} \right)$$

$$I_1(s) = V \left(\frac{s^2 RLC + R + sL}{sLR} \right)$$

$$V(s) = \frac{I_1 \cdot sLR}{s^2 RLC + sL + R}$$

$$I_2(s) = \frac{V(s)}{R}$$

$$= \frac{I_1(s) sL}{s^2 RLC + sL + R}$$

$$T(s) = \frac{I_2(s)}{I_1(s)} = \frac{sL}{s^2 RLC + sL + R}$$

If $i_1(t) = 10 \cos(100t)$ mA, we have $T(100j) = 0.1980 \angle 78.5788^\circ$

So,

$$i_2(t) = 10 \cdot 0.1980 \cos(100t + 78.58^\circ) \text{ mA}$$


If $i_1(t) = 5 \cos(1000t)$ mA, $T(1000j) = 1 \angle 0^\circ$, so

$$i_{2sc}(t) = i_1(t)$$

If $i_1(t) = 5 \cos(10000t)$ mA $T(10000j) = 0.198 \angle -78.5788^\circ$

$$i_{2sc}(t) = 0.99 \cos(10000t - 78.58^\circ) \text{ mA}$$

12.4

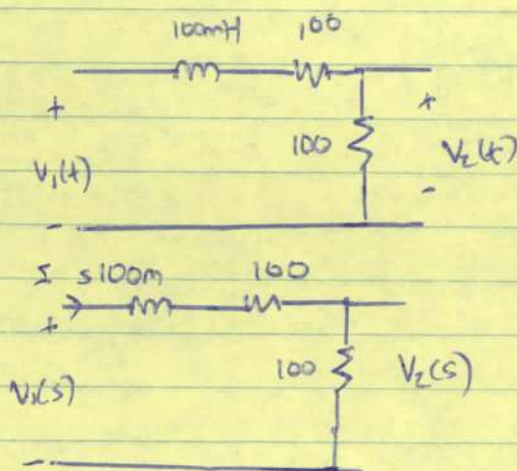

$$I(s) = \frac{V_1(s)}{200 + 0.1s}$$

$$V_2(s) = \frac{V_1(s) \cdot 100}{200 + 0.1s}$$

$$T(s) = \frac{100}{200 + 0.1s} = \frac{1000}{s + 2000} = \frac{0.5(2000)}{s + 2000}$$

We see immediately that this is a first order low pass response,


DC GAIN, $s=0 \Rightarrow T(s=0) = 0.5$

Infinite frequency gain $T(s \rightarrow \infty) = 0$

Cutoff frequency, $\omega_c = 2000 \text{ rad/s}$.

MAGNITUDE PLOT

PHASE PLOT

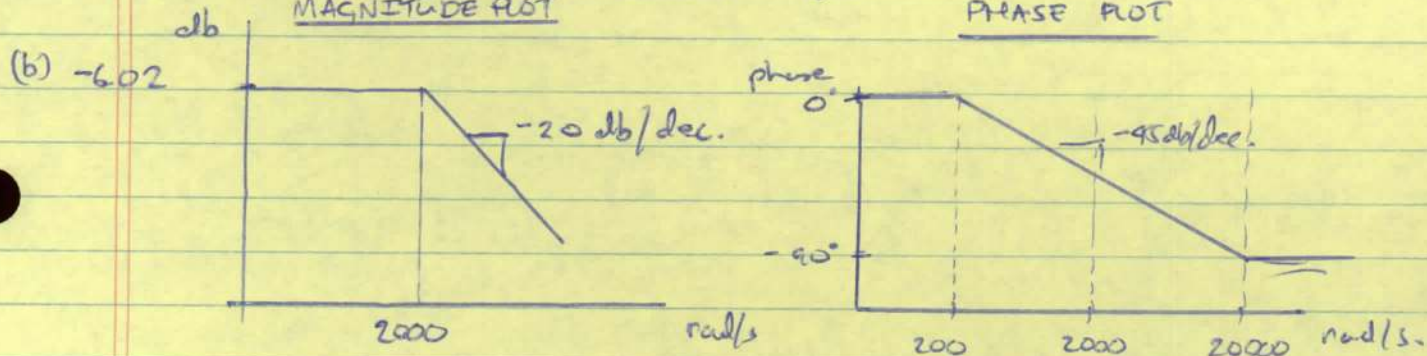

(c) Calculate the gain at $\omega = 0.1\omega_c$, $\omega = 10\omega_c$,

$$T(j\omega) = \frac{1000}{j\omega + 2000}$$

$$T(200) = \frac{1000}{200j + 2000} = 0.4975 \angle -5.7106$$

So gain is 0.4975 or -6.0638 db,

$$T(20000) = \frac{1000}{20000j + 2000} = 0.04975 \angle -84.289$$

So gain is 0.04975 or -26.0638 db

$$T(2000) = \frac{1000}{j2000 + 2000} = 0.3535 \angle -45$$

So gain is 0.3535 or -9.0308999 db

(e) ~~1 octave down is half the cutoff frequency, so $\omega = 1000$ rad/sec.~~

~~$$T(1000) = \frac{1000}{j1000 + 2000} = 0.4 - 0.2j = 0.4472 \angle -26.565^\circ$$~~


1 octave past cutoff is $2\omega_c = 4000$,

$$T(4000) = \frac{1000}{4000j + 2000} = 0.2236 \angle -63.435$$

Gain is 0.2236 or -13.0103 db,

At the passband the gain is -6.0638 db, so the dB difference
is $13.0103 - 6.0638 = \underline{\underline{6.9465 \text{ db down}}}$

12.7

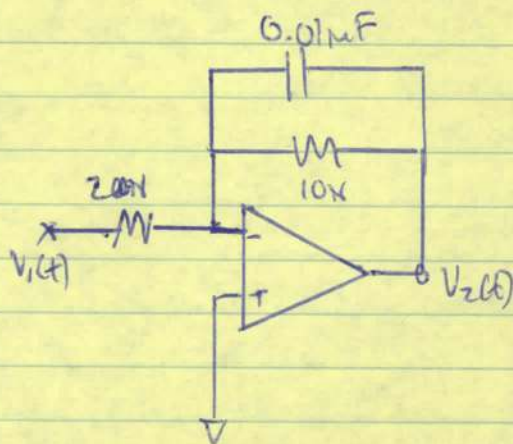

We know the transfer function of this circuit from our prior analysis:

$$T(s) = -\frac{R_2}{R_1} \cdot \frac{1}{1 + R_2 C s}$$

$$\text{where } R_1 = 20k\Omega \\ R_2 = 10k\Omega \\ C = 0.01\mu F$$


We can again see from the form of the transfer function that this circuit has a first order (low pass) response.

$$\text{DC gain} = \frac{-R_2}{R_1} = \underline{\underline{-5}}$$

$$\text{Infinite frequency gain} = 0$$

$$\text{Cutoff frequency } \omega_c = \frac{1}{R_2 C} = \underline{\underline{10000 \text{ rad/s}}}$$

(15) Straight line approximation

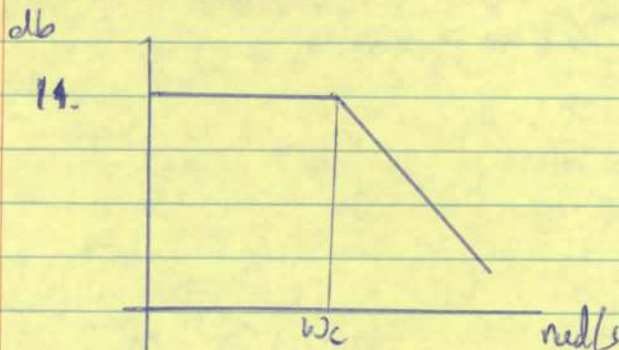

Compute gain at $0.1\omega_c$, ω_c and $10\omega_c$

$0.1\omega_c$

$$|T(j0.1\omega_c)| = \left| -5 \cdot \frac{1}{1 + 0.1m \times (1000)} \right| = 4.975$$

so gain is 4.975 or 13.936db


ω_c

$$|T(j\omega_c)| = 3.5355 \text{ or } \underline{10.97db}$$

$$10\omega_c \quad |T(j10\omega_c)| = 0.4975 \text{ or } -6.06db$$

(e) You would change R_1 by a factor of 5.


12.31

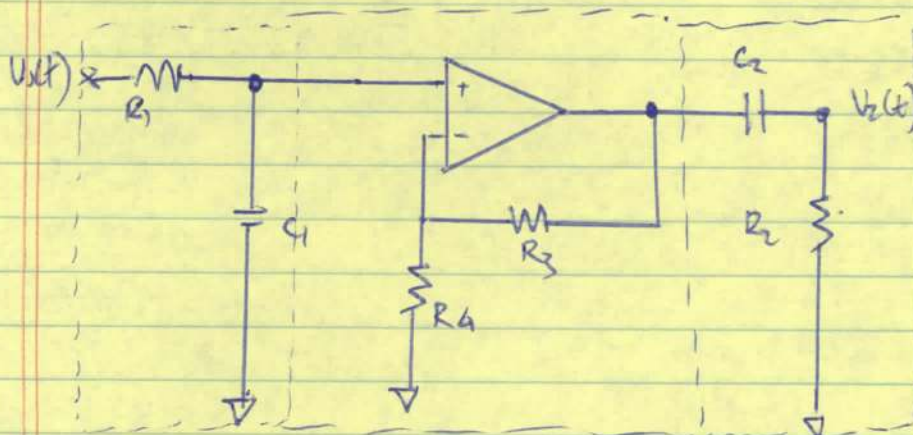

R_1 & C_1 control the cutoff frequency of a ^{low} ~~high~~ pass filter while R_2 & C_2 control the cutoff frequency of a ^{high} ~~low~~ pass filter. The passband gain is controlled by R_3 & R_4 (which we see are arranged in an non inverting amplifier configuration)

We want the ^{low pass} ~~high pass~~ filter to have a cutoff frequency of 40000 rad/s ,
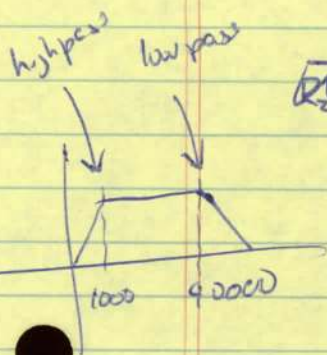
$$\text{so } \frac{1}{R_2 C_2} = 40000, \Rightarrow R_2 = 25 \Omega, C_2 = 1 \text{ nF}$$



$$\frac{1}{R_1 C_1} =$$

$$\frac{1}{R_1 C_1} = 40000, \Rightarrow R_1 = 25 \Omega, C_1 = 1 \text{ nF}$$

$$\frac{1}{R_2 C_2} = 1000, \Rightarrow R_2 = 10 \Omega, C_2 = 0.1 \mu\text{F}$$

$$1 + \frac{R_3}{R_4} = 100, \Rightarrow R_3 = 99 \Omega, R_4 = 1 \Omega$$

Passband gain is $\left(\frac{R_2}{R_1}\right) \cdot \left(\frac{R_4}{R_3}\right) = \underline{R_4 = 10^4 \Omega}$