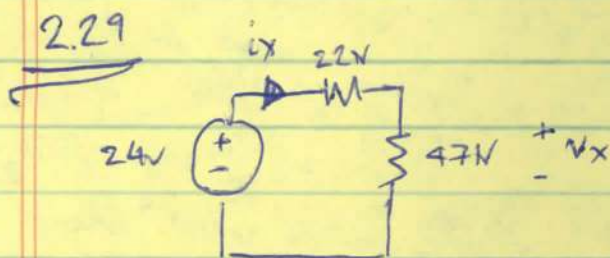


H/W2 solutions

Amit Pandey (1)




We start by finding i_x ,

$$i_x = \frac{24}{22\Omega + 47\Omega} = \underline{\underline{0.348 \text{ mA}}}$$

and now we can easily compute V_x
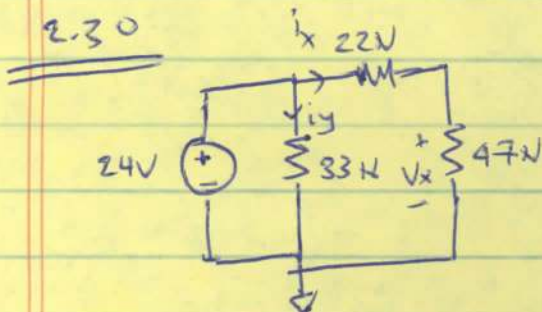
$$\begin{aligned} V_x &= 47\Omega \times i_x \\ &= \underline{\underline{16.348 \text{ V}}} \end{aligned}$$



a We have two circuit elements in parallel with each other where one element is the same circuit as we examined in the question above.

• Therefore, i_x and V_x will be the exactly the same as they were in the previous question


• Compute i_y :

$$i_y = \frac{24}{33\Omega} = \underline{\underline{0.727 \text{ mA}}}$$

(2)

- The power supplied by the circuit will increase. The total power for the second circuit is $(i_x + i_y)24$, while the total power for the first circuit is $i_x(24)$

2.33

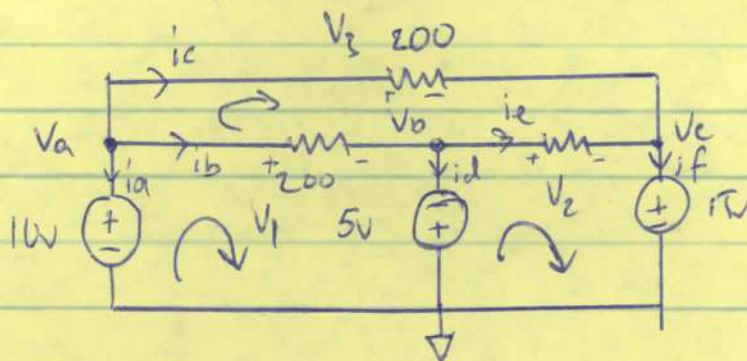

- (a) • Assign three voltages V_a, V_b, V_c as well as assigning ground (0V) as the bottom wire in our circuit diagram

- Assign currents $i_a, i_b, i_c, i_d, i_e, i_f$

- (b) $V_a = 10V$, $V_c = 15V$ } This follows automatically from the selection of ground

Let us now use KVL to find the voltage across each of the resistors

$$10 - V_1 + 5 = 0$$

$$\Rightarrow V_1 = \underline{15 \text{ volts}}$$

$$-5 - V_2 - 15 = 0$$

$$V_2 = \underline{-20 \text{ volts}}$$

$$-V_3 + V_2 + V_1 = 0$$

$$\Rightarrow V_3 = \underline{-5 \text{ volts}}$$

(3)


Now, we can find the currents.

$$i_b = 15/200 \text{ amps}$$

$$i_d = -20/200 \text{ amps}$$

$$i_c = -5/200 \text{ amps}$$

2.41

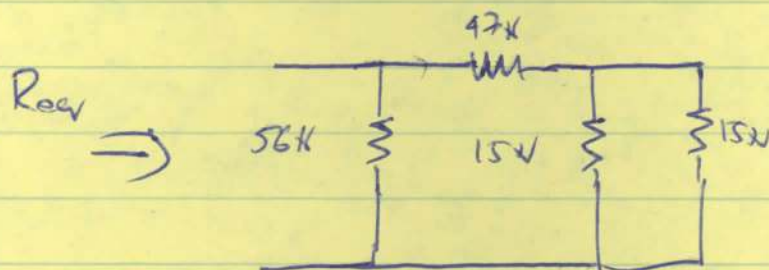


$$R_{eq} = 56k \parallel (47k + 15k \parallel 15k)$$

$$= \underline{\underline{27619.91}}$$


2.47

A-B

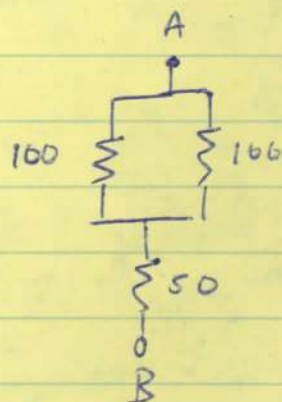


$$R_{eq} = 100$$

A-C

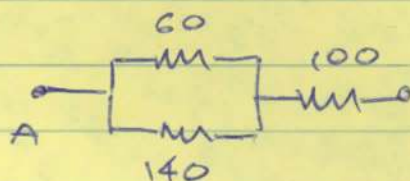


$$R_{eq} = 142$$


(9)

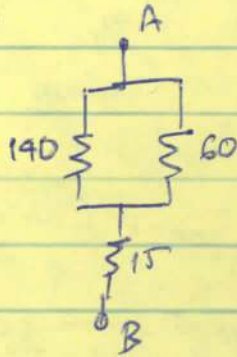A-D


$$R_{eq} = 57.12$$

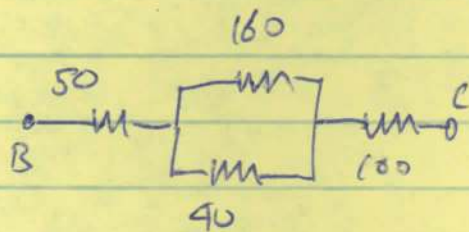B-C

$$R_{eq} = 182$$



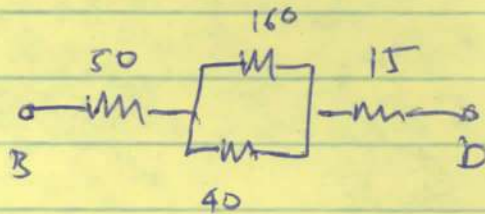
B-D

$$R_{eq} = 97$$

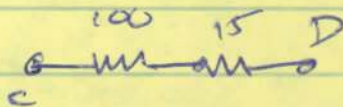
C-D

$$R_{eq} = 115$$

(5)

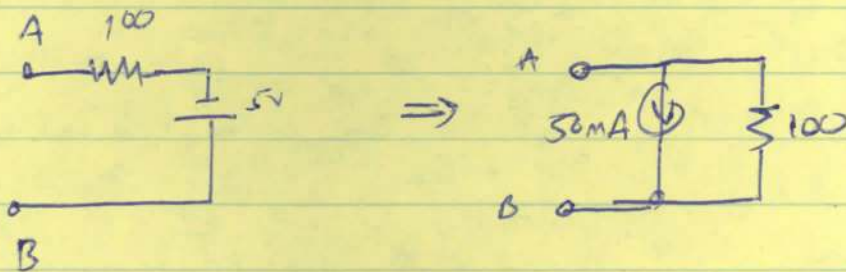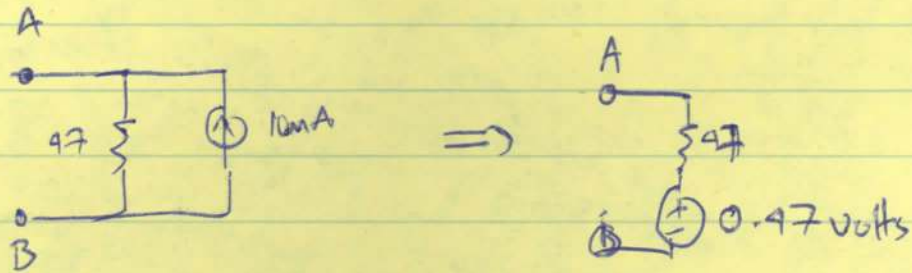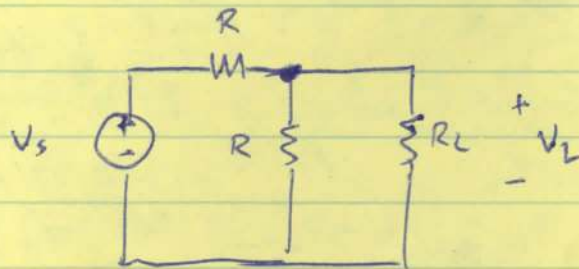2-502-59

This is equivalent to

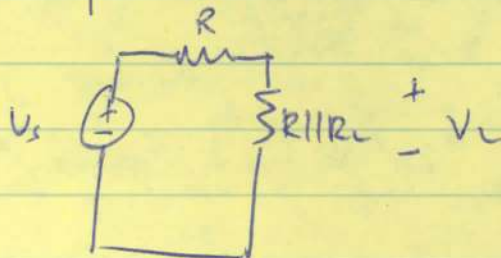

where


$$R \parallel R_L = \frac{R R_L}{R + R_L}$$

then

$$V_L = \left(\frac{V_s}{R + \frac{R R_L}{R + R_L}} \right) \frac{R R_L}{R + R_L}$$

$$= \frac{V_s - R R_L}{R(R + R_L) + R R_L} = \frac{V_s R R_L}{R^2 + 2 R R_L}$$


2-60

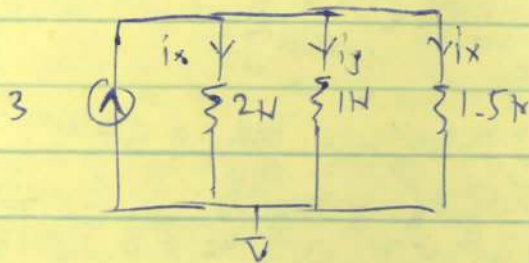

$$i_x = \frac{3 \cdot 600}{2600} = \text{~~0.692~~ } 0.692$$





$$i_y = \frac{3 \cdot (2k \parallel 1.5k)}{1k + (2k \parallel 1.5k)} = 1.387$$
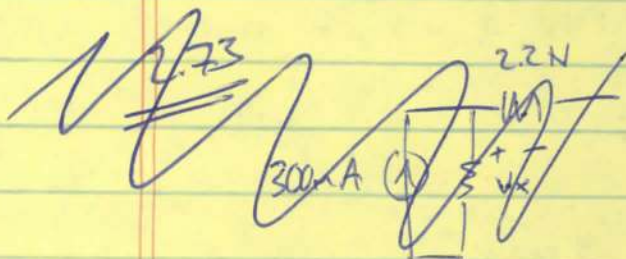
$$i_z = \frac{3 \cdot (2k \parallel 1k)}{(2k \parallel 1k) + 1.5k} = 0.923$$



273

273

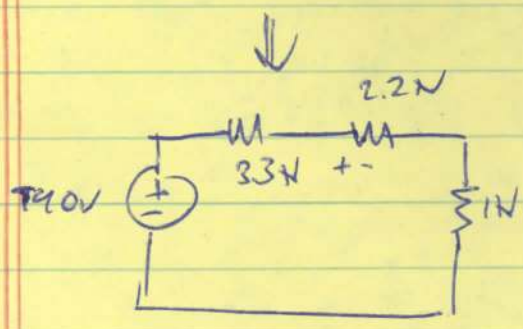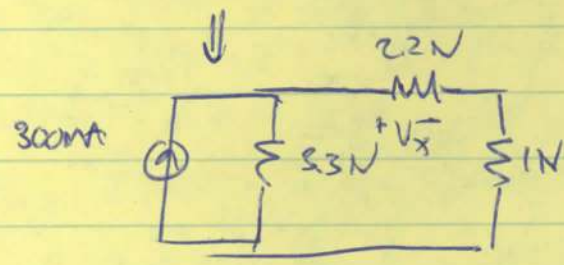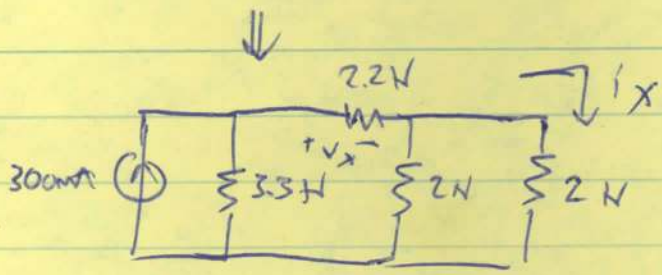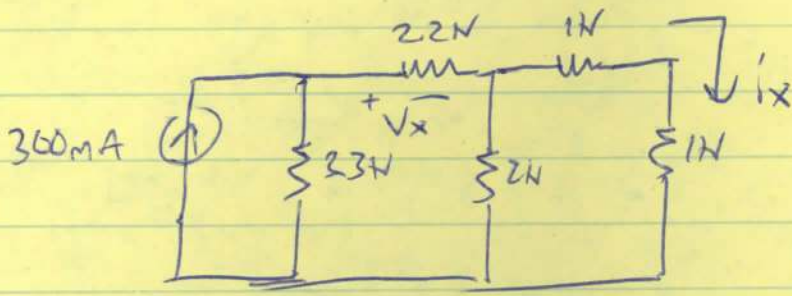

$$V_x = \left(\frac{9.90}{3.3N + 2.2N + 1N} \right) \cancel{2.2N}$$



$$= 1.5231 \text{ volts}$$

$$= 335.1 \text{ volts}$$

$$P_x = \cancel{V_x} \times \cancel{I_x} = (3.3V \times 2.2N + 1N)$$

$$= 150.78W$$

Now, we compute i_x

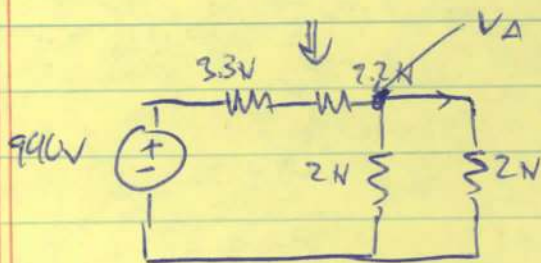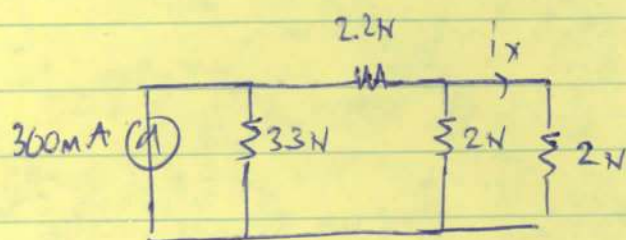


$$\text{so, } I_x = \left(\frac{990}{6.5k} \right) \frac{1k}{2k} = \underline{\underline{76.154 \text{ mA}}}$$

$$\text{where } V_A = \frac{990}{6.5k} \cdot 1k$$


$$\text{and we have } i_x = \frac{V_A}{2k}$$

To compute P_x


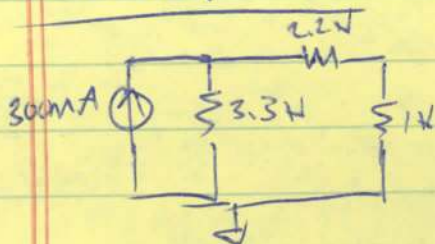


$$\begin{aligned} \text{so } P &= I^2 R \\ &= (300\text{mA})^2 \times (3.3k \parallel 3.2k) \\ &= \underline{\underline{146.2 \text{ W}}} \end{aligned}$$

2.7A

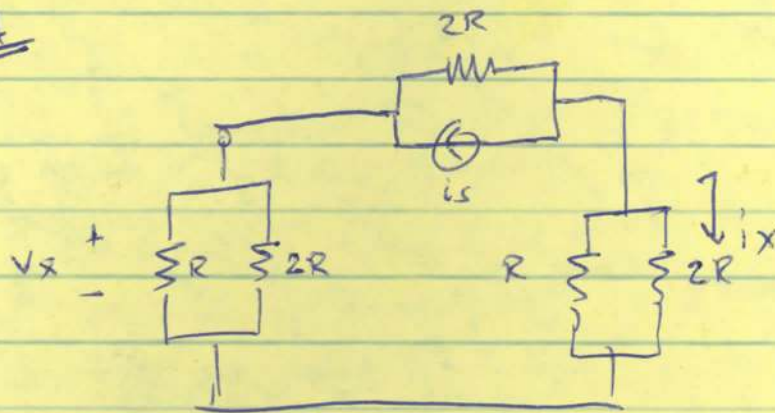

Do a source transformation

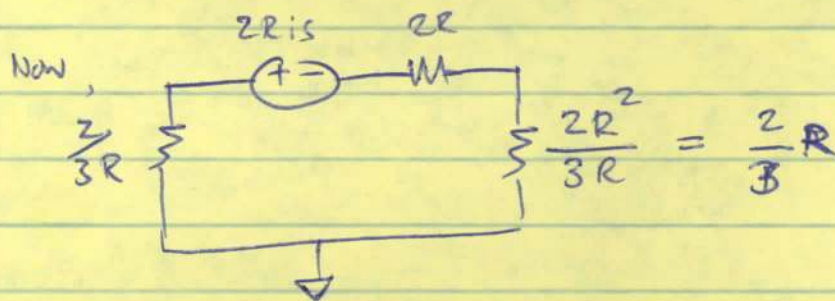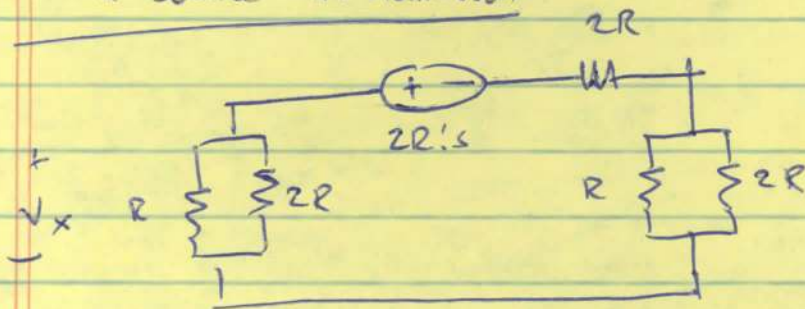

Now, to find V_x , we use a voltage divider

$$V_x = \frac{2Ri_s}{\frac{4R}{3} + 2R} \cdot \frac{2R}{3} = \frac{2Ri_s}{\frac{10R}{3}} \cdot \frac{2R}{3}$$

$$V_x = \frac{4}{10} Ri_s = \frac{2}{5} Ri_s$$

$$I_x = \frac{V_x}{2R} = \underline{\underline{\frac{1}{5} I_s}}$$