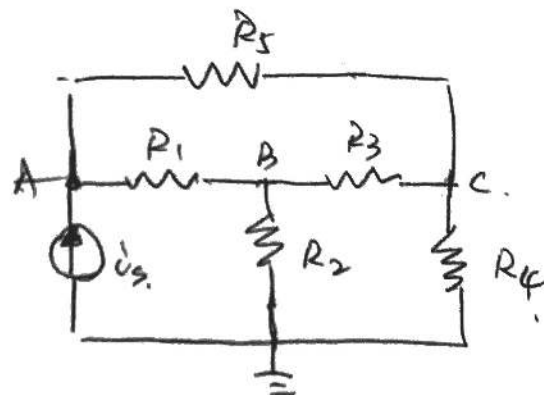


HW #3 Solution

3.1.

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_5} & -\frac{1}{R_1} & -\frac{1}{R_5} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_5} & -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} i_{s1} \\ 0 \\ 0 \end{pmatrix}$$



3.2

$$a) \begin{bmatrix} \frac{1}{5} + \frac{1}{10} + \frac{1}{15} & -\frac{1}{15} \\ -\frac{1}{15} & \frac{1}{5} + \frac{1}{15} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 0 \\ i_s \end{pmatrix} \quad w/ \quad i_s = 3A$$

$$b) \text{ Solve: } \boxed{V_A = 2.1429 V, V_B = 11.7857 V}$$

c) Current flow 5Ω ~~connected~~ (connected to B):

$$i_1 = \frac{V_B}{5\Omega} = 2.3571 A$$

$$i_2 \text{ through } 15\Omega : i_2 = 3A - 2.3571 A = 0.6429 A$$

$$i_3 \text{ through } 10\Omega : i_3 = \frac{V_A}{10\Omega} = 0.2143 A$$

$$i_x = i_2 - i_3 = \boxed{0.4286 A}$$

$$\boxed{V_x = V_B = 11.7857 V}$$

3.5

a.)

$$A: \frac{V_A}{10k\Omega} + \frac{V_A - V_B}{10k\Omega} = 10mA$$

$$B: V_B = 5V$$

$$C: \frac{V_C}{10k\Omega} + \frac{V_C - V_B}{10k\Omega} + 10mA = 0$$

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{10} & 0 \\ 0 & \frac{1}{10} + \frac{1}{10} \end{bmatrix} \begin{pmatrix} V_A \\ V_C \end{pmatrix} = \begin{pmatrix} 10mA + \frac{V_B}{10k\Omega} \\ -10mA + \frac{V_B}{10k\Omega} \end{pmatrix}$$

$$b) V_A = \pm 2.5 V, V_C = -47.5 V$$

$$c) V_x = V_A - V_C = 100 V$$


$$-I_x + \frac{V_A - V_B}{10k\Omega} + \left(-\frac{V_B - V_C}{10k\Omega} \right) = 0$$

$$I_x = 4.75 mA + 5.25 mA$$

$$\boxed{I_x = 10 mA}$$

3.8

a)

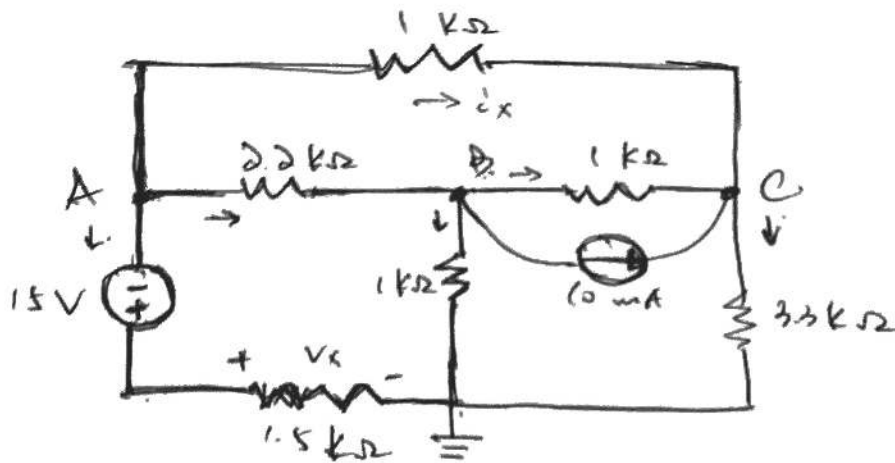

b)

$$A: \frac{V_A - V_B}{2.2k\Omega} + \frac{V_A - V_C}{1k\Omega} + \frac{V_A + 15V}{1.5k\Omega} = 0$$

$$B: \frac{V_B}{1k\Omega} + \frac{V_B - V_A}{2.2k\Omega} + \frac{V_B - V_C}{1k\Omega} + 10mA = 0$$


$$C: \frac{V_C - V_A}{1k\Omega} + \frac{V_C - V_B}{1k\Omega} + \frac{V_C}{33k\Omega} - 10mA = 0$$

$$\begin{bmatrix} \frac{1}{2.2} + \frac{1}{1} + \frac{1}{1.5} & -\frac{1}{2.2} & -\frac{1}{1} \\ -\frac{1}{2.2} & \frac{1}{1} + \frac{1}{2.2} + \frac{1}{1} & -\frac{1}{1} \\ -\frac{1}{1} & -\frac{1}{1} & \frac{1}{1} + \frac{1}{1} + \frac{1}{33} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} -\frac{15V}{1.5k\Omega} \\ -10mA \\ 10mA \end{pmatrix}$$

$$V_x = V_A + 15V = 8.714V$$

$$i_x = \frac{V_A - V_C}{1k\Omega} = -5.482mA$$

3.16

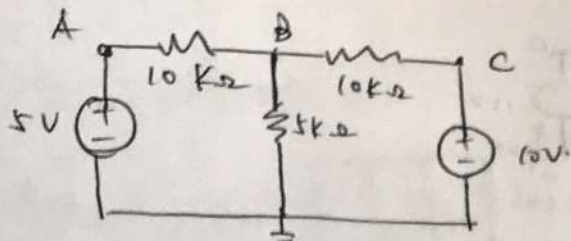

or

A : $V_A = 5V$

C : $V_C = 10V$

B : $\frac{V_A - V_B}{10k\Omega} + \frac{0 - V_B}{5k\Omega} + \frac{V_C - V_B}{10k\Omega} = 0$

$\Rightarrow V_B \left(\frac{1}{10k\Omega} + \frac{1}{5k\Omega} + \frac{1}{10k\Omega} \right) = \frac{V_A}{10k\Omega} + \frac{V_C}{10k\Omega}$


or $\left[\frac{1}{10k\Omega} + \frac{1}{5k\Omega} + \frac{1}{10k\Omega} \right] (V_B) = \left(\frac{V_A}{10k\Omega} + \frac{V_C}{10k\Omega} \right)$

3.17

A : $V_A = V_S$

B : $\frac{V_B - V_A}{R_A} + \frac{V_B}{R_B} + \frac{V_B - V_C}{R_C} = 0$

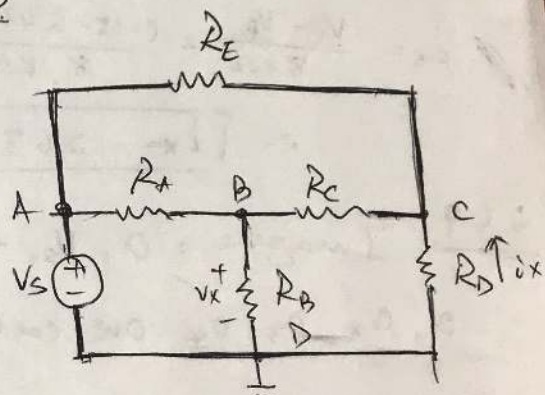C : $\frac{V_C - V_B}{R_C} + \frac{V_C}{R_D} + \frac{V_C - V_A}{R_E} = 0$




$$\begin{bmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{bmatrix} \begin{pmatrix} V_B \\ V_C \end{pmatrix} = \begin{pmatrix} V_A/R_A \\ V_A/R_E \end{pmatrix}$$

$V_X = V_B$

$i_X = \frac{0 - V_C}{R_D}$

3.23

b)

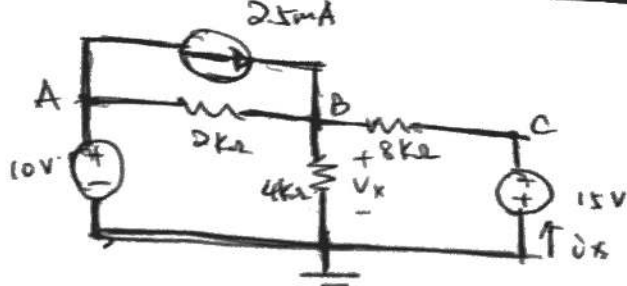

$$A: V_A = 10V$$

$$C: V_C = -15V$$

$$B: \frac{V_B - V_A}{2k\Omega} + \frac{V_B - 0}{4k\Omega} + \frac{V_B - V_C}{8k\Omega} - 2.5mA = 0$$

rewrite B:

$$\left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{8k\Omega}\right)(V_B) = (2.5mA + \frac{10V}{2k\Omega} + \frac{-15V}{8k\Omega})$$

d)

$$\text{Solve for } V_B: V_B = \frac{45}{7} V = 6.43 V$$

$$V_B = \boxed{V_x = 6.43 V}$$

$$i_x = \frac{V_C - V_B}{8k\Omega} = \frac{(-15 - 6.43)V}{8k\Omega} \approx -2.68 A$$

$$\therefore \boxed{i_x = -2.68 A}$$

3.49 Imagine: $a_1 V_{s1} + a_2 V_{s2} + a_3 V_{s3} + a_4 V_{s4} = V_o$


a_1, a_2, a_3, a_4 are coefficients for input voltage.

$$\begin{pmatrix} 2 & 4 & -4 & 1 \\ 1 & 2 & 2 & 1.5 \\ 1 & 4 & 2 & 2 \\ 0 & 5 & 3 & -1 \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{pmatrix} = \begin{pmatrix} 20 \\ -4 \\ -1 \\ 3 \end{pmatrix} \Rightarrow \begin{cases} a_1 = 1 \\ a_2 = 2 \\ a_3 = -3 \\ a_4 = -2 \end{cases}$$

$$\therefore \boxed{V_o = V_{s1} + 2V_{s2} - 3V_{s3} - 2V_{s4}}$$

3.50

Source transformation:

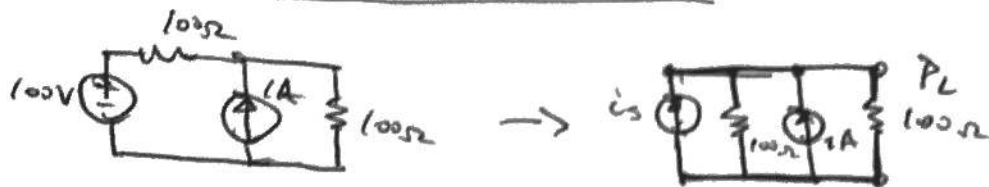

$$i_s = \frac{100V}{100\Omega} = 1A$$

↓ 2 current sources in parallel

$$i_x = \frac{1}{2} \cdot 2A = 1A$$




$$P_L = i_x^2 \cdot R_L = 100W$$

or Nodal Analysis:

A:

$$V_A = 100V$$

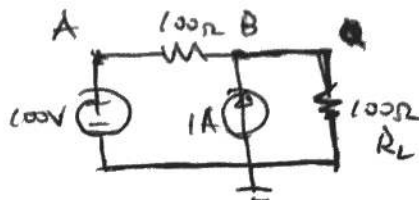



$$\underline{B}: \frac{V_B - V_A}{100\Omega} + \frac{V_B}{100\Omega} - 1A = 0$$

$$\Rightarrow \left(\frac{1}{100\Omega} + \frac{1}{100\Omega} \right) (V_B) = \left(\frac{V_A}{100\Omega} + 1A \right)$$

$$V_B = 100V$$

$$P_L = \frac{V_B^2}{R_L} = \frac{(100V)^2}{100\Omega} = 100W$$

3.52

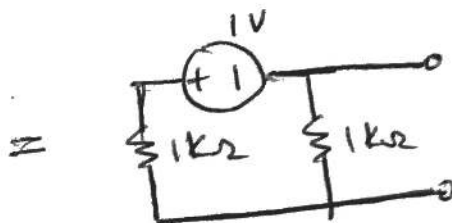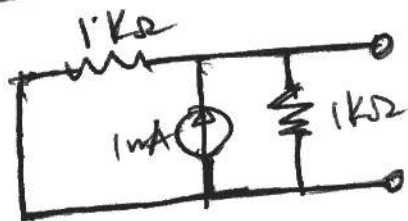


$$R_T = 1k\Omega \parallel 1k\Omega$$

$$R_T = 0.5k\Omega$$

$$V_T = \frac{1k\Omega}{1k\Omega + 1k\Omega} \cdot 1V = 0.5V$$

$$I_N = \frac{V_T}{R_T} = 1mA$$


3.5]

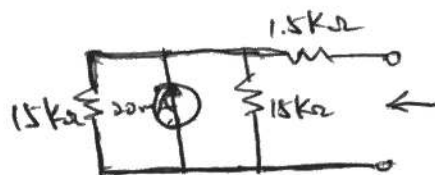

$$R_N = R_T = 15k\Omega \parallel 15k\Omega + 1.5k\Omega$$

$$R_N = 9k\Omega$$

Source transform:

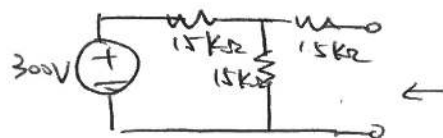


$$V_T = \frac{15k\Omega}{15k\Omega + 15k\Omega} \cdot 300V$$

$$V_T = 150V$$

$$i_N = \frac{V_T}{R_T} = 16.67mA \Rightarrow$$

Norton equivalent:

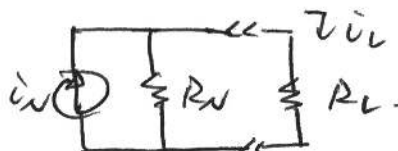

$$i_L = \frac{G_L}{G_N + G_L} i_N = \frac{i_N}{1 + \frac{R_L}{R_N}}$$

when $R_L =$

$4.7k\Omega$	$i_L = 10.95mA$
$15k\Omega$	$i_L = 6.25mA$
$48k\Omega$	$i_L = 1.95mA$