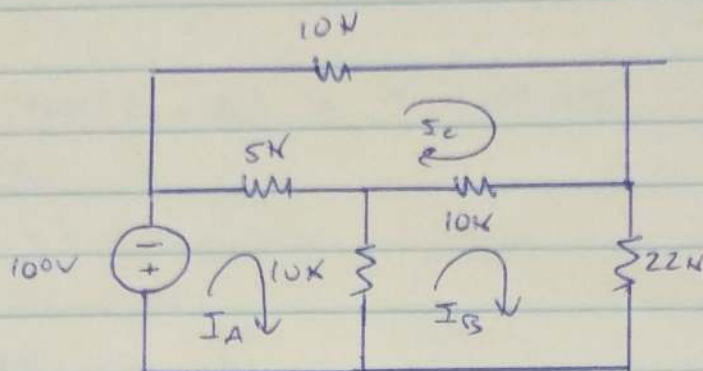


(1)

HW4 solutions

3.14

We start by formulating the mesh currents in the circuit

 I_A

$$100 - 5k(I_A - I_C) - 10k(I_A - I_B) = 0$$

$$\underline{I_B} \quad -10k(I_B - I_C) - 22k I_B - 10k(I_B - I_A) = 0$$

$$\underline{I_C} \quad -10k I_C - 10k(I_C - I_B) - 5k(I_C - I_A) = 0$$

With these three equations, we can formulate a matrix

$$\begin{bmatrix} 15k & -10k & -5k \\ -10k & 42k & -10k \\ -5k & -10k & 25k \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} -100 \\ 0 \\ 0 \end{bmatrix}$$

Using Matlab to solve, we get

$$\begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} -9.7938 \\ -3.0928 \\ -3.1951 \end{bmatrix} \text{ mA}$$


(2)

Now, we can solve for V_x and i_x .

$$V_x = -10k(I_B - I_C) = -1.0369 \text{ volts.}$$

$$i_x = i_c.$$

3.18

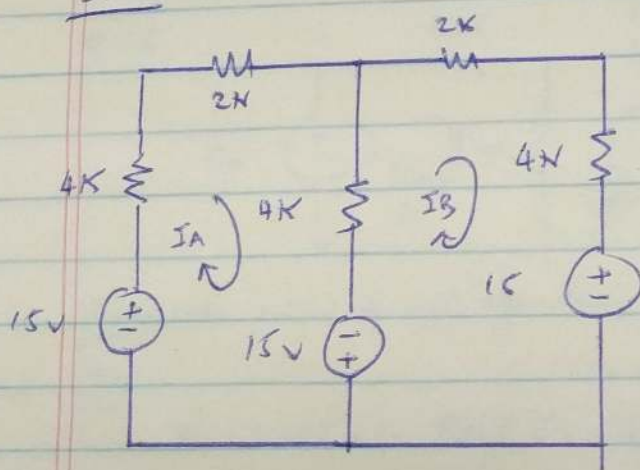

Formulate mesh current equations

I_A

$$15 - 4kI_A - 2kI_A - 4k(I_A - I_B) + 15 = 0$$

I_B

$$-2kI_B - 4kI_B - 15 - 15 - 4k(I_B - I_A) = 0$$

From which we can formulate our matrix equation

$$\begin{bmatrix} 10k & -4k \\ -4k & 10k \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 30 \\ -30 \end{bmatrix}$$

using MATLAB, we get

$$\begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 2.1429 \\ -2.1429 \end{bmatrix} \text{ mA}$$


(3)

$$V_x = 4N \times I_B$$

$$= -8.5714 \text{ Volts}$$

$$I_x = I_B - I_A$$

$$= -4.2857 \text{ mA}$$

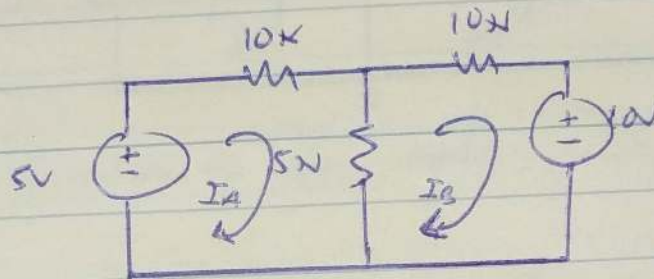3.16

Formulate mesh current equations

 I_A

$$5 - 10N I_A - 5N (I_A - I_B) = 0$$

 I_B

$$-10 - 10N I_B - 5N (I_B - I_A) = 0$$


From here we can formulate our matrix equation

$$\begin{bmatrix} 15N & -5N \\ -5N & 15N \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 5 \\ -10 \end{bmatrix}$$

$$\begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 0.1250 \\ -0.1250 \end{bmatrix} \text{ mA}$$

$$V_x = 10N \cdot I_A = 1.25 \text{ Volts}$$

$$I_x = I_A - I_B = \underline{\underline{0.75 \text{ mA}}}$$

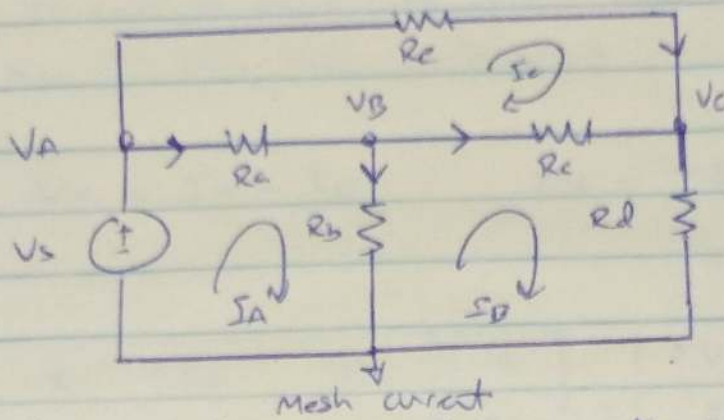3.17

let us formulate the ~~node voltage~~ equations

IA

$$V_s - R_a(I_a - I_c) - R_b(I_a - I_b) = 0$$

IB

$$-R_b(I_b - I_a) - R_c(I_b - I_c) - R_d I_b = 0$$

IC

$$-I_c R_e - R_c(I_c - I_b) - R_a(I_c - I_a) = 0$$

Now let's formulate the node-voltage equations.

$$V_D = 0$$

$$V_A = V_s$$

Equation at B

$$\frac{V_s - V_B}{R_a} = \frac{V_B}{R_b}$$

Equation at C

$$\frac{V_A - V_C}{R_e} + \frac{V_B - V_C}{R_c} = \frac{V_C}{R_d}$$

(5)


(c) It will be easier to solve node-voltage equations as there are only two unknowns

$$(d) \quad V_x = I_A - I_B, \quad I_x = -I_B$$

where:

$$\begin{bmatrix} R_a + R_b & -R_b & -R_a \\ -R_b & R_b + R_c + R_d & -R_c \\ -R_a & -R_c & R_a + R_c + R_e \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} +V_S \\ 0 \\ 0 \end{bmatrix}$$

(6)

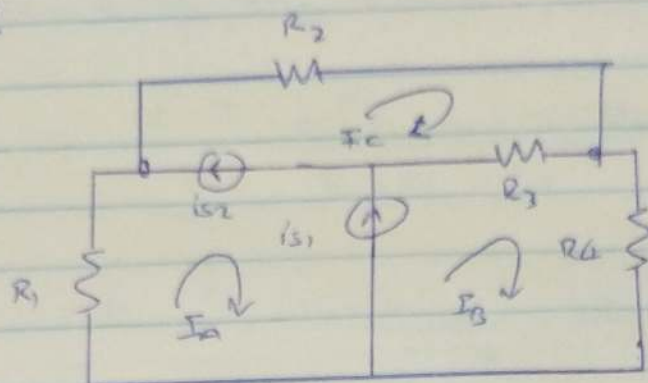3.19

we have the following super-mesh current relationships:

$$I_B - I_A = i_{s1}$$

$$I_C - I_A = i_{s2}$$

and we can now formulate a super mesh by removing these current sources and formulating the mesh equation

$$R_1 I_A + R_2 I_C + R_4 I_B = 0$$

now, let's write expressions for I_A , I_B & I_C .

(I_A)

$$R_1 I_A + R_2 (i_{s2} + I_A) + R_4 (i_{s1} + I_A) = 0$$

$$I_A (R_1 + R_2 + R_4) = -R_4 i_{s1} - R_2 i_{s2}$$

$$I_A = \frac{-i_{s1} R_4 - R_2 i_{s2}}{R_1 + R_2 + R_4}$$

(7)

In a similar way, we have

$$i_B = \frac{i_{s1}(R_1 + R_2) - i_{s2}R_2}{R_1 + R_2 + R_4}$$


$$i_C = \frac{-i_{s1}R_4 + i_{s2}(R_1 + R_4)}{R_1 + R_2 + R_4}$$

and we have

$$V_x = -i_B R_4$$

$$= \left(\frac{i_{s1}(R_1 + R_2) - i_{s2}R_2}{R_1 + R_2 + R_4} \right) R_4$$

8.22

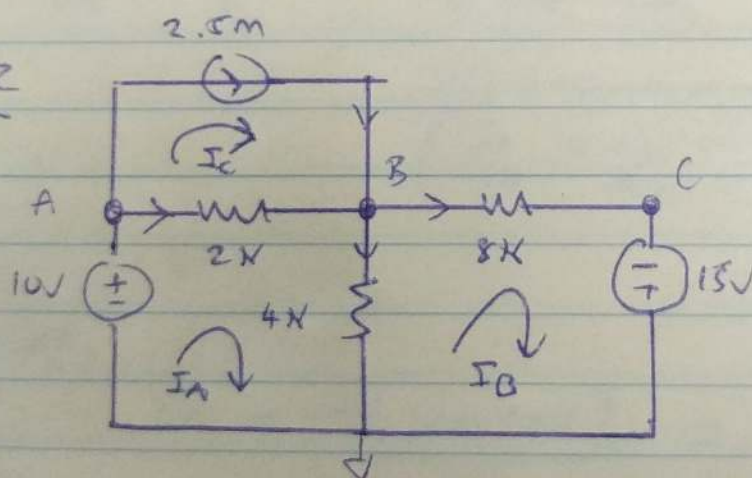

$$I_C = 2.5 \text{ mA}$$

$$10 - 2k(I_A - I_C) - 4k(I_A - I_B) = 0$$

$$-4k(I_B - I_A) - 8kI_B + 15 = 0$$

} mesh current equations

(c) If we had used the node voltage equations, we would only have a single unknown, vs 2 unknowns for mesh currents

8

If we formulate node-voltage equations we have,

$$V_A = 10V \quad V_D = 0$$

$$V_C = -15V,$$

and

$$\frac{V_A - V_B}{2K} + 2.5m = \frac{V_B}{4K} + \frac{V_B - V_C}{8K}$$

so,

$$V_B \left(\frac{1}{4K} + \frac{1}{8K} + \frac{1}{2K} \right) = 2.5m + \frac{10}{2K} - \frac{15}{8K}$$

$$V_B = \frac{2.5m + \frac{10}{2K} - \frac{15}{8K}}{\left(\frac{1}{4K} + \frac{1}{8K} + \frac{1}{2K} \right)} = \underline{\underline{6.429V}}$$


so that

$$i_x = \frac{-(V_B + 15)}{8K} = \underline{\underline{-2.679mA}}$$

$$V_x = V_D =$$

(9)

3.26

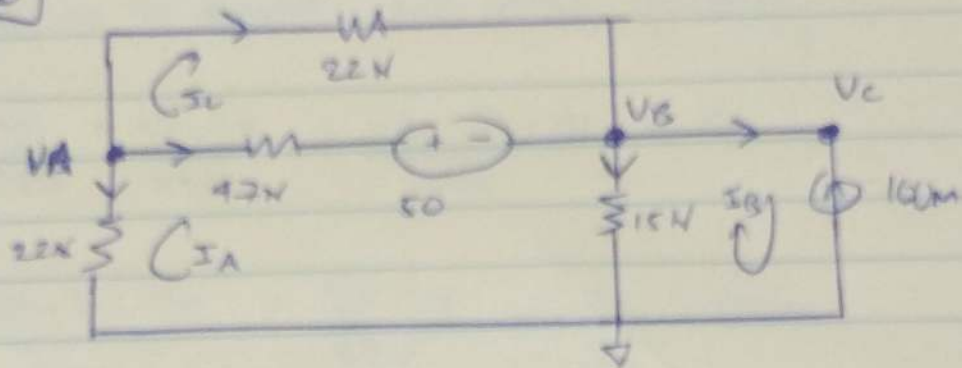

$$(a) -22k I_A - 47k(I_A - I_C) - 50 - 15k(I_A - I_B) = 0$$

$$I_B = -100mA$$

$$-22k I_C + 50 - 47k(I_C - I_A) = 0$$

$$\begin{bmatrix} 22k + 47k + 15k & -47k \\ -47k & 22k + 47k \end{bmatrix} \begin{bmatrix} I_A \\ I_C \end{bmatrix} = \begin{bmatrix} -50 \\ 50 \end{bmatrix}$$

$$\begin{bmatrix} I_A \\ I_C \end{bmatrix} = \begin{bmatrix} -29.2 \\ -19.1 \end{bmatrix} mA$$

(10)

Now we can formulate node-voltage equations

$$\frac{V_A}{22k} + \frac{V_A - V_B}{22k} + \frac{V_A - 50 - V_B}{47k} = 0$$



$$\frac{V_A - 50 - V_B}{47k} + \frac{V_A - V_B}{22k} = \frac{V_B}{15k} - 100m$$

$$\begin{bmatrix} \frac{1}{22k} + \frac{1}{47k} + \frac{1}{22k} & -\frac{1}{47k} - \frac{1}{22k} \\ -\frac{1}{22k} - \frac{1}{47k} & \frac{1}{22k} + \frac{1}{15k} + \frac{1}{47k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 50/47k \\ -50/47k + 100m \end{bmatrix}$$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 641.5 \\ 1062.6 \end{bmatrix} \text{ Volts}$$

(11)


3.98

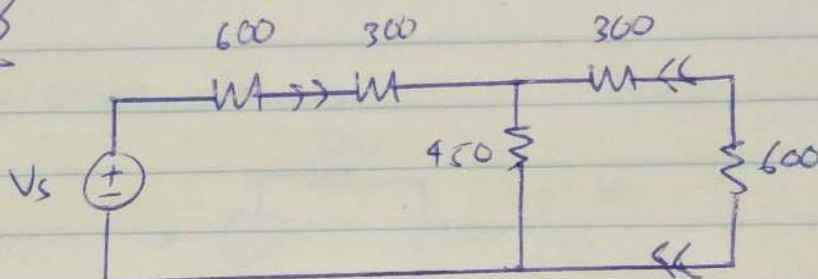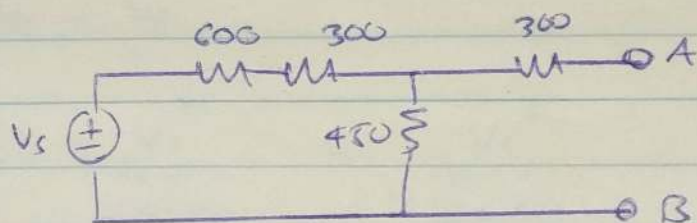Find Thevenin circuit without ~~attaching~~ load

$$R_{th} = 300 + 900 \parallel 450 = 600$$

$$V_{th} = \frac{V_s - 450}{1350} = \frac{V_s}{3}$$

Now:

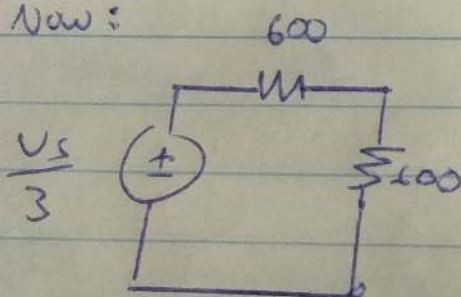


after we add load back.

$$V_L = \frac{V_s}{6},$$

$$P_L = \frac{V^2}{R} = \frac{V_s^2}{36 \times 600} = \frac{V_s^2}{21600}$$

(12)

Now, remove attenuator

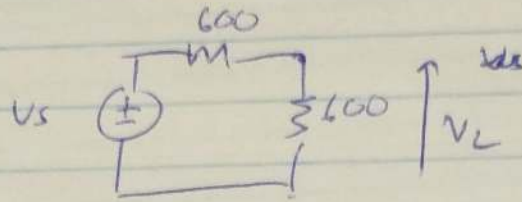

$$\text{so } V_L = \frac{V_s}{2}$$

$$P_L = \frac{V_s^2}{4 \times 600} = \frac{V_s^2}{2400}$$

This is the power gain if we remove attenuator from circuit.

$$\frac{P_{L, \text{noatten}}}{P_{L, \text{atten}}} = \frac{V_s^2}{2400} \times \frac{21600}{V_s^2} = \underline{\underline{9}}$$


$$20 \log_{10}(9) = \underline{\underline{19.0849 \text{ dB}}}$$

(or can compute $\frac{P_{L, \text{atten}}}{P_{L, \text{noatten}}}$)


(13)

3/10

Two possible solutions are shown here. For full points, students need two solutions with the corresponding weight of each one.

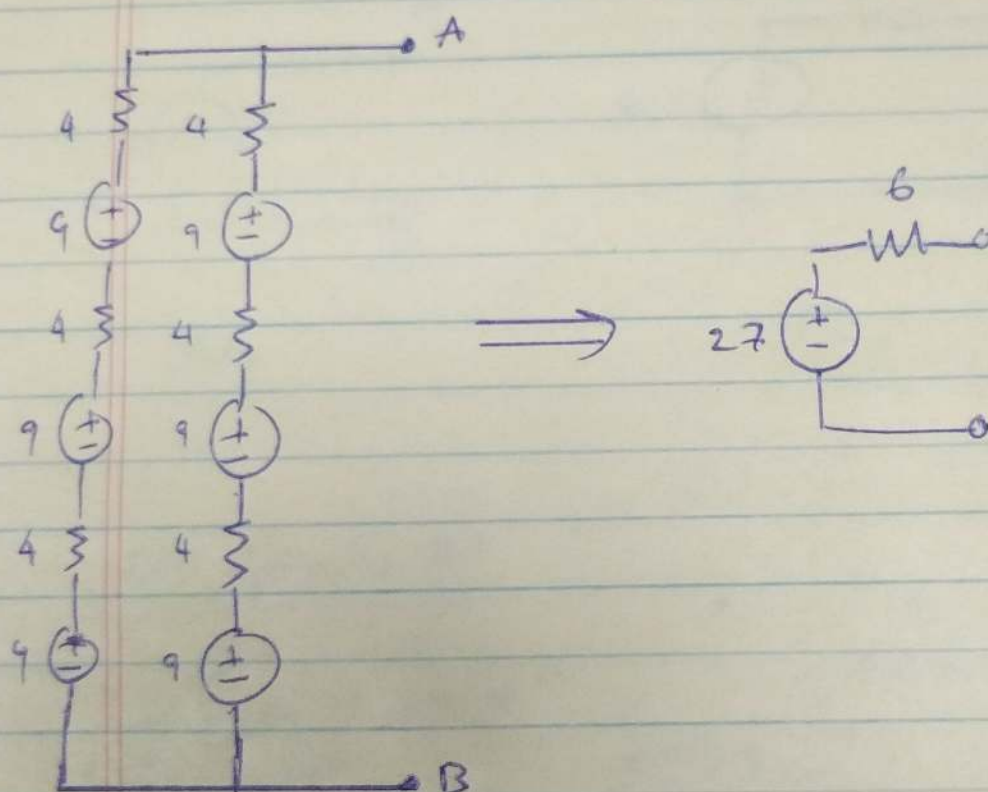Alternative # 1

So we have the following arrangement

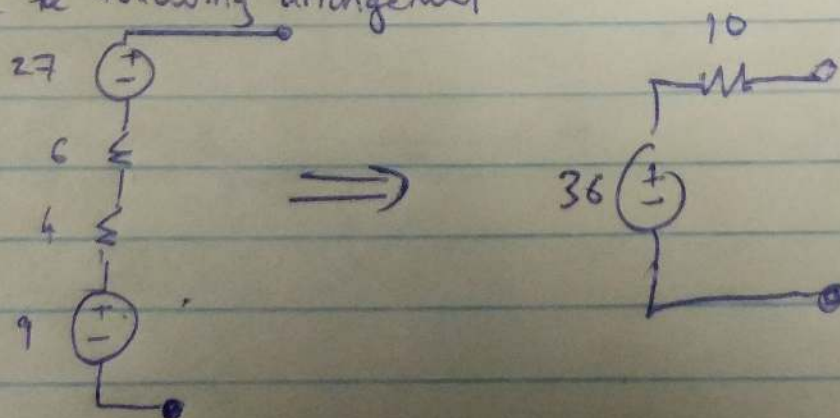


which has a weight of $(30 \times 6) + 30 = \underline{\underline{210g}}$


(14)

3-10³

Team A

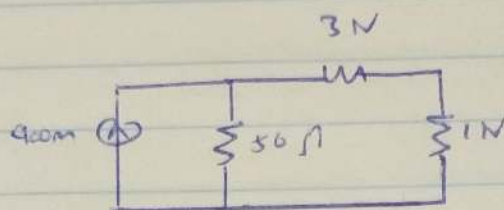


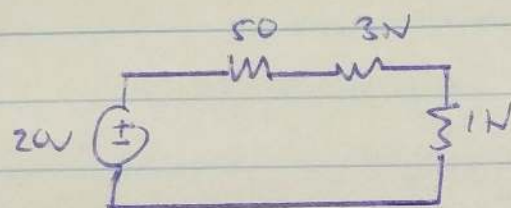To find P_L , let's do a source transformation



$$P_L = 24.3865 \text{ mW}$$

Team B

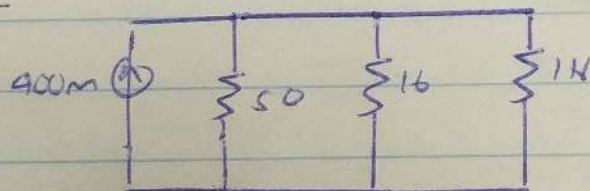

$$P_L = 22.9481 \text{ mW}$$

So for 10% tolerance, both circuits are acceptable but only team A's solution is feasible for 5% tolerance

- Number of parts is same for both designs.
- If we consider E12 resistance values, the 3N resistor can either be 2.7N (which gives $P_L = 28.4 \text{ mW}$) or 3.3N (which gives $P_L = 21.14 \text{ mW}$)
- 16 ohm resistor can be 15 ohm ($P_L = 20.8 \text{ mW}$) or 18 ohm ($P_L = 27.30 \text{ mW}$)