


MAE 140: Linear Circuits – Winter 2013

Circuit Demonstration #3



Audio Mixer



What is an audio mixer?

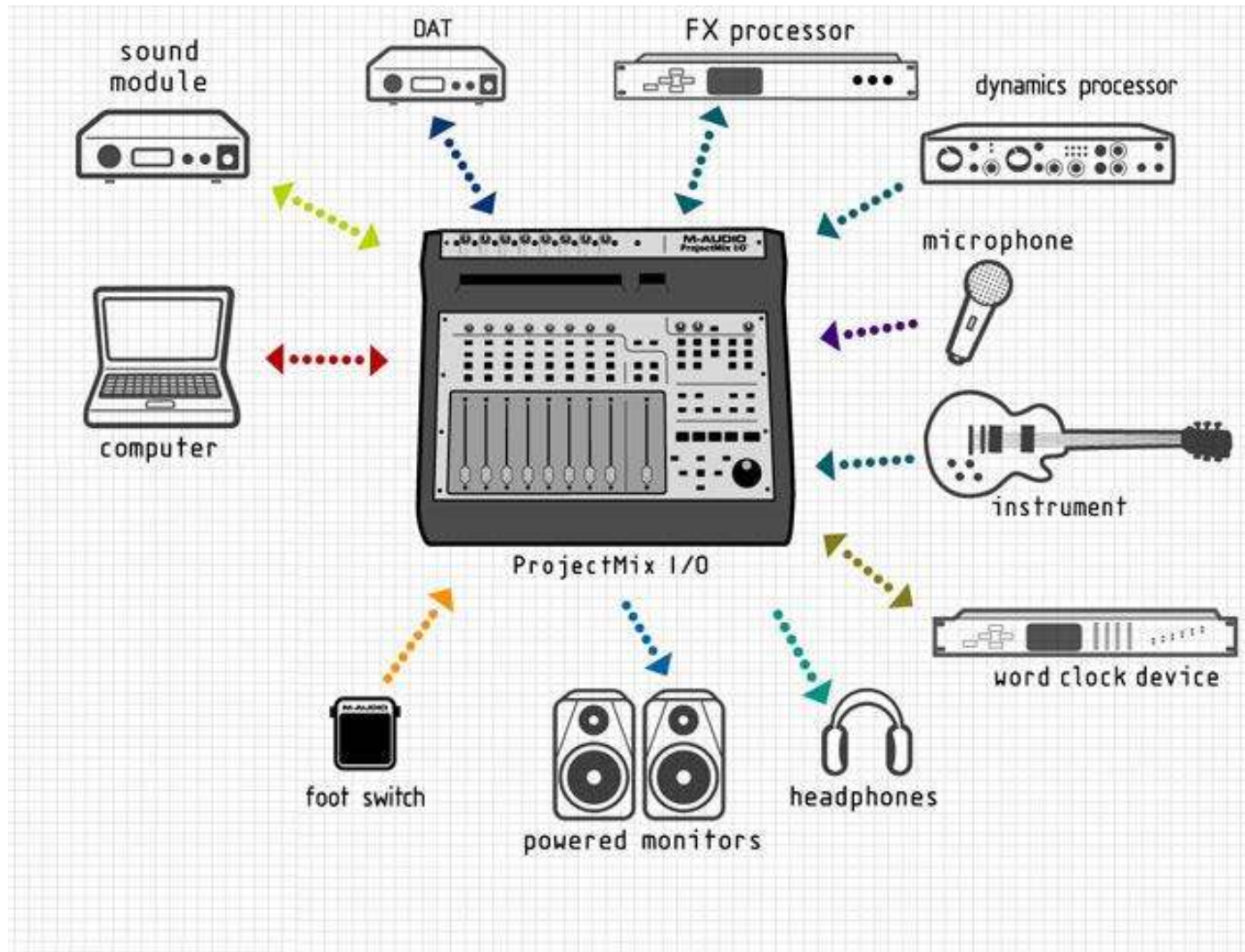

2-channel audio mixer using LM324

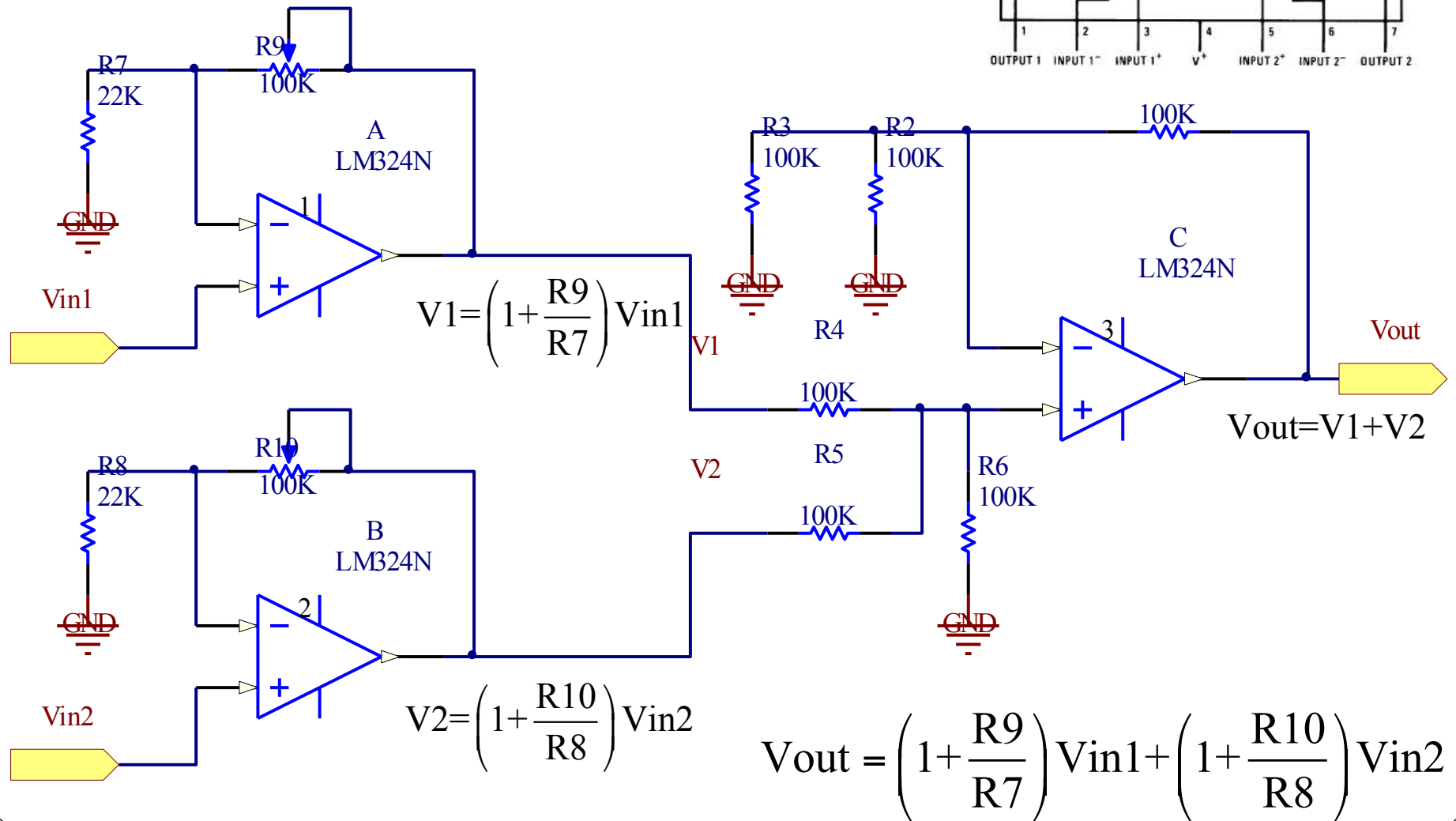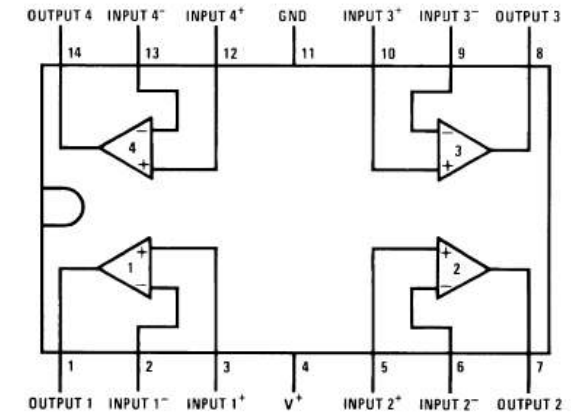

Experiment Setup

