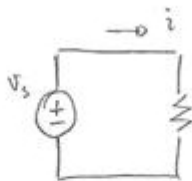


1-13

$$V_s = 12V$$

$$P = 200W$$



(a)

$$P = IV$$


$$200 = i \cdot 12$$

$$i = 16\frac{2}{3}A$$

(b)

$$\left(\frac{200}{12}A\right)^{-1} \times 100Ah = \boxed{6 \text{ hours}}$$

1-21

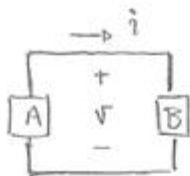

(a) $v = +33V, i = -2.2A$

B transfers power to A

$B \rightarrow A$

$$P = iv = 72.6W$$

(b) $v = -12V, i = -1.2mA$

$A \rightarrow B$

$$P = 14.4mW$$

(c) $v = 37.5V, i = 40mA$

$A \rightarrow B$

$$P = 1.5W$$

(d) $v = -15V, i = -43mA$

$A \rightarrow B$

$$P = 645mW$$

2-5



$$0.01 = \frac{50}{R_x}$$


$$R_x = 5000 \Omega$$

$$P = IV$$

$$= 0.01 \cdot 50 = 0.5 \text{ W}$$

$$P = 0.5 \text{ W}$$

2-10

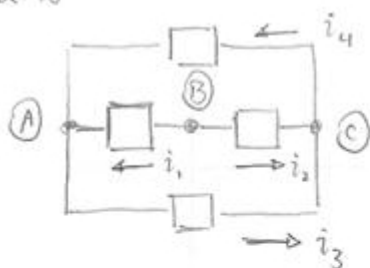

$$i_2 = 2 \text{ A}$$

$$i_3 = -5 \text{ A}$$

KCL @ C

$$i_2 + i_3 - i_4 = 0$$

$$2 - 5 - i_4 = 0$$

$$i_4 = -3 \text{ A}$$


KCL @ A

$$i_1 + i_4 - i_3 = 0$$

$$i_1 - 3 + 5 = 0$$

$$i_1 = -2 \text{ A}$$

2-13 (a)

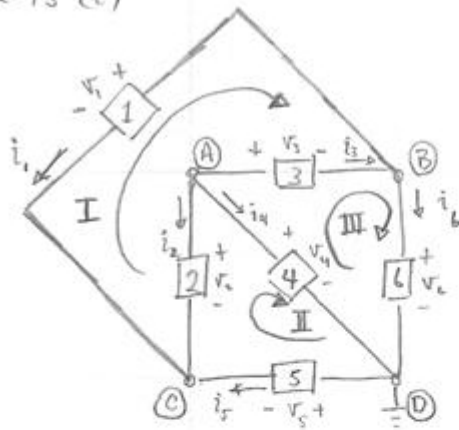

Nodes are A, B, C, D

Loops are I, II, III

(b) No single element is connected in series or parallel w/ another single element

(c)

KCL

$$A: -i_2 - i_3 - i_4 = 0$$

$$B: -i_1 + i_3 - i_6 = 0$$

$$C: i_1 + i_2 + i_5 = 0$$

$$D: i_4 - i_5 + i_6 = 0$$


KVL

$$I: v_1 + v_3 - v_2 = 0$$

$$II: v_2 - v_4 - v_5 = 0$$

$$III: -v_3 - v_6 + v_4 = 0$$

2-28

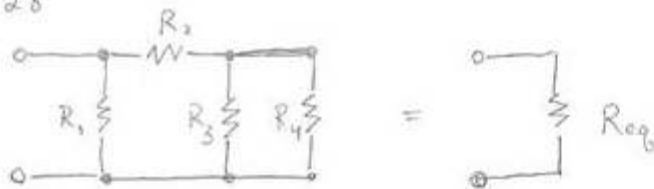

$$R_1 = 160 \Omega$$

$$R_2 = 30 \Omega$$

$$R_3 = 15 \Omega$$

$$R_4 = 30 \Omega$$


$$R_1 \parallel (R_2 \oplus (R_3 \parallel R_4))$$

$$R_{3,4} = \frac{R_3 R_4}{R_3 + R_4} = \frac{15 \cdot 30}{15 + 30} = 10 \Omega$$

$$R_{2,3,4} = R_2 + R_{3,4} = 30 + 10 = 40 \Omega$$

$$R_{eq} = \frac{R_1 R_{2,3,4}}{R_1 + R_{2,3,4}} = \frac{160 \cdot 40}{160 + 40} = 32 \Omega$$

2-40

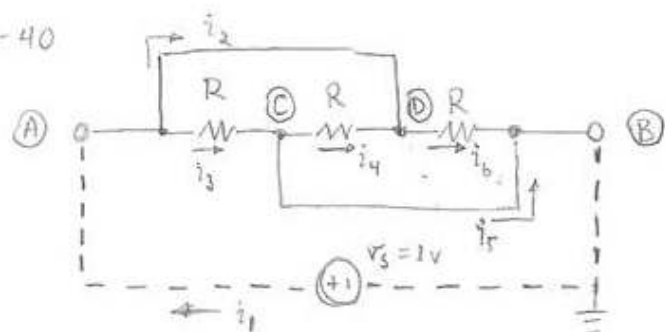

* Nodes A & D are shorted

⇒ they are the same node!

⇒ $\phi_A = \phi_D = v_s = 1V$

* Notation: ϕ_A = voltage measured @ node A relative to ground

* Likewise $\phi_C = \phi_B = 0V$

KCL @ A

$$i_1 - i_3 + i_4 - i_6 = 0 \quad (1)$$

By Ohm's Law:

$$i_1 = \frac{v_s - 0}{R_{eq}} = \frac{1}{R_{eq}} \quad (2)$$

$$i_3 = \frac{v_s - \phi_C}{R} = \frac{1}{R} \quad (3)$$

2-40 cont


$$i_4 = \frac{\phi_C - \phi_D}{R} = \frac{0 - 1}{R} = -\frac{1}{R} \quad (4)$$

$$i_6 = \frac{\phi_D - 0}{R} = \frac{1}{R} \quad (5)$$

Subst. 2, 3, 4, 5 → (1)

$$\frac{1}{R_{eq}} - \frac{1}{R} + \left(-\frac{1}{R}\right) - \frac{1}{R} = 0$$
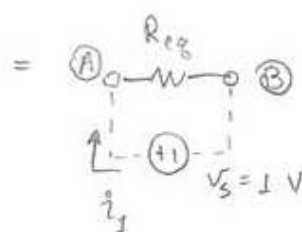
$$\therefore \boxed{R_{eq} = \frac{R}{3}}$$



Equivalent circuit

Notes: An equivalent resistance will draw the same current from any voltage source, so i_1 in the eq. ckt is equal to i_1 in the original. This is a fail-safe method for determining eq. resistance in a purely resistive array. (For ease of computation, I chose a source voltage of 1V)

Always pay attention to short circuits. Doing so will save you much grief both in this class and in the real(ish) world.

The ground node will produce your dependent equation if you correctly set-up the problem.