

1.14) Incandescent lamp $100 \text{ W} \times 1000 \text{ h} = 100 \text{ kWh}$
 Fluorescent lamp $12 \text{ W} \times 1000 \text{ h} = 12 \text{ kWh}$

$$100 - 12 = 88 \text{ kWh (less energy)}$$

$$88 \text{ kWh} \times 7.2 \text{ cents/kWh} = \boxed{633.6 \text{ cents cheaper}}$$

1.22)

Device 1 $\Rightarrow P = i \cdot v = 15 \cdot (-1) = \boxed{-15 \text{ W (delivering)}}$

Device 2 $\Rightarrow P = 5 \cdot 1 = \boxed{5 \text{ W (absorbing)}}$

Device 3 $\Rightarrow P = 10 \cdot 2 = \boxed{20 \text{ W (absorbing)}}$

Device 4 $\Rightarrow P = (-10)(-1) = \boxed{10 \text{ W (absorbing)}}$

Device 5 $\Rightarrow P = 20(-3) = \boxed{-60 \text{ W (delivering)}}$

Device 6 $\Rightarrow P = 20 \cdot 2 = \boxed{40 \text{ W (absorbing)}}$


Power balance

$$\boxed{-15 - 60 + 5 + 20 + 10 + 40 = 0 \quad \checkmark}$$

$$2.5) \quad V = IR, \Rightarrow R = \frac{V}{I} = \frac{100V}{0.01A} = \boxed{10k\Omega}$$

$$P = VI = 100 \times 0.01 = \boxed{1W}$$

2.15) a) and d)

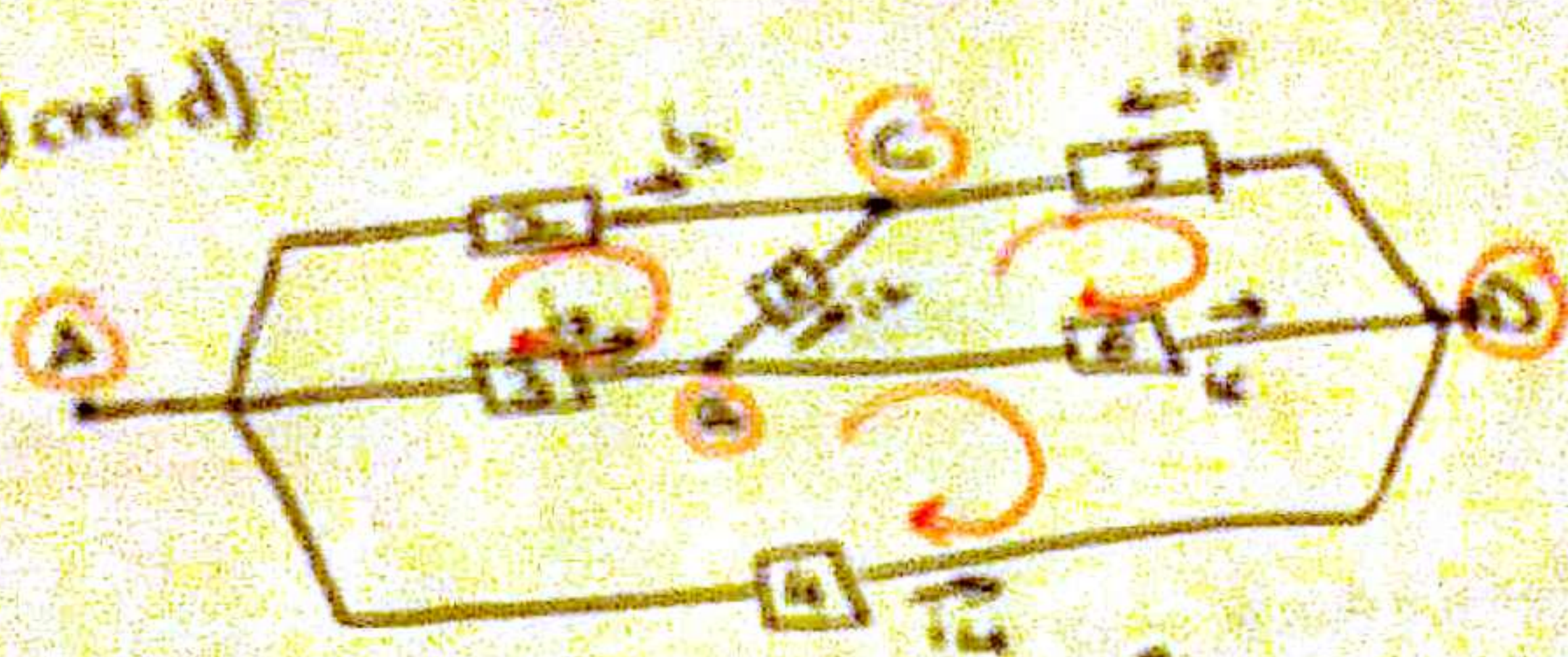

This is same as Figure 2.13

$$\begin{aligned} \text{Node A: } -i_2 - i_3 - i_4 &= 0 & \text{Node C: } i_2 + i_5 + i_1 &= 0 \\ \text{Node B: } i_3 - i_1 - i_6 &= 0 & \text{Node D: } -i_5 + i_6 + i_4 &= 0 \end{aligned}$$

$$c) \quad i_1 = -20mA, i_2 = -12mA, i_3 = 50mA$$

Using Node A

$$i_4 = -i_2 + i_3 = +12mA + 50mA = \boxed{62mA}$$

Using Node B

$$i_6 = i_3 - i_1 = 50mA - (-20mA) = \boxed{70mA}$$


Using Node C

$$i_5 = -i_2 - i_1 = 32mA$$

Check Node D

$$-32 + 70 - 38 = 0 \quad \checkmark$$

2.24)

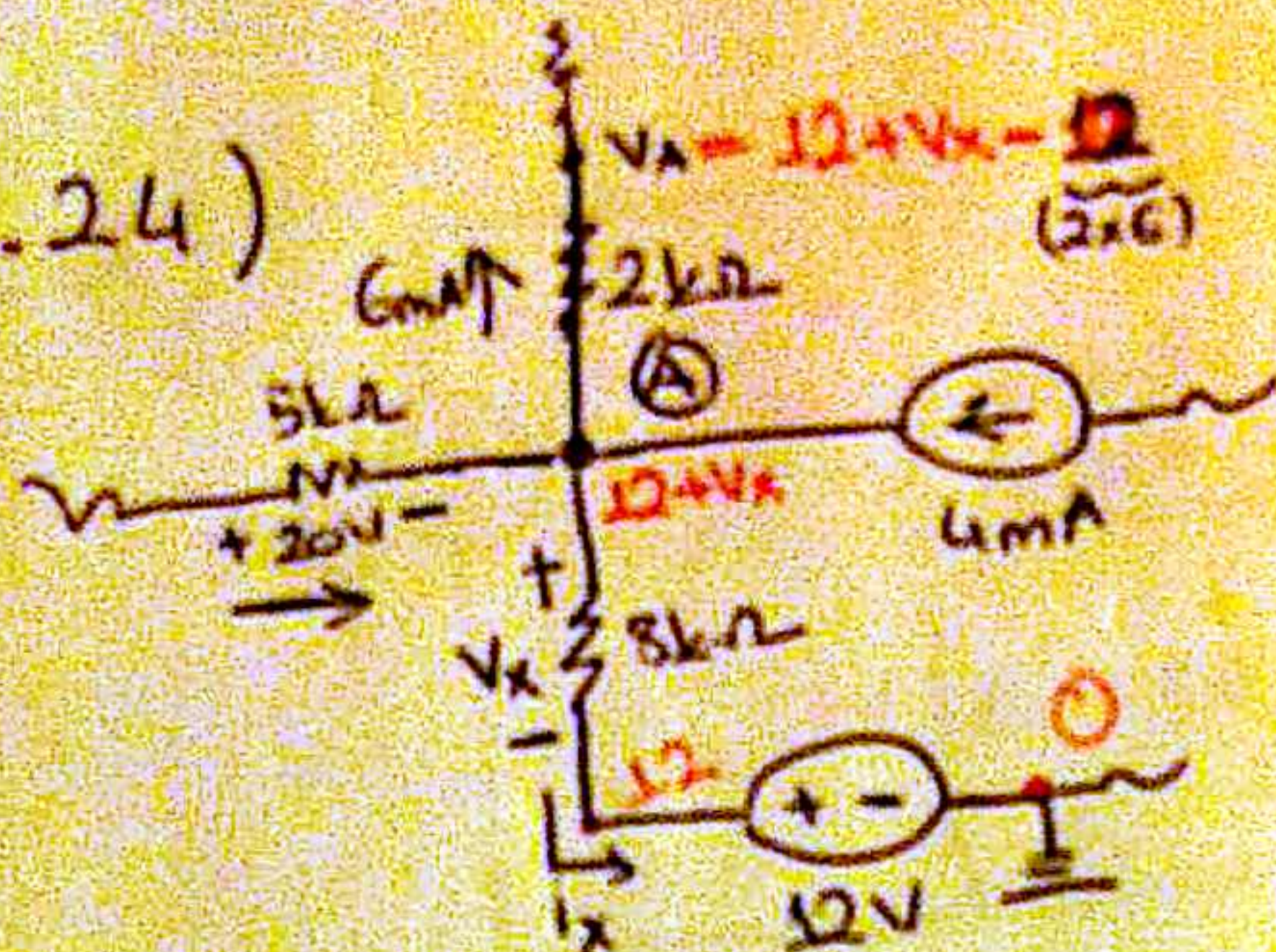

a) Applying KCL @ node (A)

$$-6\text{mA} + 4\text{mA} + \frac{20\text{V}}{5\text{k}\Omega} = i_x$$

$$\Rightarrow i_x = 2\text{mA}$$



$$\Rightarrow V_x = 8\text{k}\Omega \left(\frac{2\text{mA}}{i_x} \right) = 16\text{V}$$


$$b) \quad 2\text{mA} - 4\text{mA} + 6\text{mA} - 4\text{mA} = 0 \quad \checkmark$$

c) Referring Figure

$$V_A = 12 + V_x - 6\text{mA} \times 2\text{k}\Omega$$

$$V_A = V_x = 16\text{V}$$

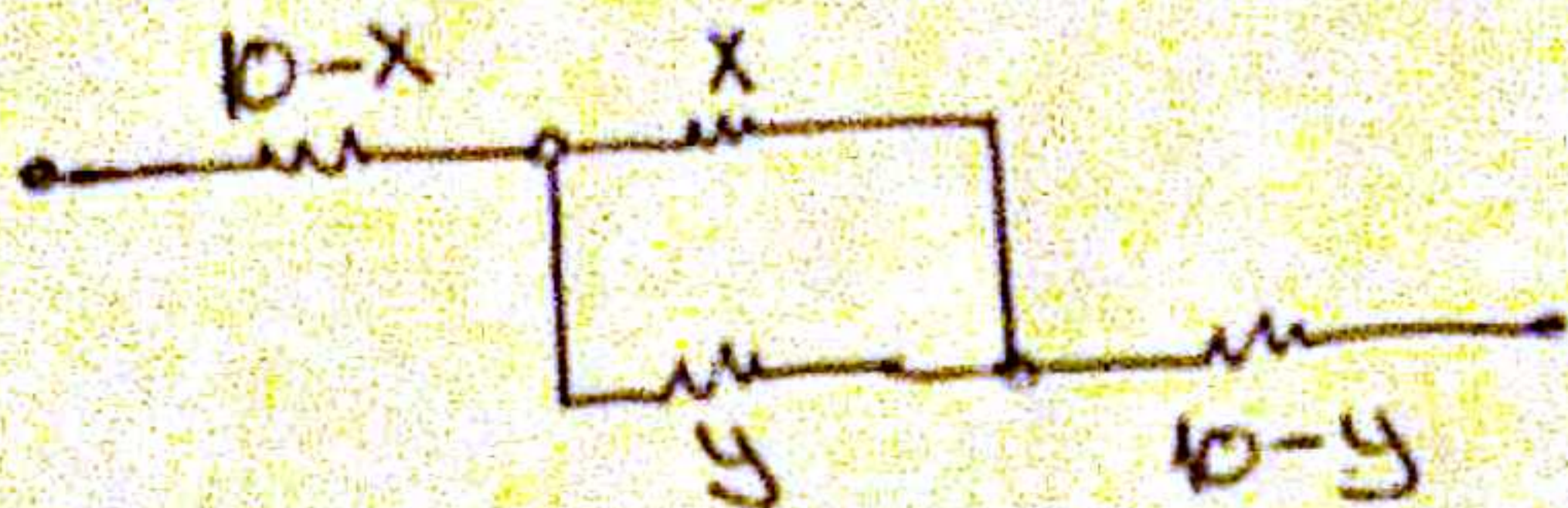2.37) The given circuit can be written in the following form



We can calculate R_{eq} in terms of x and y

$$R_{eq} = 20 - (x+y) + \frac{xy}{(x+y)}$$

Defining $P = x+y$ and $x = P-y$

$$R_{eq} = 20 - (P) + \frac{(P-y)y}{P}$$

$$= 20 - (P-y) - \frac{y^2}{P}$$

Because of physical limitations $x, y > 0$, ~~and~~ so

$(P-y) > 0$ and $\frac{y^2}{P} > 0$. Then the maximum

value for $R_{eq} = 20$
 max

2.37) cont.

To find the min. value of D_{eq} , we need to find the max. value of the following expression

$$f(x,y) = \underbrace{(p-y)}_x + \frac{y^2}{p}$$

$$0 \leq x \leq 10$$

$$0 \leq y \leq 10$$

$$0 \leq x+y=p \leq 20$$

Choosing $x=10, y=10$, we get


$$f(10,10) = 15$$

Then

$$D_{eq, \min} = 20 - 15 = 5$$

$$5 \leq D_{eq} \leq 20$$

2.44)

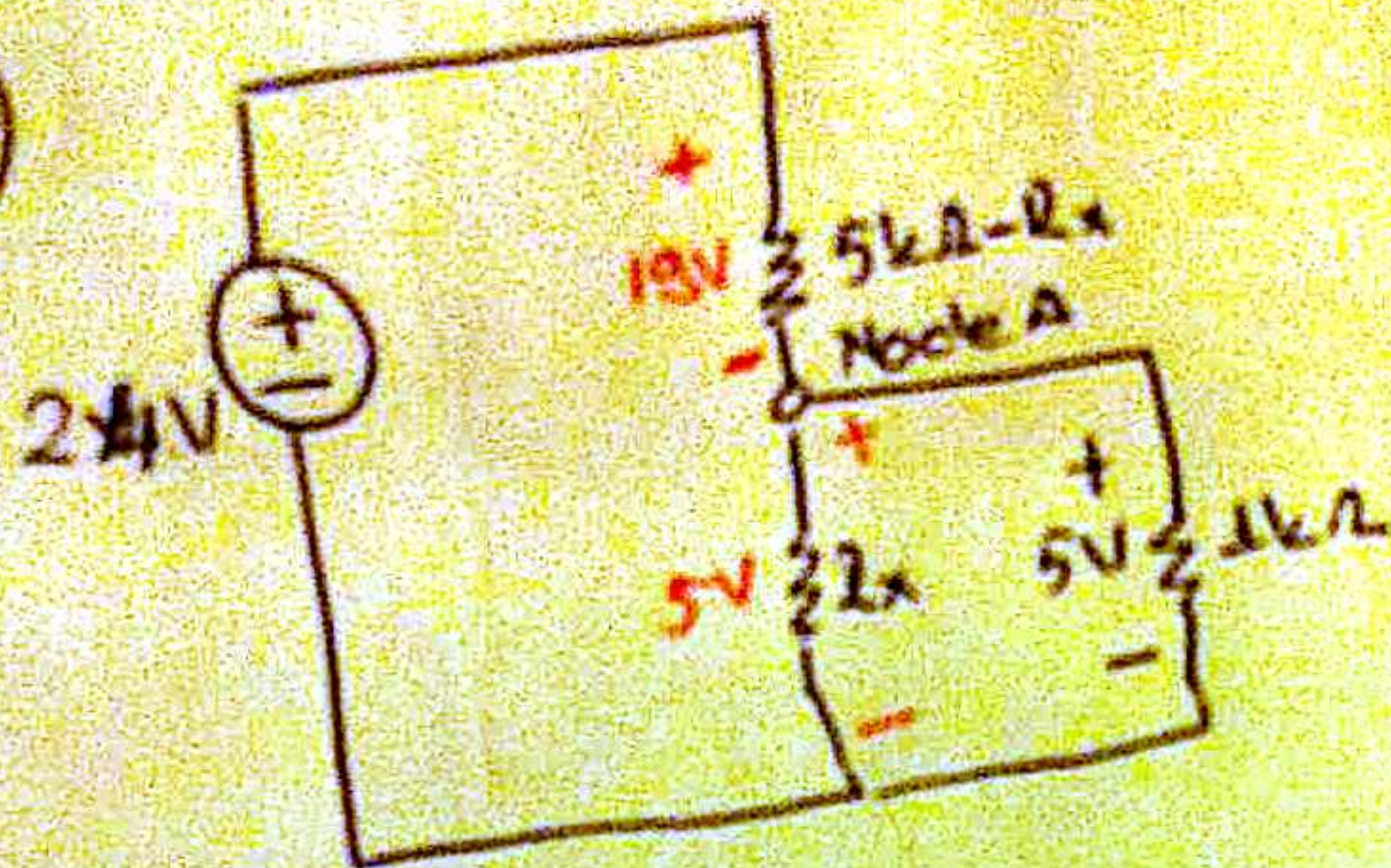

KCL @ Node A

$$\frac{19}{(5 - R_x)} - \frac{5V}{R_x} - \frac{5}{1} = 0$$

$$\Rightarrow 5R_x^2 - R_x - 25 = 0$$


The positive root of the equation

$$R_x \approx 2.34 \text{ k}\Omega$$

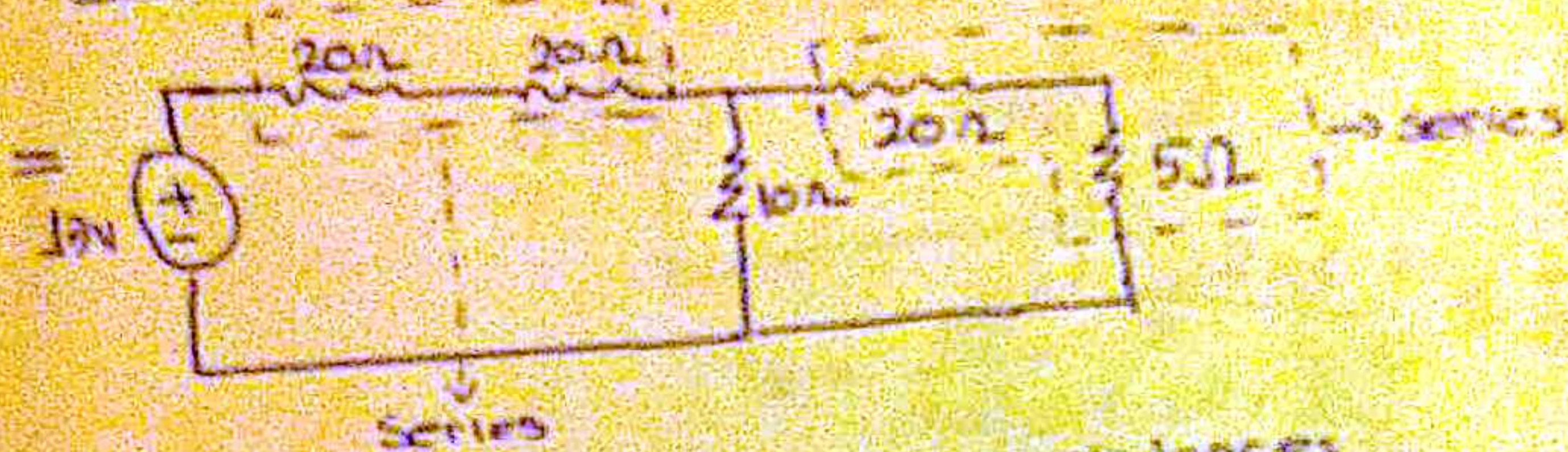
2-53) Use circuit reduction to find V_x in Figure



First Step: Source transformation and parallel resistances



Second Step: Two series resistances

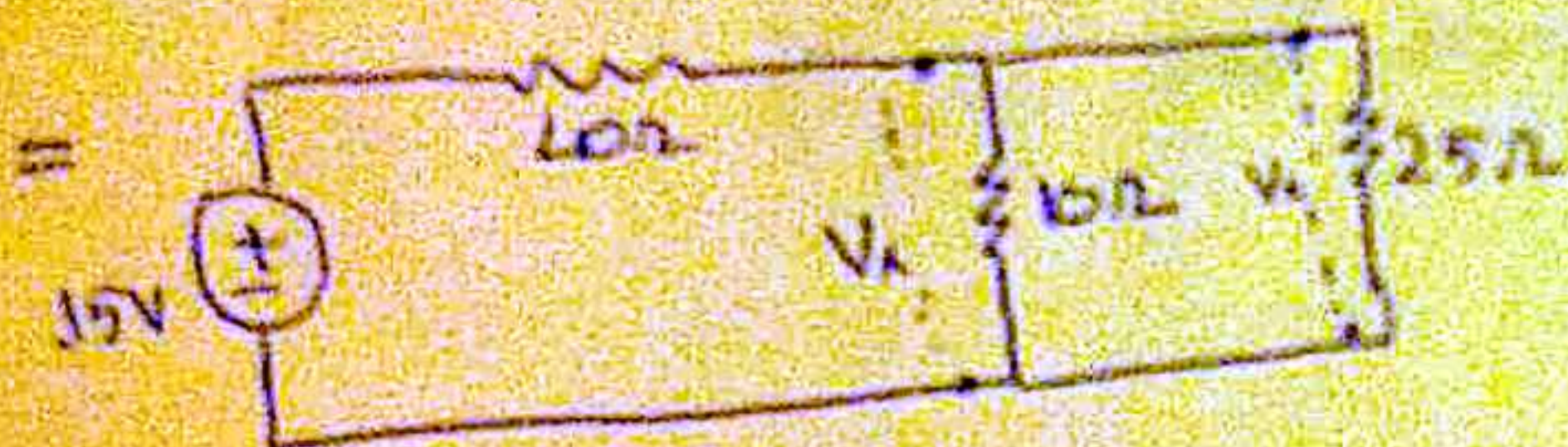

Resistance 10Ω and 25Ω are parallel so the potential difference

Then we can reduce them into one resistance still have same potential difference V_x

Third step: Parallel Resistances




Fourth step: Voltage division

$$V_x = \frac{\frac{50}{7}}{(40 + \frac{50}{7})} \cdot 15 = \frac{50}{\frac{310}{7}} \cdot \frac{15}{1} = \frac{25}{11} V$$

P.S.: You can solve this question in different way.
For example, you can transform the source after
Second step and apply current division and ohm's law

2.53) cont.




Fifth Step

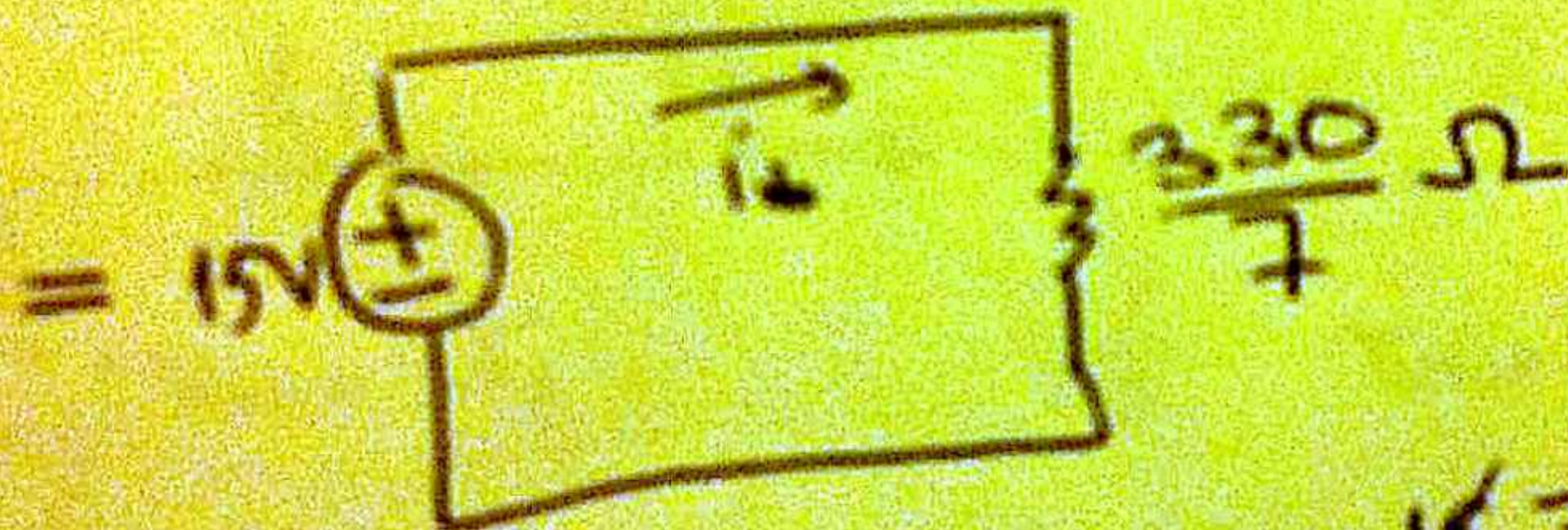

$$i_c = \frac{15}{\frac{330}{7}} = \frac{15 \cdot 7}{330} = \frac{7}{22}$$

$$P = V \cdot i = 15 \cdot \frac{7}{22} = \boxed{\frac{105}{22} \text{ W}}$$

3.36) a)

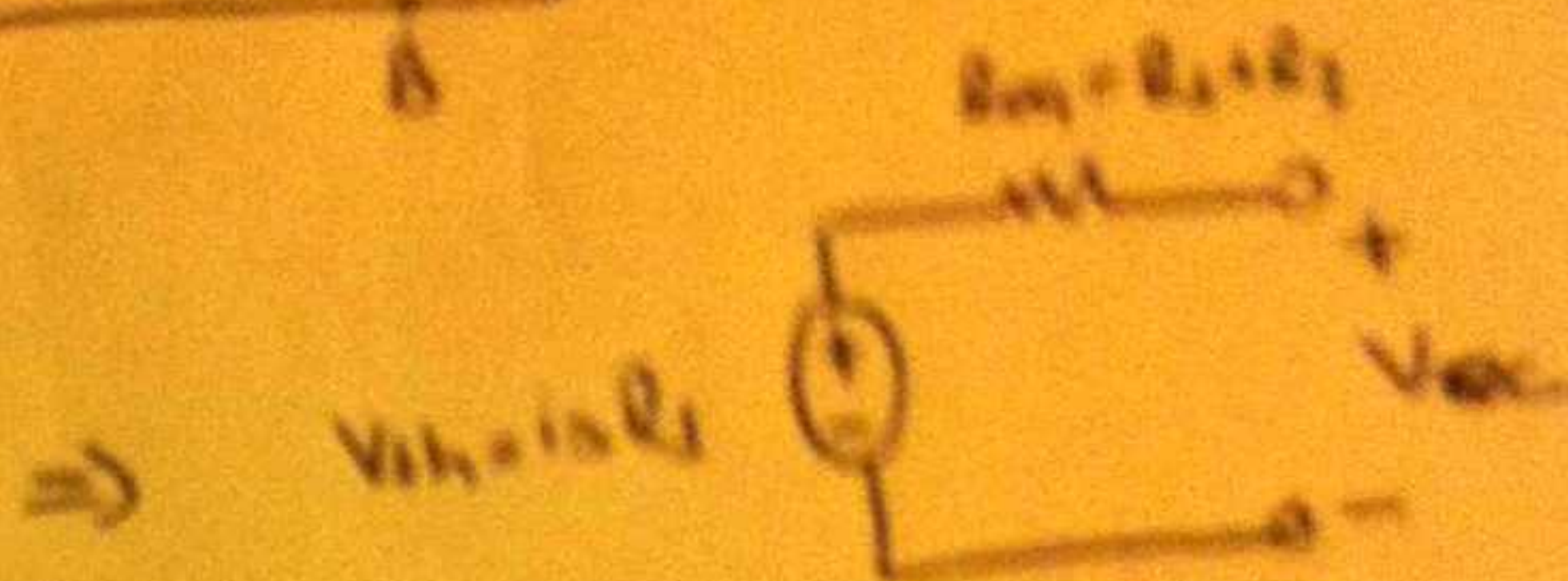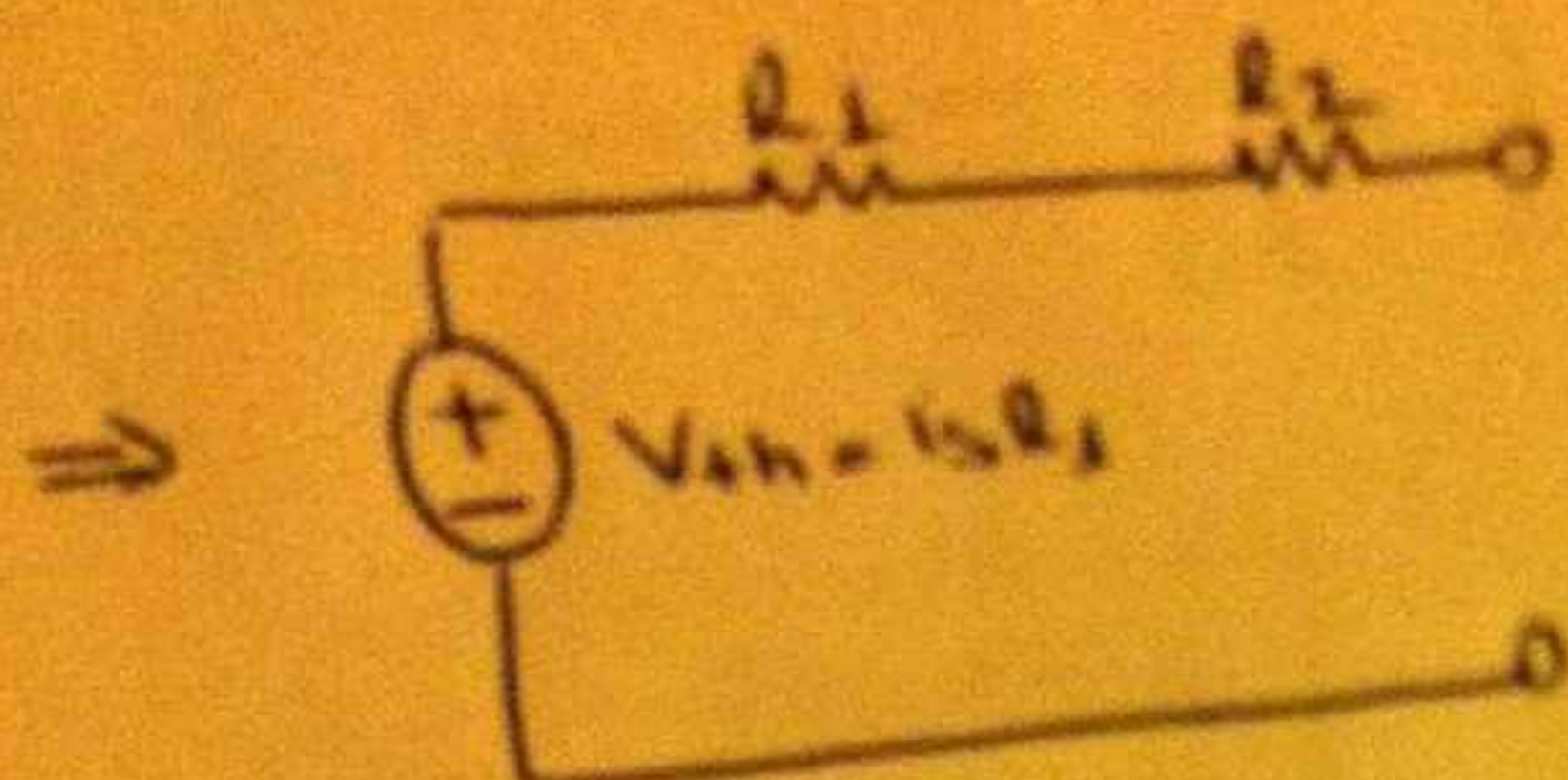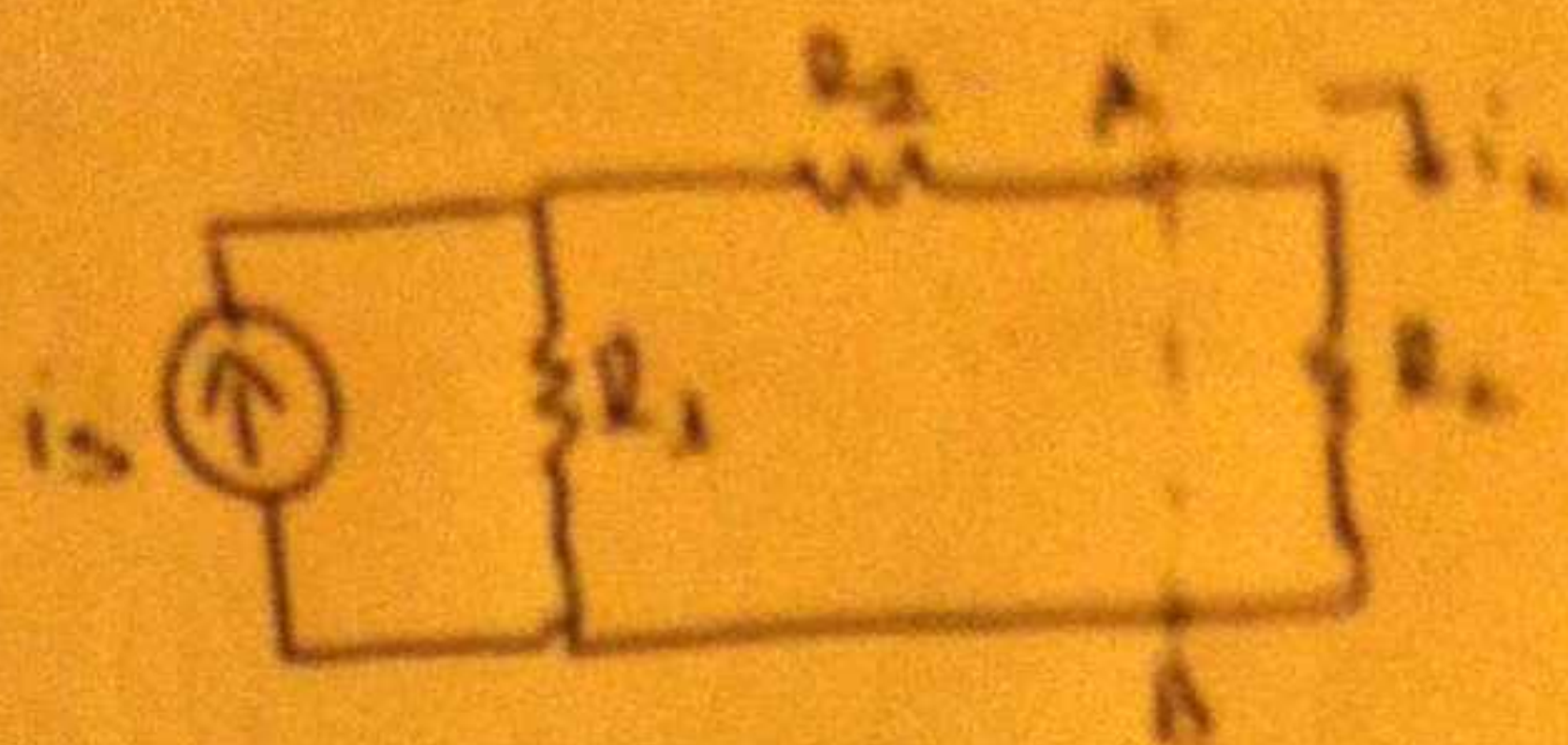


$$V_{oc} = V_{th} = i_s R_1$$

$$i_{sc} = \frac{V_{th}}{R_1 + R_2} = \frac{i_s R_1}{R_1 + R_2}$$

b)

$$i_L = \frac{V_{th}}{R_1 + R_2 + R_L} = \frac{i_s R_1}{R_1 + R_2 + R_L}$$

c)

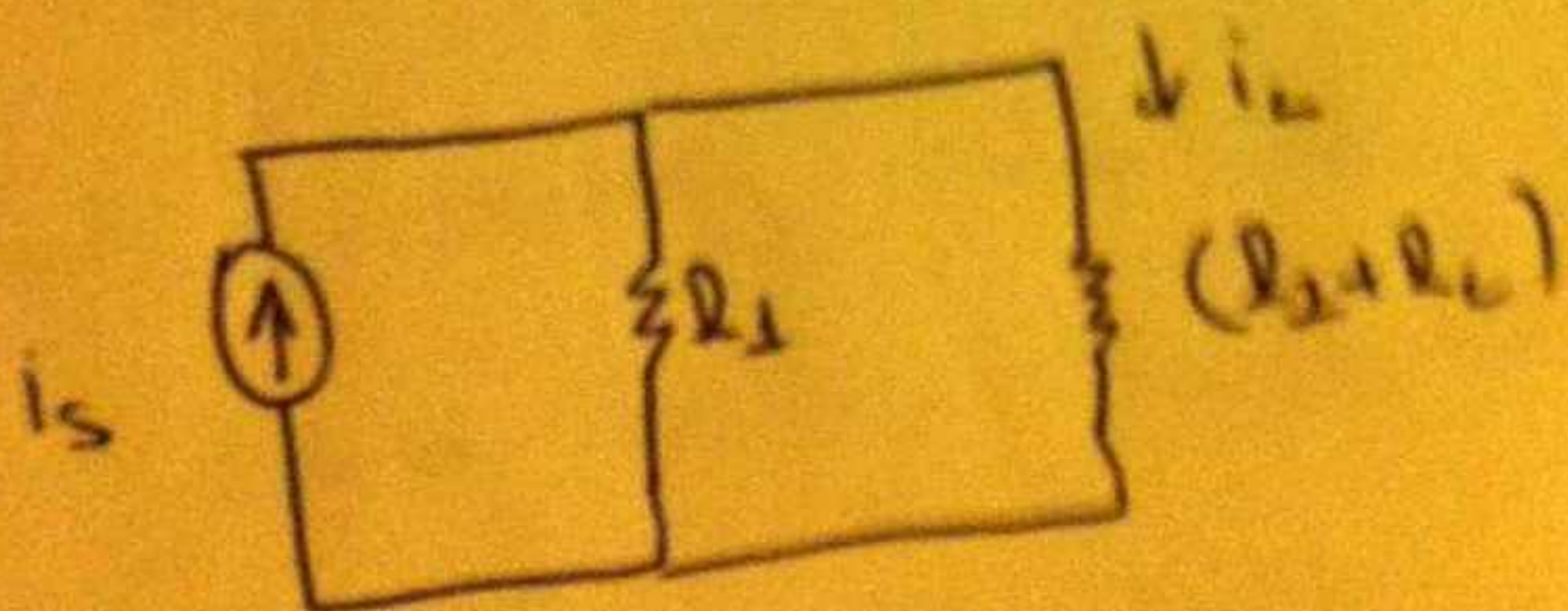


Using current division

$$i_L = \frac{R_1}{R_1 + R_2 + R_L} i_s$$

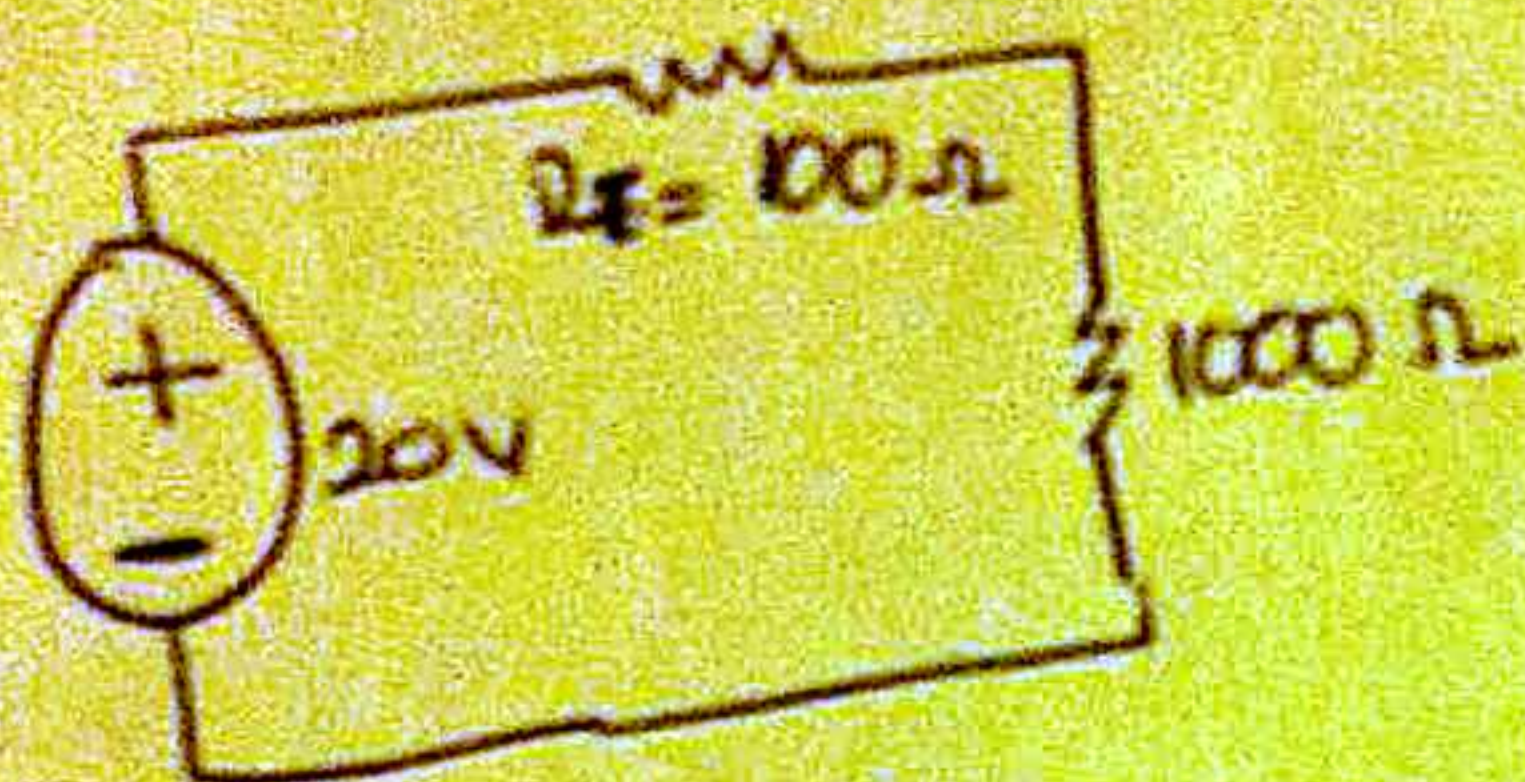3.43) This question is the application of (eq 3-27) in the book

$$i = \left(-\frac{1}{100} \right) v + \frac{20}{100} \rightarrow V_L$$



Voltage division

$$V = \frac{1000}{(1000+100)} \cdot 20$$

$$V = \frac{200}{11}$$

or

Simply, using $V = i R_L$, we can write current as $i = \frac{V}{R_L}$. Substituting "i" into given equation, we get $5V + 500 \frac{V}{R_L} = 100$.

Substituting $R_L = 1000\Omega$ and solving for V, we obtain

$$V = \frac{200}{11}$$