

MAE140 Win12 HW1 Solutions

T R & T, 1.14, 1.22, 1.24, 2.2, 2.5, 2.11, 2.17, 2.23, 2.28, 2.38

1-14

$(100\text{W}-12\text{W}) \cdot 1000\text{h} = 88\text{kWh}$ (less energy)
 $88\text{kWh} \cdot 7.2 \text{ cents/kWh} = 633.6 \text{ cents cheaper}$

1-22

Device 1: $P = v \cdot i = 15 \cdot (-1) = -15\text{W}$ (delivering)

Device 2: $P = v \cdot i = 5 \cdot 1 = 5\text{W}$ (absorbing)

Device 3: $P = 10 \cdot 2 = 20\text{W}$ (absorbing)

Device 4: $P = (-10) \cdot (-1) = 10\text{W}$ (absorbing)

Device 5: $P = 20 \cdot (-3) = -60\text{W}$ (delivering)

Device 6: $P = 20 \cdot 2 = 40\text{W}$ (absorbing)

Power balance:

$$-15 + 5 + 20 + 10 - 60 + 40 = 0$$

1-24

From the figure, it's easy to tell that:

$$v_2 = 10\text{ V}, v_3 = 0\text{ V}, v_5 = v_6 = -5\text{ V}$$

2-2

$$P = i^2 R \Rightarrow i = \sqrt{\frac{P}{R}} = \sqrt{\frac{12\text{ mW}}{6.2\text{ k}\Omega}} = \sqrt{\frac{60}{31}}\text{ mA} \approx 1.39\text{ mA}$$


2-5

$$v = iR \Rightarrow R_x = \frac{50\text{ V}}{10\text{ mA}} = 5\text{ k}\Omega$$

$$P = vi = 50\text{ V} \times 10\text{ mA} = 500\text{mW}$$

2-11

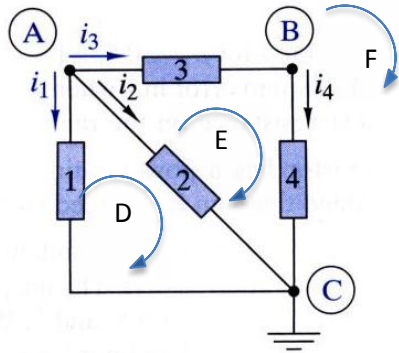(a) All the nodes: A, B and C. The loops: D, E and F



(b) 3 in series with 4, 1 in parallel with 2

(c) KCL:

$$A: -i_1 - i_2 - i_3 = 0$$

$$B: i_3 - i_4 = 0$$

$$C: i_1 + i_2 + i_4 = 0$$

KVL:

$$D: -v_1 + v_2 = 0$$

$$E: -v_2 + v_3 + v_4 = 0$$

$$F: -v_1 + v_3 + v_4 = 0$$


2-17

Using KCL, we can get the equations:

$$A: i_1 - i_2 + i_3 - i_4 = 0 \Rightarrow i_1 = 10 + 15 + 5 = 30 \text{ mA}$$

$$C: -i_3 + i_4 + i_5 = 0 \Rightarrow i_5 = -15 - 5 = -20 \text{ mA}$$

2-23

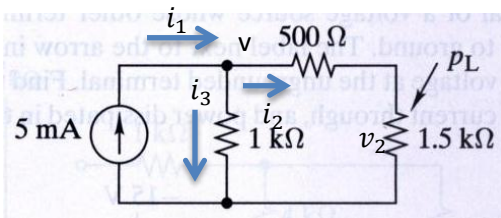

Using KCL, we can get:

$$i_1 - i_2 - i_3 = 0$$

So

$$i_2 + i_3 = \frac{v}{(0.5 + 1.5)k\Omega} + \frac{v}{1k\Omega} = i_1 = 5 \text{ mA} \Rightarrow v = \frac{10}{3} \text{ V}$$

According to voltage divide rule,


$$v_2 = \frac{1.5}{2} v = 2.5 \text{ V}$$

Then,

$$i_2 = \frac{v_2}{1.5k\Omega} = \frac{5}{3} \text{ mA}$$

$$P = i_2 v_2 = \frac{5}{3} \cdot 2.5 = 4.17 \text{ mW}$$


2-28

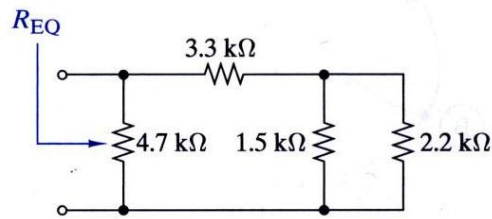

- 1) $1.5\text{ k}\Omega$ and $2.2\text{ k}\Omega$ are in parallel. $R_1 = \left(\frac{1}{1.5} + \frac{1}{2.2}\right)^{-1} = 0.89\text{ k}\Omega$
- 2) R_1 and $3.3\text{ k}\Omega$ are in series. $R_2 = 3.3 + R_1 = 4.19\text{ k}\Omega$
- 3) $4.7\text{ k}\Omega$ and R_2 are in parallel.

$$R_{EQ} = \left(\frac{1}{4.7} + \frac{1}{4.19}\right)^{-1} = 2.22\text{ k}\Omega$$

2-38

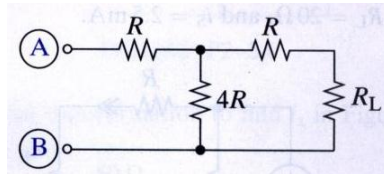

$$R_{AB} = R + \left(\frac{1}{4R} + \frac{1}{(R + R_L)}\right)^{-1} = R + \frac{4R(R + R_L)}{5R + R_L} = R_L$$

$$\Rightarrow R_L^2 = 9R^2 \Rightarrow R = R_L/3$$