

MAE140 Win12 HW3 Solutions

T R & T, 3.1, 3.3, 3.6, 3.7, 3.9, 3.10, 3.12, 3.15 b) and d), 3.71, 3.74

3-1

(a) Writing node-voltage equations by inspection, we can get:

Node A:

$$\left(\frac{1}{40} + \frac{1}{30}\right)v_A - \frac{1}{30}v_B = 2$$

Node B:

$$-\frac{1}{30}v_A + \left(\frac{1}{30} + \frac{1}{20} + \frac{1}{80}\right)v_B = 0$$

Written in matrix form $\mathbf{Ax} = \mathbf{b}$

$$\begin{bmatrix} \left(\frac{1}{40} + \frac{1}{30}\right) & -\frac{1}{30} \\ -\frac{1}{30} & \left(\frac{1}{30} + \frac{1}{20} + \frac{1}{80}\right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

(b) Solve the equations or matrix form, we can get

$$v_A = 42.79 \text{ V}, v_B = 14.88 \text{ V}$$

(c)

$$v_x = v_A - v_B = 27.91 \text{ V}$$

$$i_x = \frac{v_B}{80} = 0.1860 \text{ A}$$

3-3

(a) Writing node-voltage equations by inspection, we can get:

Node A:

$$\left(\frac{1}{4k\Omega} + \frac{1}{2k\Omega}\right)v_A - \frac{1}{2k\Omega}v_B = 20\text{mA} - 20\text{mA} = 0$$

Node B:

$$-\frac{1}{2k\Omega}v_A + \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{2k\Omega}\right)v_B = -20\text{mA}$$

Written in matrix form $\mathbf{Ax} = \mathbf{b}$

$$\begin{bmatrix} \left(\frac{1}{4k\Omega} + \frac{1}{2k\Omega}\right) & -\frac{1}{2k\Omega} \\ -\frac{1}{2k\Omega} & \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{2k\Omega}\right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} 0 \\ -20 \end{bmatrix}$$

(b) Solve the equations or matrix form, we can get

$$v_A = -14.545 \text{ V}$$


$$v_B = -21.818 \text{ V}$$

(c)

$$v_x = \frac{v_B}{2} = -10.909 \text{ V}$$

$$i_x = \frac{v_A - v_B}{2k\Omega} = 3.6364 \text{ mA}$$

3-6

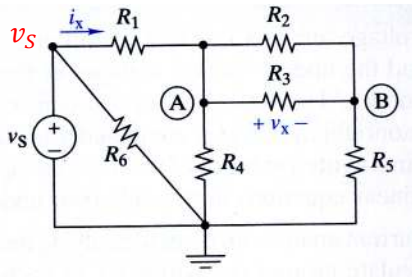

(a) Writing node-voltage equations by method 2, we can get:

Node A:

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right)v_A - \left(\frac{1}{R_2} + \frac{1}{R_3}\right)v_B = \frac{v_S}{R_1}$$

Node B:

$$-\left(\frac{1}{R_2} + \frac{1}{R_3}\right)v_A + \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5}\right)v_B = 0$$

Written in matrix form $\mathbf{Ax} = \mathbf{b}$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) & -\left(\frac{1}{R_2} + \frac{1}{R_3}\right) \\ -\left(\frac{1}{R_2} + \frac{1}{R_3}\right) & \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5}\right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} \frac{v_S}{R_1} \\ 0 \end{bmatrix}$$

(b) By solving the two equations or the matrix form, we can get

$$\begin{aligned} v_A &= 9 \text{ V}, v_B = 6 \text{ V} \\ i_x &= \frac{v_S - v_A}{R_1} = 1.5 \text{ mA} \\ v_x &= v_A - v_B = 3 \text{ V} \end{aligned}$$

3-7

(a) Writing node-voltage equations by inspection, we can get:

Node A:

$$\left(\frac{1}{R_1} + \frac{1}{R_4}\right)v_A - \frac{1}{R_1}v_B - \frac{1}{R_4}v_C = i_{s1}$$

Node B:

$$-\frac{1}{R_1}v_A + \left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_B + 0 \cdot v_C = i_{s2}$$

Node C:

$$-\frac{1}{R_4}v_A - 0 \cdot v_B + \left(\frac{1}{R_3} + \frac{1}{R_4}\right)v_C = -i_{s2}$$


Written in matrix form $\mathbf{Ax} = \mathbf{b}$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_4}\right) & -\frac{1}{R_1} & -\frac{1}{R_4} \\ -\frac{1}{R_1} & \left(\frac{1}{R_1} + \frac{1}{R_2}\right) & 0 \\ -\frac{1}{R_4} & 0 & \left(\frac{1}{R_3} + \frac{1}{R_4}\right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} i_{s1} \\ i_{s2} \\ -i_{s2} \end{bmatrix}$$

(c) By solving the two equations or the matrix form, we can get

$$v_A = 5.98 \text{ V}, v_B = 5.34 \text{ V}, v_C = -1.41 \text{ V}$$

3-9

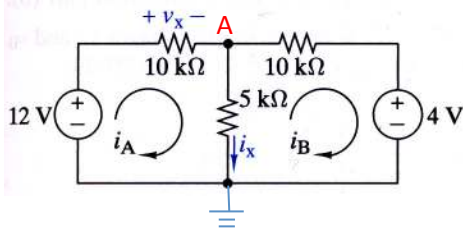

(a) Writing node-voltage equations by inspection, we can get:


$$\text{Node A: } \left(\frac{1}{10k\Omega} + \frac{1}{5k\Omega} + \frac{1}{10k\Omega} \right) v_A - \frac{1}{10k\Omega} \cdot 12V - \frac{1}{10k\Omega} \cdot 4V = 0$$

(b) Solving the equation, we can get $v_A = 4V$.

$$\text{So } i_A = \frac{12 - v_A}{10k\Omega} = 0.8 \text{ mA}, i_B = \frac{v_A - 4}{10k\Omega} = 0A$$

(c) $v_x = 12 - v_A = 8V, i_x = \frac{v_A}{5k\Omega} = 0.8 \text{ mA}$

3-10

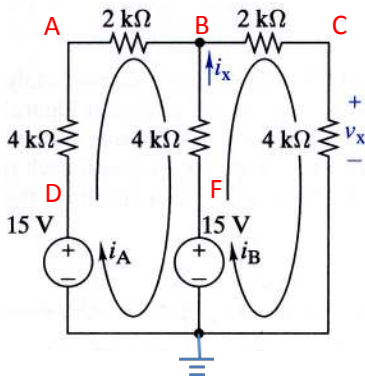

(a) Using method 2, writing node-voltage equations by inspection, we can get:

$$\text{Node A: } \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} \right) v_A - \frac{1}{2k\Omega} v_B - \frac{1}{4k\Omega} v_D = 0$$

$$\text{Node B: } -\frac{1}{2k\Omega} v_A + \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{2k\Omega} \right) v_B - \frac{1}{2k\Omega} v_C - \frac{1}{4k\Omega} v_F = 0$$

$$\text{Node C: } -\frac{1}{2k\Omega} v_B + \left(\frac{1}{4k\Omega} + \frac{1}{2k\Omega} \right) v_C = 0$$

Knowing $v_D = 15V, v_F = 15V$, we can get the matrix form:

$$\begin{bmatrix} \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} \right) & -\frac{1}{2k\Omega} & 0 \\ -\frac{1}{2k\Omega} & \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{2k\Omega} \right) & -\frac{1}{2k\Omega} \\ 0 & -\frac{1}{2k\Omega} & \left(\frac{1}{4k\Omega} + \frac{1}{2k\Omega} \right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} \frac{15}{4k\Omega} \\ \frac{15}{4k\Omega} \\ 0 \end{bmatrix}$$


(b) Solving the matrix, we can get

$$v_A = 12.14V, v_B = 10.71V, v_C = 7.14V$$

$$v_x = v_C = 7.14V$$

$$i_x = \frac{15V - v_B}{4k\Omega} = 1.07 \text{ mA}$$

3-12

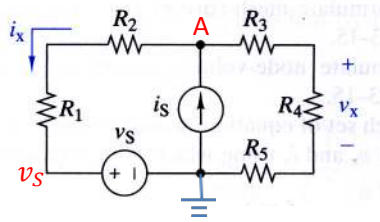

(a) Use method 2 to write node-voltage equation.

$$\text{Node A: } \left(\frac{1}{R_1+R_2} + \frac{1}{R_3+R_4+R_5} \right) v_A - \frac{1}{R_1+R_2} v_S - i_S = 0 \Rightarrow v_A = 37.5V$$

$$(b) v_x = \frac{R_4}{R_3+R_4+R_5} v_A = 18.75V, i_x = \frac{v_A-v_S}{R_1+R_2} = 0.025 A$$

(c) The total power $P = i_S v_A = 3.75W$. Noting that the voltage source is absorbing power.

3-15

(b) Using method 2 to write node-voltage equation.


$$\text{Node B: } -\frac{1}{2k\Omega} v_A + \left(\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{8k\Omega} \right) v_B - \frac{1}{8k\Omega} v_C = 5mA$$

Noting that $v_A = 40V$, $v_C = -25V$, so we can get $v_B = 25V$

$$(d) v_x = v_B = 25V$$

$$i_x = \frac{v_C-v_B}{8k\Omega} = -6.25mA.$$

3-71

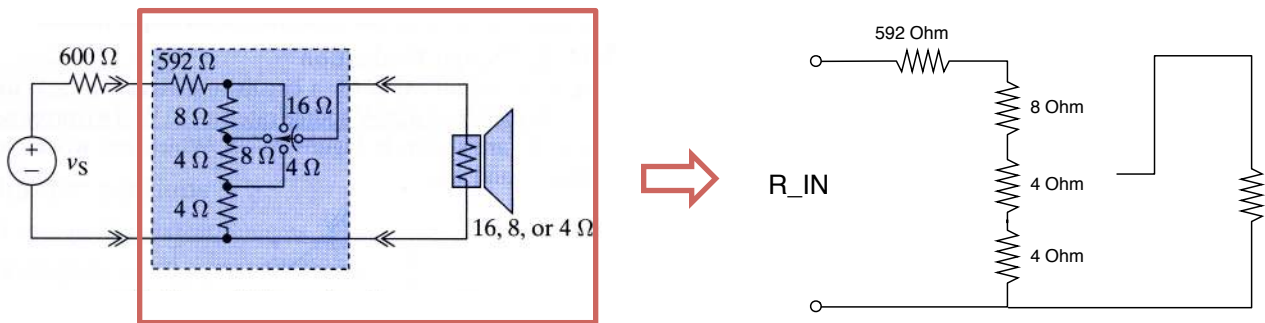


As shown in the figure, we can get R_{IN} when the connected speaker are 16, 8, 4Ω.

$$R_{IN} = 592 + (8 + 4 + 4) || 16 = 600 \Omega$$

$$R_{IN} = 592 + 8 + (4 + 4) || 8 = 604 \Omega$$

$$R_{IN} = 592 + 8 + 4 + 4 || 4 = 608 \Omega$$

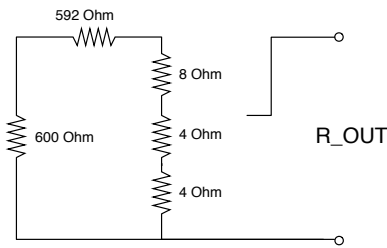The company claims that R_{IN} can vary in the range [588, 612]. So the claim for R_{IN} is true.



Now we calculate the value of R_{OUT} .


$$R_{OUT} = (600 + 592) || (8 + 4 + 4) = 15.79\Omega \text{ It is in the range of } 16 \pm 2\%.$$

$$R_{OUT} = (600 + 592 + 8) || (4 + 4) = 7.95\Omega \text{ It is in the range of } 8 \pm 2\%.$$

$$R_{OUT} = (600 + 592 + 8 + 4) || 4 = 3.98\Omega \text{ It is in the range of } 4 \pm 2\%.$$

The claim of the company is true.

3-74

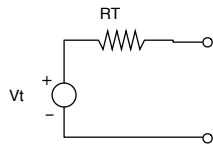

To design a battery with large voltage, we need to combine batteries with small voltage. Since our goal voltage is 36V, there are only two ways to achieve it with given batteries: 4 first type or 9 second type.

If we choose first type, which is 4 batteries with $v_{OC} = 9V$, $R_t = 4\Omega$ in series, $R_T = 4 \times 4\Omega = 16\Omega > 10\Omega$.

If we choose second type, which is 9 batteries with $v_{OC} = 4V$, $R_t = 0.5\Omega$ in series, $R_T = 9 \times 0.5\Omega = 4.5\Omega < 10\Omega$.

It's clear that we have to choose second type. Also the weight of the combination is less for the second one.

The result is choosing 9 second type batteries in series.