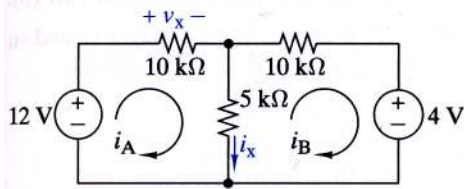


MAE140 Win12 HW4 Solutions

T R & T, 3.9, 3.10, 3.12, 3.15 a) and c), 3.20 a) and b), 3.22, 3.26, 4.2, 4.6, 4.13

3-9



- (a) To write mesh-current equations by inspection, we note that the total resistances in mesh A and B are $10k\Omega + 5k\Omega$, and $10k\Omega + 5k\Omega$, respectively. The resistance common to meshes A and B is $5k\Omega$. Using these observations, we write the mesh equations as,

$$\text{Mesh A: } (10k\Omega + 5k\Omega)i_A - 5k\Omega i_B - 12V = 0$$

$$\text{Mesh B: } (10k\Omega + 5k\Omega)i_B - 5k\Omega i_A + 4V = 0$$

- (b) Solving the equations, we can get:


$$i_A = 0.8mA, i_B = 0mA$$

- (c) Using the results,

$$v_x = 10k\Omega i_A = 8V$$

$$i_x = i_A - i_B = 0.8mA$$

3-10

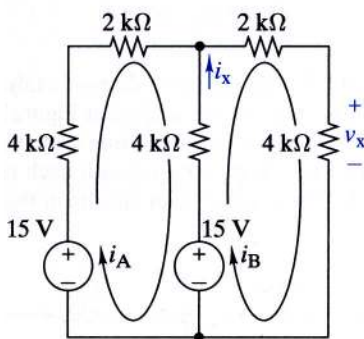

- (a) Writing mesh-current equations by inspection, we can get:

$$\text{Mesh A: } (4k\Omega + 2k\Omega + 4k\Omega)i_A - 4k\Omega i_B - 15V + 15V = 0$$

$$\text{Mesh B: } (4k\Omega + 2k\Omega + 4k\Omega)i_B - 4k\Omega i_A - 15V = 0$$

- (b) Solving the matrix, we can get


$$i_A = 0.7143 \text{ mA}, i_B = 1.7857 \text{ mA}$$

- (c) Using the results,

$$v_x = 4k\Omega i_B = 7.14V$$

$$i_x = i_B - i_A = 1.07 \text{ mA}$$

3-12

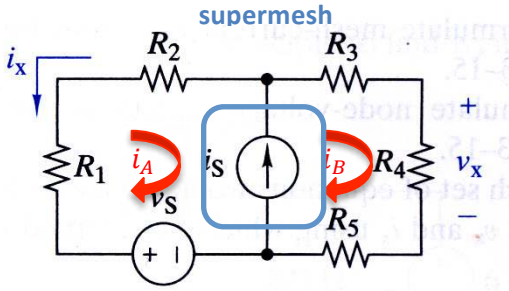

(a) Creating a supermesh as shown in the figure, we can get

$$i_s = i_B - i_A$$

$$(R_1 + R_2)i_A + (R_1 + R_2 + R_3)i_B - v_s = 0$$

(b) Using the given values, we can get

$$i_A = -25\text{mA}, \quad i_B = 75\text{mA}$$

So we obtain,


$$v_x = i_B R_4 = 18.75\text{V}$$

$$i_x = -i_A = 0.025\text{ A}$$

(c) The total power $P = i_A^2(R_1 + R_2) + i_B^2(R_3 + R_4 + R_5) - i_A v_s = 3.75\text{W}$.

Please pay attention to the direction of the current and voltage.

3-15

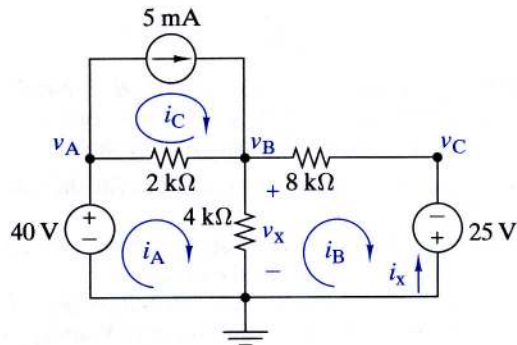

(a) Writing mesh-current equations by inspection, we can get:


$$\text{Mesh A: } i_A(2\text{k}\Omega + 4\text{k}\Omega) - i_B \cdot 4\text{k}\Omega - i_C \cdot 2\text{k}\Omega = 40\text{V}$$

$$\text{Mesh B: } -i_A \cdot 4\text{k}\Omega + i_B(4\text{k}\Omega + 8\text{k}\Omega) = 25\text{V}$$

$$\text{Mesh C: } i_C = 5\text{mA}$$

(c) Node voltage; there is only one equation to solve.

3-20

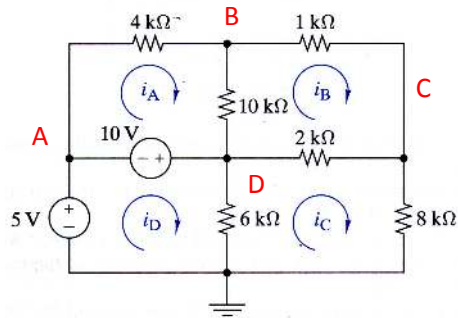

(a) Writing the mesh-current equations by inspection, we can get:

$$\text{Mesh A: } (4k\Omega + 10k\Omega)i_A - 10k\Omega \cdot i_B + 10 = 0$$

$$\text{Mesh B: } -10k\Omega i_A + (1k\Omega + 10k\Omega + 2k\Omega)i_B - 2k\Omega i_C = 0$$

$$\text{Mesh C: } -2k\Omega i_B + (2k\Omega + 8k\Omega + 6k\Omega)i_C - 6k\Omega i_D = 0$$

$$\text{Mesh D: } 6k\Omega i_D - 6k\Omega i_C - 10 - 5 = 0$$

Write in matrix form:

$$\begin{bmatrix} (4k\Omega + 10k\Omega) & -10k\Omega & 0 & 0 \\ -10k\Omega & (1k\Omega + 10k\Omega + 2k\Omega) & -2k\Omega & 0 \\ 0 & -2k\Omega & (2k\Omega + 8k\Omega + 6k\Omega) & -6k\Omega \\ 0 & 0 & -6k\Omega & 6k\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \\ 0 \\ 15 \end{bmatrix}$$

Solving the equations, we can get

$$i_A = -1.2565 \text{ mA}$$

$$i_B = -0.7592 \text{ mA}$$

$$i_C = 1.3482 \text{ mA}$$

$$i_D = 3.8482 \text{ mA}$$

(b) By looking at the figure, we can find $v_A = 5V$, $v_D = 15V$. Then we can write the node-voltage equations.

$$\text{Node B: } -\frac{1}{4}v_A + \left(\frac{1}{4} + \frac{1}{10} + 1\right)v_B - v_C - \frac{1}{10}v_D = 0$$

$$\text{Node C: } -v_B + \left(1 + \frac{1}{2} + \frac{1}{8}\right)v_C - \frac{1}{2}v_D = 0$$

Solving the equations, we can get

$$v_B = 10.0262 \text{ V}$$

$$v_C = 10.7853 \text{ V}$$


It's obvious that node-voltage needs less effort.

3-22

Using current division, we can get

$$i_O = \left[\frac{\frac{1}{R_3 + R_4}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3 + R_4}} \right] i_S \Rightarrow K = \frac{i_O}{i_S} = \frac{\frac{1}{R_3 + R_4}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3 + R_4}}$$


3-26

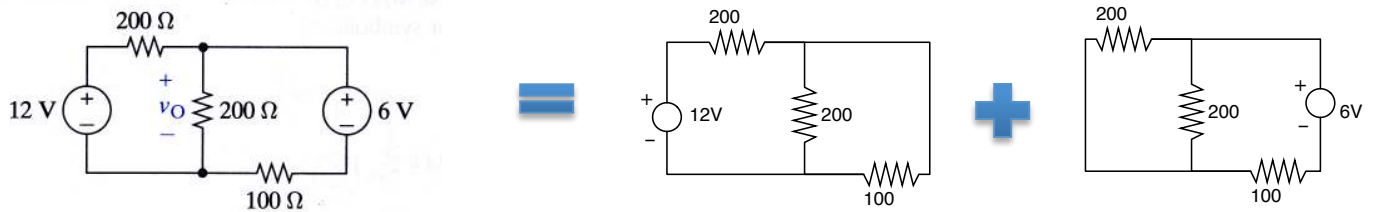

$$v_{O1} = 12V \cdot \left(\frac{200 \parallel 100}{200 + 200 \parallel 100} \right) = 3V \quad v_{O2} = 6V \cdot \left(\frac{200 \parallel 200}{100 + 200 \parallel 200} \right) = 3V$$

$$v_O = v_{O1} + v_{O2} = 6V$$

4-2

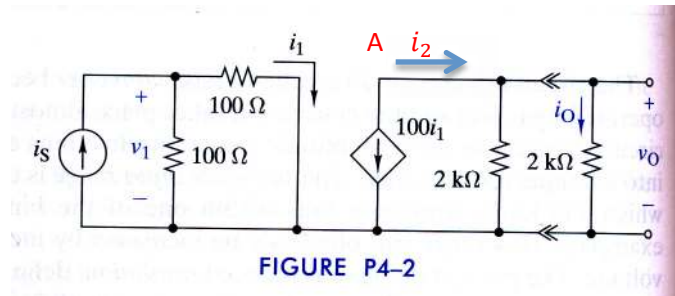

Using the current division in the input circuit, we can get

$$i_1 = \frac{100}{100 + 100} i_S = \frac{1}{2} i_S$$

Similarly, the output current i_O can be found in the output circuit by current division.

$$i_O = \frac{2}{2 + 2} i_2 = \frac{1}{2} i_2$$

At node A, KCL requires that $i_2 = -100i_1 = -50i_S$. So we can get

$$i_O = \frac{1}{2} i_2 = -25i_S \Rightarrow \frac{i_O}{i_S} = -25$$

Using Ohm's law, we can get

$$v_O = 2000i_O = -5 \times 10^4 i_S$$

$$v_1 = 100i_1 = 50i_S$$

$$\frac{v_O}{v_1} = \frac{-5 \times 10^4 i_S}{50i_S} = -1000$$

The power supplied by the independent current source is

$$P_S = (100 \parallel 100) i_S^2 = 0.2 \text{ mW}$$

The power delivered to the $2k\Omega$ load is

$$P_O = 2000i_O^2 = 5W$$

4-6 Find an expression for the current gain i_O/i_S in Figure P4-6. (Hint: Apply KCL at node A.)

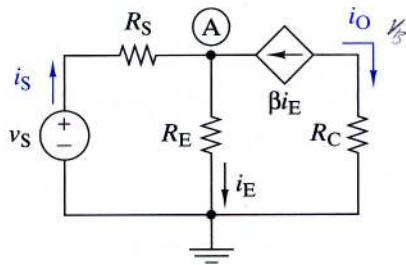


FIGURE P4-6

Applying KCL at node A, we can get:

$$i_S + \beta i_E - i_E = 0 \Rightarrow i_E = \frac{1}{1 - \beta} i_S$$

$$i_O = -\beta i_E = \frac{\beta}{\beta - 1} i_S \Rightarrow \frac{i_O}{i_S} = \frac{\beta}{\beta - 1}$$

4-13 Find R_{IN} in Figure P4-13.

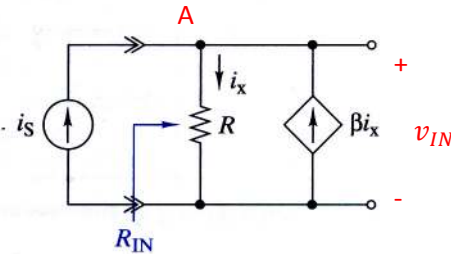


FIGURE P4-13

Using Ohm's law, we can get

$$R_{IN} = \frac{v_{IN}}{i_S} = \frac{i_x R}{i_S}$$

At node A, applying KCL,

$$i_S - i_x + \beta i_x = 0 \Rightarrow i_x = \frac{1}{1 - \beta} i_S$$

So the result is

$$R_{IN} = \frac{1}{1 - \beta} R$$