

MAE140 Win12 HW7 Solutions

T R & T, 10.4, 10.8, 10.10, 10.12, 10.14, 10.20, 10.22, 10.24, 10.32, 10.35

10-4

$$Z_{EQ}(s) = 2R + \frac{1}{\frac{1}{R} + \frac{1}{Ls}} = R \left[\frac{3Ls + R}{Ls + R} \right] = 3R \left[\frac{s + \frac{R}{3L}}{s + \frac{R}{L}} \right]$$

Pole at $s = -R/L$

Zero at $s = -R/(3L)$

10-8

$$Z_{EQ}(s) = \frac{1}{2Cs} + \left(2R + \frac{1}{Cs} \right) || 2R = \frac{8R^2C^2s^2 + 8RCs + 1}{8RC^2s^2 + 2Cs}$$

Poles at $s=0$ and $s=-1/(4RC)$

Zeros at $s = \frac{-2 \pm \sqrt{2}}{4RC}$

10-10

$$Z_{EQ}(s) = 2Ls + \frac{1}{\frac{1}{R} + \frac{1}{Ls}} + 2R = \frac{(2Ls + R)(Ls + 2R)}{Ls + R}$$

Pole at $s = -R/L$. Select $R=20k\Omega$, $L=10H$

10-12

The initial condition of the inductor is $i_L(0) = 0$.

Changing the circuit into s-domain and using KVL at $t>0$, we can get:

$$\frac{V_A}{s} - L[sI_L(s) - i_L(0)] - I_L(s)R = 0$$

Solving for $I_L(s)$, we get

$$I_L(s) = \frac{V_A}{L} \left[\frac{1}{s(s + \frac{R}{L})} \right] = \frac{V_A}{R} \left[\frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right]$$

$$i_L(t) = \mathcal{L}^{-1}\{I_L(s)\} = \frac{V_A}{R} \left(1 - e^{-\left(\frac{R}{L}\right)t} \right) u(t)$$

10-14

The initial conditions of the capacitor are $i_c(0) = 0$, $v_c(0) = -\frac{V_A}{2}$.

Changing the circuit into s-domain and using KCL at $t > 0$, we can get:

$$\frac{\frac{V_A}{s} - V_C(s)}{R} - \frac{V_C(s)}{R} - I_C(s) = 0$$


Where $I_C(s) = C(V_C(s)s - v_c(0))$

Solving for $V_C(s)$, we can get

$$V_C(s) = V_A \left(\frac{1}{2s} - \frac{1}{s + \frac{2}{RC}} \right)$$

$$v_C(t) = \mathcal{L}^{-1}\{V_C(s)\} = \frac{V_A}{2} - V_A e^{-\frac{2}{RC}t}$$

10-20

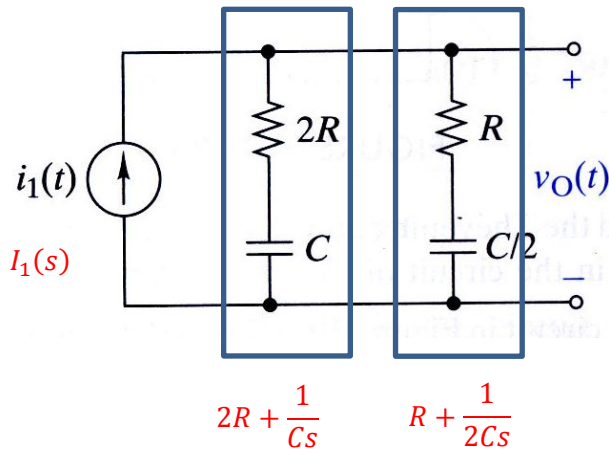


Change the circuit into s-domain and replace the elements by an equivalent impedance.

$$Z_{EQ} = \left(2R + \frac{1}{Cs} \right) \parallel \left(R + \frac{1}{2Cs} \right) = \frac{(2RCs + 1)(RCs + 2)}{3Cs(RCs + 1)}$$

$$V_O(s) = Z_{EQ} I_1(s) = \frac{(2RCs + 1)(RCs + 2)}{3Cs(RCs + 1)} I_1(s)$$

10-22 By voltage division


$$V_{Rzs}(s) = \frac{R \cdot V_S(s)}{\frac{1}{C \cdot s + \frac{1}{L \cdot s}} + R} = \frac{R \cdot V_S(s) \cdot (L \cdot C \cdot s^2 + 1)}{R \cdot L \cdot C \cdot s^2 + L \cdot s + R} = \frac{\left(s^2 + \frac{1}{L \cdot C}\right) \cdot V_S(s)}{s^2 + \frac{s}{R \cdot C} + \frac{1}{L \cdot C}}$$
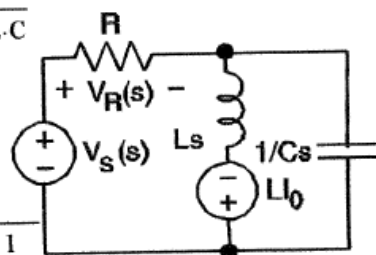
$$V_{Rzi}(s) = \frac{\left(\frac{1}{C \cdot s + \frac{1}{R}}\right) \cdot L \cdot I_0}{L \cdot s + \left(\frac{1}{C \cdot s + \frac{1}{R}}\right)} = \frac{R \cdot L \cdot I_0}{R \cdot L \cdot C \cdot s^2 + L \cdot s + R} = \frac{\frac{I_0}{C}}{s^2 + \frac{s}{R \cdot C} + \frac{1}{L \cdot C}}$$


(b)

$$V_R = V_{Rzs} + V_{Rzi} = \frac{\left(s^2 + \frac{1}{LC}\right) V_S(s) + \frac{I_0}{C}}{s^2 + \frac{s}{RC} + \frac{1}{LC}} = \frac{\frac{15 * s^2 + 30000000}{s} + 10000}{s^2 + \frac{2000 * s}{3} + 2000000}$$

$$v_R(t) = \mathcal{L}^{-1}\{V_R(s)\} = 15u(t)$$

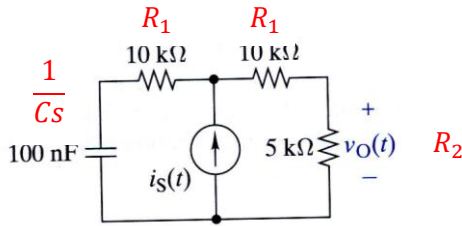10-24


Transforming the circuit into the s-domain and using current division, we can get

$$I_O(s) = \frac{\frac{1}{R_1 + R_2}}{\frac{1}{R_1 + R_2} + \frac{1}{R_1 + \frac{1}{Cs}}} I_S(s) = \frac{0.4(s + 1000)}{s + 400} I_S(s)$$


Where $I_S(s) = \mathcal{L}\{i_S(t)\} = 2.5 \frac{1}{s + 400}$.

$$I_O(s) = \frac{s + 1000}{(s + 400)^2} = \frac{1}{s + 400} + \frac{600}{(s + 400)^2}$$

$$i_O(t) = \mathcal{L}^{-1}\{I_O(s)\} = (e^{-400t} + 600te^{-400t})u(t)$$

The forced pole at $s = -400 \text{ rad/s}$, the natural pole at $s = -400 \text{ rad/s}$

10-32

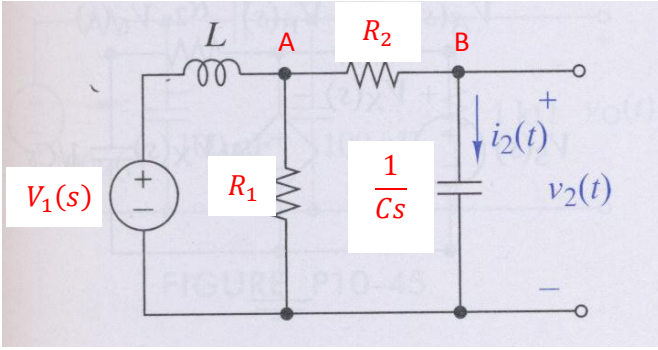

(a) Node-Voltage

Node A:

$$\left(\frac{1}{R_1} + \frac{1}{Ls} + \frac{1}{R_2}\right)V_A - \frac{1}{R_2}V_B = \frac{V_1}{Ls}$$

Node B:

$$-\frac{1}{R_2}V_A + \left(\frac{1}{R_2} + Cs\right)V_B = 0$$

$$\Delta(s) = \begin{vmatrix} \frac{1}{R_1} + \frac{1}{Ls} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + Cs \end{vmatrix} = \frac{LC(R_1 + R_2)s^2 + (L + CR_1R_2)s + R_1}{LR_1R_2s}$$

$$\Delta_B(s) = \begin{vmatrix} \frac{1}{R_1} + \frac{1}{Ls} + \frac{1}{R_2} & \frac{V_1}{Ls} \\ -\frac{1}{R_2} & 0 \end{vmatrix} = \frac{V_1}{LR_2s}$$

(b) Solve for $V_B(s)$ by Cramer's rule,

$$V_2(s) = V_B = \frac{\Delta_B(s)}{\Delta(s)} = \frac{R_1V_1}{LC(R_1 + R_2)s^2 + (L + CR_1R_2)s + R_1}$$

(c) The zeros of $\Delta(s)$ are natural poles:

$$s = \left(-\frac{1}{2}\right) \frac{L + CR_1R_2 \pm \sqrt{(L + CR_1R_2)^2 - 4LCR_1(R_1 + R_2)}}{LC(R_1 + R_2)}$$

The pole of $\Delta_B(s)$ is the forced pole $s=0$.

(d) Substitute the values into the equation, we can get

$$V_2(s) = \frac{7500}{s\left(\frac{s^2}{1000} + s + 500\right)}$$


$$v_2(t) = \mathcal{L}^{-1}\{V_2(s)\} = (15 - 15(\cos(500t) + \sin(500t))e^{-500t})u(t)$$

10-35 (a) Mesh-current eqs.

$$\begin{pmatrix} R_1 + \frac{1}{C_1 \cdot s} & \frac{-1}{C_1 \cdot s} \\ \frac{-1}{C_1 \cdot s} & R_2 + \frac{1}{C_1 \cdot s} + \frac{1}{C_2 \cdot s} \end{pmatrix} \cdot \begin{pmatrix} I_A(s) \\ I_B(s) \end{pmatrix} = \begin{pmatrix} V_1(s) \\ 0 \end{pmatrix}$$

(b)
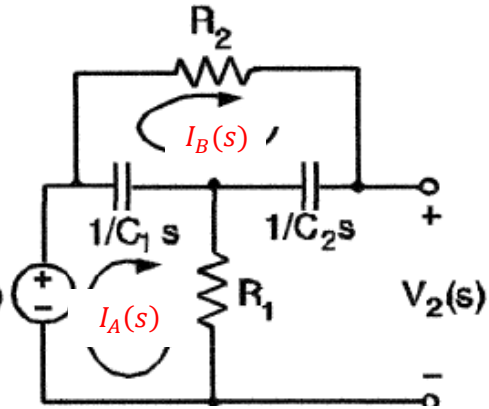
$$\Delta(s) = \frac{R_1 \cdot R_2 \cdot C_1 \cdot C_2 \cdot s^2 + (R_1 \cdot C_1 + R_2 \cdot C_2 + R_1 \cdot C_2) \cdot s + 1}{C_1 \cdot C_2 \cdot s^2} V_1(s)$$



$$\Delta_B = \begin{vmatrix} \frac{1}{R_1} + \frac{1}{C_1 s} & V_1 \\ -\frac{1}{C_1 s} & R_2 + \frac{1}{C_1 s} + \frac{1}{C_2 s} \end{vmatrix}$$

$$I_B(s) = \frac{\Delta_B(s)}{\Delta(s)} = \frac{C_2 s}{C_1 C_2 R_1 R_2 s^2 + (C_1 R_1 + C_2 R_1 + C_2 R_2) s + 1} V_1(s)$$

$$V_2(s) = V_1 - I_B R_2 = \frac{C_1 C_2 R_1 R_2 s^2 + (C_1 R_1 + C_2 R_1) s + 1}{C_1 C_2 R_1 R_2 s^2 + (C_1 R_1 + C_2 R_1 + C_2 R_2) s + 1} V_1(s)$$