

MAE140 Win12 HW8 Solutions


T R & T, 11.8, 11.9, 11.10, 11.11, 11.26, 11.28, 11.52, 11.64, 12.14, 12.56

11-8

$$T_1(s) = \frac{I_2(s)}{I_1(s)} = \frac{R}{3R + Ls}$$

Pole at $s = -3R/L$. Choosing $R = 500 \Omega$, $L = 3H$, we can get the pole at $s = -500$ rad/s. The answer is not unique.

11-9

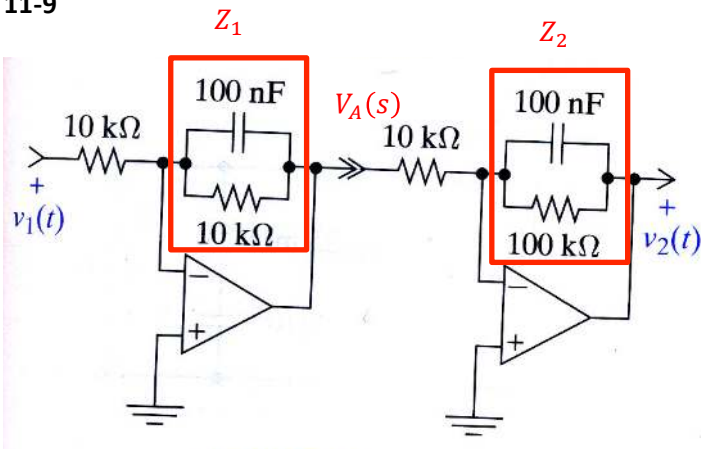

Transfer the circuit into s-domain and using the properties of inverting Amps. We can get

$$\frac{V_A}{V_1} = -\frac{Z_1}{10 \text{ k}\Omega}, \frac{V_2}{V_A} = -\frac{Z_2}{10 \text{ k}\Omega}$$


$$\text{Where } Z_1 = \frac{10 \text{ k}\Omega \cdot \frac{1}{100 \text{ nF} \cdot s}}{10 \text{ k}\Omega + \frac{1}{100 \text{ nF} \cdot s}}, Z_2 = \frac{100 \text{ k}\Omega \cdot \frac{1}{100 \text{ nF} \cdot s}}{100 \text{ k}\Omega + \frac{1}{100 \text{ nF} \cdot s}}$$

So we can obtain:

$$T_V(s) = \frac{V_2}{V_1} = \frac{Z_1 Z_2}{(10 \text{ k}\Omega)^2} = \frac{10^6}{(s + 100)(s + 1000)}$$

Poles at $s = -100$, $s = -1000$.

11-10

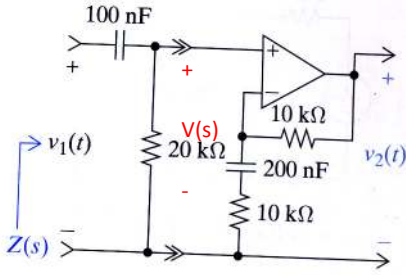

Transform the circuit into s-domain and get the transfer function.

$$T_1(s) = \frac{V(s)}{V_1(s)} = \frac{20k\Omega}{\frac{1}{s \cdot 100nF} + 20k\Omega}, T_2 = \frac{V_2(s)}{V(s)} = \frac{10k\Omega + \frac{1}{s \cdot 200nF} + 10k\Omega}{10k\Omega + \frac{1}{s \cdot 200nF}}$$

$$T_V(s) = T_1(s)T_2(s) = \frac{s(8 \times 10^{-6}s + 2 \times 10^{-3})}{(2 \times 10^{-3}s + 1)^2}$$

Poles: double pole at $s = -500$, Zeros at $s = 0$ and $s = -250$

11-11

$$Z(s) = 20k\Omega + \frac{1}{s \cdot 100nF} = \frac{2 \times 10^4 s + 10^{-7}}{s}$$

11-26

$$\frac{V_2(s)}{V_1(s)} = \frac{1 + s^2 LC}{1 + sRC + s^2 LC}$$

where $R = 100\Omega$, $C = 20\mu F$, $L = 25mH$.

$$T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \frac{1 + (j\omega)^2 LC}{1 + j\omega RC + (j\omega)^2 LC}$$

(a) $\omega = 225.08 \text{ rad/s}$, $\frac{V_2(j\omega)}{V_1(j\omega)} = 0.9079e^{-j24.79^\circ}$, $v_2(t) = 4.54 \cos(225.08t - 24.79^\circ)$.

(b) $\omega = 10 \text{ krad/s}$, $\frac{V_2(j\omega)}{V_1(j\omega)} = 0.9258e^{j22.20^\circ}$, $v_2(t) = 4.54 \cos(10kt + 22.20^\circ)$.

(c) $\omega = 0$, $v_2(t) = 5$.

11-28

$$\frac{I_2(s)}{I_1(s)} = -\frac{R_1}{R_1 + R_2 + sL}$$

When $\omega = 500 \text{ rad/s}$, $\frac{I_2(j\omega)}{I_1(j\omega)} = -0.199e^{-j5.71^\circ}$, $i_2(t) = 1.99 \cos(500t - 5.71^\circ)$

When $\omega = 5000 \text{ rad/s}$, $\frac{I_2(j\omega)}{I_1(j\omega)} = -0.1414e^{-j45^\circ}$ and $i_2(t) = 1.414 \cos(5000t - 45^\circ)$.

11-52

$$T_V(s) = \pm \frac{100(s + 1000)}{(s + 100)(s + 10,000)} = \mp T_1(s) \cdot T_2(s) = \mp \left(-\frac{100}{s + 100} \right) \left(\frac{s + 1000}{s + 10,000} \right)$$


Use a two-stage design.

$$T_1(s) = -\frac{100}{s+100} = -\frac{\frac{1}{R_1}}{\frac{1}{R_2} + C_2 \cdot s}$$

$$k_m := 10^{10}, R_1 = R_2 = \frac{k_m}{100} = 1 \times 10^8, C_2 = \frac{1}{k_m} = 1 \times 10^{-10}$$

$$T_2(s) = \frac{s+1000}{s+10,000} = -\frac{\frac{1}{R_1} + C_1 s}{\frac{1}{R_1} + \frac{1}{R_2} + C_1 \cdot s}$$
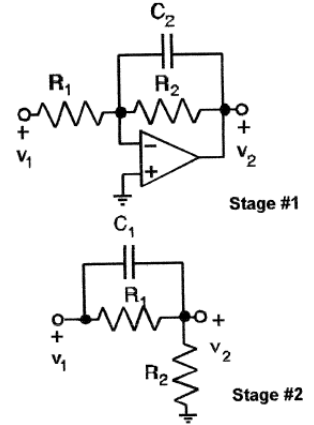
$$k_m := 10^{10}, R_1 = \frac{k_m}{1000} = 1 \times 10^7, R_2 = \frac{k_m}{10,000 - 1000} = \frac{1}{9} \times 10^7, C_1 = \frac{1}{k_m} = 1 \times 10^{-10}$$



11-64

(a) No.

(b) 1st stage: $T_1(s) = -\frac{R}{R + \frac{1}{Cs}}$, 2nd stage: $T_2(s) = -\frac{R \cdot \frac{1}{Cs}}{R + \frac{1}{Cs}}$

$$T_V(s) = \frac{sRC}{1 + sRC} + \frac{1}{1 + sRC} = 1$$

(c) Whatever the input, the output is the same as the input.

(d) It can be used as a voltage-follower. The output is the same as the input, and the input is not influenced by the loading.

12-14

$$T_V(s) = \left(\frac{\frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} \right) \left(\frac{R_4 + R_3}{R_4} \right) \left(\frac{R_2}{R_2 + \frac{1}{C_2 s}} \right) = \left(\frac{1/R_1 C_1}{s + 1/R_1 C_1} \right) \left(\frac{R_4 + R_3}{R_4} \right) \left(\frac{s}{s + 1/R_2 C_2} \right)$$

It can be seen that the two RC-constants $R_1 C_1$ and $R_2 C_2$ determine the cutoff frequencies.

We have $\omega_1 = \frac{1}{R_1 C_1} = 2500 \text{ rad/s}$, $\omega_2 = \frac{1}{R_2 C_2} = 100 \text{ rad/s}$

Since the gain is 30, we have $\frac{R_4 + R_3}{R_4} = 30$

Then choose the value of each item.

12-56

First-Order Filter Company:

$$T_V(s) = 9.2 \cdot \frac{1}{s \cdot 3.3k\Omega \cdot 3.3nF + 1}$$

Simply Filters, Ltd:

$$T_V(s) = \frac{68 + 8.2}{8.2} \frac{1}{s \cdot 3.3k\Omega \cdot 3.3nF + 1} = 9.3 \frac{1}{s \cdot 3.3k\Omega \cdot 3.3nF + 1}$$

The two circuits have the same transfer function. But the sensor drives the filter input with a $1k\Omega$ source resistance. So we choose the first circuit.