

A place to network and exchange ideas.

MAE 140, Winter 2014, HW #1 Solns:

problem 1-14:

Let IL stand for Incandescent Lamp, and CFL stand for Compact fluorescent lamp; then based on the problem statement, the following holds:

$$\text{IL: } \begin{cases} P_{IL} = 100 \text{ W} \\ V_{IL} = 120 \text{ V} \end{cases}, \quad \text{CFL: } \begin{cases} P_{CFL} = 16 \text{ W} \\ V_{CFL} = 120 \text{ V} \end{cases}$$

Moreover, provided the total time-duration, $T = 1000 \text{ hrs}$, and that electricity costs $C = 7.8 \text{ ¢/kWh}$, one can compute the following:

$$C_{IL} = P_{IL} \times T \times C = 100 \times 10^3 \times 7.8 \Rightarrow \boxed{C_{IL} = 780 \text{ ¢}}$$

100 kWh

$$C_{CFL} = P_{CFL} \times T \times C = 16 \times 10^3 \times 7.8 \Rightarrow \boxed{C_{CFL} = 124.8 \text{ ¢}}$$

16 kWh

Hence, comparing C_{IL} and C_{CFL} ; one infers that $C_{IL} - C_{CFL} = 655.2 \text{ ¢}$ and so CFL is 655.2 Cents cheaper compared to IL.

problem 1-16:

According to the problem statement, the maximum current that the fuse can tolerate is 5 A ; i.e., $i_{fuse} = 5 \text{ A}$.

Besides, each string has 25 bulbs each of which rated at 7 W , therefore, $P_{string} = 25 \times 7 \Rightarrow \boxed{P_{string} = 175 \text{ W}}$. On the other hand, provided that the string

A place to network and exchange ideas.

are connected to a NOR circuit, and that $i_{\text{NOR}} = 5 \text{ A}$, the maximum power can be computed as: $P_{\text{max}} = 120 \times 5 = 600 \text{ W}$ and therefore, minimum # of possible strings:

$$n_{\text{strings}} = \frac{P_{\text{max}}}{P_{\text{string}}} = \frac{600}{175} = 3.43.$$

Therefore, min number of strings = 3.

problem 1-22:

According to the problem statement and the current/voltage values provided for every device, we can compute the following, where P_i , v_i , and i_i stand for the power, voltage and current of the i^{th} device, respectively:

$$P_1 = v_1 i_1 = 15 \times -1 \Rightarrow P_1 = -15 \text{ W} < 0 \Rightarrow \text{Delivering power}$$

$$P_2 = v_2 i_2 = 5 \times 1 \Rightarrow P_2 = +5 \text{ W} > 0 \Rightarrow \text{Absorbing power}$$

$$P_3 = v_3 i_3 = 10 \times 2 \Rightarrow P_3 = +20 \text{ W} > 0 \Rightarrow \text{Delivering power}$$

$$P_4 = v_4 i_4 = -10 \times -1 \Rightarrow P_4 = +10 \text{ W} > 0 \Rightarrow \text{Absorbing power}$$

$$P_5 = v_5 i_5 = 20 \times -3 \Rightarrow P_5 = -60 \text{ W} < 0 \Rightarrow \text{Delivering power}$$

$$P_6 = v_6 i_6 = 20 \times 2 \Rightarrow P_6 = +40 \text{ W} > 0 \Rightarrow \text{Absorbing power}$$

Moreover one can perform the power balance as follows:

$$\sum_{i=1}^6 P_i = P_1 + P_2 + P_3 + P_4 + P_5 + P_6 = -15 + 5 + 20 + 10 - 60 + 40 = 0,$$

which further validates the computations.

A place to network and exchange ideas.

prob 2-10

Provided the informati in the proble statement, $R = 56 \text{ k}\Omega = 5.6 \times 10^4 \Omega$, in additi, $i = 2.2 \text{ mA} = 2.2 \times 10^{-3} \text{ A}$, and there fore voltage across the resistor: $V = Ri = (5.6 \times 10^4) \times (2.2 \times 10^{-3}) \Rightarrow \boxed{V = 123.2 \text{ V}}$.

prob 2-6:

According to figure P2-6 and the information therein:

$$i = 10 \text{ mA} = 10^{-2} \text{ A}, V = 100 \text{ V} \Rightarrow R_x = \frac{V}{i} = \frac{100}{10^{-2}} \Rightarrow \boxed{R_x = 10 \text{ k}\Omega}.$$

In additi, the power delivered to the resistor can be computed as follows:

$$P = Vi = 10^2 \times 10^{-2} \Rightarrow \boxed{P = 1 \text{ W}}.$$

prob 2-9:

According to the proble statement, $R = 100 \text{ k}\Omega = 10^5 \Omega$, in additi,

$P_{\text{max}} = 0.125 \text{ W}$; there fore, the maximum voltage can be computed as

follows:

$$P_{\text{max}} = \frac{V_{\text{max}}^2}{R} \Rightarrow V_{\text{max}} = \sqrt{P_{\text{max}} \cdot R} = \sqrt{0.125 \times 10^5} \Rightarrow \boxed{V_{\text{max}} = \pm 111.80 \text{ V}}.$$

A place to network and exchange ideas.

Problem 2-12:

Let R and T stand for the resistance and temperature, respectively. Then, according to the problem statement we know:

$$\begin{cases} R_1 = 5 \times 10^3 \Omega \\ T_1 = 25^\circ \text{C} \end{cases} \quad \begin{cases} R_2 = 340 \Omega \\ T_2 = 100^\circ \text{C} \end{cases}$$

and that there is a linear relationship between R and T . Therefore, in other words, we are looking for unknown parameters, a and b in $R = aT + b$ equation. Provided, R_1, T_1 & R_2, T_2 values we can perform the following:

$$\begin{cases} R_1 = aT_1 + b \\ R_2 = aT_2 + b \end{cases} \Rightarrow \begin{cases} 5 \times 10^3 = 25a + b \\ 340 = 100a + b \end{cases} \Rightarrow a = \frac{340 - 5 \times 10^3}{75}$$

$$\Rightarrow a = -62.133 \Rightarrow R_1 = -62.133 T_1 + b \Rightarrow b = 5 \times 10^3 + 62.133 \times 25$$

$$\Rightarrow b = 6.55 \times 10^3$$


therefore, $R = -62.133 T + 6.55 \times 10^3$. Provided this latter eq'n, we

can find T^* at which $R = 10^3 \Omega$:

$$10^3 = -62.133 T^* + 6.55 \times 10^3 \Rightarrow T^* = \frac{5.55 \times 10^3}{62.133} \Rightarrow T^* = 89.32^\circ \text{C}$$

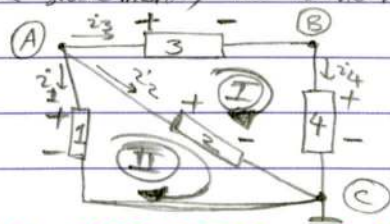Problem 2-15:

According to the problem statement, the considered circuit is as follows:



SOCIETY for INDUSTRIAL and APPLIED MATHEMATICS

A place to network and exchange ideas.

(a) The nodes on this circuit are $\textcircled{A}$, $\textcircled{B}$ and $\textcircled{C}$. In addition we have drawn loops $\textcircled{I}$ and $\textcircled{II}$ on this circuit.

(b) According to the def'n of elements be connected in series or parallel, it can be observed that:

Elements 3 and 4 are connected in series.

Elements 1 and 2 are connected in parallel.

Element 1 is in parallel w/ the equivalent element of 3 and 4.

Element 2 is in parallel w/ the equivalent element of 3 and 4.

(c) We shall first write KCL eqns for each node, $\textcircled{A}$, $\textcircled{B}$, $\textcircled{C}$ as follows:

$$\text{node } \textcircled{A}: i_1 + i_2 + i_3 = 0,$$

$$\text{node } \textcircled{B}: i_3 - i_4 = 0,$$

$$\text{node } \textcircled{C}: i_4 + i_2 + i_1 = 0.$$

Referring to the circuit and provided the signs assigned to each element, KVL eqns can be written for loops $\textcircled{I}$ and $\textcircled{II}$ as follows:

$$\text{loop } \textcircled{I}: V_3 + V_4 - V_2 = 0,$$


$$\text{loop } \textcircled{II}: V_2 - V_1 = 0,$$

where V_i denotes the voltage across the element i .


A place to network and exchange ideas.

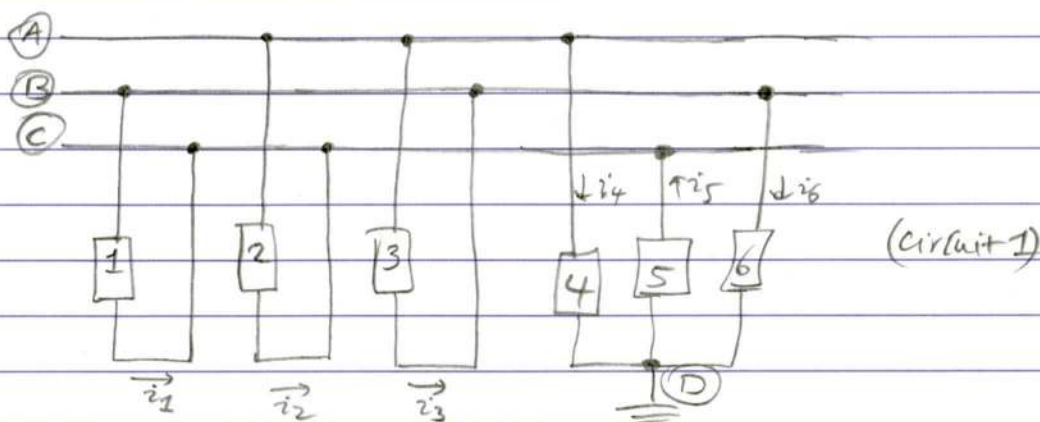problem 2-20:

let us first recall the circuit provided in Fig. P2-20:



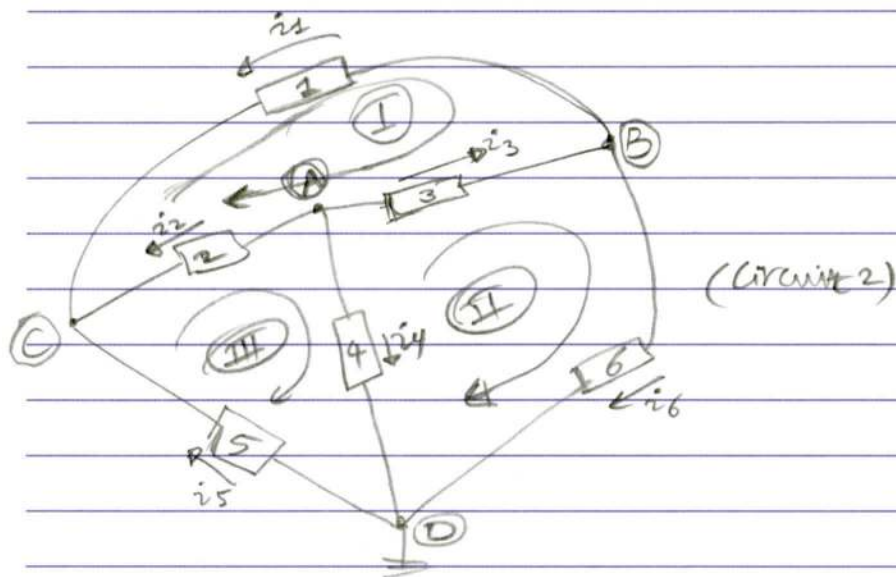then, by rearranging different elements of this circuit, in order to avoid overcrossing of various wires, we obtain the following circuit:



In the rest of our analysis, we shall focus on Circuit 2, provided circuits 1 and 2 are equivalent.

(a) Referring to Circuit 2, our nodes are A, B, C and D; in addition, we consider loops I, II and III.

SOCIETY for INDUSTRIAL and APPLIED MATHEMATICS

A place to network and exchange ideas.

(b) KCL eqns for our designated nodes yield:

$$\text{node (A): } i_2 + i_3 + i_4 = 0$$

$$\text{node (B): } i_1 + i_6 = i_3$$

$$\text{node (C): } i_1 + i_2 + i_5 = 0$$

$$\text{node (D): } i_4 + i_6 = i_5$$

(c) Given $i_1 = -20\text{mA}$, $i_2 = -12\text{mA}$, and $i_3 = 50\text{mA}$ and by KCL eqns obtained in step (b), we find i_4 , i_5 and i_6 as follows:

$$i_2 + i_3 + i_4 = 0 \Rightarrow -12 + 50 + i_4 = 0 \Rightarrow i_4 = -38\text{mA}$$


$$i_1 + i_6 = i_3 \Rightarrow -20 + i_6 = 50 \Rightarrow i_6 = 70\text{mA}$$

$$i_1 + i_2 + i_5 = 0 \Rightarrow -20 - 12 + i_5 = 0 \Rightarrow i_5 = 32\text{mA}$$

(d) Provided our rearrangement on circuit 1 which resulted in circuit 2, we conclude that these two circuits are equivalent. On the other hand, it is easy to verify that Circuit 2 and the one drawn in Fig. P2-17 are equivalent; therefore, we conclude that circuit 1, i.e., Fig. P2-20 and Fig. P2-17 are indeed identical.

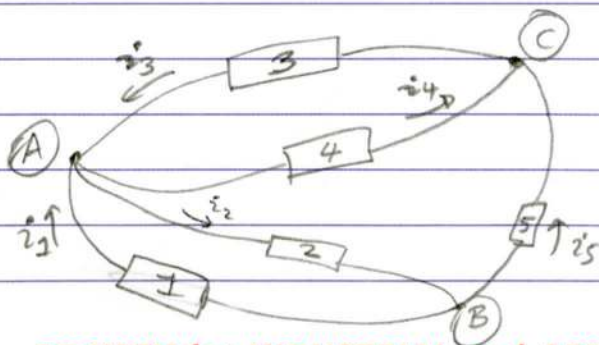Problem 2-22:

Referring to the circuit drawn in Fig P2-22, that is recalled below:



A place to network and exchange ideas.

we first write KCL eqns associated to each node A, B and C:

$$\begin{cases} \text{node A: } i_3 + i_1 - i_2 - i_4 = 0, \\ \text{node B: } i_2 - i_1 - i_5 = 0, \\ \text{node C: } i_4 + i_5 - i_3 = 0, \end{cases}$$

then, given $i_1 = 25 \text{ mA}$, $i_2 = 10 \text{ mA}$ and $i_3 = -15 \text{ mA}$, we obtain i_4 and i_5 as follows:

$$\begin{cases} i_3 + i_1 - i_2 - i_4 = 0 \Rightarrow -15 + 25 - 10 - i_4 = 0 \Rightarrow i_4 = 0 \text{ mA} \\ i_2 - i_1 - i_5 = 0 \Rightarrow 10 - 25 - i_5 = 0 \Rightarrow i_5 = -15 \text{ mA} \\ i_4 + i_5 - i_3 = 0 \Rightarrow 0 + (-15) - (-15) = 0 \checkmark \end{cases}$$



END of HW #1 solns