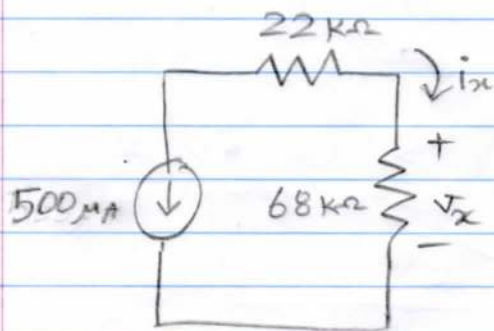


MAE 140
HW #2
Winter 2014


2-25



$$i_x = -500 \mu\text{A}$$

$$v_x = (68 \text{ k}\Omega) \times (i_x) = 68 \times 10^3 \times (-500) \times 10^{-6} = -34 \text{ V}$$

2-28

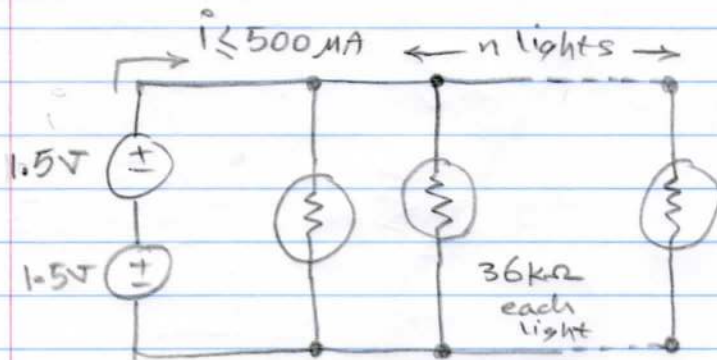

$$V_{\text{total}} = 1.5 + 1.5 = 3 \text{ V}$$

$$i_{\text{max}} = 500 \mu\text{A}$$

$$V_{\text{total}} = R_{\text{eq}} i_{\text{max}} \Rightarrow R_{\text{eq}} = \frac{3}{500 \times 10^{-6}} = 6 \text{ k}\Omega$$


↓
Resistor equivalent of possible lights

Parallel of "n" resistors (R_{eq});

$$\frac{1}{R_{\text{eq}}} = \underbrace{\frac{1}{36 \text{ k}\Omega} + \frac{1}{36 \text{ k}\Omega} + \dots}_{n}$$

$$\Rightarrow \frac{1}{R_{\text{eq}}} = \frac{n}{36 \text{ k}\Omega} \xrightarrow{R_{\text{eq}} = 6 \text{ k}\Omega} n = 6$$

2-32

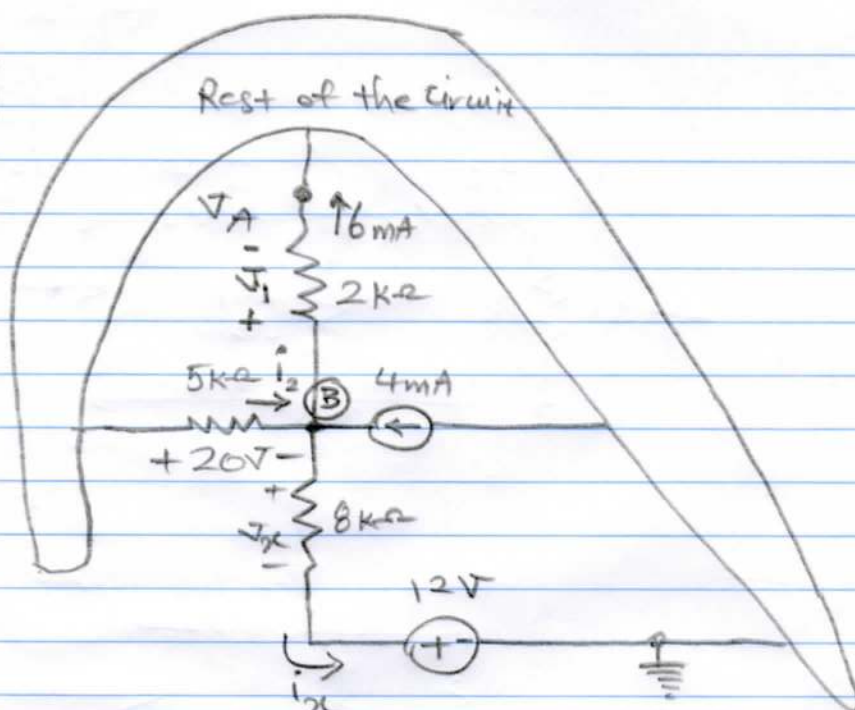

(a) Elements equations

$$\begin{cases} V_1 = 2k\Omega \times 6mA = 12V \\ 20V = 5k\Omega \times i_2 \Rightarrow i_2 = 4mA \\ V_x = 8k\Omega \times i_x \end{cases}$$

KCL at (B): $-6mA + i_2 + 4mA - i_x = 0 \Rightarrow i_x = 2mA$

Thus, $V_x = 8k\Omega \times 2mA = 16V$

(b) Sum of the currents into the rest of the circuit is as;




$$6mA - i_2 - 4mA + i_x = 6mA - 4mA - 4mA + 2mA = 0mA$$

(c) $V_1 = 12V \leftarrow$ this is voltage across the $2k\Omega$ resistor

V_A with respect to the ground ($\frac{1}{\equiv}$) is as;


$$V_A = -V_1 + V_x + 12 = -12 + 16 + 12 = 16V$$

2-36

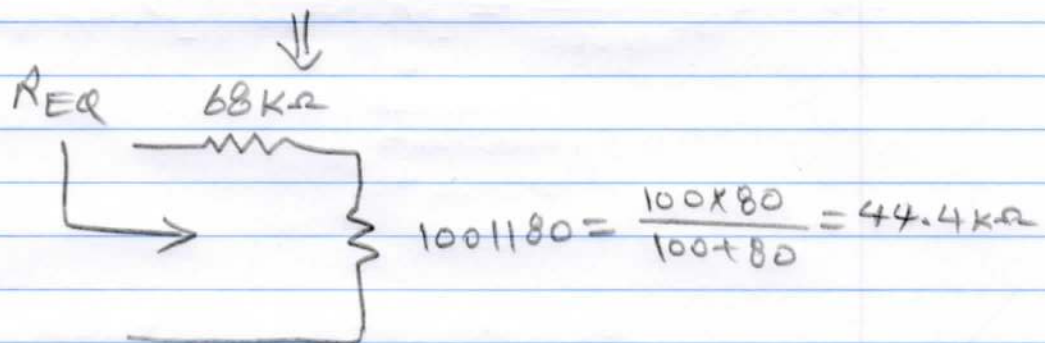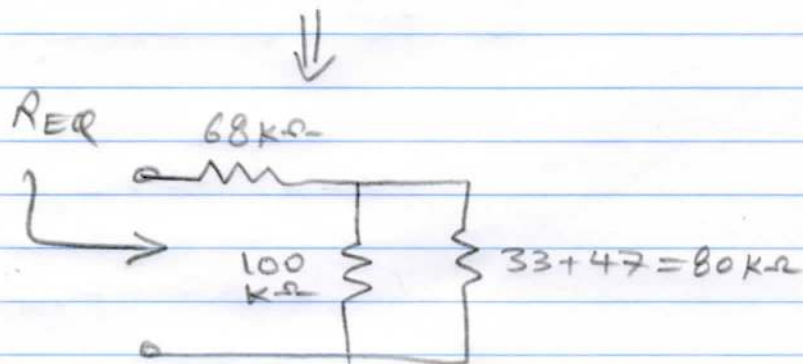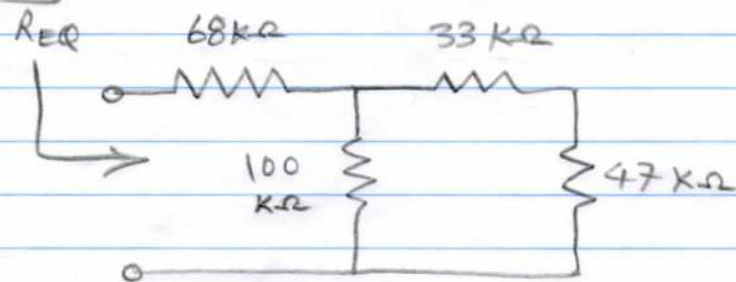

$$\Rightarrow R_{EQ} = 68 + 44.4 = 112.4\text{ k}\Omega$$


2-38

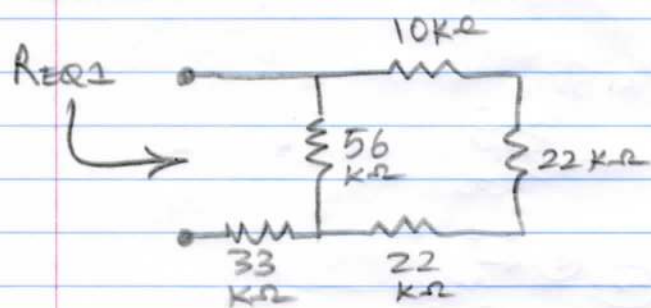

$$10 + 22 + 22 = 54\text{ k}\Omega$$

$$56 \parallel 54 = \frac{56 \times 54}{56 + 54} = 27.49\text{ k}\Omega$$







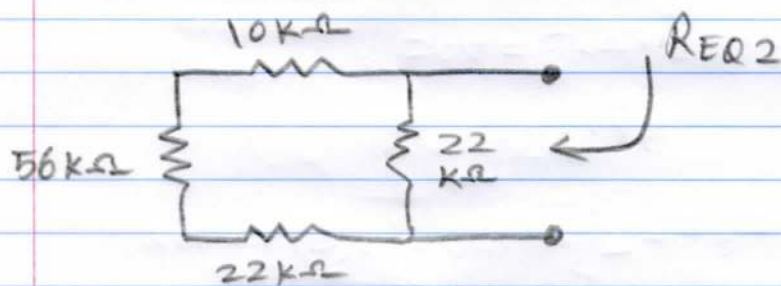
$$\Rightarrow R_{EQ1} = 27.49 + 33 = 60.49\text{ k}\Omega$$





$$56 + 10 + 22 = 88\text{ k}\Omega$$

$$\Rightarrow R_{EQ2} = 88 \parallel 22 = 17.6\text{ k}\Omega$$

2-43

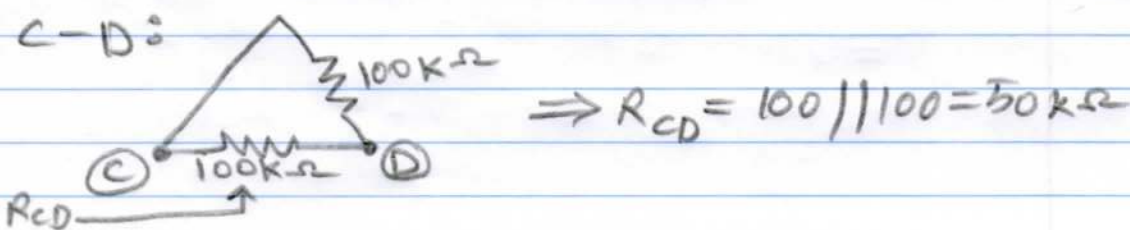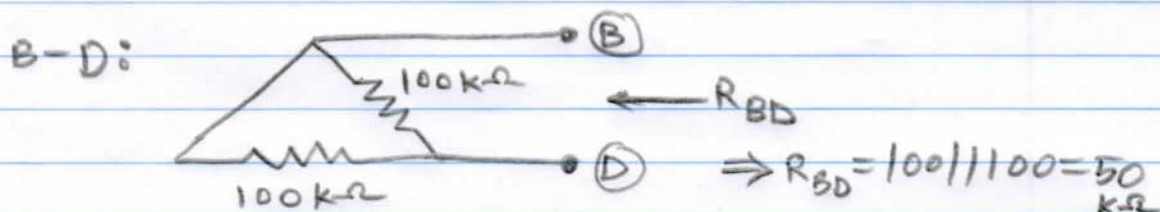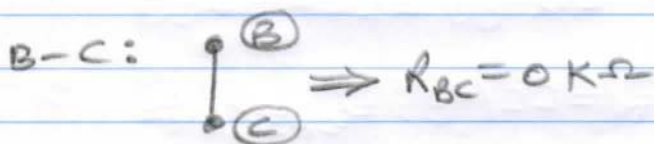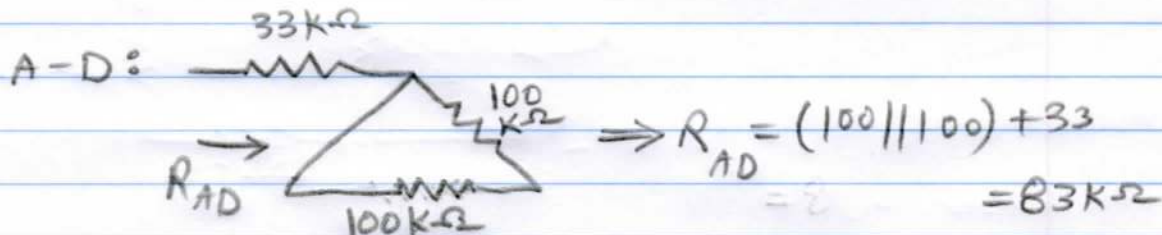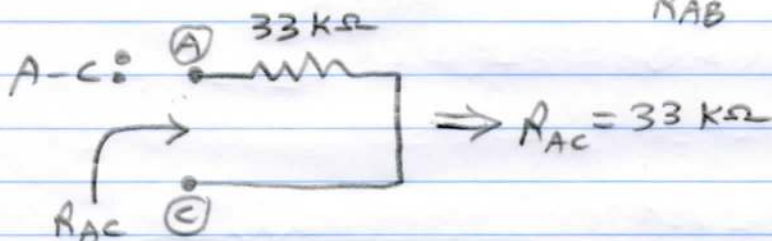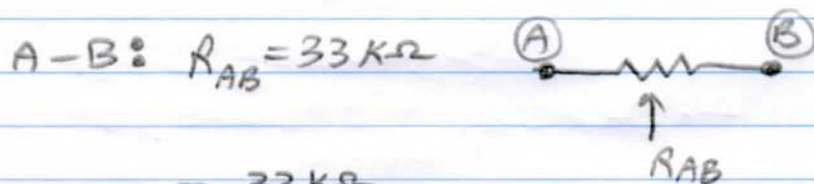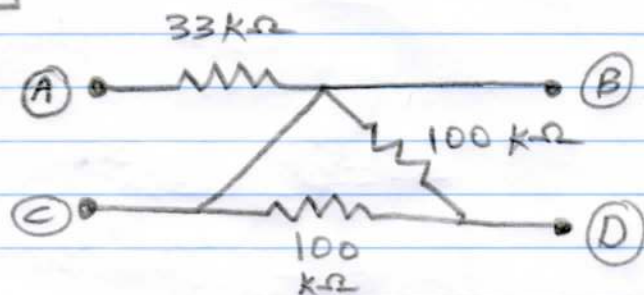



2-55

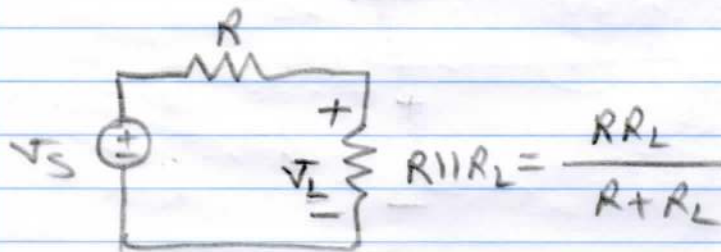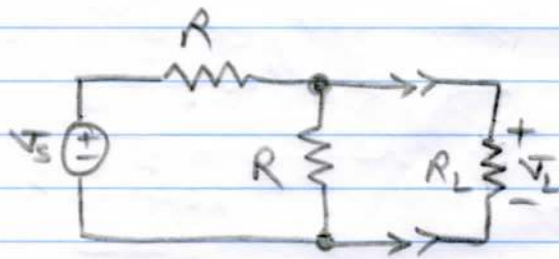

Voltage division rule:

$$V_L = \frac{\left(\frac{R R_L}{R + R_L} \right) (V_S)}{R + \frac{R R_L}{R + R_L}} = \frac{R_L V_S}{2 R_L + R}$$

2-60

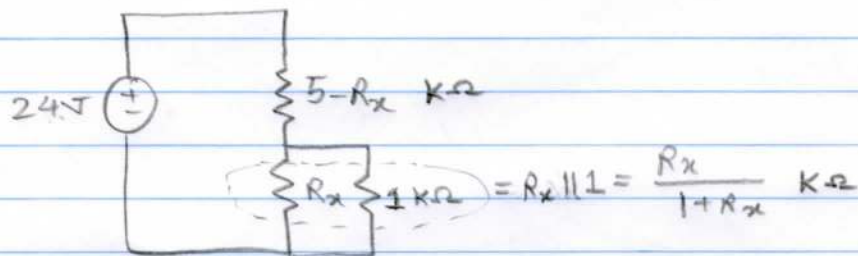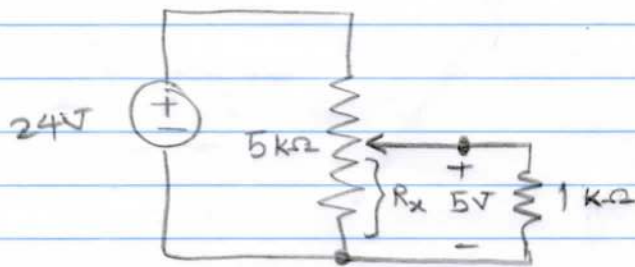



Use voltage division rule, we can obtain the voltage across $\frac{R_x}{1+R_x}$ which is 5V as;

$$V = \frac{\left(\frac{R_x}{1+R_x}\right)(24)}{5 - R_x + \frac{R_x}{1+R_x}} = 5$$

$$\Rightarrow 5 = \frac{\left(\frac{R_x}{1+R_x}\right)(24)}{5 - R_x + \frac{R_x}{1+R_x}}$$

$$\Rightarrow R_x \approx 2.34 \text{ k}\Omega$$

2-70

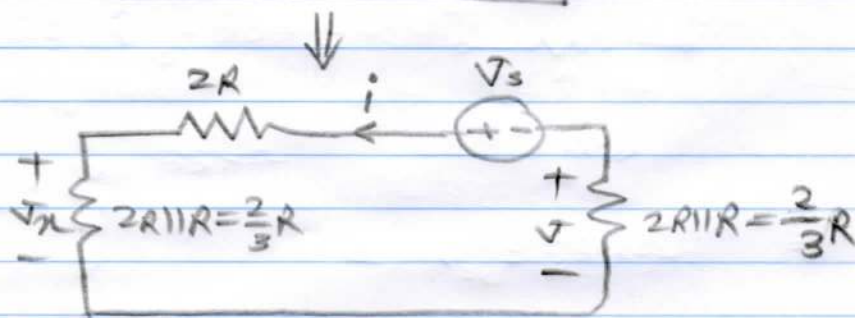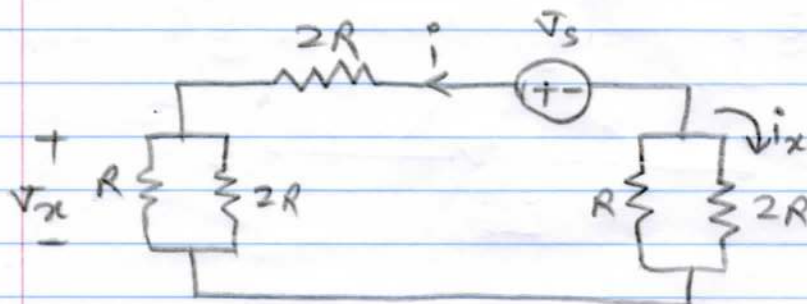



Voltage division:

$$V_x = \frac{2/3 R}{2R + 2/3 R + 2/3 R} \times V_s = 0.2 V_s$$

Note that $V = -V_x = -0.2 V_s$

$$\Rightarrow i_x = \frac{-0.2 V_s}{2R} = -\frac{V_s}{10R}$$

2-73

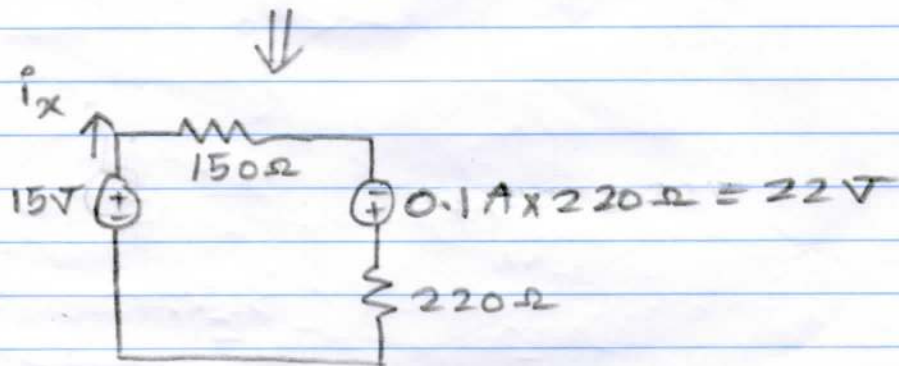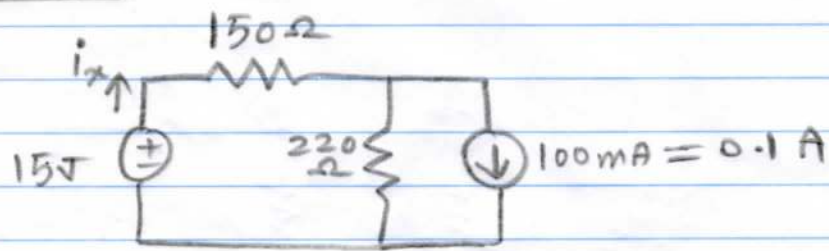

Using KVL:

$$-15 + 150i_x - 22 + 220i_x = 0$$

$$\Rightarrow i_x = 0.1\text{A} = 100\text{mA}$$