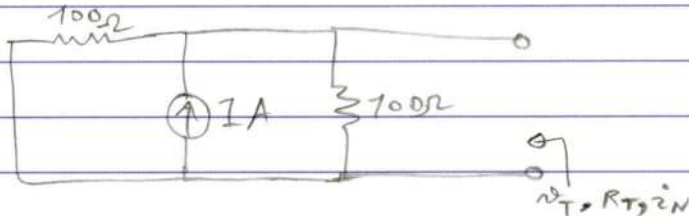


A place to network and exchange ideas.

MAE 140, Winter 2014, HW#3 Sol'n's:


Problem 3-48:

We would like to find Thevenin and Norton equivalent circuits for the following circuit:




Norton equivalent circuit:

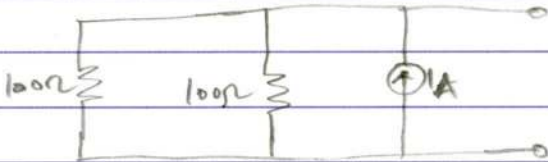In order to find Norton equivalent circuit, we swap the wires containing 1A current source and 100Ω resistance. Therefore, we obtain the following circuit:



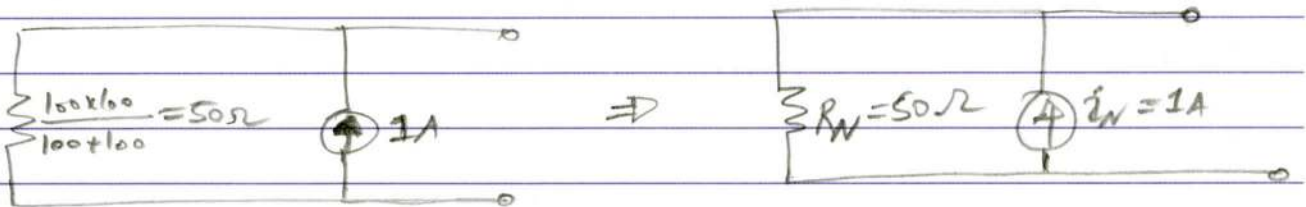in which the two 100Ω resistances are in parallel, therefore the equivalent resistance can be obtained as in the following circuit:




Indeed, this latter circuit represents the Norton equivalent circuit, w/ $R_N = 50\Omega$ and $I_N = 1A$.

Thevenin equivalent circuit:

In order to find Thevenin equivalent circuit, we shall apply

A place to network and exchange ideas.

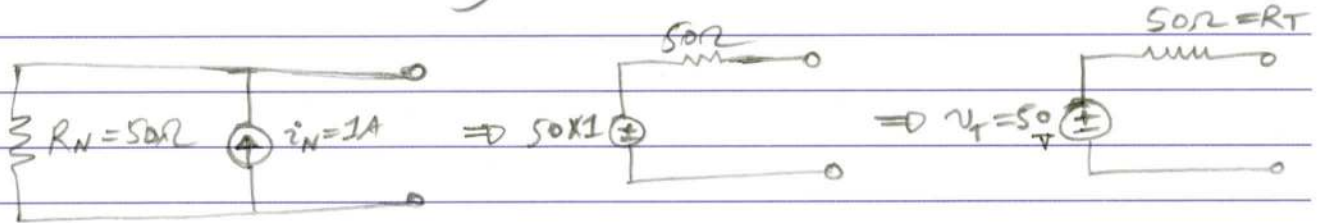Source transformation technique on the derived Norton equivalent circuit, which then results the following circuit:




Indeed, this last circuit represents Thévenin equivalent circuit w/

$$V_T = 50V \text{ and } R_T = 50\Omega.$$




problem 3-49:

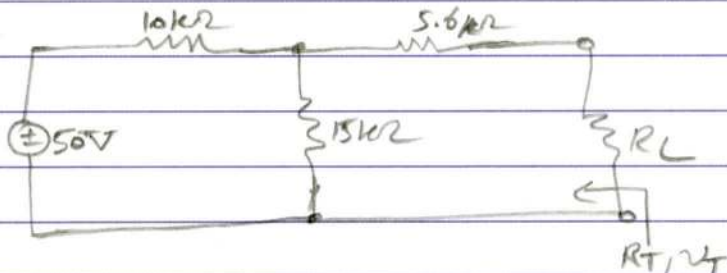
(a) we shall derive the Thévenin equivalent circuit for the following circuit, seen from R_L :



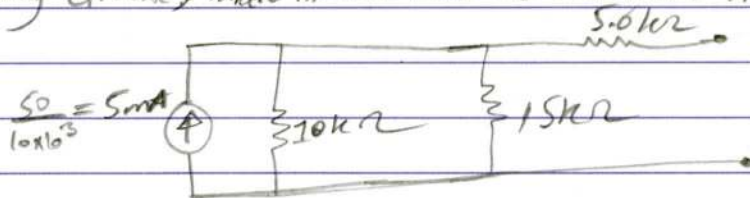we shall first apply source transformation technique where we obtain the following circuit, where we note that R_L is removed in order to avoid potential confusion:




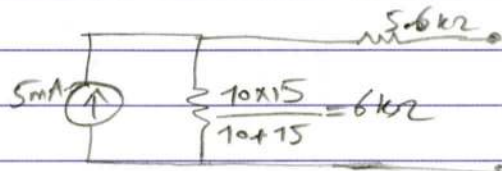Then, computing the equivalent resistance for 10kΩ and 15kΩ resistances, results in the following circuit:




A place to network and exchange ideas.

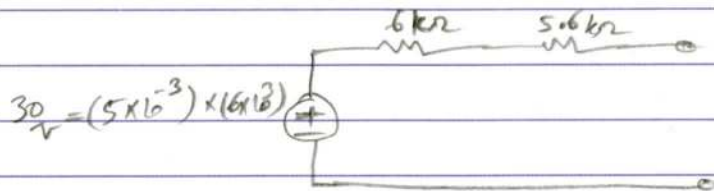Once more, applying source transformation technique results in the following circuit:




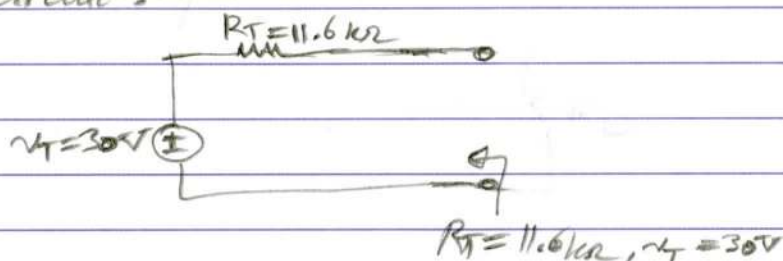where the provided $6k\Omega$ and $5.6k\Omega$ resistances are in series, we obtain the following circuit:



where the Thévenin equivalent circuit is drawn w/ $R_T = 11.6k\Omega$ and $V_T = 30V$.

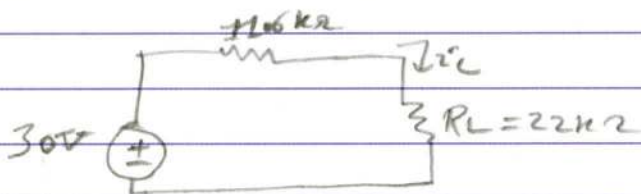
(b) For $R_L = 22k\Omega$, we can find i_L , referring to the Thévenin equivalent circuit obtained above:



$$\Rightarrow i_L = \frac{30V}{(22 + 11.6) \times 10^3} \Rightarrow \boxed{i_L = 0.893 \text{ mA}}$$

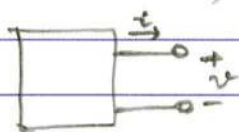problem 3-58


According to the problem statement, we know that for the circuit shown below:




we have $i = 1A$, when $v = 0V$, that is to say the short-circuit current is $1A$, as

A place to network and exchange ideas.

shown in the following circuit:

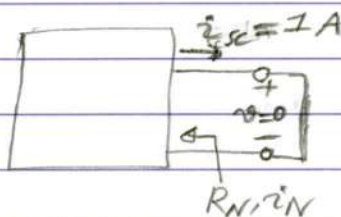

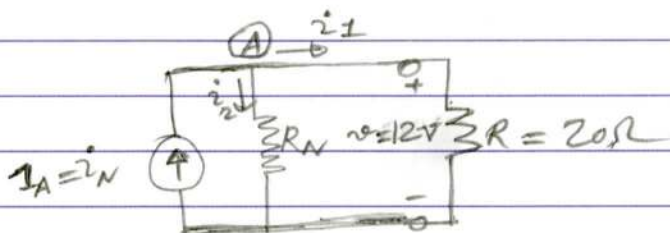This is indeed the value of the Norton equivalent of the circuit in the box, i.e., $i_N = i_{sc} = 1A$. We shall then find R_N according to the fact that $v = 12V$ when a 20Ω resistance is connected, this is shown in the following circuit:




First: given $R = 20\Omega$ and $v = 12V \Rightarrow i_1 = \frac{12}{20} \Rightarrow \boxed{i_1 = 0.6A}$

Second: KCL at node A: $i_N = i_1 + i_2 \Rightarrow i_2 = i_N - i_1 = 1 - 0.6 \Rightarrow \boxed{i_2 = 0.4A}$

Third: provided $R = 20\Omega$ and R_N are in parallel, thus the voltage drop across R_N is also $12V \Rightarrow R_N = \frac{12V}{i_2 = 0.4A} \Rightarrow \boxed{R_N = 30\Omega}$

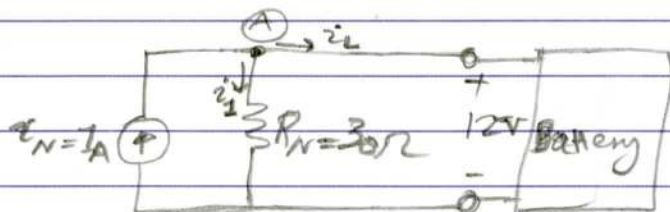Therefore, having obtained Norton equivalent circuit w/ $i_N = 1A$ and $R_N = 30\Omega$, we can find the current delivered to a $12V$ battery as in the following:




voltage drop across $R_N = 30\Omega$ is $12V \Rightarrow i_1 = \frac{12}{30} \Rightarrow \boxed{i_1 = 0.4A}$

KCL at node A: $i_L = i_N - i_1 \Rightarrow i_L = 1 - 0.4 \Rightarrow \boxed{i_L = 0.6A}$; which is the answer.

A place to network and exchange ideas.

problem 3-28

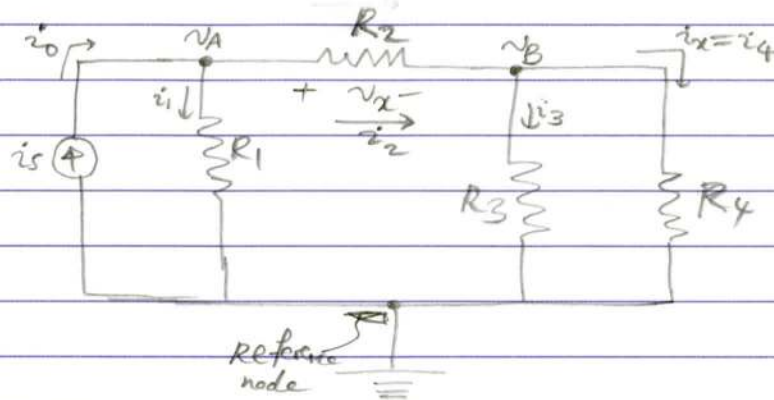(a) Given the following circuit, we shall formulate the node-voltage eq's as follows:



The reference node, node voltages and the currents associated to each branch are shown on the circuit. We shall then proceed as follows:

First: we note that there are 2 nodes in the circuit, A and B, therefore we shall employ the method by inspection in order to obtain the final result. In order to do so, we need to develop conductance matrix $G = [G_{ij}]$ w/ the following properties:

(a) $G_{ii} =$ Sum of conductances connected to node i ,

(b) $G_{ij} = -$ Conductance b/w node i and node j .

Moreover, in $GV = i$ eq'n, the vector i constitutes current sources entering node i , and vector V constitutes the node voltages. In the next step, these points are elaborated.

Second:

$$GV = i \Rightarrow \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} i_5 \\ 0 \end{bmatrix}$$

↑ provided i_s enters node A and no current source enters node B.

inspecting the circuit:

$$\begin{cases} G_{11} = \frac{1}{R_1} + \frac{1}{R_2} & G_{12} = -\frac{1}{R_2} \\ G_{21} = -\frac{1}{R_2} & G_{22} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{cases} \Rightarrow G = \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix}$$

A place to network and exchange ideas.

$$\Rightarrow \underbrace{\begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & +(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}) \end{pmatrix}}_A \underbrace{\begin{pmatrix} v_A \\ v_B \end{pmatrix}}_x = \underbrace{\begin{pmatrix} i_s \\ 0 \end{pmatrix}}_b \quad (*)$$

(b) We then solve (*) for v_A and v_B , on this way we have used Cramer's rule† which is discussed below:

$$A = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & +(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}) \end{pmatrix} \Rightarrow \det(A) = + \left(\frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_1 R_4} + \frac{1}{R_2 R_3} + \frac{1}{R_2 R_4} \right)$$

$$A_A = \begin{pmatrix} i_s & -\frac{1}{R_2} \\ 0 & +(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}) \end{pmatrix} \Rightarrow \det(A_A) = +i_s \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$A_B = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & i_s \\ -\frac{1}{R_2} & 0 \end{pmatrix} \Rightarrow \det(A_B) = +i_s \left(\frac{1}{R_2} \right)$$

$$\Rightarrow v_A = \frac{\det(A_A)}{\det(A)} \Rightarrow v_A = i_s \left(\frac{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}{\frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_1 R_4} + \frac{1}{R_2 R_3} + \frac{1}{R_2 R_4}} \right)$$

and,

$$v_B = \frac{\det(A_B)}{\det(A)} \Rightarrow v_B = i_s \left(\frac{\frac{1}{R_2}}{\frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_1 R_4} + \frac{1}{R_2 R_3} + \frac{1}{R_2 R_4}} \right)$$

† We would like to note that Cramer's rule is employed here, nonetheless other approaches, e.g., Gauss-Jordan elimination, may be used, as well.

A place to network and exchange ideas.

(C) v_x and i_x can be then obtained as follows:


$$v_x = v_A - v_B \Rightarrow v_x = i_s \left(\frac{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} - \frac{1}{R_2}}{\frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_1 R_4} + \frac{1}{R_2 R_3} + \frac{1}{R_2 R_4}} \right)$$

$$\Rightarrow v_x = \left(\frac{\frac{1}{R_3} + \frac{1}{R_4}}{\frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_1 R_4} + \frac{1}{R_2 R_3} + \frac{1}{R_2 R_4}} \right) i_s$$

$$i_x = i_4 = \frac{v_B}{R_4} \Rightarrow i_x = i_s \left(\frac{\frac{1}{R_2 R_4}}{\frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_1 R_4} + \frac{1}{R_2 R_3} + \frac{1}{R_2 R_4}} \right)$$

problem 3-3

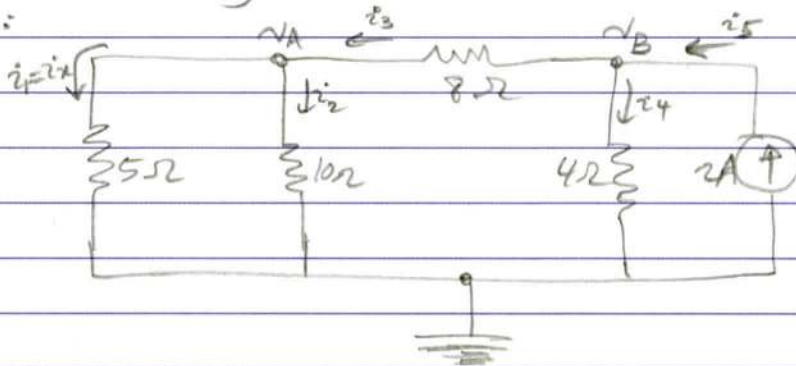(a) Given the following circuit, we shall formulate the node-voltage eqns as follows:



The reference node, node voltages, and the currents associated to each branch are shown on the circuit. We shall then proceed as follows:

First: we note that there are 2 nodes in the circuit, A and B, therefore we employ the method by inspection in order to obtain the final result. On this way, we need to develop matrix G as in $G V = i$. The properties of this matrix has been discussed in problem 3-2.

Solved:

$$GV = i \Rightarrow \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

provided there is no current source connected to A and there is 2A current source connected to B.

inspecting the circuit:

$$\begin{cases} G_{11} = \frac{1}{5} + \frac{1}{10} + \frac{1}{8} = \frac{17}{40} & G_{12} = -\frac{1}{8} \\ G_{21} = -\frac{1}{8} & G_{22} = \frac{1}{8} + \frac{1}{4} = \frac{3}{8} \end{cases}$$

$$\Rightarrow G = \begin{bmatrix} \frac{17}{40} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{3}{8} \end{bmatrix}; v = \begin{bmatrix} v_A \\ v_B \end{bmatrix}; i = \begin{bmatrix} 0 \\ 2 \end{bmatrix}$$

$$\Rightarrow \underbrace{\begin{pmatrix} \frac{17}{40} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{3}{8} \end{pmatrix}}_A \underbrace{\begin{pmatrix} v_A \\ v_B \end{pmatrix}}_X = \underbrace{\begin{pmatrix} 0 \\ 2 \end{pmatrix}}_b \quad (*)$$

(b) we then solve (*) for v_A and v_B , by using Cramer's rule, as discussed below:

$$A = \begin{pmatrix} \frac{17}{40} & -\frac{1}{8} \\ -\frac{1}{8} & \frac{3}{8} \end{pmatrix} \Rightarrow \det(A) = \frac{17}{40} \times \frac{3}{8} - \left(-\frac{1}{8}\right)\left(-\frac{1}{8}\right) \Rightarrow \boxed{\det(A) = \frac{23}{160}}$$

$$A_A = \begin{pmatrix} 0 & -\frac{1}{8} \\ 2 & \frac{3}{8} \end{pmatrix} \Rightarrow \boxed{\det(A_A) = \frac{1}{4}} \quad A_B = \begin{pmatrix} \frac{17}{40} & 0 \\ -\frac{1}{8} & 2 \end{pmatrix} \Rightarrow \boxed{\det(A_B) = \frac{17}{20}}$$

$$\Rightarrow v_A = \frac{\det(A_A)}{\det(A)} = \frac{1/4}{23/160} \Rightarrow \boxed{v_A = \frac{40}{23} \text{ V}}$$

and,

$$v_B = \frac{\det(A_B)}{\det(A)} = \frac{17/20}{23/160} \Rightarrow \boxed{v_B = \frac{136}{23} \text{ V}}$$

A place to network and exchange ideas.


(c) v_x and i_x can be then obtained as follows:

$$v_x = v_B - 0 = 0 \quad \boxed{v_x = \frac{136}{23} \text{ V}}$$

$$i_x = i_1 = \frac{v_A}{5} = \frac{40}{23} \times \frac{1}{5} = 0 \quad \boxed{i_x = \frac{8}{23} \text{ A}}$$

problem 3-5:

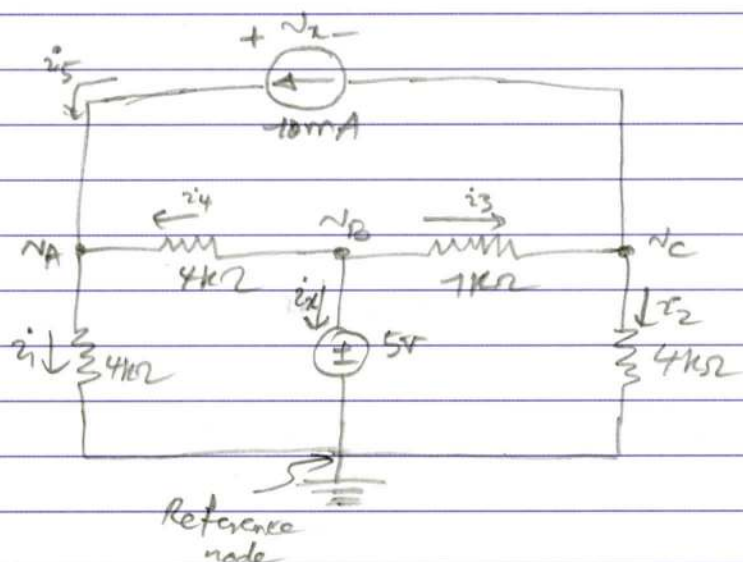(a) Given the following circuit, we shall formulate the node-voltage eqns as follows:



The reference node, node voltages, and the currents associated to each branch are shown on the circuit. We note that provided there is a voltage source of 5V in the circuit, we still refer to the second method, i.e., we consider $v_B = 5\text{V}$ in our subsequent analysis, as discussed in the following:

First: we derive Gv=i eq'n for nodes A, B, and C, considering i_x as our current source leaving node B. Therefore, we obtain:

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} 10\text{m} \\ -i_x \\ -10\text{m} \end{bmatrix}$$

$$\begin{aligned} G_{11} &= \frac{1}{4k} + \frac{1}{4k}; & G_{12} &= -\frac{1}{4k}; & G_{13} &= 0 \\ G_{21} &= -\frac{1}{4k}; & G_{22} &= \frac{1}{4k} + \frac{1}{1k} + 0.5; & G_{23} &= -\frac{1}{1k} \\ G_{31} &= 0; & G_{32} &= -\frac{1}{1k}; & G_{33} &= \frac{1}{1k} + \frac{1}{4k} \end{aligned}$$

and $v_B = 5\text{V}$.

A place to network and exchange ideas.

Accordingly, we shall obtain the following eqns:

$$\begin{cases} \left(\frac{1}{4k} + \frac{1}{4k}\right) V_A + \left(-\frac{1}{4k}\right) 5 = 10 \text{ m} \\ -\frac{1}{4k} V_A + \left(\frac{1}{4k} + \frac{1}{1k}\right) 5 - \frac{1}{1k} V_C = -i_x \\ \left(-\frac{1}{1k}\right) 5 + \left(\frac{1}{1k} + \frac{1}{4k}\right) V_C = -10 \text{ m} \end{cases} \Rightarrow \begin{cases} \left(\frac{1}{4k} + \frac{1}{4k}\right) V_A = 10 \text{ m} + \frac{5}{4} \text{ m} \quad (*) \\ \left(\frac{1}{1k} + \frac{1}{4k}\right) V_C = -10 \text{ m} + 5 \text{ m} \quad (**) \\ i_x = \left[V_C + \frac{1}{4} V_A - \left(\frac{1}{4} + 1\right) 5 \right]_{\text{mA}} \quad (***) \end{cases}$$

Therefore, provided eqns (*) and (**), we get the following matrix form, wherein we have simplified both RHS and LHS of the eqns:

$$\Rightarrow \underbrace{\begin{pmatrix} 0.5 & 0 \\ 0 & 1.25 \end{pmatrix}}_A \underbrace{\begin{pmatrix} V_A \\ V_C \end{pmatrix}}_x = \underbrace{\begin{pmatrix} 17.25 \\ -5 \end{pmatrix}}_b \quad (*)$$

(b) We then solve (*) for V_A and V_C :

$$V_A = \frac{17.25}{0.5} = 2 \times 17.25 \Rightarrow \boxed{V_A = 22.5 \text{ V}}$$

$$V_C = \frac{-5}{1.25} \Rightarrow \boxed{V_C = -4 \text{ V}}$$

(c) V_x and i_x can be then obtained as follows:

$$V_x = V_A - V_C = 22.5 - (-4) \Rightarrow \boxed{V_x = 26.5 \text{ V}}$$

recalling (***) for i_x :


$$i_x = \left[V_C + \frac{1}{4} V_A - 5 \left(1 + \frac{1}{4}\right) \right]_{\text{mA}} = \left[-4 + \frac{1}{4} (22.5) - 5 \left(\frac{5}{4}\right) \right]_{\text{mA}}$$

$$\Rightarrow \boxed{i_x = -4.625 \text{ mA}}$$

A place to network and exchange ideas.

problem 3-60

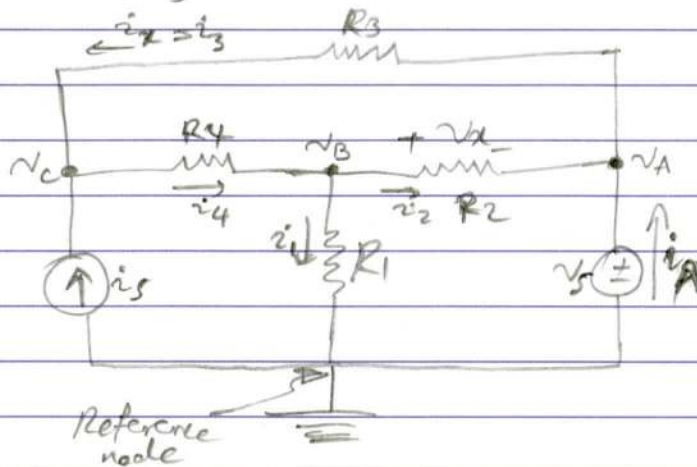(a) Given the following circuit, we shall formulate the node-voltage eqns as follows:



The reference node, node voltages, and the currents associated to each branch are shown on the circuit. We also note that provided there is a voltage source of V_5 in the circuit, we shall refer to the second method, i.e., we consider $V_A = V_5$ in our subsequent analysis, as discussed in the following:

First: we derive G_{ij} eqn for nodes A, B, and C, considering i_A as the current source approaching node A. Therefore, one obtains:

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_A \\ 0 \\ i_S \end{bmatrix}$$

$G_{11} = \frac{1}{R_2} + \frac{1}{R_3}$; $G_{12} = -\frac{1}{R_2}$; $G_{13} = -\frac{1}{R_3}$;
 $G_{21} = -\frac{1}{R_2}$; $G_{22} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4}$;
 $G_{23} = -\frac{1}{R_4}$; $G_{31} = -\frac{1}{R_3}$; $G_{32} = -\frac{1}{R_4}$;
 $G_{33} = \frac{1}{R_3} + \frac{1}{R_4}$ and $V_A = V_5$

Accordingly, we shall obtain the following eqns:

$$\begin{cases} \left(\frac{1}{R_2} + \frac{1}{R_3}\right) V_5 - \frac{1}{R_2} V_B - \frac{1}{R_3} V_C = i_A \\ -\frac{1}{R_2} V_5 + \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4}\right) V_B - \frac{1}{R_4} V_C = 0 \\ -\frac{1}{R_3} V_5 - \frac{1}{R_4} V_B + \left(\frac{1}{R_3} + \frac{1}{R_4}\right) V_C = i_S \end{cases}$$

A place to network and exchange ideas.

where then by some rearrangement of terms, we shall obtain:

$$\left\{ \begin{aligned} \left(\frac{1}{R_2} + \frac{1}{R_3} \right) v_s - \frac{1}{R_2} v_B - \frac{1}{R_3} v_C &= i_A \quad (*) \\ \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) v_B - \frac{1}{R_4} v_C &= \frac{1}{R_2} v_s \quad (**) \\ -\frac{1}{R_4} v_B + \left(\frac{1}{R_3} + \frac{1}{R_4} \right) v_C &= i_s + \frac{1}{R_3} v_s \quad (***) \end{aligned} \right.$$

Therefore, writing eqns (*) and (***) in matrix form, we get:

$$\Rightarrow \underbrace{\begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_4} & \frac{1}{R_3} + \frac{1}{R_4} \end{pmatrix}}_A \underbrace{\begin{pmatrix} v_B \\ v_C \end{pmatrix}}_x = \underbrace{\begin{pmatrix} \frac{1}{R_2} v_s \\ i_s + \frac{1}{R_3} v_s \end{pmatrix}}_b \quad (*)$$

(b) Having derived (*) and for $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$, $v_s = 25 \text{ V}$ and $i_s = 1 \text{ mA}$, we solve for v_B and v_C

$$\begin{pmatrix} 3 \times 10^{-4} & -10^{-4} \\ -10^{-4} & 2 \times 10^{-4} \end{pmatrix} \begin{pmatrix} v_B \\ v_C \end{pmatrix} = \begin{pmatrix} 2.5 \times 10^{-3} \\ 10^{-3} + 2.5 \times 10^{-3} \end{pmatrix} = \begin{pmatrix} 2.5 \times 10^{-3} \\ 3.5 \times 10^{-3} \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} 3 & -1 \\ -1 & 2 \end{pmatrix} \begin{pmatrix} v_B \\ v_C \end{pmatrix} = \begin{pmatrix} 25 \\ 35 \end{pmatrix} \Rightarrow \begin{cases} v_B = 17 \text{ V} \\ v_C = 26 \text{ V} \end{cases}$$

where then referring to the circuit, i_x and v_x can be expressed as follows:


$$v_x = v_B - v_A = v_B - v_s = 17 - 25 \Rightarrow v_x = -8 \text{ V}$$

$$i_x = i_3 = \frac{v_A - v_C}{R_3} = \frac{25 - 26}{10 \times 10^3} \Rightarrow i_x = -0.1 \text{ mA}$$

A place to network and exchange ideas.

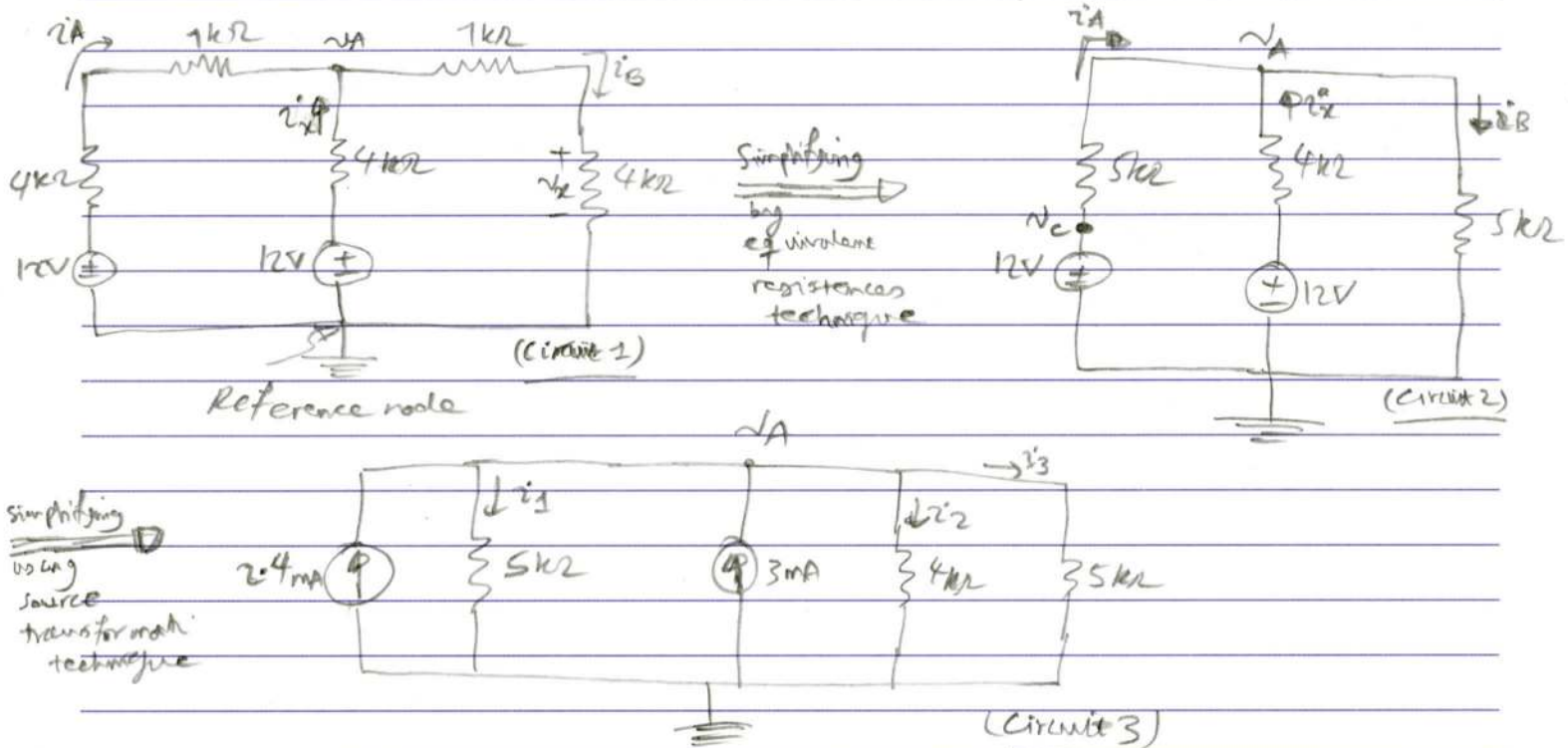problem 3-15:

For the following circuit, we shall first find V_A by formulating node-voltage eqs as discussed below, where we use source transformation technique to transform the voltage to current source as shown in the following figure.



Referring to circuit 3, we write KCL at node A:

$$\text{KCL at node A: } 2.4 \times 10^{-3} + 3 \times 10^{-3} = i_1 + i_2 + i_3$$

$$\Rightarrow 5.4 \times 10^{-3} = \frac{V_A}{5} \times 10^{-3} + \frac{V_A}{4} \times 10^{-3} + \frac{V_A}{5} \times 10^{-3} \Rightarrow 5.4 = V_A (0.2 + 0.25 + 0.2)$$

$$\Rightarrow V_A = \frac{5.4}{0.65} \Rightarrow \boxed{V_A = 8.308 \text{ V}}$$

Having found V_A , we then refer to circuit 2 to find i_A , i_x , and i_B , where we note $V_C = 12 \text{ V}$:

$$i_A = \frac{V_C - V_A}{5 \times 10^3} = \frac{12 - 8.308}{5 \times 10^3} \Rightarrow \boxed{i_A = 0.738 \text{ mA}} ; i_B = \frac{V_A}{5 \times 10^3} = \frac{8.308 \times 10^{-3}}{5} \Rightarrow \boxed{i_B = 1.66 \text{ mA}}$$

A place to network and exchange ideas.


Then, KCL at (A) on circuit 2: $i_x = i_B - i_A = 1.66 - 0.738 \Rightarrow \boxed{i_x = 0.922 \text{ mA}}$

At last, we shall find v_x , referring to circuit 1:

$$v_x = 4 \times 10^3 \times i_B = 4 \times 10^3 \times 1.66 \times 10^{-3} \Rightarrow \boxed{v_x = 6.64 \text{ V}}$$

problem 3-26:

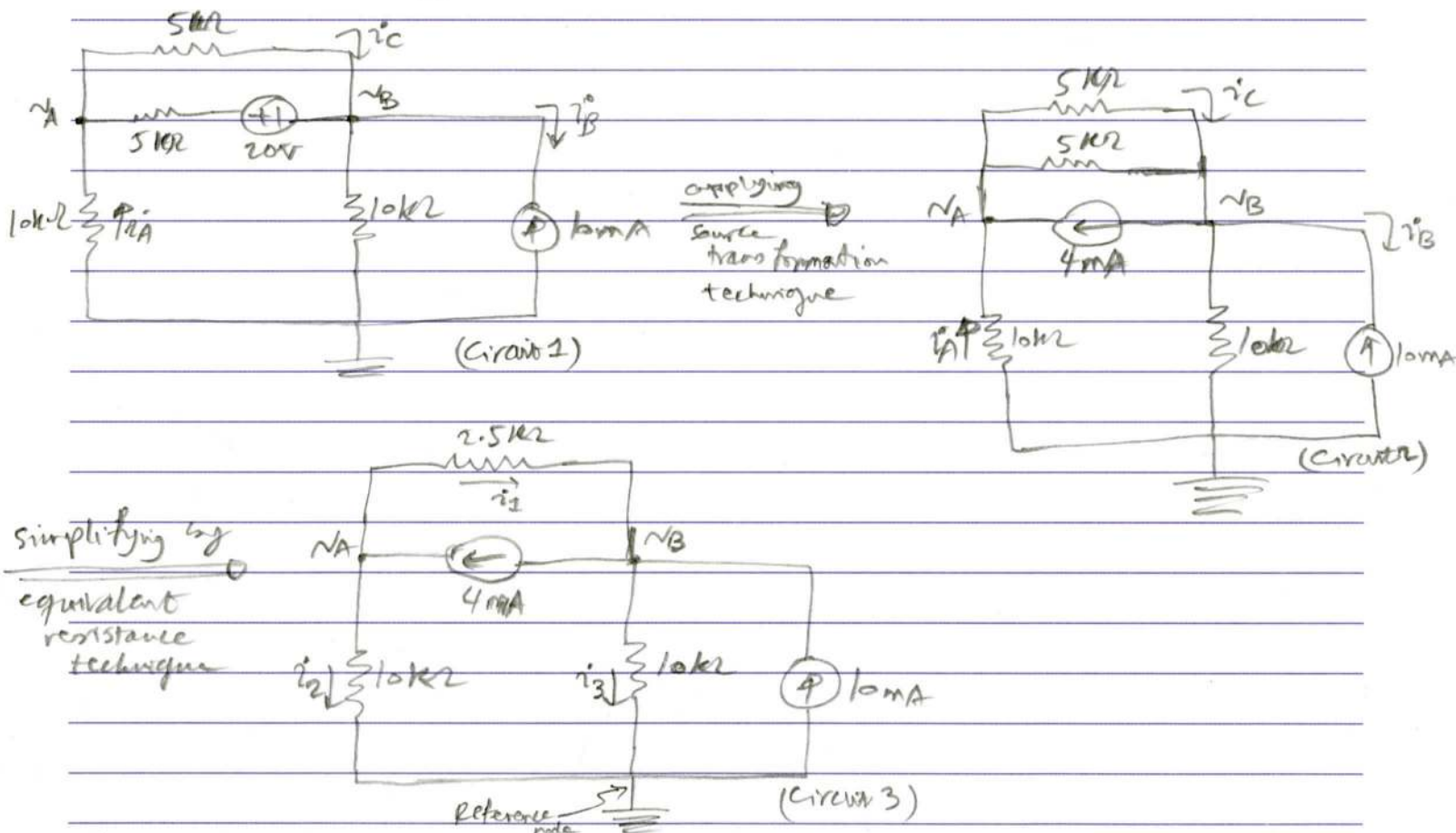(b) For the following circuit, we shall develop node-voltage eq's, where we have used the source transformation technique to transform the voltage source to a current source as shown in the following figure:



Referring to circuit 3: we note that there are 2 nodes in the circuit, A and B, therefore, we employ the method by inspection in order to obtain the final result. On this way,

A place to network and exchange ideas.

We need to develop matrix G as in $GV=i$. The properties of this matrix has been discussed in prob 3-2

$$GV=i \Rightarrow \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4 \times 10^{-3} \\ (10-4) \times 10^{-3} \end{bmatrix}$$

provided current source of 4mA approaching node A. And that total current of (10-4) mA approaching B

inspecting the circuit:

$$\begin{cases} G_{11} = \frac{1}{2.5k} + \frac{1}{10k} = 0.5 \times 10^{-3} \\ G_{12} = \frac{1}{2.5k} = 0.4 \times 10^{-3} \\ G_{21} = \frac{1}{2.5k} = 0.4 \times 10^{-3} \\ G_{22} = \frac{1}{2.5k} + \frac{1}{10k} = 0.5 \times 10^{-3} \end{cases}$$

which then in matrix form:

$$\underbrace{\begin{pmatrix} 5 & -4 \\ -4 & 5 \end{pmatrix}}_A \underbrace{\begin{pmatrix} V_A \\ V_B \end{pmatrix}}_x = \underbrace{\begin{pmatrix} 40 \\ +60 \end{pmatrix}}_b \quad (*)$$

(d) We then solve (*) for V_A, V_B , by using Cramer's rule to obtain V_A and V_B :

$$A = \begin{pmatrix} 5 & -4 \\ -4 & 5 \end{pmatrix} \Rightarrow \det(A) = 9$$

$$AB = \begin{pmatrix} 5 & 40 \\ -4 & 60 \end{pmatrix} \Rightarrow \det(AB) = 460$$

$$AA = \begin{pmatrix} 40 & -4 \\ +60 & 5 \end{pmatrix} \Rightarrow \det(AA) = 440$$

$$\Rightarrow V_A = \frac{\det(AA)}{\det(A)} = \frac{440}{9} \text{ V} \quad \text{and} \quad V_B = \frac{\det(AB)}{\det(A)} = \frac{460}{9} \text{ V}$$


At last, referring to Circuit 2:

$$i_B = -10 \text{ mA} \quad i_C = \frac{V_A - V_B}{5k} = \frac{440/9 - 460/9}{5 \times 10^3} \Rightarrow i_C = -0.44 \text{ mA}$$

$$i_A = \frac{0 - V_A}{10k} = \frac{-440/9}{10 \times 10^3} \Rightarrow i_A = -4.89 \text{ mA}$$

problem 3-27 s

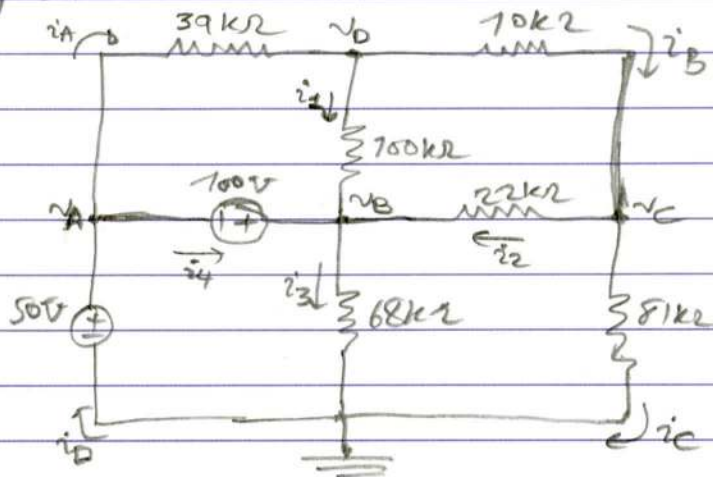- (c) For the circuit shown in the following figure, we shall formulate node-voltage eqns:



On this way, we use the first method where we know $V_A = 50V$ and that

$$V_B - V_A = 100 \Rightarrow V_B = 150V$$

First: We derive $G_{ij} = \frac{1}{R_{ij}}$ eqn for nodes A, B, C, and D, considering i_D and i_A as current sources approaching/leaving nodes A and B. Therefore, one obtains:

$$\begin{bmatrix} G_{11} & G_{12} & G_{13} & G_{14} \\ G_{21} & G_{22} & G_{23} & G_{24} \\ G_{31} & G_{32} & G_{33} & G_{34} \\ G_{41} & G_{42} & G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} i_D - i_A \\ i_A \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned} G_{11} &= \frac{1}{39k}, G_{12} = 0, G_{13} = 0, G_{14} = -\frac{1}{39k} \\ G_{21} &= 0, G_{22} = \frac{1}{100k} + \frac{1}{22k} + \frac{1}{68k} \\ G_{23} &= -\frac{1}{22k}, G_{24} = -\frac{1}{100k} \\ G_{31} &= 0, G_{32} = -\frac{1}{22k}, G_{33} = \frac{1}{22k} + \frac{1}{10k} + \frac{1}{81k} \\ G_{34} &= -\frac{1}{10k}, G_{41} = -\frac{1}{39k}, G_{42} = -\frac{1}{100k} \\ G_{43} &= -\frac{1}{10k}, G_{44} = \frac{1}{100k} + \frac{1}{10k} + \frac{1}{39k} \end{aligned}$$

and $V_A = 50, V_B = 150$

Accordingly, we shall obtain the following eqns:

$$\begin{cases} \frac{1}{39k} 50 - \frac{1}{39k} V_D = i_D - i_A \\ \left(\frac{1}{100k} + \frac{1}{22k} + \frac{1}{68k} \right) 150 = \frac{1}{22k} V_C - \frac{1}{100k} V_D = i_A \\ \left(\frac{1}{22k} \right) 150 + \left(\frac{1}{22k} + \frac{1}{10k} + \frac{1}{81k} \right) V_C - \frac{1}{10k} V_D = 0 \\ -\frac{1}{39k} 50 - \frac{1}{100k} 150 - \frac{1}{10k} V_C + \left(\frac{1}{100k} + \frac{1}{10k} + \frac{1}{39k} \right) V_D = 0 \end{cases}$$

A place to network and exchange ideas.

where by some rearrangement terms yields:

$$\left\{ \frac{1}{39k} 50 - \frac{1}{39k} V_D = 24 \right. \quad (*)$$

$$\left\{ \left(\frac{1}{100k} + \frac{1}{22k} + \frac{1}{81k} \right) 150 - \frac{1}{22k} V_C - \frac{1}{100k} V_D = 24 \right. \quad (**)$$

$$\left\{ -\frac{1}{22k} 150 + \left(\frac{1}{22k} + \frac{1}{10k} + \frac{1}{81k} \right) V_C - \frac{1}{10k} V_D = 0 \right. \quad (***)$$

$$\left\{ -\frac{1}{39k} 50 - \frac{1}{100k} 150 - \frac{1}{10k} V_C + \left(\frac{1}{100k} + \frac{1}{10k} + \frac{1}{39k} \right) V_D = 0 \right. \quad (****)$$

Eq'ns (**) and (****) can be written in a matrix form which results the following:

$$\begin{pmatrix} \frac{1}{22} + \frac{1}{10} + \frac{1}{81} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{100} + \frac{1}{10} + \frac{1}{39} \end{pmatrix} \begin{pmatrix} V_C \\ V_D \end{pmatrix} = \begin{pmatrix} \frac{+150}{22} \\ \frac{+150}{100} + \frac{50}{39} \end{pmatrix}$$

(d) we shall then solve the latest result of the previous section, using Cramer's rule:

$$A = \begin{pmatrix} \frac{1}{22} + \frac{1}{10} + \frac{1}{81} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{100} + \frac{1}{10} + \frac{1}{39} \end{pmatrix} \Rightarrow \boxed{\det(A) = 0.0114}$$

$$A_D = \begin{pmatrix} \frac{150}{22} & -\frac{1}{10} \\ \frac{150}{100} + \frac{50}{39} & \frac{1}{100} + \frac{1}{10} + \frac{1}{39} \end{pmatrix} \Rightarrow \boxed{\det(A_D) = 1.1208}$$

$$A_C = \begin{pmatrix} \frac{1}{22} + \frac{1}{10} + \frac{1}{81} & \frac{150}{22} \\ -\frac{1}{10} & \frac{150}{100} + \frac{50}{39} \end{pmatrix} \Rightarrow \boxed{\det(A_C) = 1.2028}$$

$$\Rightarrow V_D = \frac{\det(A_D)}{\det(A)} = \frac{1.1208}{0.0114} \Rightarrow \boxed{V_D = 98.32 \text{ V}}$$

and,

$$V_C = \frac{\det(A_C)}{\det(A)} = \frac{1.2028}{0.0114} \Rightarrow \boxed{V_C = 105.51 \text{ V}}$$

A place to network and exchange ideas.

which when recalling $V_A = 50V$, $V_B = 105V$, by referring to the circuit, we obtain:

$$i_A = \frac{V_A - V_D}{39 \times 10^3} = \frac{50 - 98.32}{39 \times 10^3} \Rightarrow i_A = \frac{-48.32}{39 \times 10^3} \Rightarrow \boxed{i_A = -1.24 \text{ mA}}$$

$$i_B = \frac{V_D - V_C}{10 \times 10^3} = \frac{98.32 - 105.51}{10 \times 10^3} \Rightarrow \boxed{i_B = -0.72 \text{ mA}}$$

$$i_C = \frac{V_E - 0}{81 \times 10^3} = \frac{105.51}{81 \times 10^3} \Rightarrow \boxed{i_C = 1.30 \text{ mA}}$$

$$i_3 = \frac{V_B - 0}{68 \times 10^3} = \frac{150}{68 \times 10^3} \Rightarrow \boxed{i_3 = 2.20 \text{ mA}}$$

$$i_1 = \frac{V_D - 150}{10^5} = \frac{98.32 - 150}{10^5} \Rightarrow \boxed{i_1 = -0.52 \text{ mA}}$$

$$i_2 = \frac{-150 + V_C}{22 \times 10^3} = \frac{-150 + 105.51}{22 \times 10^3} \Rightarrow \boxed{i_2 = -2.02 \text{ mA}}$$

Then, recalling eqns (4) and (5) from previous part, we can obtain i_D and i_4 :

$$\left\{ \frac{1}{39k} 50 - \frac{1}{39k} (98.32) = i_D - i_4 \Rightarrow \boxed{i_D = 3.5060 \text{ mA}} \right.$$

$$\left\{ \left(\frac{1}{100k} + \frac{1}{22k} + \frac{1}{68k} \right) 150 - \frac{1}{22k} (105.51) - \frac{1}{100k} (98.32) = i_4 \Rightarrow \boxed{i_4 = 4.7450 \text{ mA}} \right.$$

END of HW#3 Soln