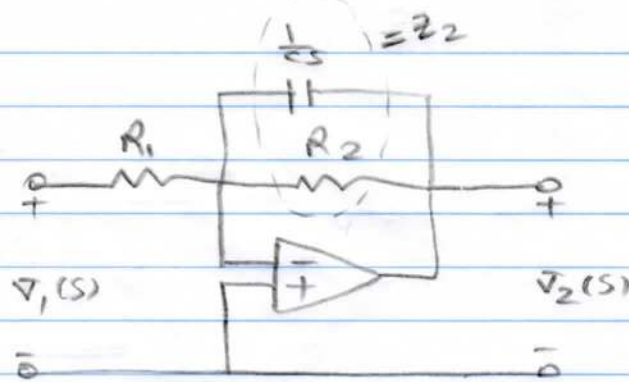


11-12



$$Z_2 = \frac{1}{Cs} \parallel R_2 = \frac{R_2}{R_2Cs + 1}$$

The circuit is an inverting op-amp:

$$\Rightarrow T_V(s) = \frac{V_2(s)}{V_1(s)} = -\frac{Z_2}{R_1} = -\frac{R_2}{R_1(R_2Cs + 1)}$$

$$\Rightarrow T_V(s) = \frac{-\frac{1}{R_1C}}{s + \frac{1}{R_2C}}$$

$$\text{pole: } s = -\frac{1}{R_2C}$$


$$\text{pole} = -250 \text{ krad/s}$$

$$\frac{R_2}{R_1} = 100 \rightarrow \text{choose } R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 100 \text{ k}\Omega$$

$$\frac{-1}{R_2C} = -250 \times 10^3$$

$$\Rightarrow C = \frac{1}{100 \times 10^3 \times 250 \times 10^3} = 0.04 \text{ nF}$$

11-13

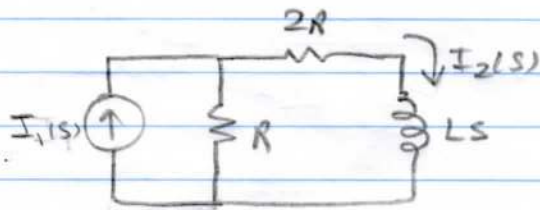

use current division:

$$I_2 = I_1 \frac{R}{R + 2R + Ls} = \frac{RI_1}{3R + Ls}$$


$$\Rightarrow T_I(s) = \frac{I_2(s)}{I_1(s)} = \frac{R}{3R + Ls}$$

$$\text{pole: } s = -\frac{3R}{L}$$

$$s = -377 \text{ rad/s} \Rightarrow \frac{3R}{L} = 377$$

$$\text{choose } R = 100 \Omega \Rightarrow L = 796 \text{ mH}$$

11-14

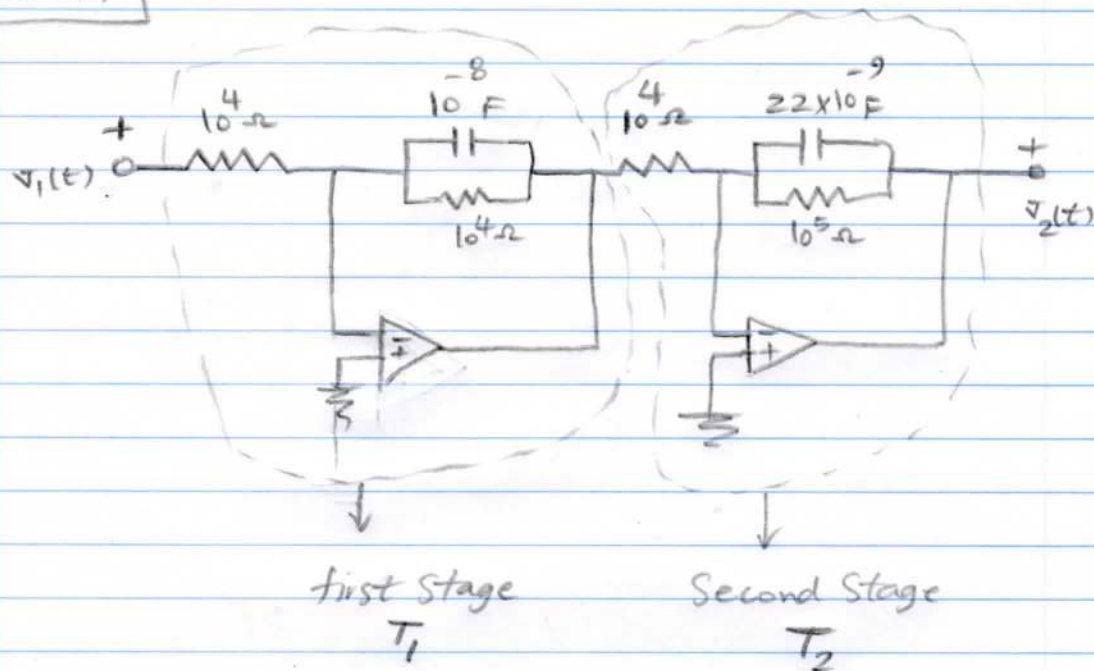

Both stages are inverting op-amp $\Rightarrow$

$$T_1 = - \frac{(10^4 // \frac{1}{10^{-8} s})}{10^4}$$


$$T_2 = - \frac{(10^5 // \frac{1}{22 \times 10^{-9} s})}{10^4}$$

$T_V(s)$ of both Stages together $= T_1 \cdot T_2$

$$\Rightarrow T_V(s) = \frac{10}{(10^{-4} s + 1)(22 \times 10^{-4} s + 1)}$$

poles: $s = -10^4, -454.55$

11-34

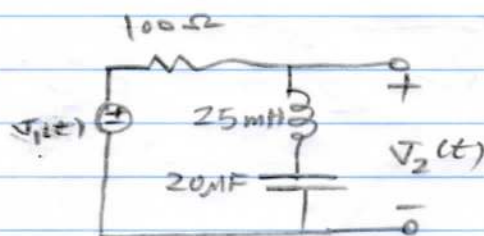

From Voltage division:

$$V_2(s) = V_1(s) \frac{sL + \frac{1}{Cs}}{R + sL + \frac{1}{Cs}} = V_1(s) \frac{s^2 + \frac{1}{CL}}{s^2 + \frac{R}{L}s + \frac{1}{CL}}$$

$$\Rightarrow T(s) = \frac{V_2(s)}{V_1(s)} = \frac{s^2 + \frac{1}{CL}}{s^2 + \frac{R}{L}s + \frac{1}{CL}} = \frac{s^2 + 2 \times 10^6}{s^2 + 4 \times 10^3 s + 2 \times 10^6}$$

poles: $s = -3414, -585.8 \text{ rad/s}$

zeros: $s = \pm 1414.2j \text{ rad/s}$

→ For $v_1(t) = 5 \cos(1414.2t) \text{ (V)}$

$\omega = 1414.2$ is one of the zeros of $T(s)$

$\Rightarrow v_{2ss}(t) = 0 \text{ (V)}$

→ For $v_1(t) = 5 \cos(1000t) \text{ (V)}, \omega = 1000$

$|T(j\omega)| = 0.2425, \angle T(j\omega) = -1.3258 \text{ rad}$


$v_{2ss}(t) = 5 |T(j\omega)| \cos(\omega t + \angle T(j\omega))$

$\Rightarrow v_{2ss}(t) \approx 1.2 \cos(1000t - 1.33) \text{ (V)}$

→ For $v_1(t) = 5 \text{ V}, V_1(s) = \frac{5}{s}, V_2(s) = T(s)V_1(s)$

$v_{2ss}(t) = \lim_{s \rightarrow 0} s V_2(s) = \lim_{s \rightarrow 0} s \frac{s^2 + 2 \times 10^6}{s^2 + 4 \times 10^3 s + 2 \times 10^6} \cdot \frac{5}{s} = 5 \text{ (V)}$

11-36

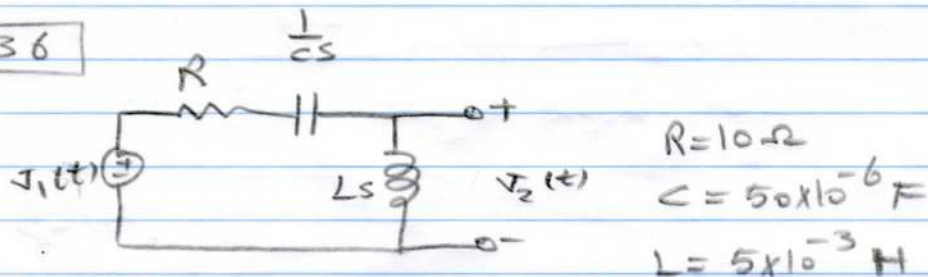

$$T(s) = \frac{V_2(s)}{V_1(s)} = \frac{Ls}{R + \frac{1}{Cs} + Ls} = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\Rightarrow T(s) = \frac{s^2}{s^2 + 2 \times 10^3 s + 4 \times 10^6}$$

poles: $s = -1000 \pm 1732j \text{ rad/s}$

zeros: $s = 0, 0 \text{ rad/s}$

For $V_1(t) = 25 \cos(2000t)$, $\omega = 2000$

$|T(j\omega)| = 1$, $\angle T(j\omega) = 1.57 \text{ rad}$


$\Rightarrow V_{2ss}(t) = 25 \cos(2000t + 1.57) \text{ (V)}$

For $V_1(t) = 25 \cos(10^4 t)$, $\omega = 10^4$

$|T(j\omega)| = 1.02$, $\angle T(j\omega) = 0.205 \text{ rad}$

$\Rightarrow V_{2ss}(t) = 25.5 \cos(10^4 t + 0.205) \text{ (V)}$

12-6

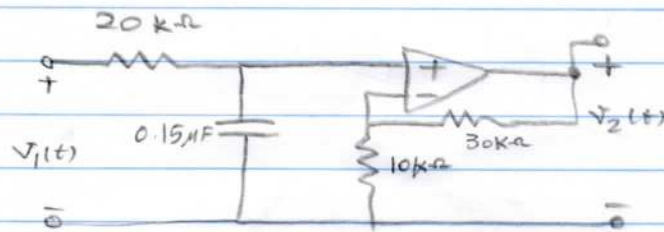


$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \underbrace{\left(\frac{10 \times 10^3 + 30 \times 10^3}{10 \times 10^3} \right)}_{\text{Non-inverting op-amp}} \underbrace{\left(\frac{1}{20 \times 10^3 + \frac{1}{0.15 \times 10^{-6} s}} \right)}_{\text{Voltage divider}}$$

$$\Rightarrow T_V(s) = \frac{1333.3}{s + 333.3}$$

(a) $T_V(s)$ is in the form of transfer function for a low-pass filter;

$$\Rightarrow \omega_c = 333.3 \frac{\text{rad}}{\text{s}} \quad \text{cutoff frequency}$$

$$s = j\omega \Rightarrow \begin{cases} |T(j0)| = 4 \Rightarrow |T(j0)| = 20 \log(4) = 12.04 \text{ dB} \\ |T(j\infty)| = \infty \end{cases}$$

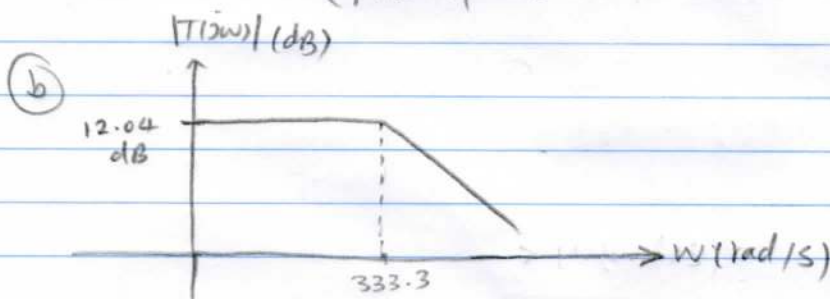


(c)

ω	$ T(j\omega) \text{ (dB)} \leftarrow 20 \log(T(j\omega))$
$0.1\omega_c$	11.99 dB
ω_c	9.03 dB
$10\omega_c$	-7.95 dB

$$\begin{aligned} \oplus & -7.95 - 9.03 \\ & = -16.98 \text{ dB} \end{aligned}$$

(e) By changing feedback resistor from 30 kΩ to 90 kΩ

12-7

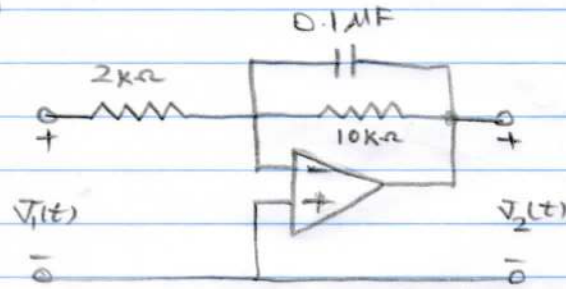


$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{-(10 \times 10^3) \left(1 + \frac{1}{0.1 \times 10^{-6} s} \right)}{2 \times 10^3}$$

$$= \frac{-5000}{s + 1000}$$

(a) $s = j\omega \Rightarrow \begin{cases} |T_V(j0)| = 5 \\ |T_V(j\infty)| = 0 \end{cases}$

$T_V(s)$ is in the form of a low-pass filter
 $\Rightarrow \omega_c = 1000 \text{ rad/s}$ cutoff frequency

(b) $|T_V(j0)| = 5 \Rightarrow |T_V(j0)| = 20 \log(5) = 13.97 \text{ dB}$

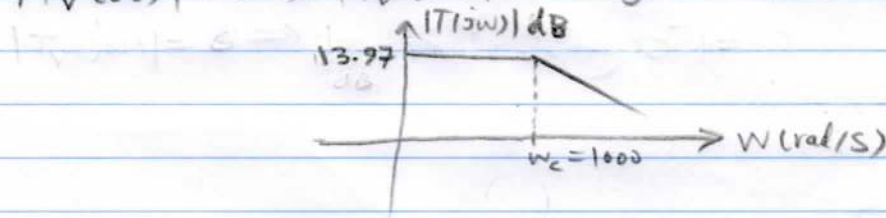


(c)

ω	$ T(j\omega) \text{ (dB)}$
$0.1\omega_c$	13.94 dB
ω_c	10.97 dB
$10\omega_c$	-6.06 dB

(e) By changing the 2-kΩ resistor with a 1-kΩ resistor

12-8

First part:

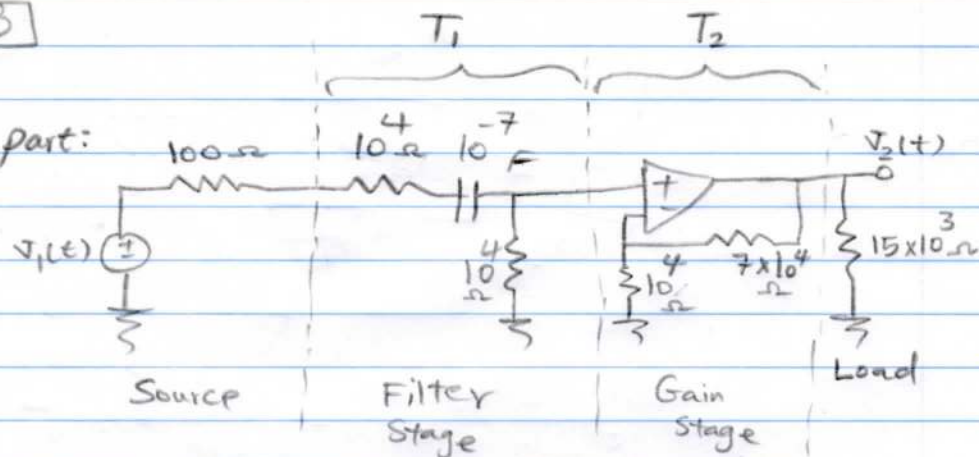


$$T_1 = \frac{10^4}{10 \cdot 100 + \frac{1}{10^{-7} s} + 10^4} = \frac{0.498 s}{s + 498}$$

$$T_2 = \frac{80 \times 10^3}{10 \times 10^3} = 8$$

$$T = T_1 \times T_2 = \frac{3.98 s}{s + 498} \Rightarrow \begin{cases} \text{pole: } s = -498 \Rightarrow \omega_c \approx -500 \\ \text{Gain} = 3.98 \\ \approx 4 \end{cases} \quad \begin{matrix} \text{cutoff } f_c \frac{\text{rad}}{s} \\ \text{frequency} \end{matrix}$$

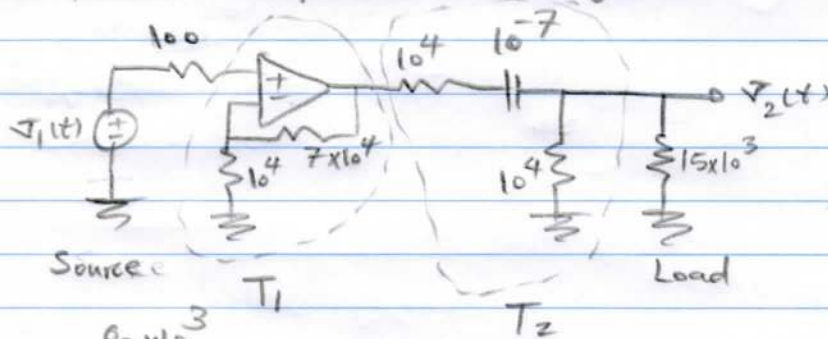Second part: Replace Gain Stage with Filter Stage as:



$$T_1 = \frac{80 \times 10^3}{10 \times 10^3} = 8$$

$$T_2 = \frac{(10^4 \parallel 15 \times 10^3)}{(10^4 \parallel 15 \times 10^3) + 10^4 + \frac{1}{10^{-7} s}} = \frac{0.375 s}{s + 625}$$

$$T = T_1 \times T_2 = \frac{3 s}{s + 625} \Rightarrow \begin{matrix} \text{pole: } s = -625 \frac{\text{rad}}{s} = \omega_c \\ \text{cutoff frequency} \end{matrix}$$

12-46

(a)
$$T(s) = \frac{700(s+10)}{(s+7)(s+100)}$$

$$T(s) = \frac{(700)(10)(\frac{s}{10}+1)}{7(\frac{s}{7}+1)(100)(\frac{s}{100}+1)}$$


$$T(s) = 10 \frac{\frac{s}{10}+1}{(\frac{s}{7}+1)(\frac{s}{100}+1)}$$

Scale factor $K_0 = 10 \Rightarrow 20 \log(10) = 20 \text{ dB}$

$$s = j\omega$$

* we can form frequencies at based on zero & poles:
 $\omega = 10 \frac{\text{rad}}{\text{s}}, 7 \frac{\text{rad}}{\text{s}}, 100 \frac{\text{rad}}{\text{s}}$

$\omega \text{ (rad/s)}$	Zero/pole	slope (dB/decade)	$ T(j\omega) \text{ (dB)}$
7	pole	-20	21.28 dB
10	zero	20	Baseline
100	pole	-20	14.40 dB

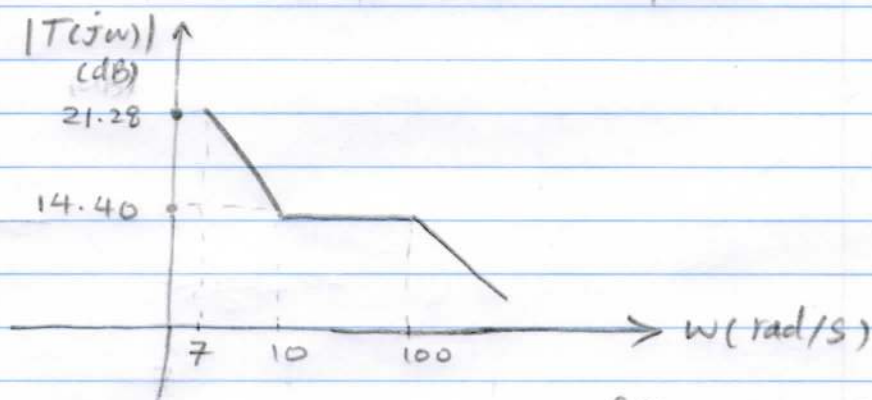

This is a low-pass filter
 passband gain is 20 dB

② There are different designs to satisfy the transfer function. there is one of possible designs:

$$\begin{aligned}
 T(s) &= \frac{700(s+10)}{(s+7)(s+100)} \\
 &= 700 \frac{1}{s+7} \frac{s+10}{s+100} \\
 &= 700 \frac{\frac{1}{s}}{1+\frac{7}{s}} + \frac{1+\frac{10}{s}}{1+\frac{100}{s}} \\
 &\quad \downarrow \quad \quad \quad \downarrow \quad \quad \quad \downarrow \\
 &\quad \text{gain coefficient} \quad T_1(s) \quad T_2(s)
 \end{aligned}$$

$$T_1(s) = \frac{\frac{1}{s}}{1+\frac{7}{s}} = \frac{\frac{1}{s}}{\frac{1}{s} + (1+\frac{6}{s})}$$


using a voltage divider with $\begin{cases} C_1 = 1F \\ R_1 = 1\Omega \\ C_2 = \frac{1}{6}F \end{cases}$

$$T_2(s) = \frac{1+\frac{10}{s}}{1+\frac{100}{s}} = \frac{1+\frac{10}{s}}{(1+\frac{10}{s}) + \frac{90}{s}}$$

using another voltage divider with $\begin{cases} R_2 = 1\Omega \\ C_2 = \frac{1}{10}F \\ C_3 = \frac{1}{90}F \end{cases}$

Gain coefficient can be satisfied with a non-inverting op-amp using $\begin{cases} R_3 = 699\Omega \\ R_4 = 1\Omega \end{cases}$

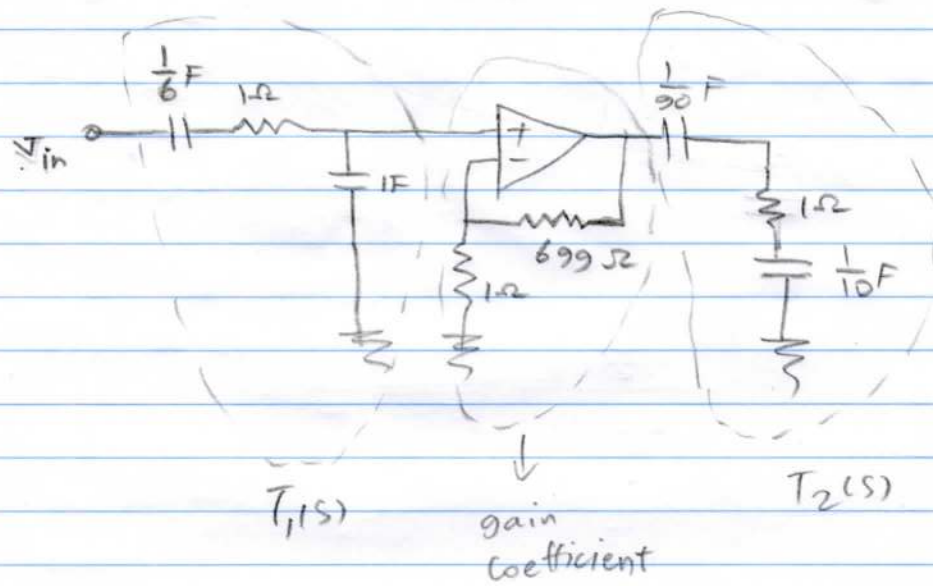The whole circuit design can then be like;



12-48

$$T(s) = \frac{100s(s+300)}{(s+30)(s+3000)}$$

① $s = j\omega$


$$T(j\omega) = \frac{100(j\omega)(300)(\frac{j\omega}{300} + 1)}{30(\frac{j\omega}{30} + 1)(3000)(\frac{j\omega}{3000} + 1)}$$

$$T(j\omega) = \frac{\frac{1}{3}(j\omega)(\frac{j\omega}{300} + 1)}{(\frac{j\omega}{30} + 1)(\frac{j\omega}{3000} + 1)}$$

Scale factor: $K = \frac{1}{3} \Rightarrow 20 \log(\frac{1}{3}) = -9.54 \text{ dB}$

② We can form frequencies at (based on zero & poles):
 $\omega = 0 \frac{\text{rad}}{\text{s}}, 30 \frac{\text{rad}}{\text{s}}, 300 \frac{\text{rad}}{\text{s}}, 3000 \frac{\text{rad}}{\text{s}}$

$\omega (\text{rad/s})$	zero/pole	Slope (dB/decade)	$ T(j\omega) $ (dB)
0	Zero	20	Baseline
30	pole	-20	17.03 dB
300	Zero	20	Baseline
3000	pole	-20	37 dB

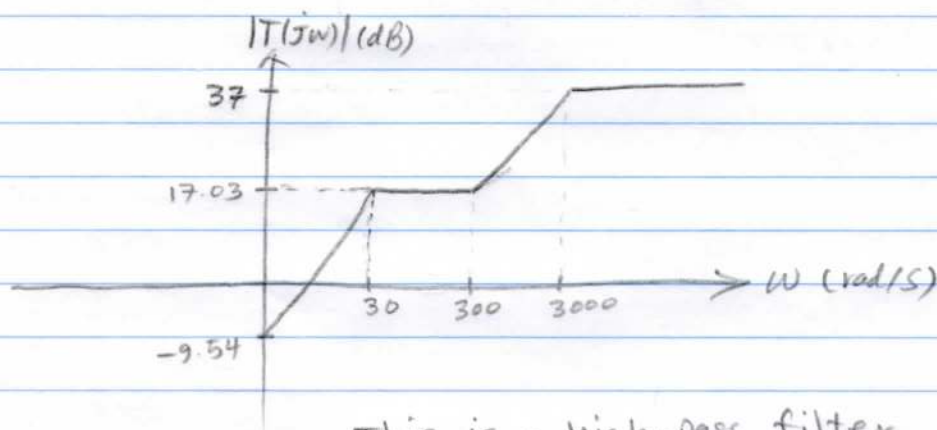

This is a high-pass filter
 passband gain is 37 dB

② There are different designs to satisfy the transfer function. Here is one of possible designs:

$$T(s) = \frac{100s(s+300)}{(s+30)(s+3000)}$$

$$= \frac{100(s+300)}{(s+30)} \times \frac{s}{(s+3000)}$$

$$= \frac{100(300s)(\frac{1}{300} + \frac{1}{s})}{30s(\frac{1}{30} + \frac{1}{s})} \times \frac{1}{1 + \frac{3000}{s}}$$

$$= (1000) \underbrace{\frac{\frac{1}{300} + \frac{1}{s}}{\frac{1}{30} + \frac{1}{s}}}_{T_1(s)} \times \underbrace{\frac{1}{1 + \frac{3000}{s}}}_{T_2(s)}$$

gain coefficient

$$T_2(s) = \frac{1}{1 + \frac{3000}{s}}$$

using a voltage divider $\Rightarrow \begin{cases} R_2 = 1 \Omega \\ C_2 = \frac{1}{3000} F \end{cases}$

$$T_1(s) = \frac{\frac{1}{300} + \frac{1}{s}}{\frac{1}{30} + \frac{1}{s}} = \frac{(\frac{1}{300} + \frac{1}{s})}{(\frac{1}{300} + \frac{1}{s}) + \frac{2}{300}}$$

using another voltage divider $\Rightarrow \begin{cases} R_1 = \frac{1}{300} \Omega \\ C_1 = 1 F \\ R_3 = \frac{2}{300} \Omega \end{cases}$

To have the gain coefficient of 1000, we can use a non-inverting op-amp with

$$R_4 = 999 \Omega \text{ and } R_5 = 1 \Omega$$

The whole circuit design can then be like;

