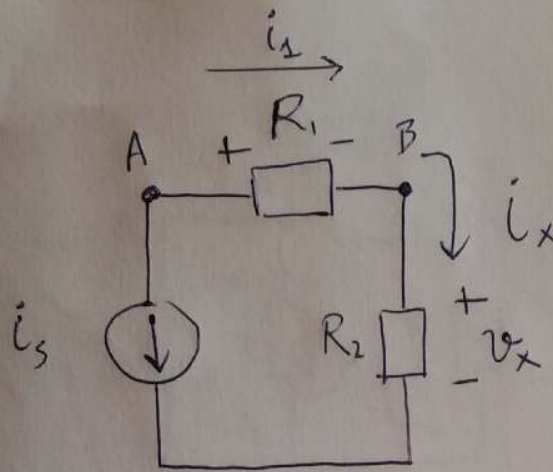


2.25



$$i_s = 500 \mu\text{A}$$


$$R_1 = 22 \text{ k}\Omega$$

$$R_2 = 68 \text{ k}\Omega$$

$$\begin{aligned} \text{KCL at (A)} : -i_s - i_1 &= 0 \\ \text{at (B)} : i_1 - i_x &= 0 \end{aligned} \Rightarrow \boxed{i_x = i_1 = -i_s = -500 \mu\text{A}}$$

$$\begin{aligned} \text{Ohm's law : } \boxed{v_x} &= i_x R_2 = -500 \mu\text{A} \cdot 68 \text{ k}\Omega = \\ &= 34000 \text{ mV} \\ &= \boxed{34 \text{ V}} \end{aligned}$$

2.27

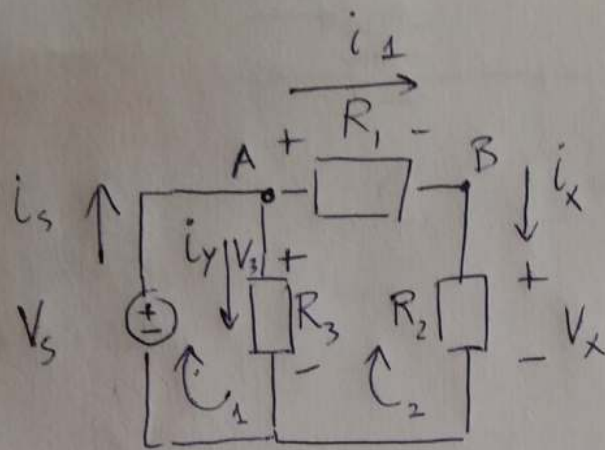

$$V_s = 18 \text{ V}$$

$$R_1 = 22 \text{ k}\Omega$$

$$R_2 = 68 \text{ k}\Omega$$

$$R_3 = 33 \text{ k}\Omega$$


$$\begin{aligned} \text{KCL at (A): } i_s - i_y - i_1 &= 0 \\ \text{at (B): } i_1 - i_x &= 0 \Rightarrow i_x = i_1 \end{aligned} \quad \Rightarrow i_x = i_s - i_y$$

$$\begin{aligned} \text{KVL at loop 1: } -V_s + V_3 &= 0 \Rightarrow V_3 = V_s = 18 \text{ V} \\ \text{at loop 2:} \end{aligned}$$

$$\text{Ohm's Law at } R_3: i_y = \frac{V_3}{R_3} = \frac{18 \text{ V}}{33 \text{ k}\Omega} = \frac{6}{11} \text{ mA}$$

If we find  $i_s$  by computing an equivalent circuit,\* we can find  $i_x$  and then  $V_x$  by Ohm's law:

\*EQUIVALENT CIRCUIT

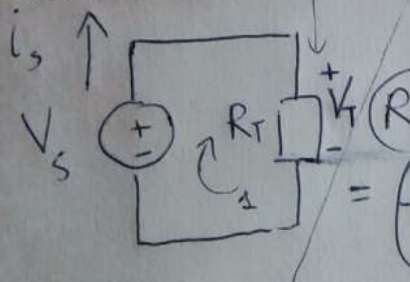

$$\begin{aligned} i_x &= i_s - i_y = 0.745 - \frac{6}{11} = 0.2 \text{ mA} \\ V_x &= i_x R_2 = 0.2 \text{ mA} \cdot 68 \text{ k}\Omega = 13.6 \text{ V} \end{aligned}$$

$$\text{KVL: } -V_s + V_T = 0 \Rightarrow V_T = V_s = 18 \text{ V}$$

$$\text{Ohm's law: } i_s = \frac{V_T}{R_T} = \frac{18 \text{ V}}{24.146 \text{ k}\Omega} = 0.745 \text{ mA}$$


2.33

(TYPO IN THE BOOK  
 $i_x = -0.5 \text{ mA}$ )

$$i_x = 0.5 \text{ mA}$$

$$R_x = 10 \text{ k}\Omega$$

$$R_y = 10 \text{ k}\Omega$$

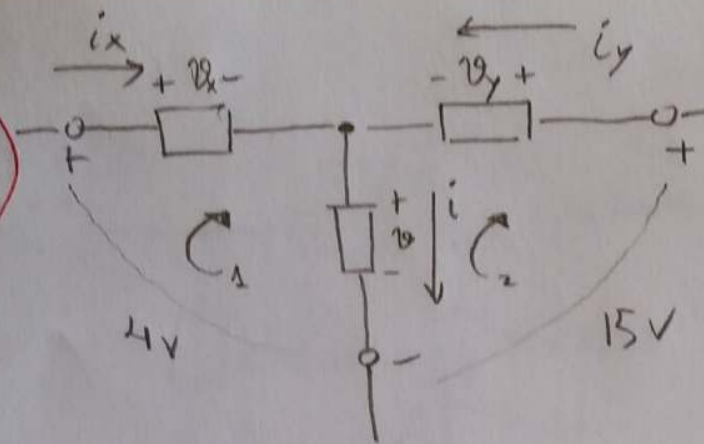

$$\text{KVL at loop 1: } v_x + v - 4\text{V} = 0 \Rightarrow v = 4\text{V} - \overset{\text{Ohm's Law}}{i_x R_x} = \boxed{-1\text{V}}$$

$$\text{at loop 2: } -v - v_y + 15\text{V} = 0 \Rightarrow v_y = 15\text{V} - v = \boxed{16\text{V}}$$

$$\text{KCL at (A): } i_x + i_y - i = 0$$

$\Downarrow$  Ohm's Law

$$0.5 \text{ mA} + \frac{v_y}{R_y} - \frac{v}{R} = 0$$

$$R = \frac{\overset{\downarrow v}{-1\text{V}}}{0.5 \text{ mA} + \frac{v_y}{R_y}} = \frac{-1\text{V}}{0.5 \text{ mA} + 1.6 \text{ mA}}$$

$$= -\frac{1}{2.1} \text{ k}\Omega = \boxed{-0.476 \text{ k}\Omega}$$

NOTE FOR READER:



Using  $i_x = -0.5 \text{ mA}$

$$v = 4\text{V} - v_x = 4\text{V} - i_x R_x = 9\text{V}$$

$$v_y = 15\text{V} - v = 15\text{V} - 9\text{V} = 6\text{V}$$


$$\text{KCL at (A) } -0.5 \text{ mA} + \frac{6\text{V}}{10 \text{ k}\Omega} - \frac{9\text{V}}{R} = 0, \quad R = \frac{9}{-0.5 + 0.6} = \boxed{90 \text{ k}\Omega}$$

2.36

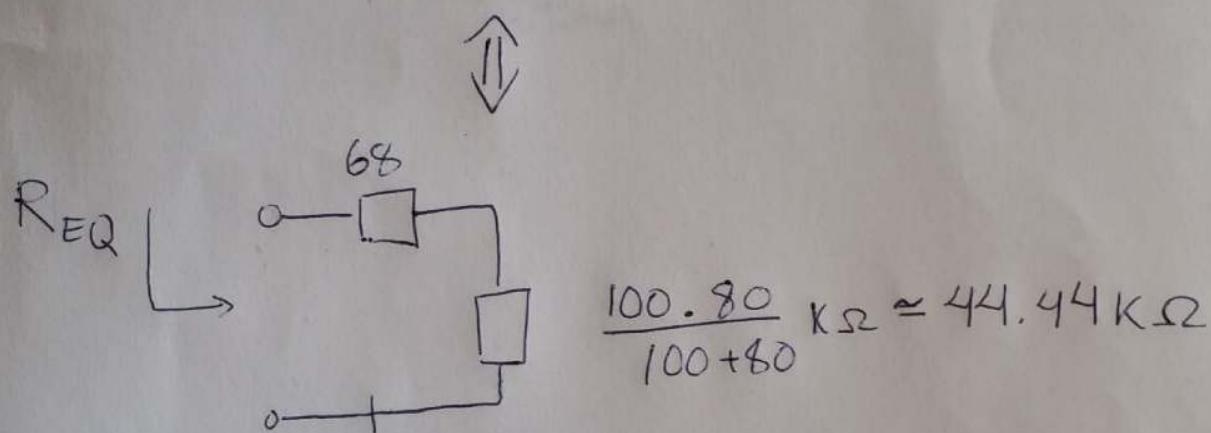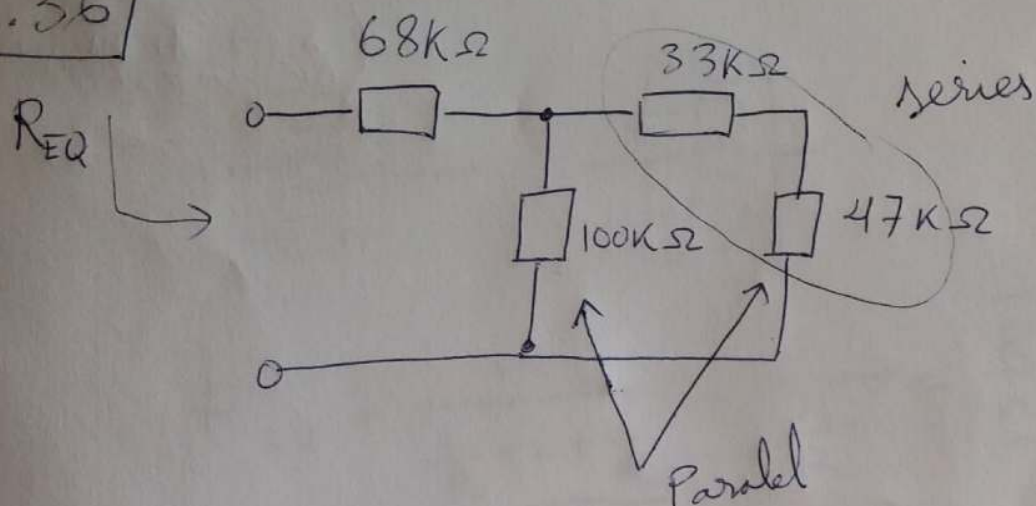

$$R_T = 68 + 44.44 \approx 112.44 k\Omega$$


2.40

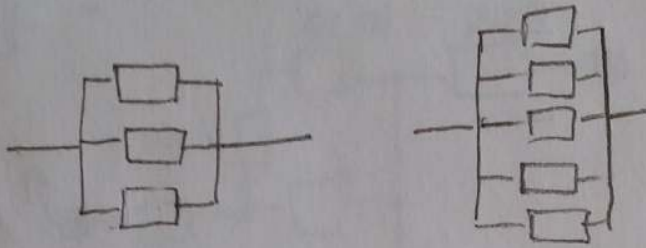


$n R_s$   
in parallel

$$R_{EQ} = \frac{1}{\underbrace{\frac{1}{R} + \dots + \frac{1}{R}}_{n \text{ times}}} = \frac{1}{\frac{n}{R}} = \boxed{\frac{R}{n}}$$

2.42

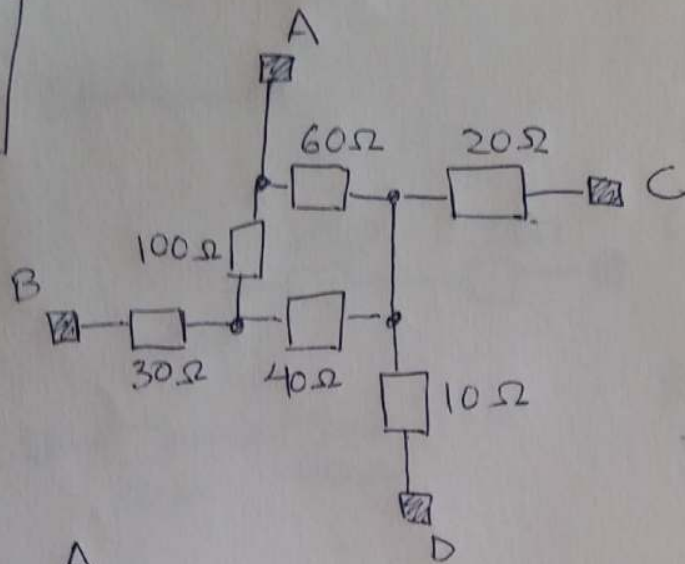


A-B

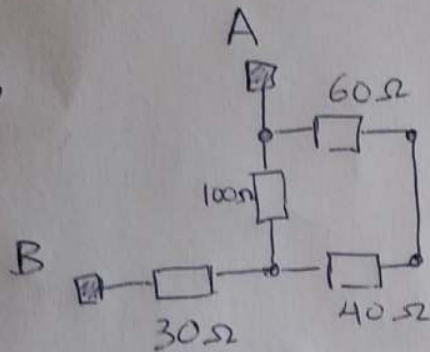

$$R_T = 30 + (100 \parallel (60 + 40))$$

$$= 30 + 50 = \underline{80 \Omega}$$

A-C

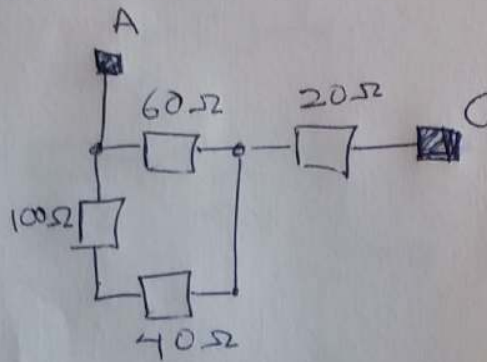


$$R_T = 20 + (60 \parallel (100 + 40))$$

$$= 20 + \frac{60 \cdot 140}{140 + 60}$$

$$= 20 + \frac{8400}{200} = 20 + 42$$

$$= \underline{62 \Omega}$$

A-D

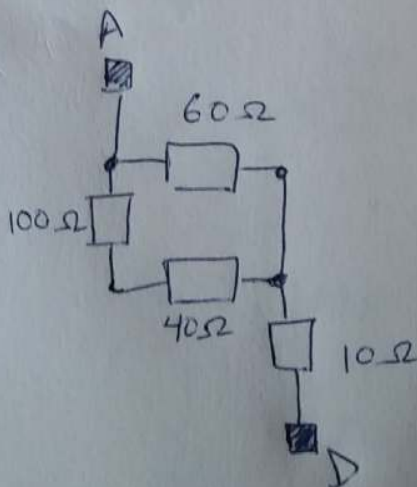


$$R_T = 10 + (60 \parallel (100 + 40))$$

$$= 10 + 42$$

$$= \underline{52 \Omega}$$


2.42 continued

B-C

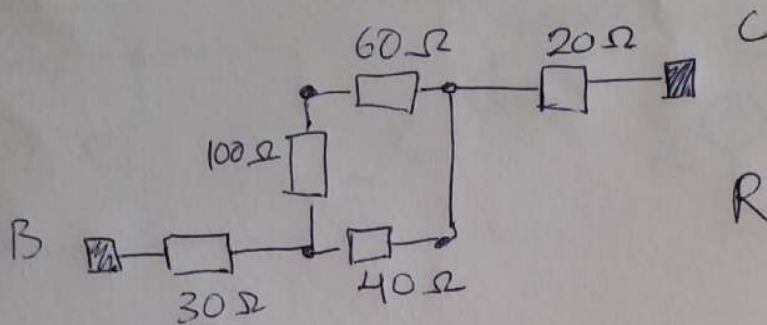


$$\begin{aligned}
 R_T &= 30 + ((100 + 60) \parallel 40) + 20 \\
 &= 50 + \frac{160 \cdot 40}{160 + 40} \\
 &= 50 + \frac{6400}{200} = \\
 &= 50 + 32 \\
 &= \boxed{82 \Omega}
 \end{aligned}$$

B-D

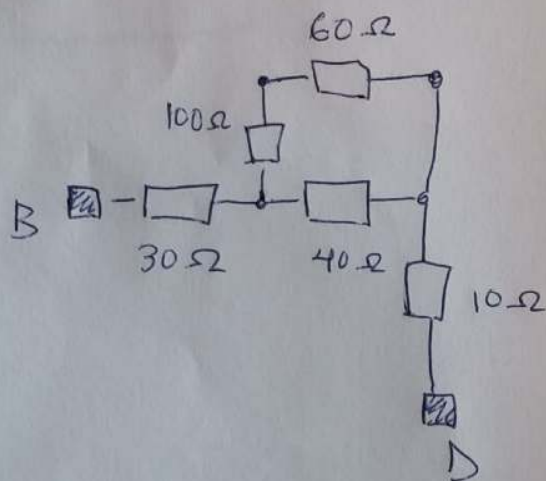


$$\begin{aligned}
 R_T &= 30 + ((100 + 60) \parallel 10) + 40 \\
 &= \cancel{30} + 32 + 10 \\
 &= \boxed{72 \Omega}
 \end{aligned}$$

C-D


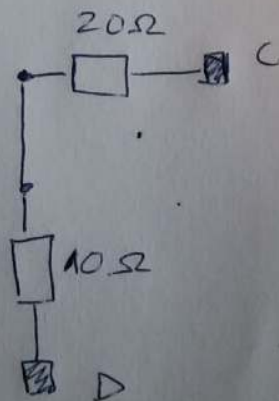


$$R_T = 20 + 10 = \boxed{30 \Omega}$$


2.55

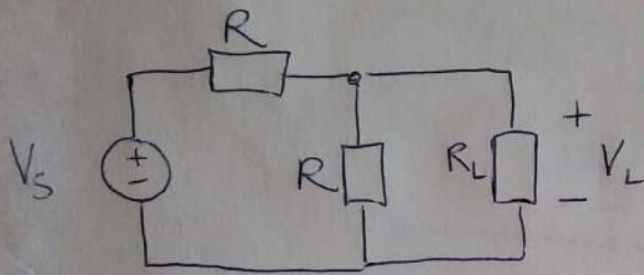

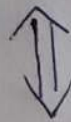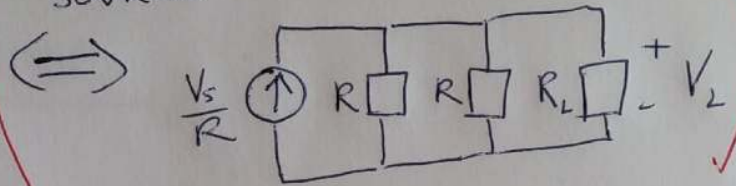alternative path  
Using EQUIVALENT SOURCE



EQUIVALENT CIRCUIT

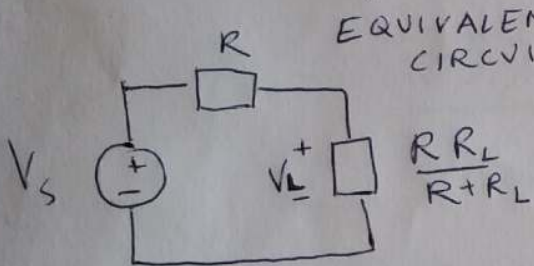

Voltage division:


$$V_L = \frac{\frac{RR_L}{R+R_L}}{\left(\frac{RR_L}{R+R_L} + R\right)} V_s$$

$$= \frac{RR_L}{RR_L + R(R+R_L)} V_s$$

$$= \frac{RR_L}{2RR_L + R^2} V_s =$$

$$= \frac{1}{2 + \frac{R}{R_L}} V_s$$


2.59

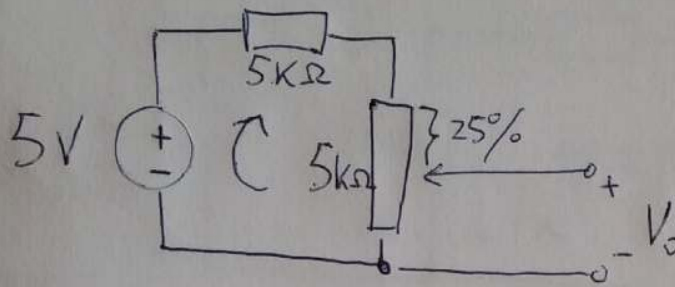


By voltage division,

$$V_o = \frac{75\% \cancel{5k\Omega} (5V)}{\cancel{5k\Omega} + \cancel{5k\Omega}} = \frac{3}{8} \cancel{(5V)} = \frac{0.375 \cancel{k\Omega}}{\cancel{k\Omega}} \times 5V = \underline{1.875V}$$



2.72

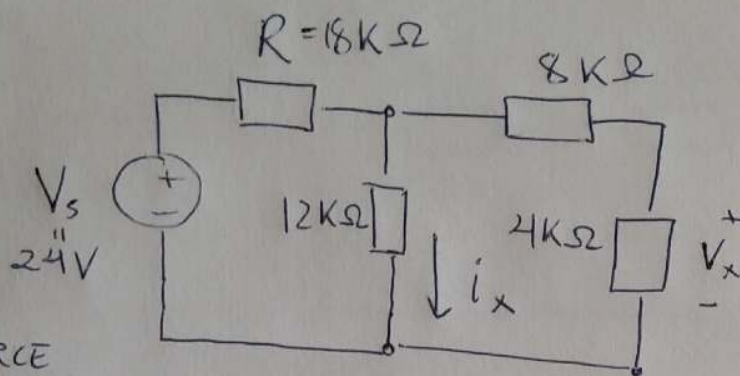

EQ. SOURCE

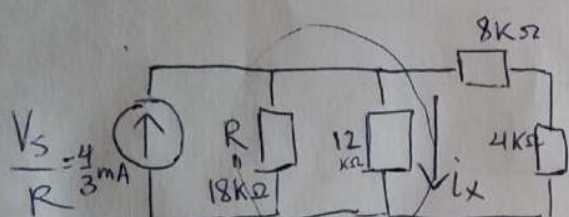

EQ. CIRCUIT A

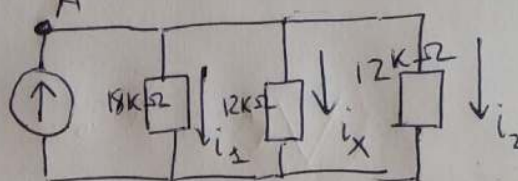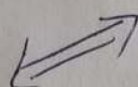

KCL at A:


$$\frac{4}{3} \text{ mA} = i_1 + i_x + i_2$$

Current division


$$i_x = \frac{\frac{1}{12}}{\frac{1}{18} + \frac{1}{12} + \frac{1}{12}} \cdot \frac{4}{3} \text{ mA}$$

$$= \frac{1}{\frac{2}{3} + 2} \cdot \frac{4}{3} \text{ mA}$$

$$= \frac{4}{2+6} = 0.5 \text{ mA}$$

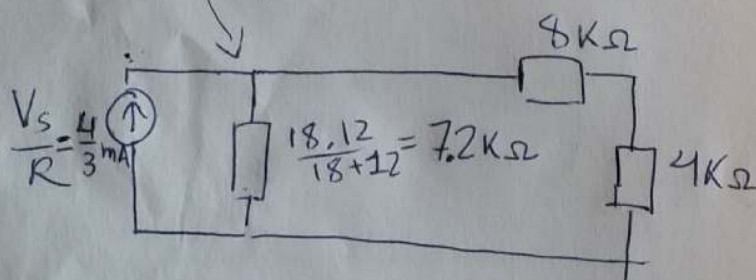


EQ. SOURCE

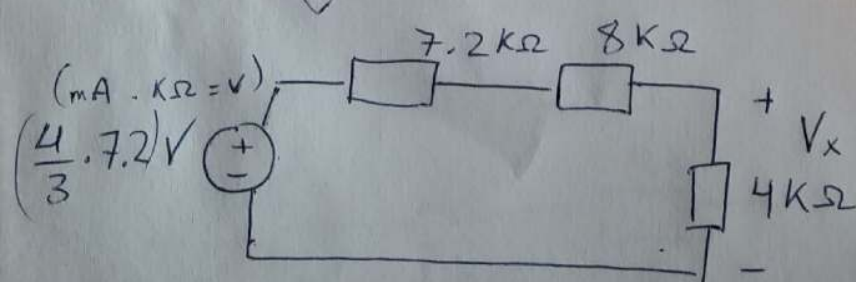


Voltage division:

$$V_x = \frac{4 \text{ k}\Omega}{4 + 7.2 + 8} \left( \frac{4}{3} \cdot 7.2 \right) = 2 \text{ V}$$


2.77

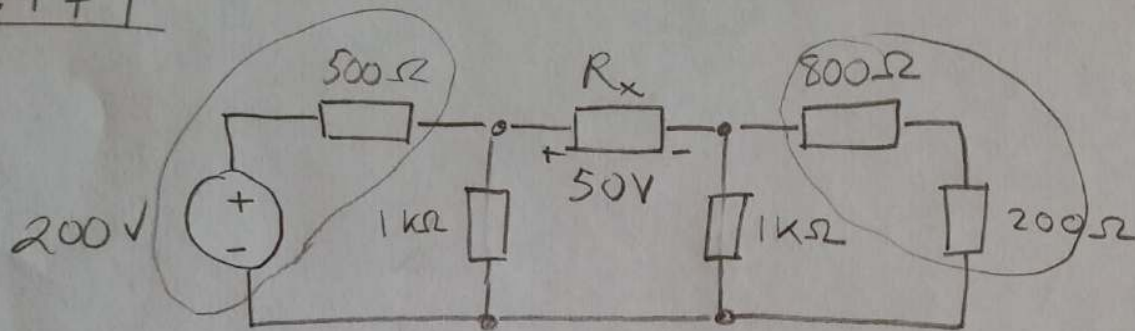

EQ. SOURCE & EQ. RESISTANCE

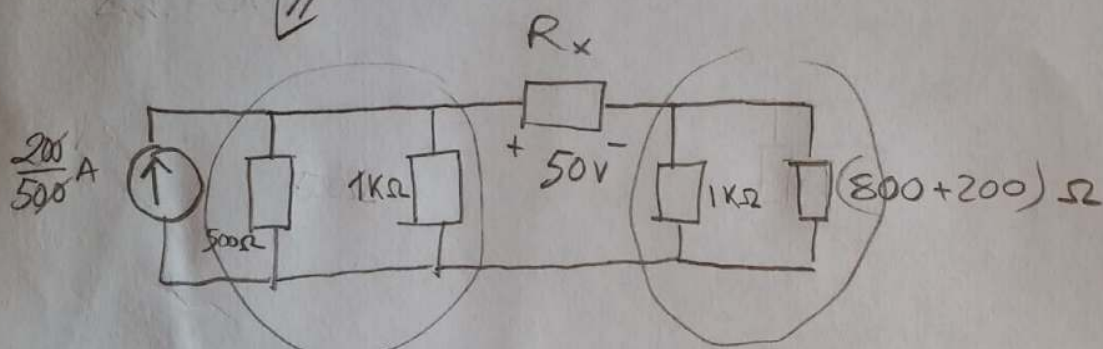


EQ. CIRCUIT

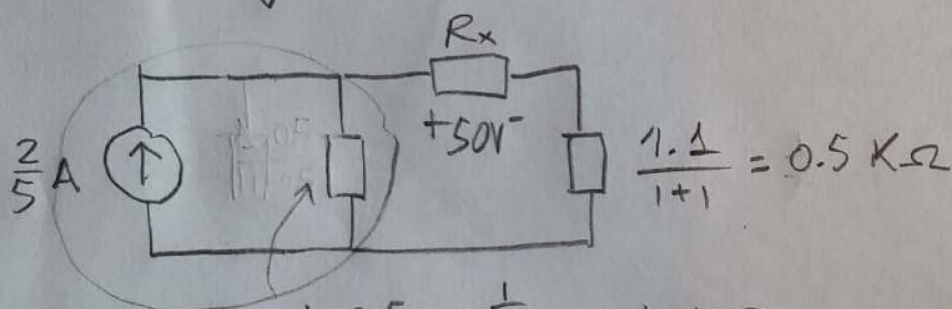

$$\frac{1 \cdot 0.5}{1+0.5} = \frac{\frac{1}{2}}{\frac{3}{2}} = \frac{1}{3} \text{ k}\Omega$$

EQ. SOURCE

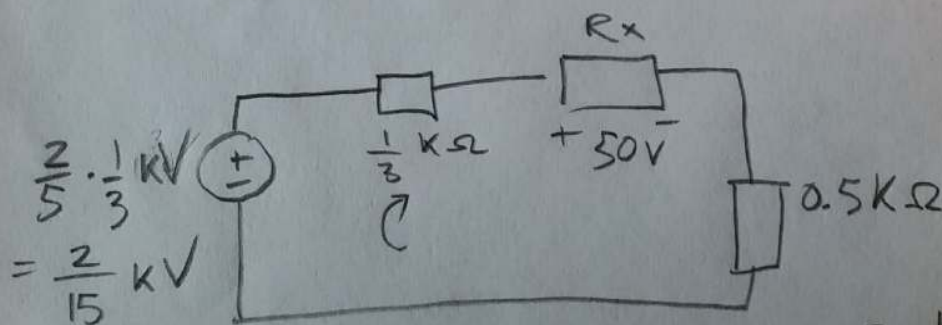

Voltage division

$$50V = \frac{R_x}{\frac{1}{3} + R_x + 0.5} \cdot \frac{2000}{15} V$$

$$\frac{200}{15} R_x = 5 \left( \frac{1}{3} + R_x + 0.5 \right);$$

$$R_x = \frac{5 \left( \frac{1}{3} + \frac{1}{2} \right)}{\frac{200}{15} - 5} = \underline{0.5 \text{ k}\Omega}$$