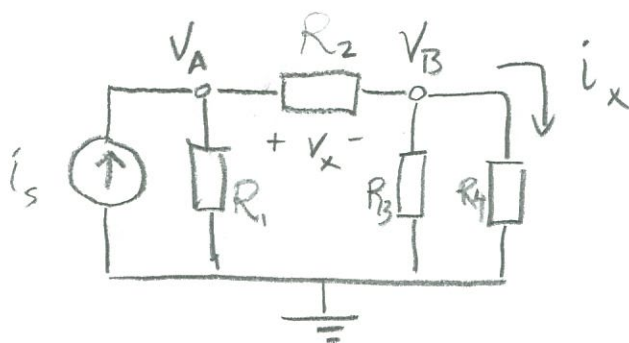


SOLUTIONS HW 3

3.2



$$A) \underbrace{(V_A - 0) \frac{1}{R_1} + (V_A - V_B) \frac{1}{R_2}}_{\text{leaving currents}} = \underbrace{i_s}_{\text{entering currents}}$$

$$B) (V_B - 0) \frac{1}{R_3} + (V_B - 0) \frac{1}{R_4} + (V_B - V_A) \frac{1}{R_2} = 0$$

System in form $[Ax=b]$ with A) and B)

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

Using Cramer, $V_A = \frac{\begin{vmatrix} i_s & -\frac{1}{R_2} \\ 0 & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{vmatrix}}{\begin{vmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{vmatrix}} = \frac{\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) i_s}{|A|}$


where $|A| = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) - \frac{1}{R_2^2}$

and $V_B = \frac{\begin{vmatrix} \frac{1}{R_1} + \frac{1}{R_2} & i_s \\ -\frac{1}{R_2} & 0 \end{vmatrix}}{|A|} = \frac{-i_s}{|A| R_2}$

Then,

$$i_x = \frac{V_B}{R_4} = \frac{-i_s}{|A| R_2 R_4}; \quad V_x = V_A - V_B = \frac{i_s}{|A|} \left(\frac{1}{R_3} + \frac{1}{R_4} \right)$$

3.3

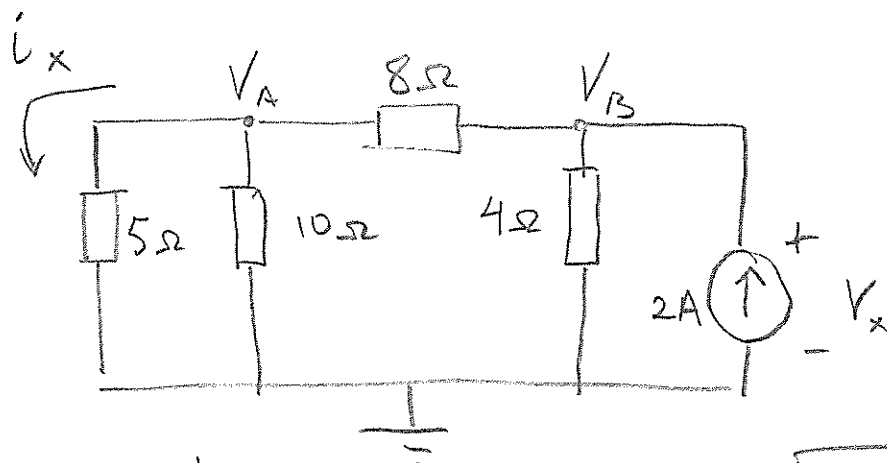

This circuit is the same as in 3.2 (except the definition of V_x) with the (nonunique) $V_B = V_A^{3.2}$, $V_A = V_B^{3.2}$, $i_s = 2A$, $R_1 = 4\Omega$, $R_2 = 8\Omega$, $R_3 = 10\Omega$, $R_4 = 5\Omega$. Therefore, using the previous expression for $A \times = b$, we have

$$|A| = \left(\frac{1}{R_1} + \frac{1}{R_2}\right)\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) - \frac{1}{R_2^2} \approx 0.144$$

$$V_A = V_B^{3.2} = \frac{i_s}{|A| R_2} \approx \frac{2A}{0.144 \cdot 8\Omega} \approx 1.73V$$

$$V_B = V_A^{3.2} = \frac{\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) i_s}{|A|} \approx \frac{0.425 \cdot 2}{0.144} =$$

$$i_x = \frac{V_A}{R_4} = \frac{1.73V}{5\Omega} = 0.346A$$

$$V_x = V_B = 5.9V$$

3.7


$$V_A = V_S$$

$$\frac{V_B - V_A}{R_1} + \frac{V_B - V_C}{R_2} - I_S = 0$$


$$\frac{V_C - V_A}{R_3} + \frac{V_C - V_B}{R_2} + \frac{V_C}{R_4} = 0$$

The circuit might be

$$V_D = 0$$

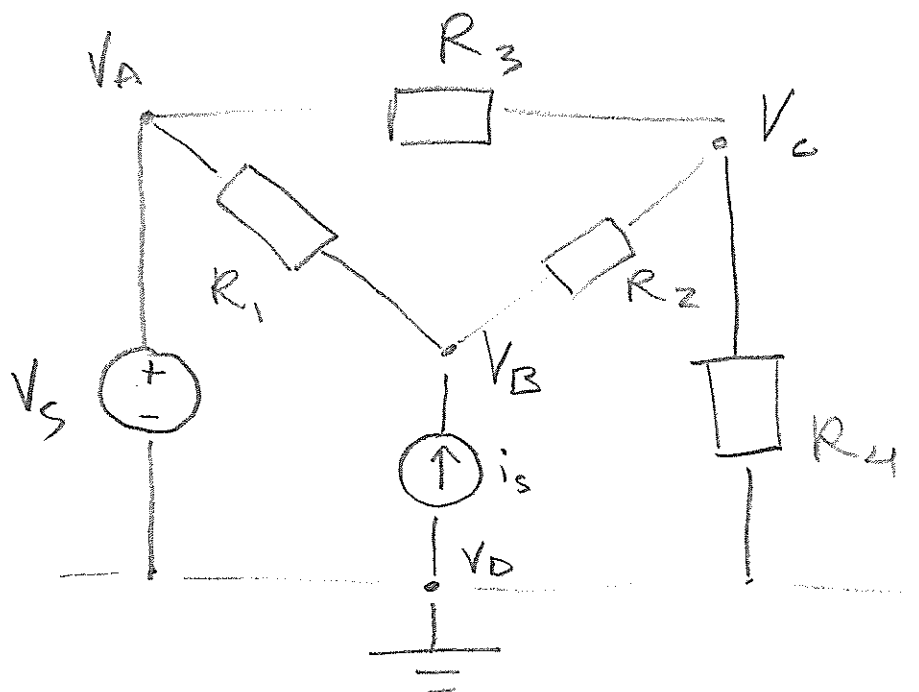

3.8

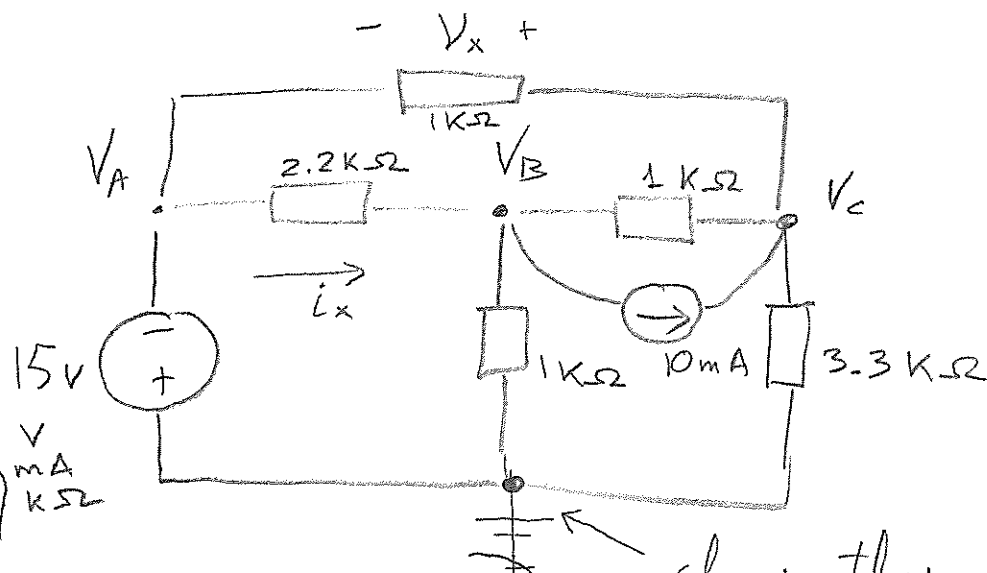

We use units $\left\{ \begin{array}{l} V \\ mA \\ k\Omega \end{array} \right.$

$$V_A = -15$$

$$\frac{V_B - V_A}{2.2} + \frac{V_B - V_C}{1} + \frac{V_B - 0}{1} = -10$$

$$\frac{V_C - V_B}{1} + \frac{V_C - 0}{3.3} + \frac{V_C - V_A}{1} = 10$$

$$\Leftrightarrow \begin{bmatrix} \frac{1}{2.2} + 1 + 1 & -1 \\ -1 & 1 + \frac{1}{3.3} + 1 \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -10 - \frac{15}{2.2} \\ 10 - 15 \end{bmatrix}$$

$$\Leftrightarrow \begin{bmatrix} 2.45 & -1 \\ -1 & 2.30 \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -3.18 \\ 25 \end{bmatrix} \Rightarrow \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -9.40 V \\ -6.25 V \end{bmatrix}$$


$$V_x = V_C - V_A = -6.25 V - (-15 V) = 8.75 V$$

$$i_x = \frac{V_A - V_B}{2.2} = \frac{-15 - (-9.40)}{2.2} = -2.55 mA$$

3-14

Units used V, k Ω , mA

FOR
INSTANCE

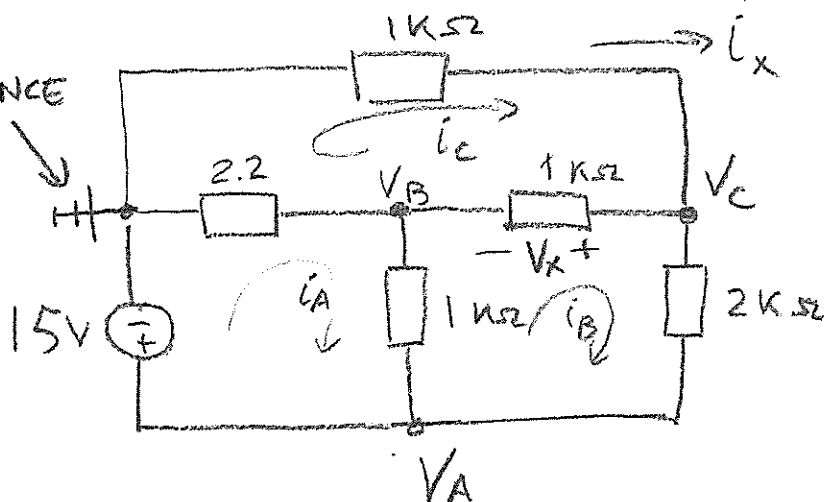

$$V_A = 15V$$

$$(B) \quad \frac{V_B - 0}{2.2} + \frac{V_B - V_C}{1} + \frac{V_B - V_A}{1} = 0$$

$$(C) \quad \frac{V_C - V_B}{1} + \frac{V_C - 0}{2} + \frac{V_C - V_A}{2} = 0$$

So we get the linear system

$$\begin{bmatrix} \frac{1}{2.2} + 1 + 1 & -1 \\ -1 & 1 + 1 + \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 15 \\ \frac{15}{2} \end{bmatrix} \Rightarrow \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 8.76 V \\ 6.50 V \end{bmatrix}$$

$$i_C = \frac{0 - V_C}{1} = -6.50 \text{ mA}$$


$$i_B = \frac{V_C - V_A}{2} = \frac{6.50 - 15}{2} = -4.25 \text{ mA}$$

$$i_A = \frac{V_B - V_A}{1} + i_B = \frac{8.76 - 15}{1} + -4.25 = -10.49 \text{ mA}$$

$$i_X = i_C = -6.50 \text{ mA}$$

$$V_X = V_C - V_B = 6.50 - 8.76 = -2.26 V$$

3.23

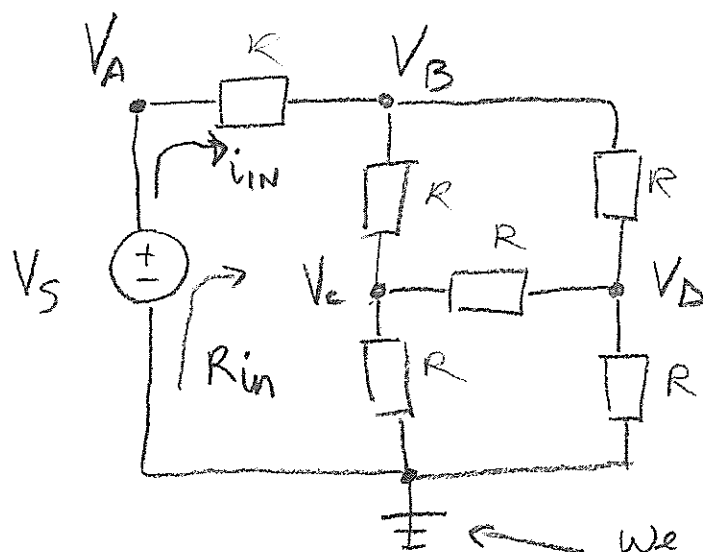

we can choose the ground here

$$V_A = V_S$$

$$\begin{bmatrix} \frac{3}{R} & -\frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{3}{R} & -\frac{1}{R} \\ -\frac{1}{R} & -\frac{1}{R} & \frac{3}{R} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} \frac{V_S}{R} \\ 0 \\ 0 \end{bmatrix}$$


$$\Rightarrow \begin{bmatrix} V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} V_S/2 \\ V_S/4 \\ V_S/4 \end{bmatrix}$$

To compute the equivalent resistance, we can compute the current through V_S and then use Ohm's law:

$$i_N = \frac{V_A - V_B}{R} = \frac{V_S - \frac{V_S}{2}}{R} = \frac{V_S}{2R}$$

$$R_{IN} = \frac{V_S}{i_N} = \frac{V_S}{\frac{V_S}{2R}} = \boxed{2R}$$

3.27

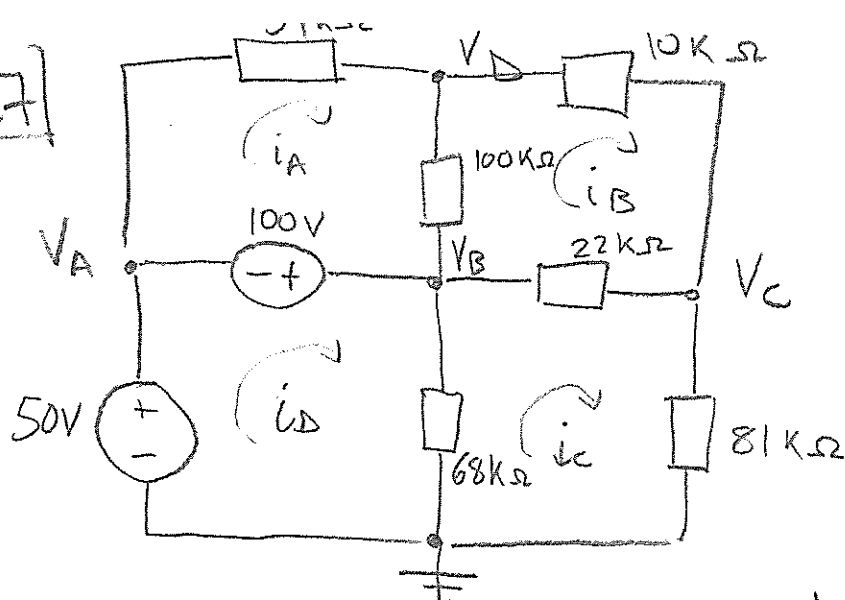

Node analysis (using the units V , $k\Omega$, mA)

(A) $V_A = 50V$

(B) $V_B - V_A = 100V \Rightarrow V_B = 100 + 50 = 150V$

(C) $\frac{V_C - V_B}{22} + \frac{V_C - 0}{81} + \frac{V_C - V_D}{10} = 0$

(D) $\frac{V_D - V_A}{39} + \frac{V_D - V_B}{100} + \frac{V_D - V_C}{10} = 0$


$$\begin{bmatrix} \frac{1}{22} + \frac{1}{81} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{39} + \frac{1}{100} + \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_C \\ V_D \end{bmatrix} = \begin{bmatrix} \frac{150}{22} \\ \frac{50}{39} + \frac{150}{100} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_C \\ V_D \end{bmatrix} \approx \begin{bmatrix} 105.49V \\ 98.28V \end{bmatrix}$$


$$i_A = \frac{V_A - V_D}{39k\Omega} \approx -1.238mA, \quad i_B = \frac{V_D - V_C}{10k\Omega}$$

$$i_C = \frac{V_C}{81k\Omega} \approx 1.30mA, \quad \frac{V_B}{68} = i_D - i_C; \quad i_D = i_C + \frac{V_B}{68} = 3.51mA$$

3.47

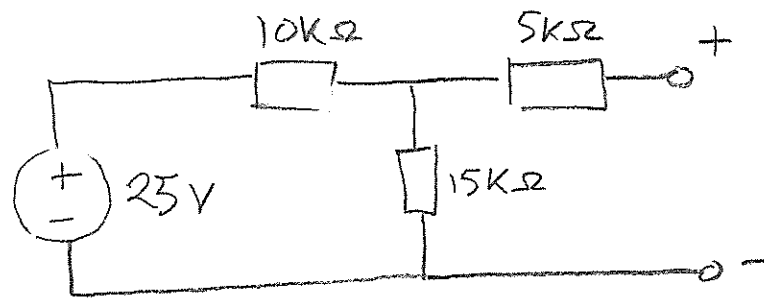


///

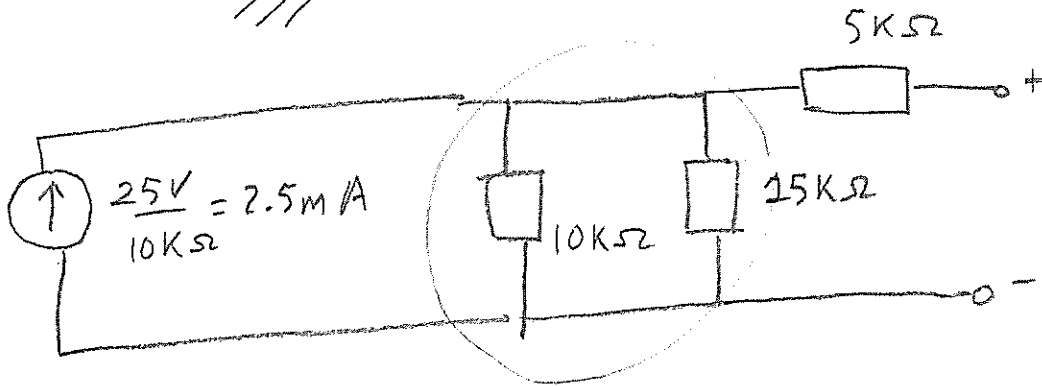


$$10 \parallel 15 = \frac{10 \cdot 15}{10 + 15} = 6 \text{ k}\Omega$$

///

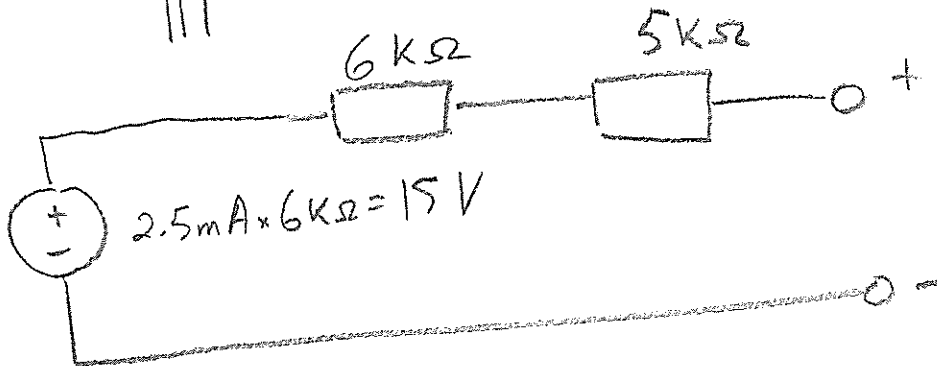


$$V_T = 15V; \quad R_T = 11 \text{ k}\Omega; \quad i_N = \frac{V_T}{R_T} = \frac{15V}{11 \text{ k}\Omega} = 1.36 \text{ mA}$$

3.52

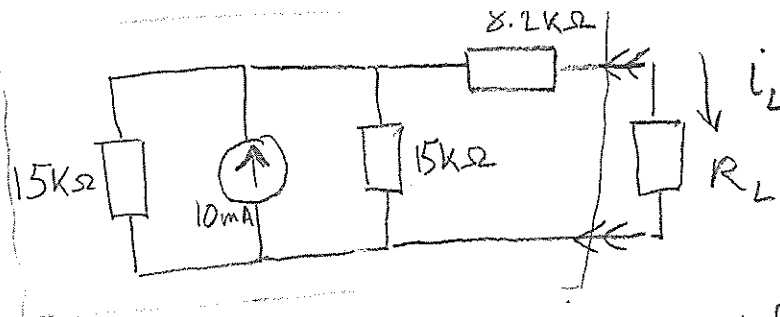


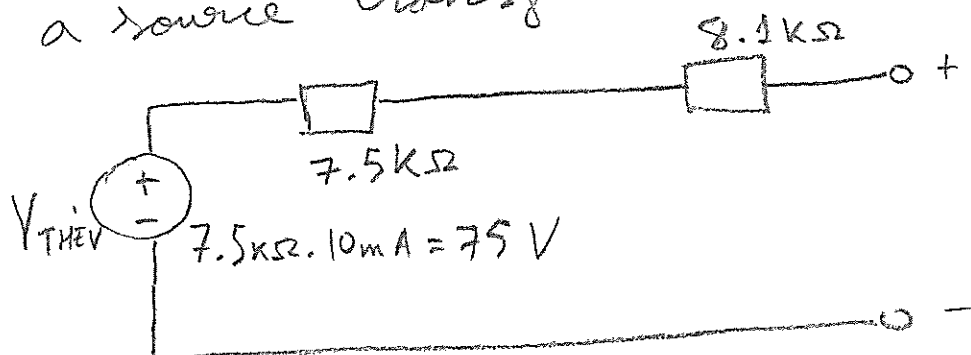We compute the Thévenin equivalent circuit by combining the parallel resistances and computing a source transformation



$$V_{THEV} = 75V$$


$$R_{THEV} = 7.5 + 8.1 = 15.6 k\Omega$$

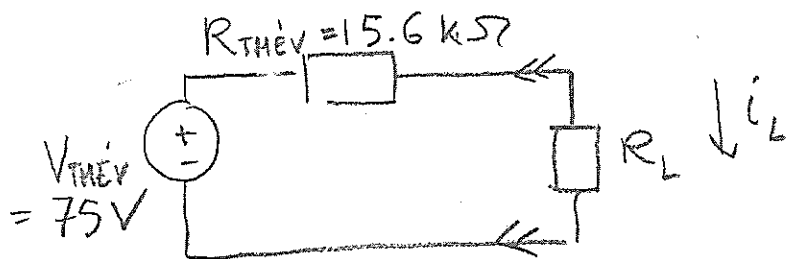

$$i_L = \frac{V_{THEV}}{R_{THEV} + R_L} = \frac{75V}{15.6k\Omega + R_L}$$

R_L	i_L
$4.7k\Omega$	$\frac{75}{15.6 + 4.7} \approx 3.70 \text{ mA}$
$15k\Omega$	$\frac{75}{15.6 + 15} \approx 2.45 \text{ mA}$
$68k\Omega$	$\frac{75}{15.6 + 68} \approx 0.89 \text{ mA}$

3.59

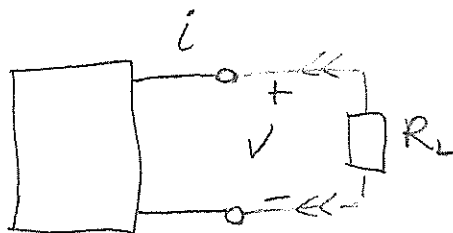

$$5V + 500i = 100$$

$$\left\{ \begin{array}{l} V = \frac{100}{5} - \frac{500}{5}i = 20 - 100i \\ \& \\ i = \frac{V}{R_L} \text{ (Ohm's law for the load)} \end{array} \right.$$

$$\Downarrow \\ V = 20 - 100\left(\frac{V}{R_L}\right);$$

$$V = \frac{20}{1 + \frac{100}{R_L}} = \frac{20}{1 + \frac{100}{500}} = \frac{20}{1 + \frac{1}{5}} = \frac{20.5}{6} \\ = \boxed{16.67 \text{ V}}$$