

Hw 4

3.2



$$\begin{aligned} I_{A'} &= I_S \\ I_{B'} &= I_A \\ I_{C'} &= I_B \end{aligned}$$



$$\rightarrow \begin{bmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} i_s R_1 \\ 0 \end{bmatrix}$$



$$I_A = \frac{\begin{vmatrix} i_s R_1 & -R_3 \\ 0 & R_3 + R_4 \end{vmatrix}}{|A|} = \boxed{\frac{i_s R_1 (R_3 + R_4)}{|A|}}$$

$$I_B = \frac{\begin{vmatrix} R_1 + R_2 + R_3 & i_s R_1 \\ -R_3 & 0 \end{vmatrix}}{|A|} = \boxed{\frac{i_s R_1 R_3}{|A|}}$$

$$V_x = (Ohm's\ law) \quad i_A R_2 = \frac{i_s R_1 R_2 (R_3 + R_4)}{|A|}$$

$$\underline{i_x} = i_B = \frac{I_S R_1 R_3}{|A|}$$

3.3

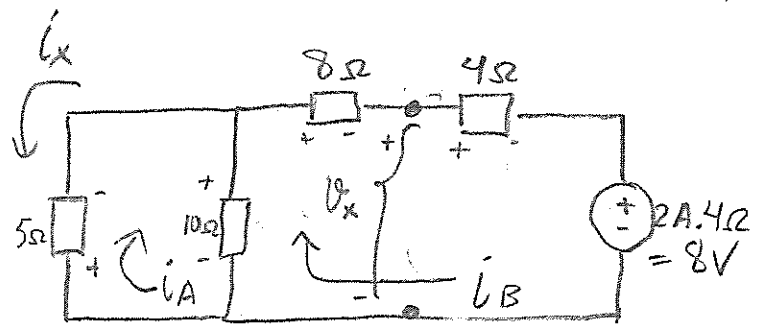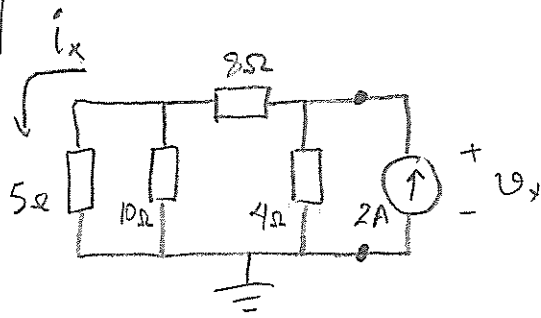

We use units Ω , A, V

Mesh (A): $5i_A + 10(i_A - i_B) = 0$

(B): $-10(i_A - i_B) + 8i_B + 4i_B + 8 = 0$


$$\Leftrightarrow \begin{bmatrix} +5+10 & -10 \\ -10 & 10+8+4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 0 \\ -8 \end{bmatrix} \Rightarrow \begin{matrix} i_A = -0.347 \text{ A} \\ i_B = -0.52 \text{ A} \end{matrix}$$

$\begin{matrix} A & & x & = & b \end{matrix}$

$$i_x = -i_A = \boxed{0.347 \text{ A}}$$

$$v_x = i_B \cdot 4\Omega + 8V = -0.52 \cdot 4 + 8 = \boxed{5.92 \text{ V}}$$

3.14

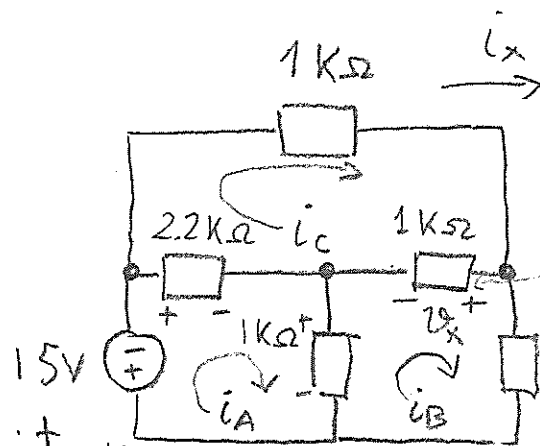

in the mesh analysis, the polarity "assigned" to the device is the opposite.

Using units $k\Omega$, mA , V

$$\text{Mesh (A): } 15 + 2.2(i_A - i_C) + 1(i_A - i_B) = 0$$

$$\text{" (B): } -1(i_A - i_B) + 1(i_B - i_C) + 2i_B = 0$$

$$\text{" (C): } -2.2(i_A - i_C) + 1i_C - 1(i_B - i_C) = 0$$


$$\Leftrightarrow \begin{bmatrix} 2.2+1 & -1 & -2.2 \\ -1 & 1+1+2 & -1 \\ -2.2 & -1 & 2.2+1+1 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -15 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow i_A = -10.48 \text{ mA} \quad i_B = -4.25 \text{ mA} \quad i_C = -6.50 \text{ mA}$$

$$i_x = i_C = \underline{-6.50 \text{ mA}}$$

$$v_x = 1k\Omega (i_C - i_B) = 1k\Omega (-6.5 - (-4.25)) \text{ mA} = \underline{-2.25 \text{ V}}$$

3.16

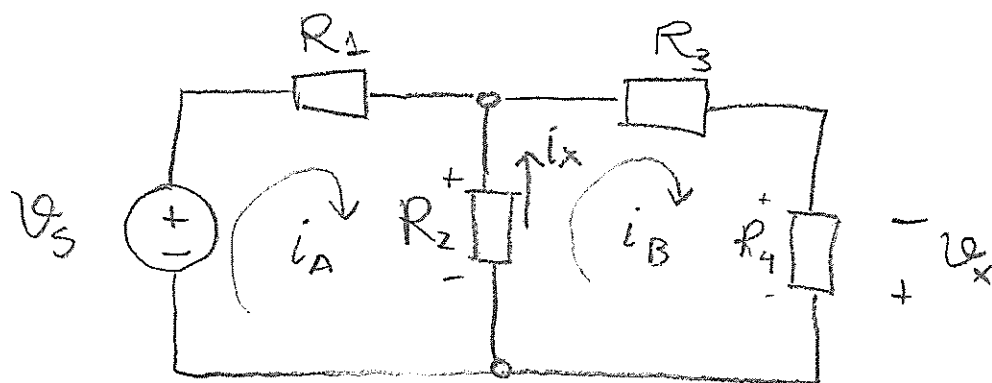

$$\text{Mesh (A)} \quad -V_s + R_1 i_A + R_2 (i_A - i_B) = 0$$

$$\text{Mesh (B)} \quad -R_2 (i_A - i_B) + R_3 i_B + R_4 i_B = 0$$

$$\Leftrightarrow \begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

(A) x = b)


$$i_A = \frac{\begin{vmatrix} V_s & -R_2 \\ 0 & R_2 + R_3 + R_4 \end{vmatrix}}{|A|} = \frac{V_s (R_2 + R_3 + R_4)}{|A|}$$

$$i_B = \frac{\begin{vmatrix} R_1 + R_2 & V_s \\ -R_2 & 0 \end{vmatrix}}{|A|} = \frac{V_s R_2}{|A|}$$

$$i_x = i_B - i_A = -\frac{V_s}{|A|} (R_3 + R_4)$$

$$V_x = -R_4 i_B = \frac{V_s R_2 R_4}{|A|}$$

3.23

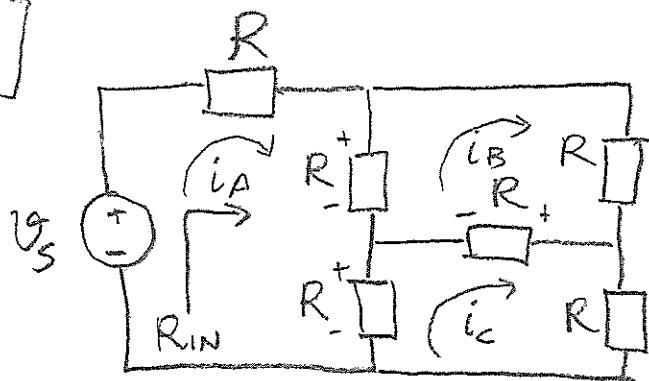

$$(A) -V_s + Ri_A + R(i_A - i_B) + R(i_A - i_C) = 0$$

$$(B) -R(i_A - i_B) + Ri_B + R(i_B - i_C) = 0$$

$$(C) -R(i_A - i_C) - R(i_B - i_C) + Ri_C = 0$$

$$\Leftrightarrow \begin{bmatrix} 3R & -R & -R \\ -R & 3R & -R \\ -R & -R & 3R \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix}$$


A x = b

$$\Rightarrow i_A = \frac{V_s}{2R} \quad i_B = \frac{V_s}{4R} \quad i_C = \frac{V_s}{4R}$$


Ohm's law

$$R_{IN} = \frac{V_s}{i_A} = \frac{V_s}{V_s/2R} = \boxed{2R}$$

3.26

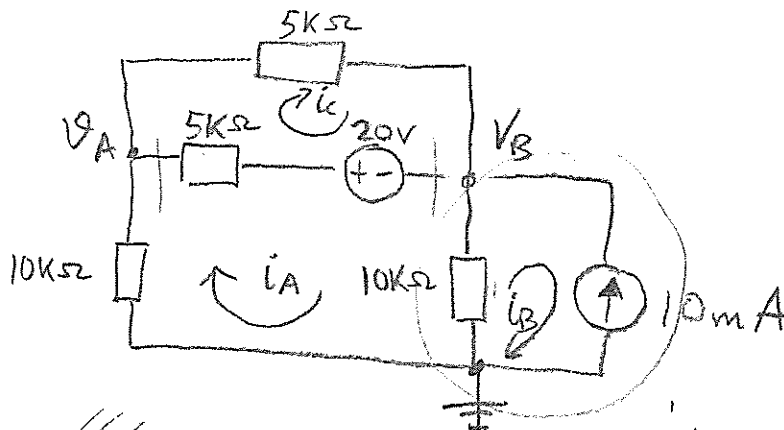

a)

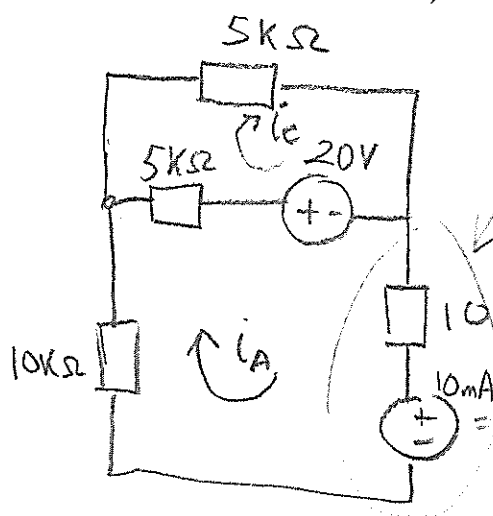

Mesh-current equations

i_A remains the same

and $i_B = -10 \text{ mA}$ *

Mesh C $5i_C - 20 + 5(i_C - i_A) = 0$


Mesh A $10i_A + 5(i_C - i_A) + 20 + 10i_A + 100 = 0$

Systems of same size

$$\Rightarrow \begin{bmatrix} 5+5 & -5 \\ -5 & 10+5+10 \end{bmatrix} \begin{bmatrix} i_C \\ i_A \end{bmatrix} = \begin{bmatrix} 20 \\ -20-100 \end{bmatrix}$$

$(i_A = -4.89 \text{ mA} \quad i_B = -10 \text{ mA}^* \quad i_C = -0.44 \text{ mA})$

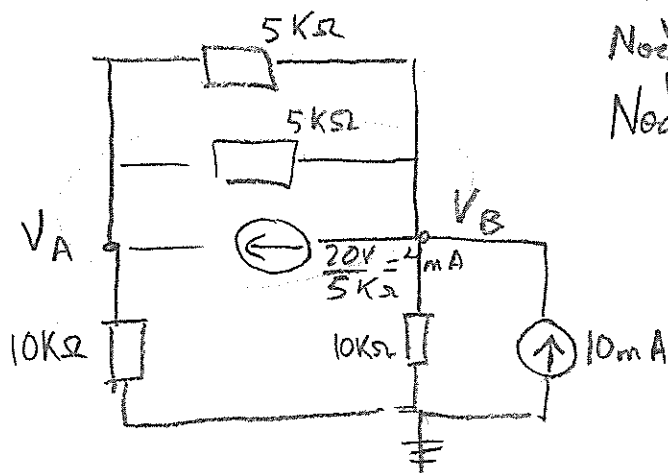b) To formulate the node-voltage equations, we compute another source transformation




Node A $\frac{V_A}{10} + \frac{(V_A - V_B)}{5} + \frac{(V_A - V_B)}{5} = 4$

Node B $\frac{V_B}{10} + \frac{V_B - V_A}{5} + \frac{V_B - V_A}{5} = 10 - 4$

$$\Rightarrow \begin{bmatrix} \frac{1}{10} + \frac{2}{5} & -\frac{2}{5} \\ -\frac{2}{5} & \frac{1}{10} + \frac{2}{5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4 \\ 6 \end{bmatrix}$$

3.27

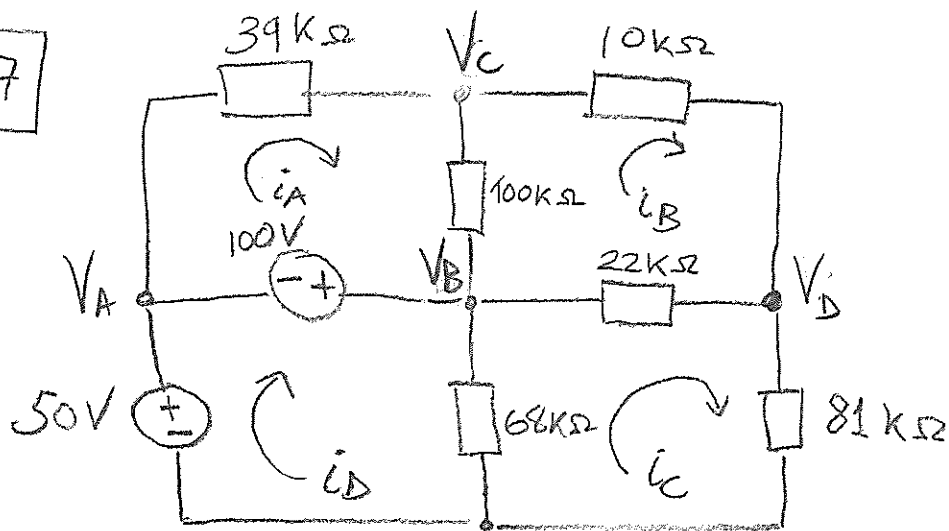

using units $k\Omega, mA, V$; $1mA = \frac{1V}{1k\Omega}$

Mesh(A): $39 i_A + 100(i_A - i_B) + 100$

(B): $-100(i_A - i_B) + 10 i_B + 22(i_B - i_C) = 0$

(C): $68(i_C - i_D) - 22(i_B - i_C) + 81 i_C = 0$

(D): $-50 - 100 - 68(i_C - i_D) = 0$

$$\Leftrightarrow \begin{bmatrix} 39+100 & -100 & 0 & 0 \\ -100 & 100+10+22 & -22 & 0 \\ 0 & -22 & 68+22+81 & -68 \\ 0 & 0 & -68 & 68 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \end{bmatrix} = \begin{bmatrix} -100 \\ 0 \\ 0 \\ 100+50 \end{bmatrix}$$

(A) x = b)

$i_A = -1.23 mA$

$i_B = -0.72 mA$

$i_C = 1.30 mA$



$i_D = 3.50 mA$

(In hw 3 we saw that we could determine right away the values of V_A and V_B , so we just needed to solve a system of 2 equations for V_C and V_D .)

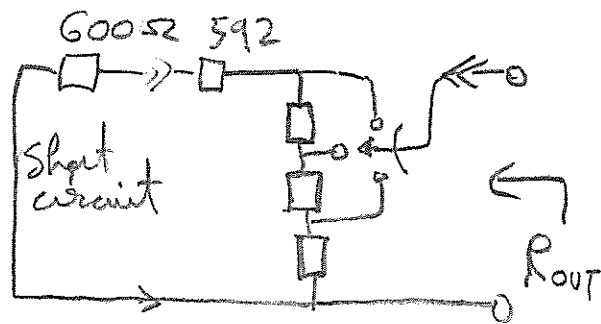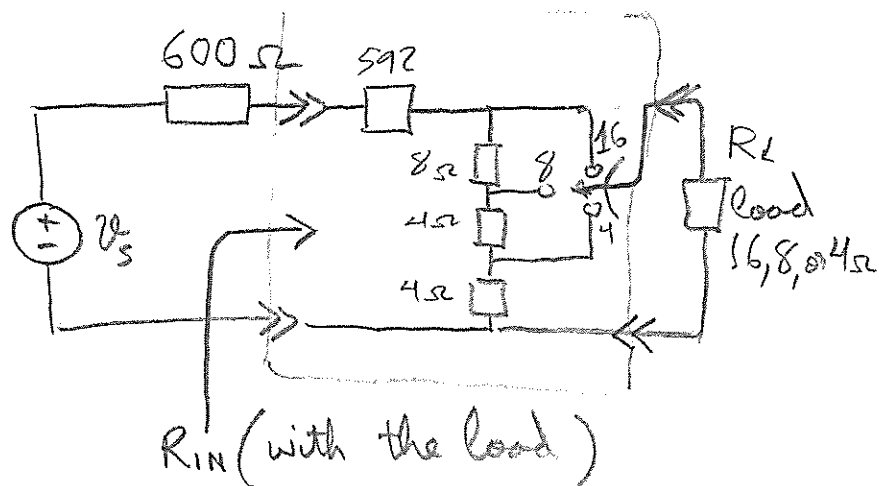3.91

NOTE FOR GRADER:

be flexible: the statement was hard to interpret.



R_{OUT} (from the perspective of the load with a short circuit where the source was)

$$R_L = 16\Omega \Rightarrow R_{IN} = 592 + (8 + 4 + 4) \parallel R_L \quad 2\% (600)$$

$$(WITH SWITCH UP) = 592 + (16 \parallel 16) = 600 \in (600 - 12, 600 + 12)$$

$$R_{OUT} = 1192 \parallel (8 + 4 + 4) = \frac{1192 \cdot 16}{1208} = 15.78 \in (16 - 0.32, 16 + 0.32)$$

$$2\% (16)$$

$$R_L = 8\Omega \Rightarrow R_{IN} = 592 + 8 + (4 + 4) \parallel R_L \quad 2\% (600)$$

$$(WITH SWITCH IN THE MIDDLE) = 592 + 8 + 4 = 604 \in (600 - 12, 600 + 12)$$

$$R_{OUT} = (1192 + 8) \parallel (4 + 4) = \frac{1200 \times 8}{1208} = 7.94$$

$$2\% (8)$$

$$R_L = 4\Omega \Rightarrow R_{IN} = 592 + 8 + 4 + (4 \parallel R_L) \in (8 - 0.16, 8 + 0.16)$$


$$(WITH SWITCH DOWN) = 606 \in (600 - 12, 600 + 12)$$

$$R_{OUT} = (1192 + 8 + 4) \parallel 4 = \frac{1204 \times 4}{1208} \approx 3.98 \in (4 - 0.08, 4 + 0.08)$$

$$2\% (4)$$


3.95

CIRCUIT 1

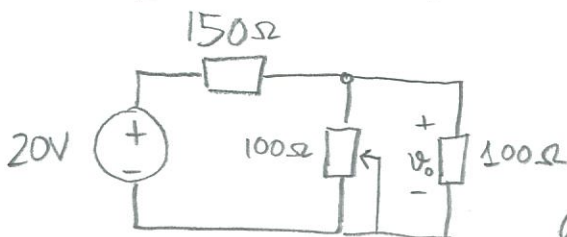


Position of the potentiometer

a)

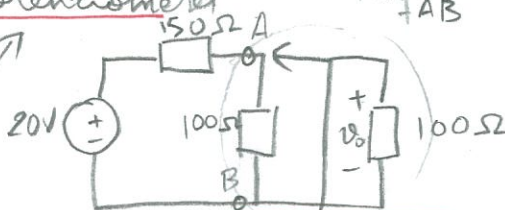


$$\Rightarrow v_o = 0V$$

$$R_{eq AB} = 0$$

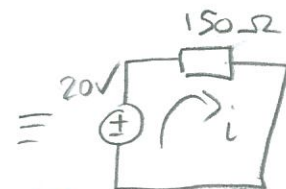


$$P = iV = \frac{V^2}{R} = \frac{20^2}{150} = 2.6W$$

b)

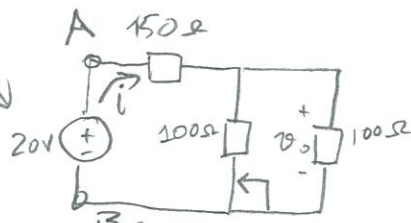

$$P = iV = \frac{V^2}{R_{eq AB}} = \frac{(20)^2}{(100 \parallel 100) + 150 \Omega} = \frac{400}{200} = 2W$$

(power delivered by source)

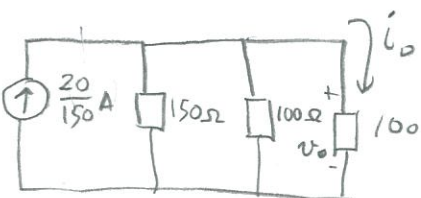


$$i_o = \frac{\frac{20}{150}}{\frac{1}{150} + \frac{1}{100} + \frac{1}{100}} = \frac{20}{150} \cdot \frac{100}{100 + 150} = \frac{20}{150} \cdot \frac{2}{3} = \frac{4}{45} A$$

$$v_o = i_o \cdot 100 \Omega = 5V$$


SAME TOPOLOGY IN THAT POSITION

CIRCUIT 2

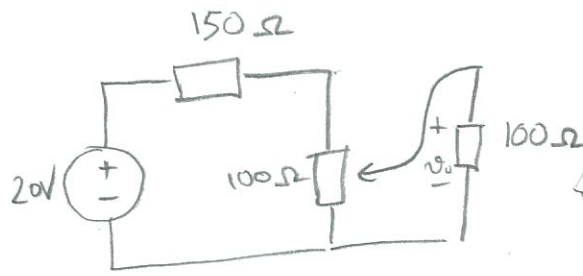

Position of the potentiometer

a)

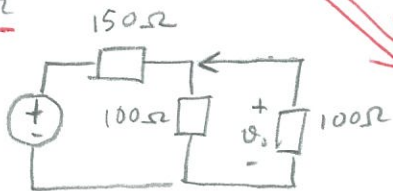


same topology as 1.b)

$$v_o = 5V$$

$$P = 2W$$

b)

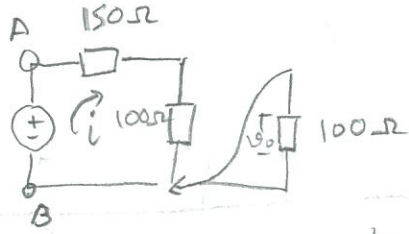


$$v_o = 0V$$

$$P = iV = \frac{V^2}{R_{eq AB}} = \frac{20^2}{250} = 1.6W$$



Both circuits drive the voltage from 0 to 5.
However, when $v_o = 0$ circuit 1 delivers 2.6W while circuit 2 delivers 1.6W.

CIRCUIT 2 consumes less to deliver the same voltage v_o

3.99

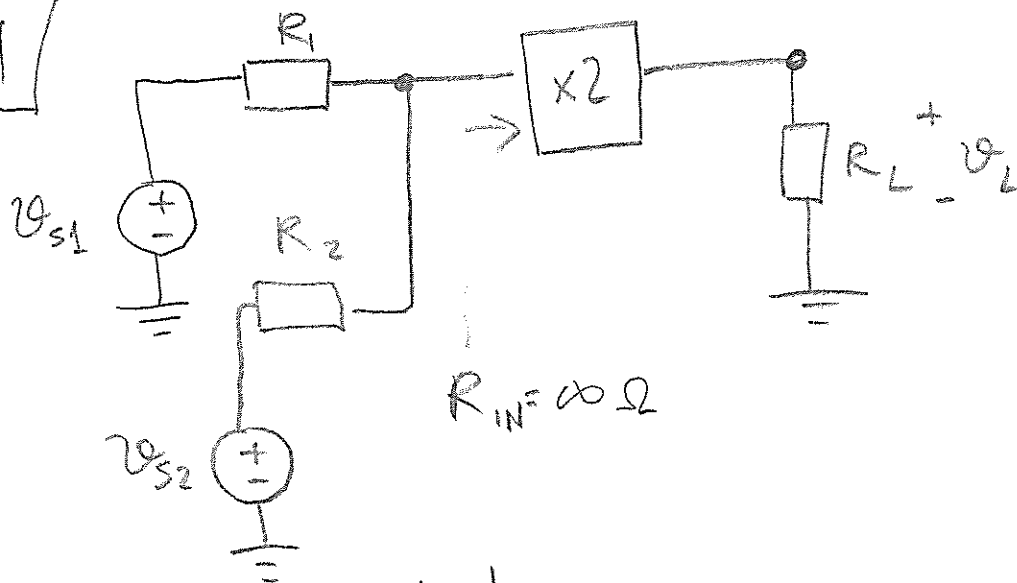

Computing equivalent sources

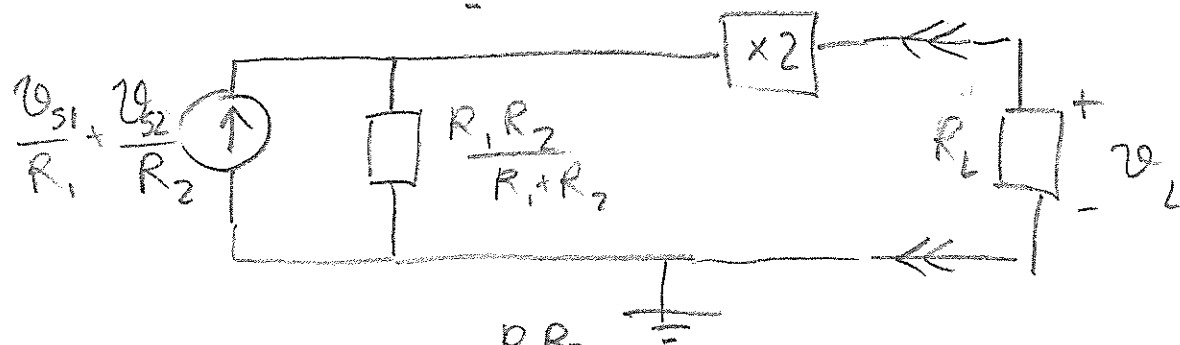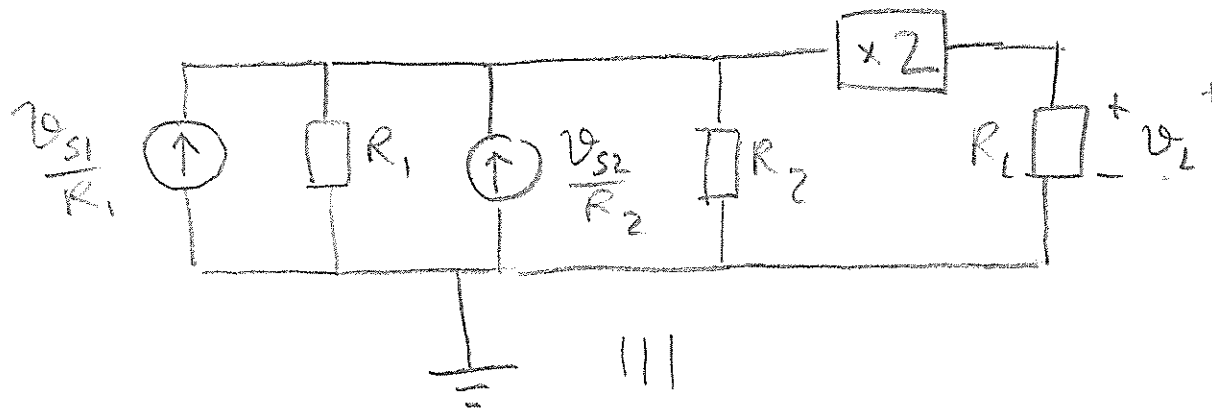

$$\begin{aligned} & \left(\frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2} \right) \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{v_{s1} R_2 + v_{s2} R_1}{R_1 R_2} \cdot \frac{R_1 R_2}{R_1 + R_2} \end{aligned}$$

$$v_L = 2 \left(\frac{v_{s1} R_2 + v_{s2} R_1}{R_1 + R_2} \right)$$