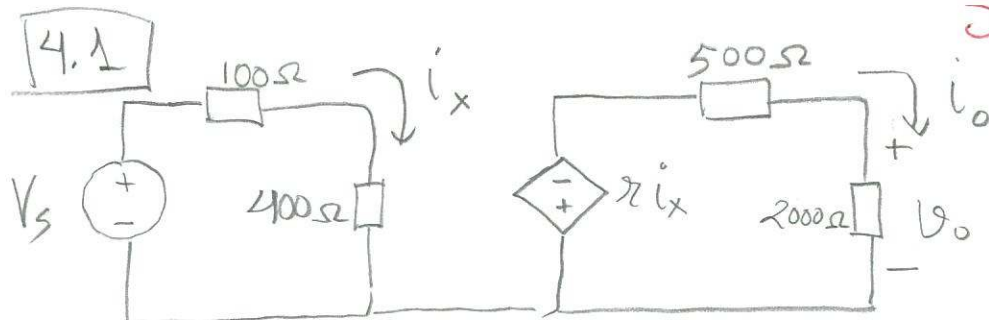




$$R = 5 \text{ k}\Omega$$

$$\frac{v_o}{V_s} = ? \quad \frac{i_o}{i_x} = ?$$


$$i_x \stackrel{(1)}{=} \frac{V_s}{(0.1 + 0.4) \text{ k}\Omega}; \quad \boxed{v_o = - \frac{2 \text{ k}\Omega}{0.5 \text{ k}\Omega + 2 \text{ k}\Omega} \cdot 2 i_x =}$$

$$\text{voltage divider} = - \frac{2 \cancel{\text{ k}\Omega} \cdot 5 \text{ k}\Omega}{2.5 \cancel{\text{ k}\Omega}} \cdot \frac{V_s}{0.5 \text{ k}\Omega} = -8 V_s \quad \boxed{}$$

The minus sign in the voltage divider comes from the polarity of the voltage dependent source

$$\boxed{i_o = \frac{v_o}{2 \text{ k}\Omega} = \frac{-8 V_s}{2 \text{ k}\Omega} \stackrel{(1)}{=} \frac{-8}{2 \cancel{\text{ k}\Omega}} \cdot 0.5 \cancel{\text{ k}\Omega} i_x = -2 i_x \quad \boxed{}$$

4.3

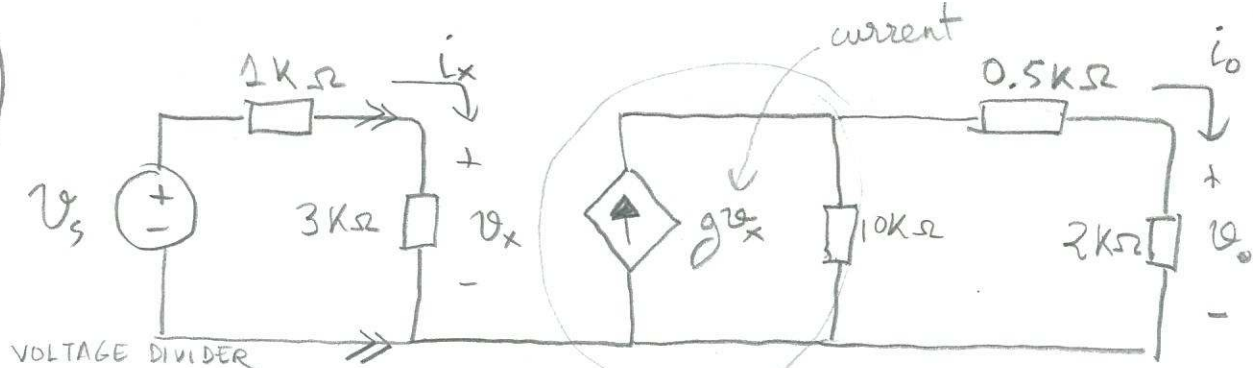


$$v_x \stackrel{\text{VOLTAGE DIVIDER}}{=} \frac{3}{1+3} v_s = 0.75 v_s \quad (2)$$

VOLTAGE DIVIDER

$$\begin{aligned} v_o &\stackrel{\text{VOLTAGE DIVIDER}}{=} \frac{2}{10+0.5+2} g v_x 10k\Omega \\ &= \frac{2}{12.5} \cdot 2 \cdot 10^{-3} \cdot 0.75 v_s \cdot 10k\Omega \\ &\stackrel{(1)}{=} 2.4 v_s \end{aligned}$$

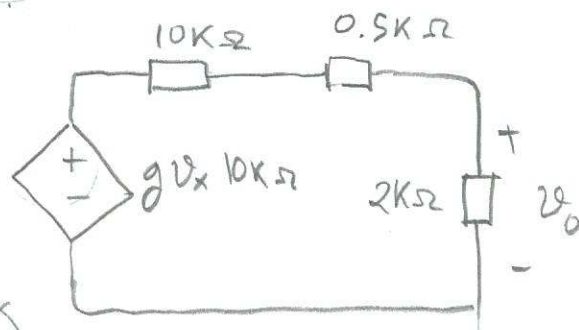(we use that $10^{-3} = \frac{1}{10^3} = \frac{1}{k\Omega}$)



$$\begin{aligned} i_o &= \frac{v_o}{2k\Omega} \stackrel{(1)}{=} \frac{2.4 v_s}{2k\Omega} \stackrel{(2)}{=} \frac{2.4 \times \left(\frac{v_x}{0.75}\right)}{2k\Omega} = \frac{2.4}{2k\Omega \times 0.75} \cdot 3k\Omega i_x \\ &= \frac{2.4 \times 3}{2 \times 0.75} i_x = 4.8 i_x \end{aligned}$$


$v_s = 5V$

$$P_{\text{delivered by source}} = v_s \cdot i_x = v_s \cdot \frac{i_o}{4.8} = v_s \cdot \frac{v_o/2k\Omega}{4.8} = \frac{v_s \cdot 2.4 v_s}{4.8 \times 2k\Omega} = 6.25 mV$$

$$\begin{aligned} P_{\text{consumed by } 2k\Omega \text{ load}} &= i_o v_o = \left(\frac{v_o}{2k\Omega}\right) \cdot v_o = \frac{v_o^2}{2k\Omega} = \frac{(2.4)^2 v_s^2}{2k\Omega} \\ &= 72 mV \end{aligned}$$

$v_s = 5V$

4.8

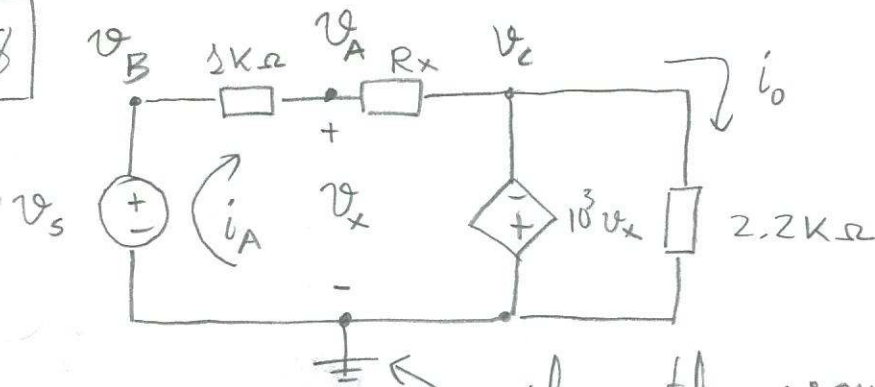

Units $k\Omega, mA, V$ choose the ground here because the
 $v_B = v_s$, $v_c = -10^3 v_x$ and $v_x = v_A$

The node equation at (A) is

$$\frac{v_A - v_B}{1} + \frac{v_A - v_c}{R_x} = 0 \Leftrightarrow \begin{bmatrix} \frac{1}{1k\Omega R_x} & -\frac{1}{1k\Omega R_x} \\ v_A \\ v_B \\ v_c \end{bmatrix} = 0$$

and substituting the values
in terms of v_s and v_x , we have

$$\left(1 + \frac{1}{R_x}\right) v_x - \frac{v_s}{1k\Omega} - \frac{1}{R_x} (-10^3 v_x) = 0$$

$$v_x \left(\frac{1}{1k\Omega} + \frac{1}{R_x} + \frac{10^3}{R_x} \right) = \frac{v_s}{1k\Omega}$$

$$v_x \approx \frac{v_s}{\frac{1001}{R_x} + \frac{1}{k\Omega}} = \frac{R_x v_s}{1001 + R_x}$$

$$i_o = \frac{v_c - 0}{2.2} = \frac{-10^3 v_x}{2.2} = \frac{-10^3 R_x v_s}{2.2k\Omega (1001 \times 10^3 + R_x)}$$

$$\frac{i_o}{v_s} = \frac{R_x}{2.2(1001 \times 10^3 + R_x)}$$

because I am using
 $k\Omega$ for R_x .

If we want the gain to be $-0.227 \frac{A}{V}$ ($-0.227 \frac{1}{\Omega}$)


we impose

$$\frac{-10^3 R_x}{2.2 \times 10^3 + 2.2 R_x} = -0.227 \frac{1}{\Omega} = -227 \frac{1}{k\Omega}$$

$$R_x = 996 k\Omega$$

to obtain $R_x (2.2(-227) + 10^3) = +2.2 \times 10^3 \times 227$; $R_x = \frac{499 \times 10^3}{500.6} k\Omega$


4.23

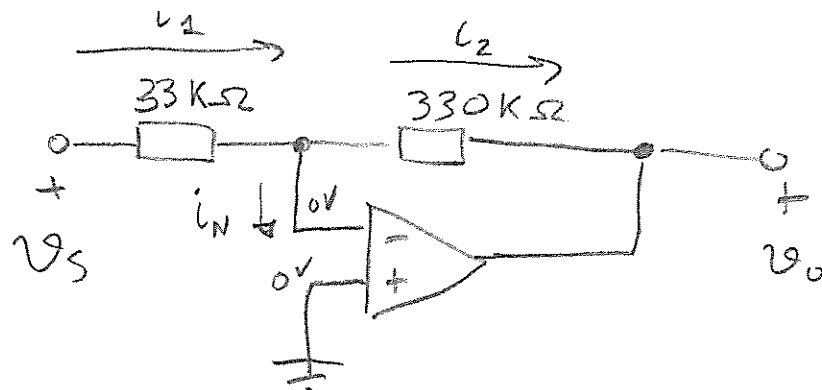

$$i_2 = \frac{V_o}{330 \text{ k}\Omega} ; i_1 = \frac{V_s}{33 \text{ k}\Omega}$$

Since $i_1 = i_2$ (because $i_N = 0$), we have
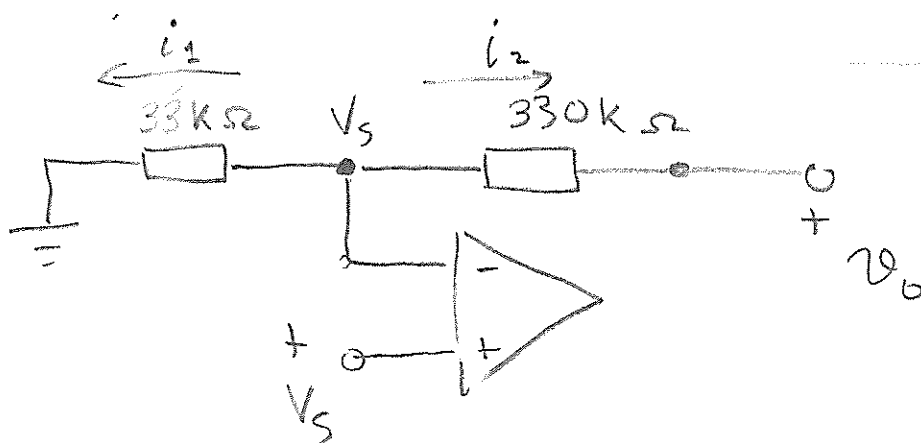
$$-\frac{V_o}{330 \text{ k}\Omega} = \frac{V_s}{33 \text{ k}\Omega} ; \boxed{V_o = -10 V_s}$$




$$i_1 = \frac{V_s - 0}{33 \text{ k}\Omega} ; i_2 = \frac{V_s - V_o}{330 \text{ k}\Omega}$$

Since $i_1 = i_2$, we have

$$\begin{aligned} \frac{V_s}{33 \text{ k}\Omega} &= \frac{V_o - V_s}{330 \text{ k}\Omega} ; \boxed{V_o = 330 V_s \left(\frac{1}{33} + \frac{1}{330} \right)} \\ &= \cancel{330} \left(\frac{10+1}{\cancel{330}} \right) V_s \\ &= \boxed{11 V_s} \end{aligned}$$

4.25

a)


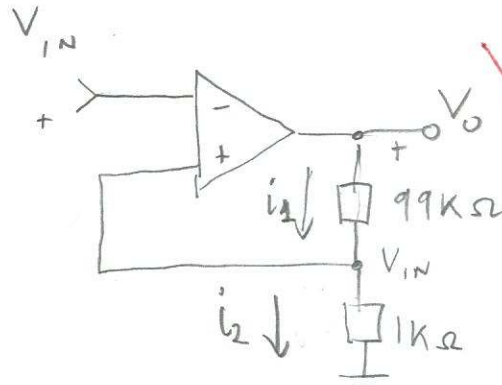


$$i_1 = \frac{V_O - V_{IN}}{99K\Omega}; \quad i_2 = \frac{V_{IN} - 0}{1K\Omega};$$

Since $i_1 = i_2 \Rightarrow \frac{V_O - V_{IN}}{99K\Omega} = \frac{V_{IN} - 0}{1K\Omega}; \quad V_O = 99V_{IN} \left(1 + \frac{1}{99}\right)$

$$= 99 \frac{100}{99} \cdot V_{IN} = 100V_{IN}$$


(*) and with practical source

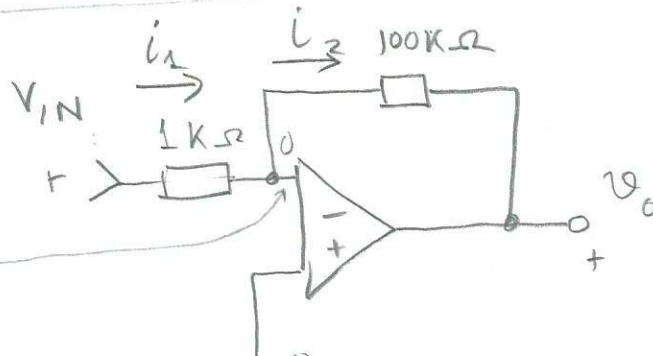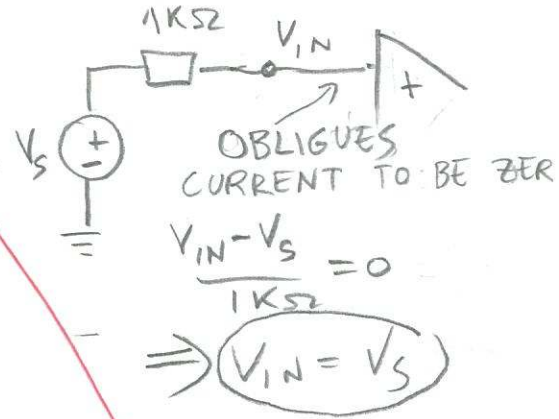

$i_N = 0$
 $i_1 = \frac{V_{IN}}{1K\Omega}; \quad i_2 = \frac{V_O - 0}{100K\Omega};$

Since $i_1 = i_2 \Rightarrow \boxed{V_O = -100 V_{IN}}$

(**) and with practical source:

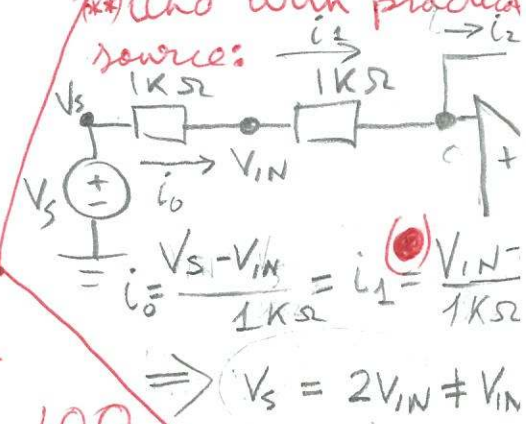

TRUE: Both circuits have a gain of 100. and -100 respect

b) WITH PRACTICAL SOURCE

CIRCUIT 2 (**)

CIRCUIT 1 (*)


Same gain because $V_{IN} = V_S$.

That is, $\boxed{V_O = 100 V_{IN} = 100 V_S}$

Different gain because $V_S = 2V_{IN}$


That is, $\boxed{V_O = -100 V_{IN} = -\frac{100}{2} V_S}$

4.26

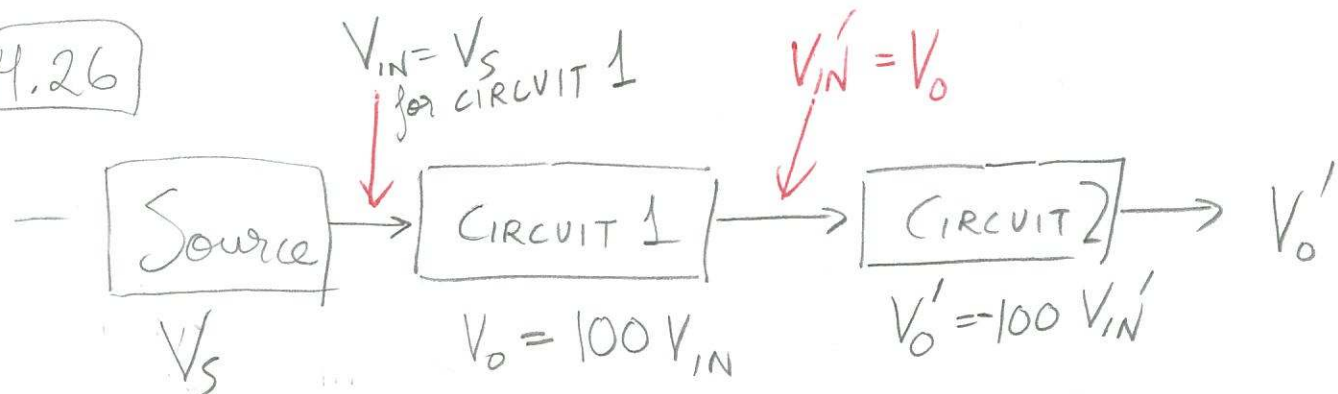


$$\text{So } V_O' = -100 V_{IN'} = -100 V_O = -100^2 V_N$$

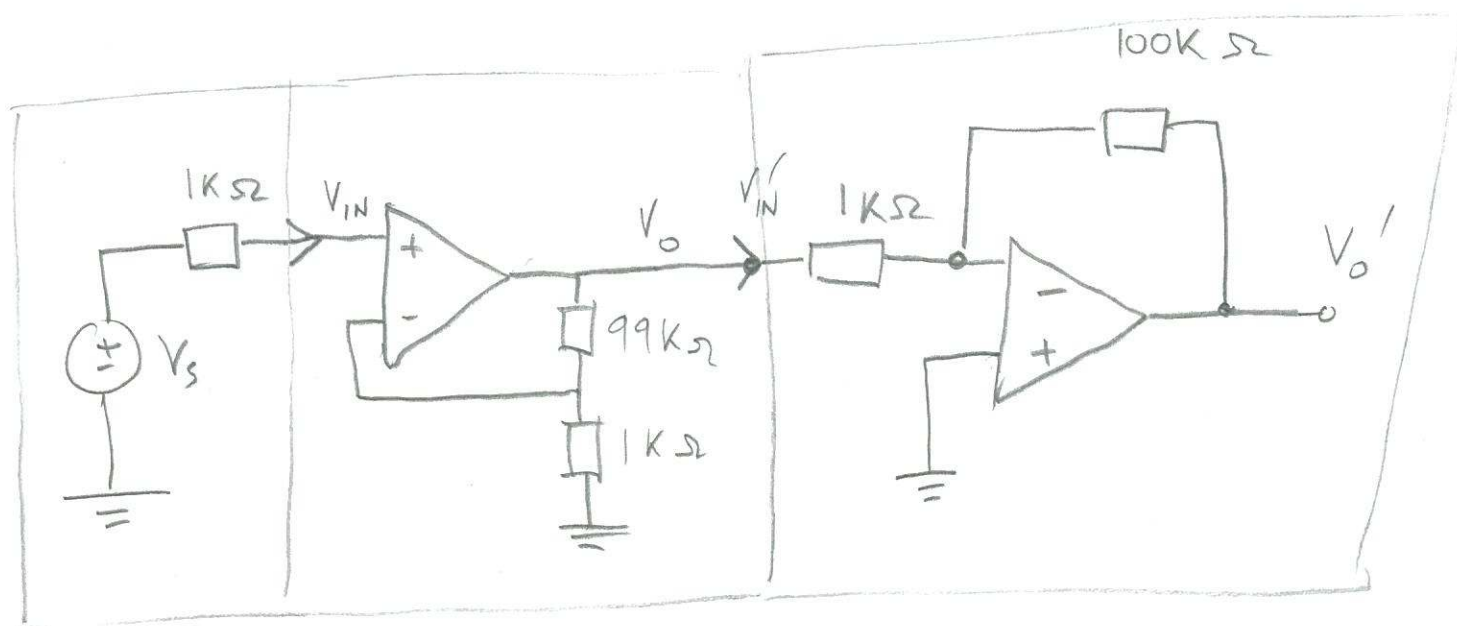We need to connect Circuit 1 first because its gain remains the same with respect to V_S .



4.36

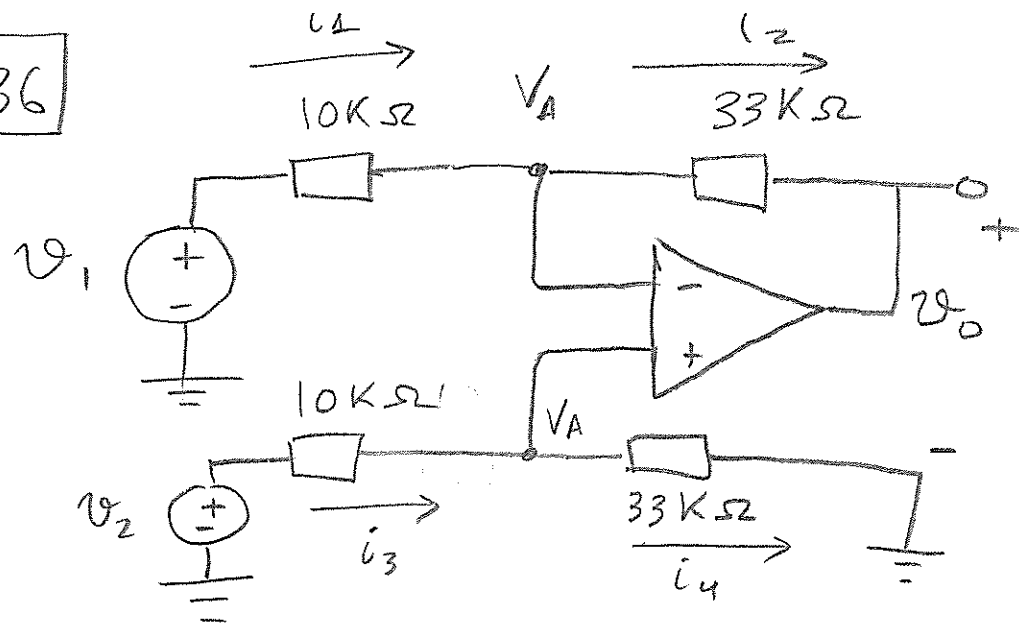


$$\text{Since } i_1 = i_2 \Rightarrow \frac{V_1 - V_A}{10} = \frac{V_A - V_0}{33} \Rightarrow V_0 = 33 \times \left(V_A \left(\frac{1}{33} + \frac{1}{10} \right) - \frac{V_1}{10} \right)$$

$$\text{Since } i_3 = i_4 \Rightarrow \frac{V_2 - V_A}{10} = \frac{V_A - 0}{33} \Rightarrow V_A \left(\frac{1}{33} + \frac{1}{10} \right) = \frac{V_2}{10}$$

So we can solve for V_A and V_0 but we just want to eliminate V_A and write V_0 in terms of V_1 and V_2 :

$$\boxed{V_0 = 33 \left(\frac{V_2}{10} - \frac{V_1}{10} \right) = -3.3 V_1 + 3.3 V_2}$$

4.38

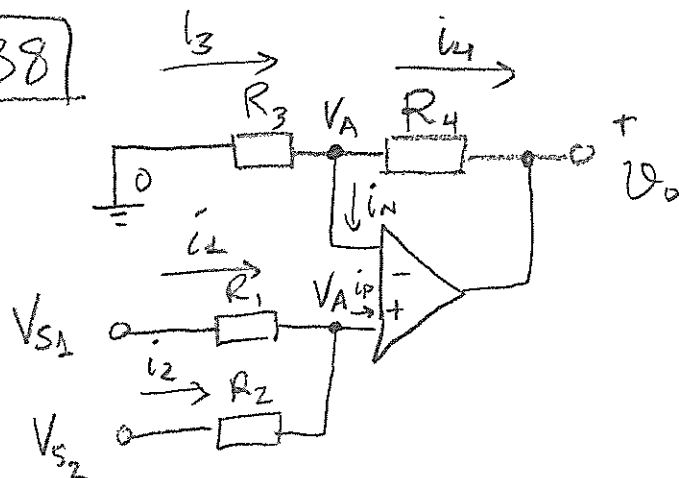

$$i_N = 0 \Rightarrow i_3 = i_4 \Rightarrow \frac{0 - V_A}{R_3} = \frac{V_A - v_o}{R_4} \quad (1)$$

$$i_P = 0 \Rightarrow i_1 + i_2 = 0 \Rightarrow \frac{V_{S1} - V_A}{R_1} + \frac{V_{S2} - V_A}{R_2} = 0 \quad (2)$$

$$\text{From (1)} \quad V_A \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{v_o}{R_4}$$

$$\text{From (2)} \quad \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_A = \frac{V_{S1}}{R_1} + \frac{V_{S2}}{R_2};$$

$$V_A = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \left(\frac{V_{S1}}{R_1} + \frac{V_{S2}}{R_2} \right) \quad (3)$$


Substituting (3) into (1), we get

$$v_o = R_4 \frac{\frac{1}{R_3} + \frac{1}{R_4}}{\frac{1}{R_1} + \frac{1}{R_2}} \left(\frac{V_{S1}}{R_1} + \frac{V_{S2}}{R_2} \right)$$

4.43

We decompose the circuit in two:


a)

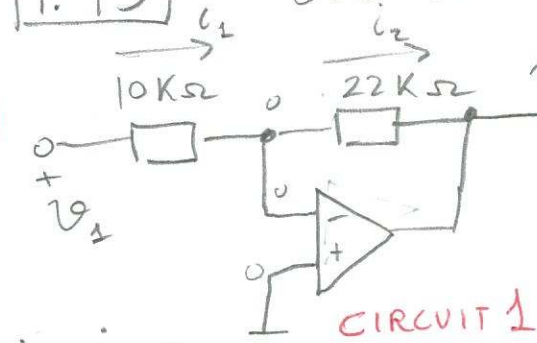

CIRCUIT 1

$$i_1 = i_2 \Rightarrow \frac{v_1 - 0}{10k\Omega} = \frac{0 - v_0'}{22k\Omega}$$

$$\Rightarrow \boxed{v_0' = -2.2 v_1}$$

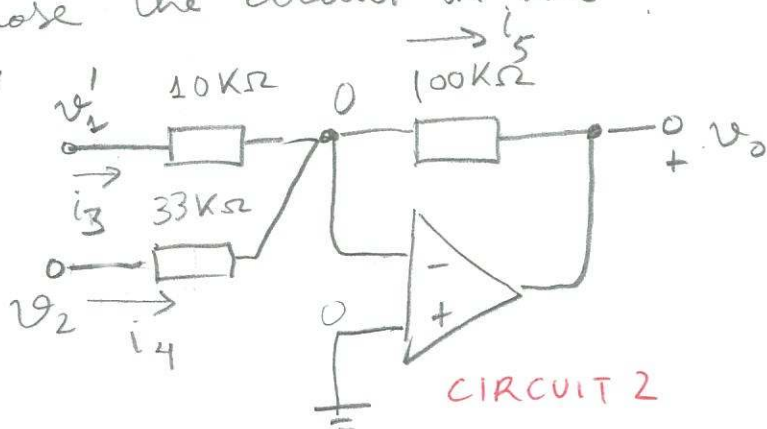

CIRCUIT 2

$$i_3 + i_4 = i_5 \Rightarrow$$

$$\frac{v_1' - 0}{10k\Omega} + \frac{v_2 - 0}{33k\Omega} = \frac{0 - v_0}{100k\Omega}$$

$$\Rightarrow \boxed{v_0 = -100 \left(\frac{v_1'}{10} + \frac{v_2}{33} \right)}$$

$$= -10v_1' - 3.03 v_2$$

Connecting the two (*) imposing

$$\boxed{v_1' = v_0'}$$

we get


$$\boxed{v_0 = -10(-2.2 v_1) - 3.03 v_2}$$

$$= +22 v_1 - 3.03 v_2$$


(*)



BLOCK DIAGRAM:

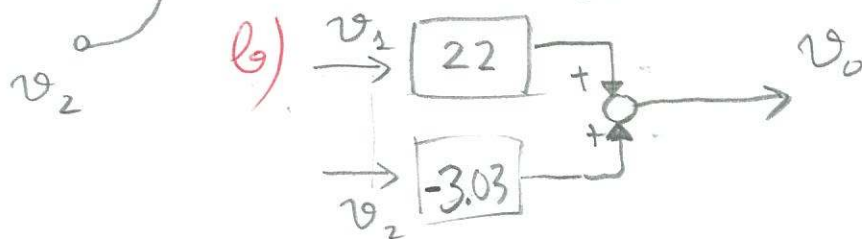

b)

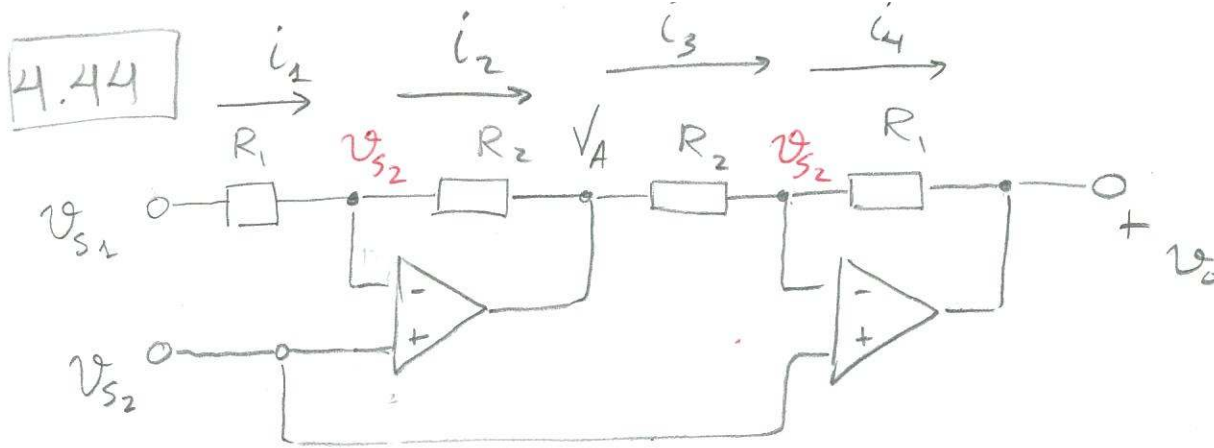

$$i_1 = i_2 \Rightarrow \frac{V_{s1} - V_{s2}}{R_1} = \frac{V_{s2} - V_A}{R_2}$$

$$i_3 = i_4 \Rightarrow \frac{V_A - V_{s2}}{R_2} = \frac{V_{s2} - V_o}{R_1}$$

One quantity is equal to minus the other. Hence, it is easy to eliminate V_A

So we can equate

$$\frac{V_{s1} - V_{s2}}{R_1} = - \frac{V_{s2} - V_o}{R_1}$$

$$\Rightarrow \boxed{V_o = V_{s1}}$$