

10.3

Solutions HW +



For the purpose of computing the impedance, we set the initial condition of the capacitor to 0.

$$a) \quad Z_{eq}(s) = \left(2R + \frac{1}{sC}\right) \parallel 2R = \frac{\left(2R + \frac{1}{sC}\right) 2R}{2R + \frac{1}{sC} + 2R}$$

$$= \frac{4R^2 s + \frac{2R}{C}}{4Rs + \frac{1}{C}} = R \frac{\left(s + \frac{1}{2RC}\right)}{s + \frac{1}{4RC}}$$

Zeros: $-\frac{1}{2RC}$

Poles: $-\frac{1}{4RC}$

To have a pole at -640 rad/s we require

$$b) \quad -\frac{1}{4RC} = -640 \text{ rad/s} \quad \text{or} \quad RC = \frac{1}{640} \text{ sec}$$

Selecting $R = 10 \text{ K}\Omega$ gives

$$C = \frac{1}{6400} \text{ mF}$$

The resulting zero is then

$$s_0 = -\frac{1}{2RC} = -\frac{1}{4RC} \cdot 2 = -640 \cdot 2 \frac{1}{s} = -1280 \text{ rad/s}$$

Note:

Henry = Ohm · sec

($v = L i'$)

Farad = sec / Ohm


$q = C v$

$i' = C v'$

and

$\frac{\text{rad}}{\text{sec}} = \frac{1}{\text{sec}}$

10.7

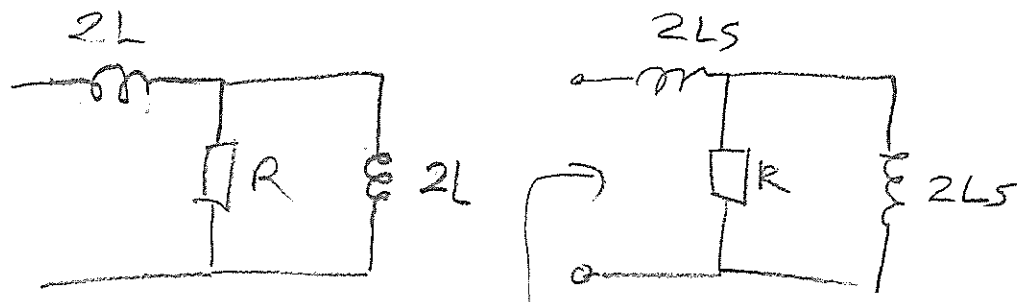

Z_{eq}

$$Z_{eq}(s) = 2Ls + (R \parallel 2Ls)$$

$$= 2Ls + \frac{R \cdot 2Ls}{R + 2Ls} = \frac{2LRS + 4L^2s^2 + R \cdot 2Ls}{R + 2Ls}$$

$$= \frac{4LRS + 4L^2s^2}{R + 2Ls} = \frac{s(2R + 2Ls)}{\frac{R}{2L} + s}$$

$$= 2L \frac{s\left(\frac{R}{L} + s\right)}{\frac{R}{2L} + s}$$

Zero: $-\frac{R}{L}$; poles $-\frac{R}{2L}$


So have a pole at -2 Krad/s , we impose

$-\frac{R}{2L} = -2 \text{ Krad/s}$. Selecting $R = 2 \text{ K}\Omega$, we need $L = 0.5 \text{ H}$


and the resulting zero is $-\frac{R}{L} = -\frac{R}{2L} \cdot 2 =$

$$= -2 \text{ Krad/s} \cdot 2 = -4 \text{ Krad/s}$$

10.17

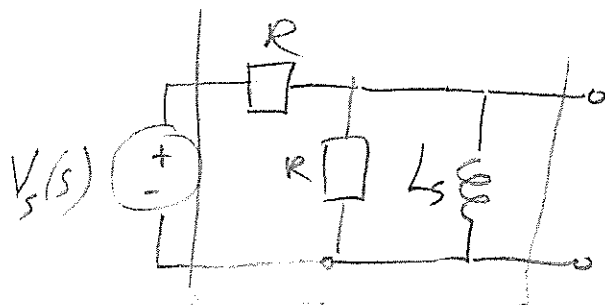

$V_T(s)$ $Z_T(s)$

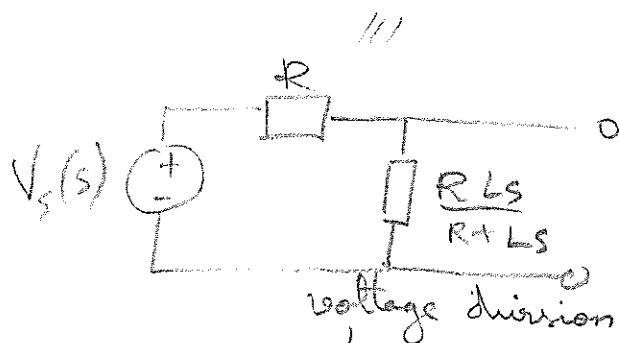

$$V_T(s) = \frac{\frac{RLs}{R+Ls}}{R + \frac{RLs}{R+Ls}}$$

$$V_s(s) = \frac{RLs}{(R+Ls)R + RLs}$$

$$= \frac{RLs}{R^2 + 2RLs} = \frac{1}{2} \frac{s}{\frac{R}{2L} + s} V_s(s)$$


$$Z_T(s) = R \parallel R \parallel Ls = \frac{R}{2} \parallel Ls = \frac{\frac{R}{2} Ls}{\frac{R}{2} + Ls} = \frac{\frac{R}{2} s}{\frac{R}{2L} + s}$$

For $V_T(s)$ to have a pole at -12 Krad/s ,

we impose $-\frac{R}{2L} = -12 \text{ Krad/s}$. Selecting

$R = 12 \text{ K}\Omega$, we get $L = 0.5 \text{ H}$.


10.19

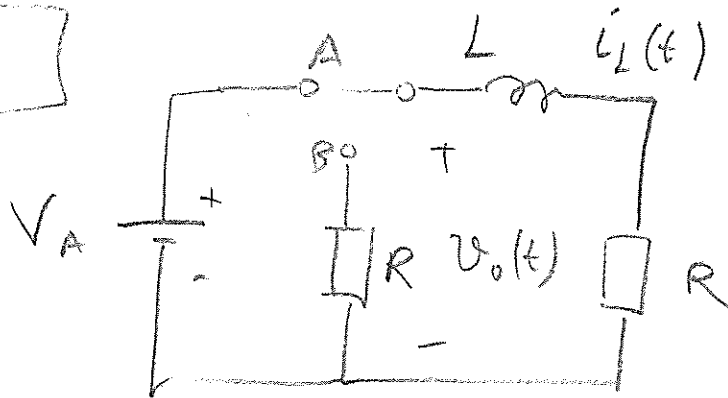

For a long time at A and then switch to B.

short circuit when switch is in position A

$$i_L(0) = \frac{V_A}{R}$$

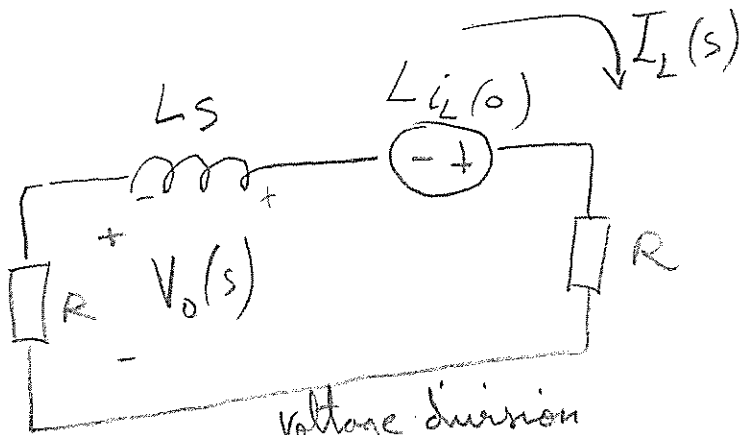

voltage division

$$V_0(s) = \frac{R}{R + Ls + R} \cdot L i_L(0) = -\frac{R}{2R + Ls} \cdot L \frac{V_A}{R}$$

because of the polarity of source


$$I = \frac{V_A}{\frac{2R}{L} + s}$$

$$I_L(s) = \frac{L i_L(0)}{2R + Ls} = \frac{L \frac{V_A}{R}}{2R + Ls} = \frac{\frac{V_A}{R}}{\frac{2R}{L} + s}$$

$$\text{So } V_0(t) = V_A e^{-\frac{2R}{L}t}$$


$$I_L(t) = \frac{V_A}{R} e^{-\frac{2R}{L}t}$$

10.29

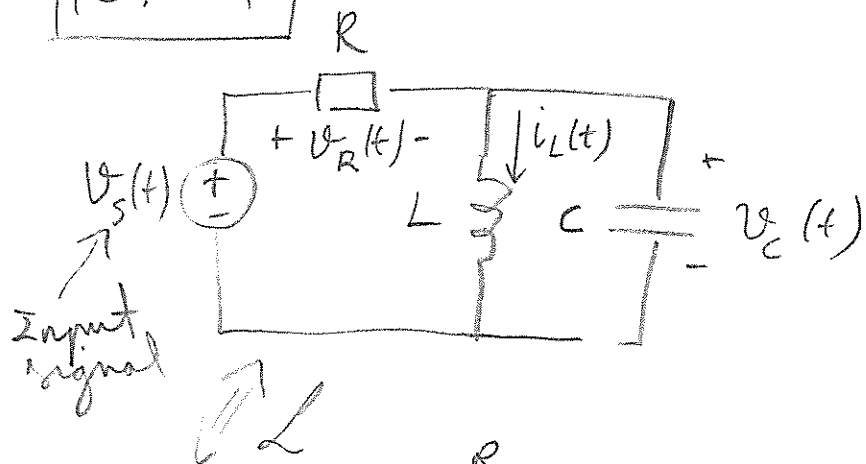


$$i_L(0) = I_0$$

$$V_C(0) = 0$$

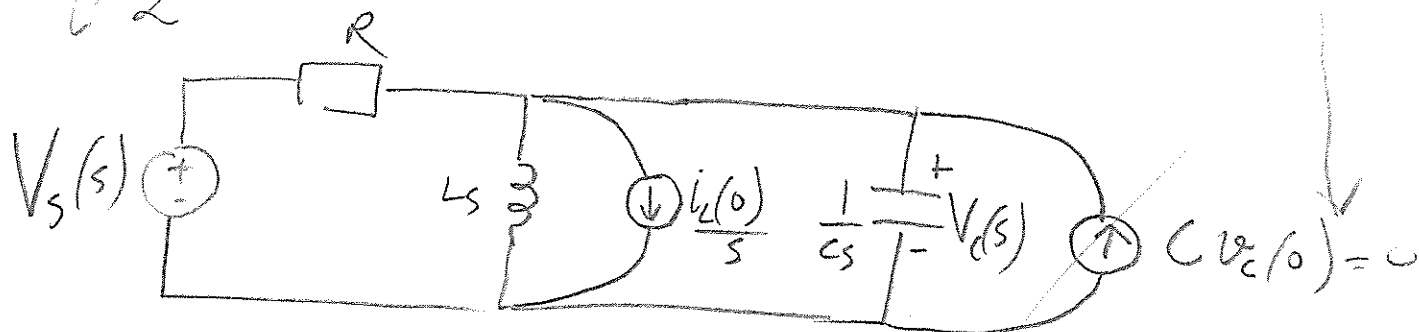

Zero input response: $V_s(s) = 0$

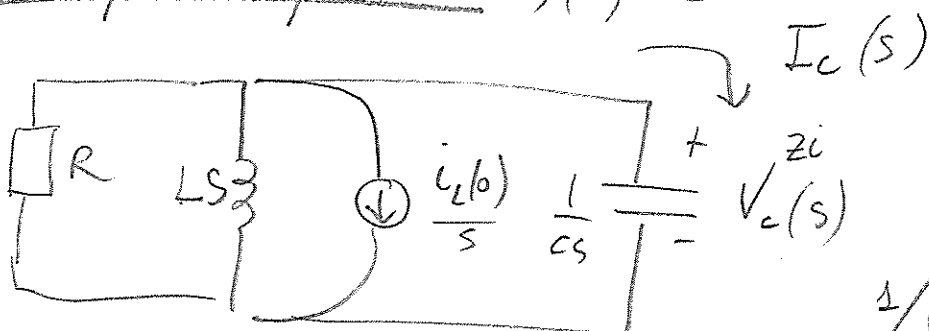

$$\text{Current division: } I_C(s) = \frac{\frac{1}{1/cs}}{\frac{1}{R} + \frac{1}{Ls} + \frac{1}{1/cs}} \left(-\frac{i_L(0)}{s} \right)$$


$$= -\frac{cs}{\frac{1}{R} + \frac{1}{Ls} + cs} \frac{i_L(0)}{s} = -\frac{c i_L(0)}{\frac{Ls + R + RLcs^2}{RLs}} = -\frac{RLcs}{R + Ls + RLcs^2} I_0$$

$$V_C^{\text{zi}}(s) = I_C(s) \cdot \frac{1}{cs} = -\frac{RL}{R + Ls + RLcs^2} I_0$$


$$= -\frac{\frac{1}{c} I_0}{\frac{1}{Lc} + \frac{1}{Rc}s + s^2}$$

10.29 / continued


Zero state response $i_L(0) = I_0 = 0$

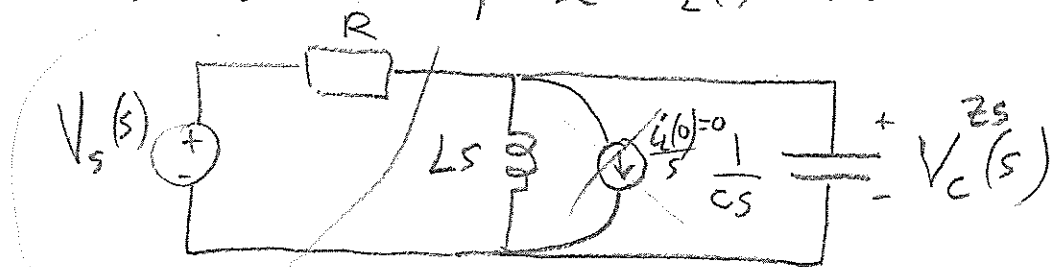

Source transformation

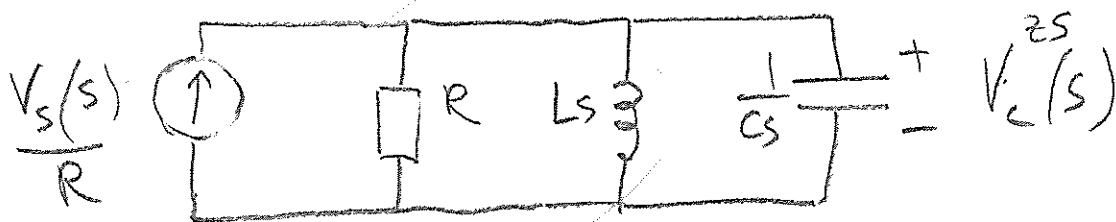


Source transformation

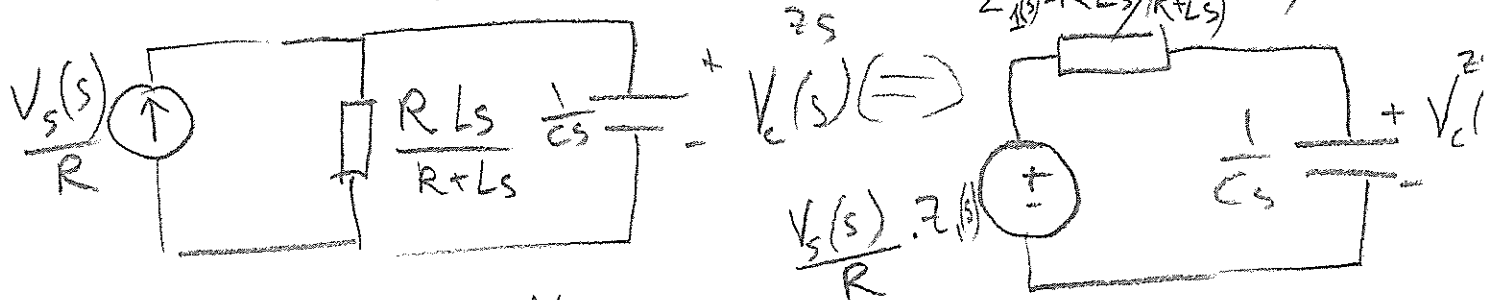


Now we use voltage division

$$\begin{aligned}
 V_c^zs(s) &= \frac{\frac{1}{cs}}{\frac{1}{cs} + Z_1(s)} \cdot \frac{V_s(s)}{R} \cdot Z_1(s) = \\
 &= \frac{V_s(s) Z_1(s)}{(1 + Z_1(s)cs)R} = \frac{V_s(s) \cancel{RLs/(R+Ls)}}{(1 + \frac{RLs}{(R+Ls)}cs) \cancel{R}} = \\
 &= \frac{Ls}{(R+Ls) + RLCs^2} V_s(s) = \frac{\frac{1}{RC}s}{\frac{1}{LC} + \frac{1}{RC}s + s^2} V_s(s)
 \end{aligned}$$

10.32

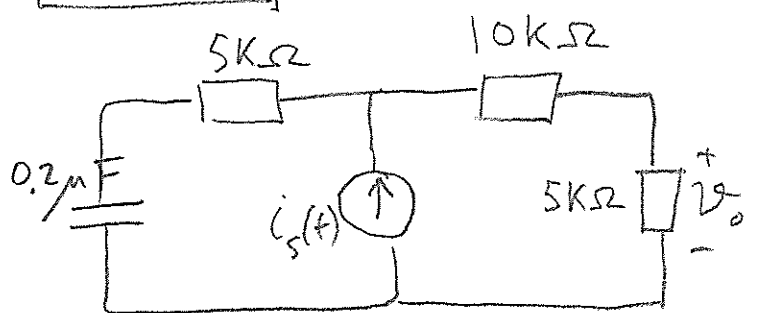

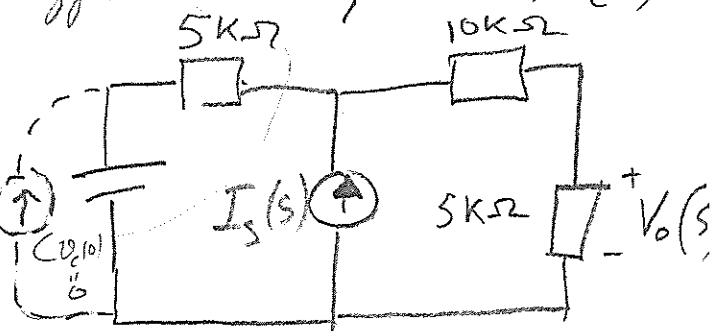No energy stored in capacitor $\Rightarrow V_o(0) = 0$





source transform.

You can use current division there or voltage divider later.

$$Z_1(s) = 5k\Omega + \frac{1}{0.2 \mu F s}$$
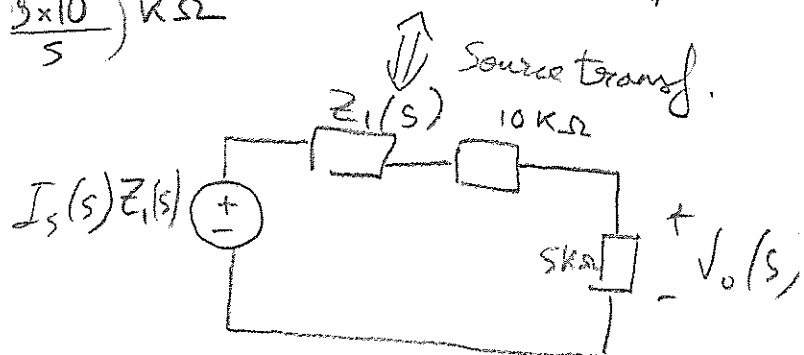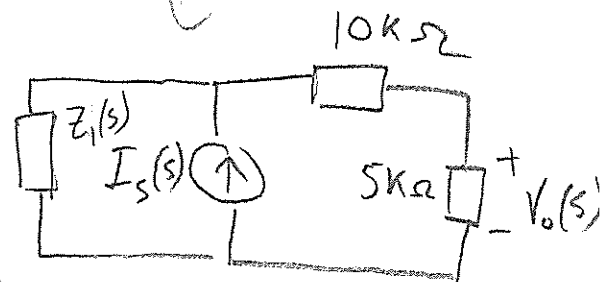
$$= 5k\Omega + \frac{5}{(10^{-3} \text{ mF})s} (5 + \frac{5 \times 10^3}{s}) k\Omega$$



Voltage division:

$$V_o(s) = \frac{5k\Omega}{5 + 10k\Omega + Z_1(s)} \cdot Z_1(s) \cdot I_s(s)$$

$$\left(I_s(s) = \frac{5}{s+500} \text{ mA} \right) = \frac{5k\Omega}{\left(15 + 5 + \frac{5 \times 10^3}{s} \right) k\Omega} \left(5 + \frac{5 \times 10^3}{s} \right) k\Omega \boxed{I_s(s)}$$

$$= \frac{(25s + 25 \times 10^3)}{20s + 5 \times 10^3} \times k\Omega \times \frac{5}{s+500} \text{ mA}$$

10.32 continued.

$$V_o(s) = 25 \frac{s+10^3}{4s+10^3} \cdot \frac{1}{s+500} \quad \begin{matrix} \text{volt. secans} \\ \downarrow \\ \text{V.s} \end{matrix}$$

proper

$$V_o(s) = \frac{K_1}{s+250} + \frac{K_2}{s+500}$$

$$\text{where } K_1 = \lim_{s \rightarrow -250} \frac{25}{4} \frac{(s+10^3)}{(s+250)(s+500)} \cdot (s+250)$$

$$= \frac{25}{4} \frac{-250+10^3}{-250+500} = \frac{25}{4} \frac{750}{250}$$

$$= \frac{25 \times 3}{4} = 18.75$$



$$K_2 = \lim_{s \rightarrow -500} \frac{25}{4} \frac{s+10^3}{s+250} \cdot \frac{(s+500)}{(s+500)}$$

$$= \frac{25}{4} \frac{500}{-250} = -\frac{25}{2} = -12.5$$

$$\text{So } V_o(t) = 18.75 \cdot e^{-250t} - 12.5 e^{-500t} \quad \checkmark$$

The forced pole comes from $i_s(t) = 5e^{-500t} \Rightarrow \frac{5}{s+500}$
I.e., the forced pole is -500.

10.46

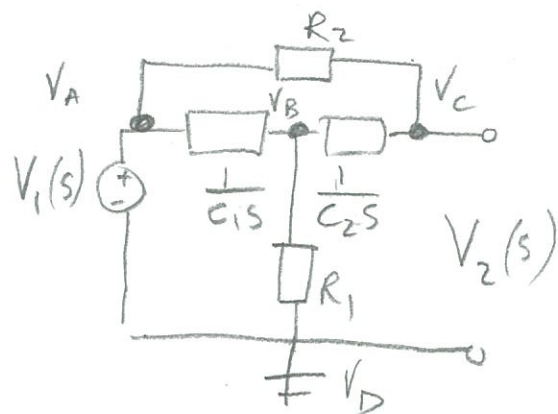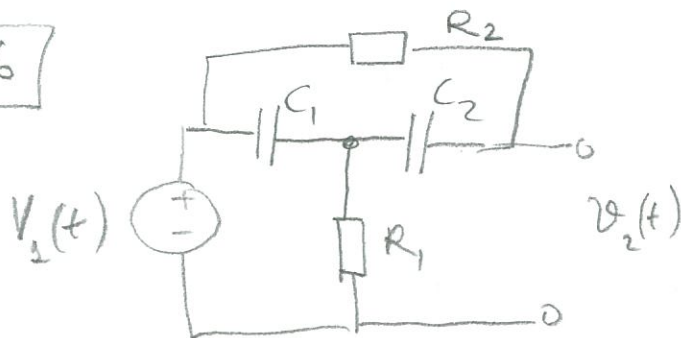

INPUT OUTPUT
 $V_D = 0$; $V_A = V_1(s)$; $V_2(s) = V_C$

Node B

$$\begin{bmatrix} A & B & C \\ -C_1 s & C_1 s + C_2 s + \frac{1}{R_1} & -C_2 s \\ -\frac{1}{R_2} & -C_2 s & C_2 s + \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C = V_2(s) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$\nearrow$ Known V_1 column

We need to solve for V_C and V_B in terms of V_A (although we just really need V_C)


$$\begin{matrix} (B) & (C) \\ \begin{bmatrix} C_1 s + C_2 s + \frac{1}{R_1} & -C_2 s \\ -C_2 s & C_2 s + \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} V_B \\ V_2(s) \end{bmatrix} & = \begin{bmatrix} C_1 s V_1(s) \\ \frac{1}{R_2} V_1(s) \end{bmatrix} \end{matrix}$$

A

CRAMER:

$$V_2(s) = \frac{\begin{vmatrix} C_1 s + C_2 s + \frac{1}{R_1} & C_1 s V_1(s) \\ -C_2 s & \frac{1}{R_2} V_1(s) \end{vmatrix}}{|A|}$$

10.53

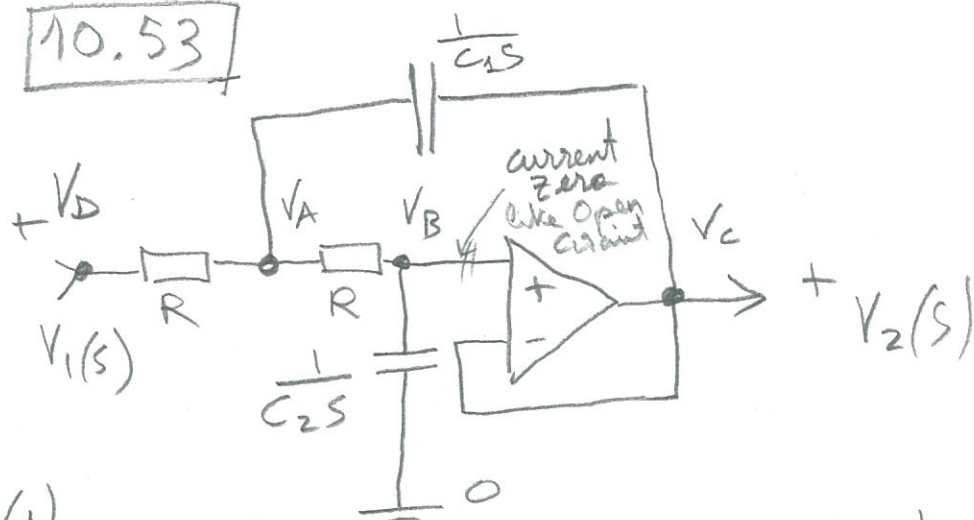

(1) $V_B = V_C$; $V_D = V_1(s)$; $V_C = V_2(s)$

Node A $\begin{bmatrix} \frac{1}{R} + \frac{1}{R} + C_1 S & -\frac{1}{R} - C_1 S & -\frac{1}{R} \end{bmatrix}$
 Node B $\begin{bmatrix} -\frac{1}{R} & \frac{1}{R} + C_2 S & 0 \end{bmatrix}$

$\begin{bmatrix} V_A \\ V_B \\ V_C = V_2(s) \\ V_D = V_1(s) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$

The unknowns are V_A, V_B, V_C .
 (since we are given $V_D = V_1(s)$ as input)

We need three equations
 (1), (2) and (3)

Using $V_B = V_C$ and moving V_D to the right hand side

Using $V_B = V_C$ and moving V_D to the right hand side

Node A $\begin{bmatrix} \frac{1}{R} + \frac{1}{R} + C_1 S & -\frac{1}{R} - C_1 S \end{bmatrix}$
 Node B $\begin{bmatrix} -\frac{1}{R} & \frac{1}{R} + C_2 S \end{bmatrix}$

$\begin{bmatrix} V_A \\ V_2(s) \end{bmatrix} = \begin{bmatrix} \frac{1}{R} V_D = V_1(s) \\ 0 \end{bmatrix}$

with $\Delta(s) = \left(\frac{2}{R} + C_1 S \right) / \left(\frac{1}{R} + C_2 S \right) - \left(\frac{1}{R} + C_1 S \right) \frac{1}{R}$

$\Delta(s) = \frac{2}{R^2} + \frac{2C_2 S}{R} + \frac{C_1 S}{R} + C_1 C_2 S^2 - \frac{1}{R^2} - \frac{C_1 S}{R} = \frac{1}{R^2} + \frac{2C_2 S}{R} + C_1 C_2 S^2$

Cramer's rule

$V_2(s) = \frac{\begin{vmatrix} \frac{2}{R} + C_1 S & \frac{1}{R} V_1(s) \\ -\frac{1}{R} & 0 \end{vmatrix}}{\Delta(s)} = \frac{V_1(s)}{R^2 \Delta(s)}$

10.53 continued.

We have seen that

$$\Delta(s) = \frac{1}{R^2} + \frac{2C_2}{R} s + C_1 C_2 s^2$$

The current determinant is then

$$\begin{aligned} \frac{\Delta(s)}{C_1 C_2} &= s^2 + \frac{2}{C_1 R} s + \frac{1}{C_1 C_2 R^2} \\ &= s^2 + 2\zeta\omega_0 s + \omega_0^2 \end{aligned}$$

$$\text{so } \omega_0^2 = \frac{1}{C_1 C_2 R^2} \quad ; \quad \omega_0 = \frac{1}{\sqrt{C_1 C_2} R}$$

$$2\zeta\omega_0 = \frac{2}{C_1 R} \quad ; \quad \zeta = \frac{1}{C_1 R \omega_0} = \frac{\sqrt{C_1 C_2} R}{C_1 R}$$


If we need $\omega_0 = 10 \text{ Krad/s}$ and $\zeta = 1$

$$\text{we impose } \frac{1}{\sqrt{C_1 C_2} R} = 10 \text{ Krad/s} \quad \sqrt{\frac{C_2}{C_1}} = 1$$

For instance, we can take $C_1 = C_2 = C$
which yields $\frac{1}{\sqrt{C_1 C_2} R} = \frac{1}{CR} = 10 \text{ Krad/s}$.

If we select $C = 0.1 \mu\text{F}$, we need $R = 1 \text{ k}\Omega$
because then $\frac{1}{CR} = \frac{1}{0.1 \mu\text{F} \cdot 1 \text{ k}\Omega} = \frac{1}{0.1 \times 10^{-6} \text{ F} \cdot 10^3 \Omega} = 10^4 \text{ rad/s}$

10.56

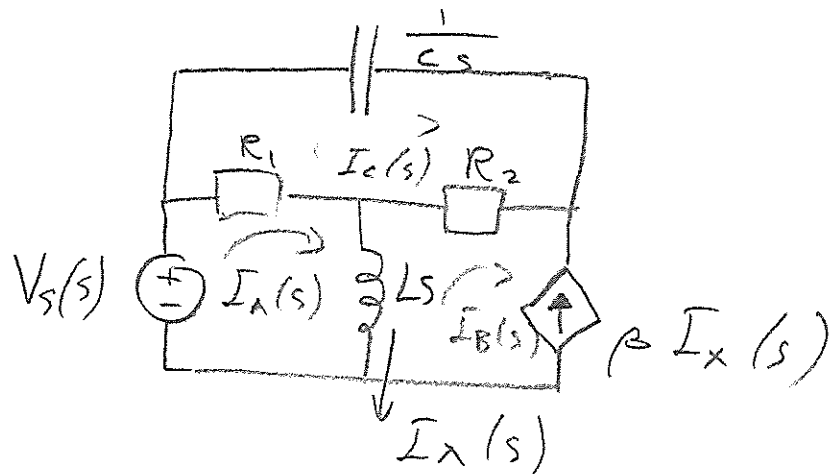

Only $I_C(s)$ and $I_A(s)$ or $I_C(s)$ and $I_B(s)$ are independent because

$$I_B(s) = -\beta I_X(s) = -\beta(I_A(s) - I_B(s))$$

$$\text{I.e., } \boxed{(1-\beta) I_B(s) = -\beta I_A(s)}$$


Mesh current equations

$$\begin{bmatrix} \frac{1}{cs} + R_1 + R_2 & -R_1 & -R_2 \\ -R_1 & R_1 + Ls & -Ls \end{bmatrix} \begin{bmatrix} I_C(s) \\ I_A(s) \\ I_B(s) = -\frac{\beta}{1-\beta} I_A(s) \end{bmatrix} = \begin{bmatrix} 0 \\ V_S(s) \end{bmatrix}$$

In terms of just $I_C(s)$ and $I_A(s)$:

$$\begin{bmatrix} \frac{1}{cs} + R_1 + R_2 & -R_1 - R_2 \left(\frac{\beta}{1-\beta} \right) \\ -R_1 & R_1 + Ls - Ls \left(\frac{\beta}{1-\beta} \right) \end{bmatrix} \begin{bmatrix} I_C(s) \\ I_A(s) \end{bmatrix} = \begin{bmatrix} 0 \\ V_S(s) \end{bmatrix}$$

10.61

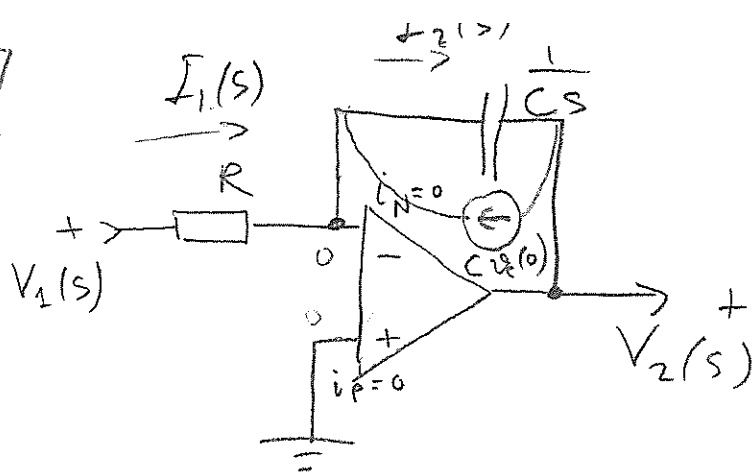

$$v_1(t) = \cos 1000t$$

$\Downarrow \mathcal{L}$

$$V_1(s) = \frac{s}{s^2 + 10^6}$$

We desire $v_2(t) = -\sin 1000t$

$$V_2(s) = -\frac{1000}{s^2 + 10^6}$$

Since $I_1(s) = I_2(s)$ (by KCL), we have

$$\frac{V_1(s) - 0}{R} = \frac{0 - V_2(s)}{\frac{1}{Cs}} \quad \text{I.e., } \boxed{V_2(s) = -\frac{1}{RCs} V_1(s)}$$

Using the desired inputs and outputs, we obtain the constraint

$$-\frac{1000}{s^2 + 10^6} = -\frac{1}{RCs} \frac{s}{s^2 + 10^6} \quad (\Rightarrow) \boxed{\frac{1}{RC} = 1000}$$

If $v_c(0) \neq 0$, we have instead

$$I_1(s) = I_2(s) - C v_c(0) \quad \text{I.e.,}$$

$$\frac{V_1(s)}{R} = -\frac{V_2(s)}{\frac{1}{Cs}} - C v_c(0) \quad \text{or} \quad V_2(s) = \frac{1}{Cs} \left(\frac{V_1(s)}{R} + C v_c(0) \right)$$

$$= \underbrace{\frac{1}{CRs} V_1(s)}_{\text{zero state}} + \underbrace{\frac{10}{s}}_{\text{zero input}} \quad \boxed{\text{10V}}$$