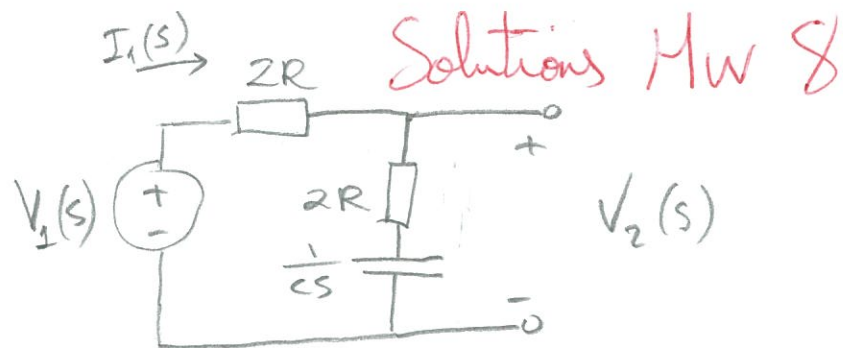


11.1



Driving point impedance (impedance seen from the source)

$$Z(s) = \frac{V_1(s)}{I_1(s)} = 2R + 2R + \frac{1}{Cs} = \frac{4RCs + 1}{Cs}$$



To compute $T_V(s) = \frac{V_2(s)}{V_1(s)}$ we do

$$V_2(s) = I_1 \cdot \left(2R + \frac{1}{Cs}\right) = \frac{V_1(s)}{Z(s)} \cdot 2R + \frac{1}{Cs}$$

$$= \frac{2R + \frac{1}{Cs}}{Z(s)} V_1(s) = \frac{Cs \left(2R + \frac{1}{Cs}\right)}{4RCs + 1} \overset{V_1(s)}{=} \boxed{\frac{2RCs + 1}{4RCs + 1}} V_1(s)$$

Alternatively, you can compute $\frac{V_2(s)}{V_1(s)}$ using voltage division.

11.7

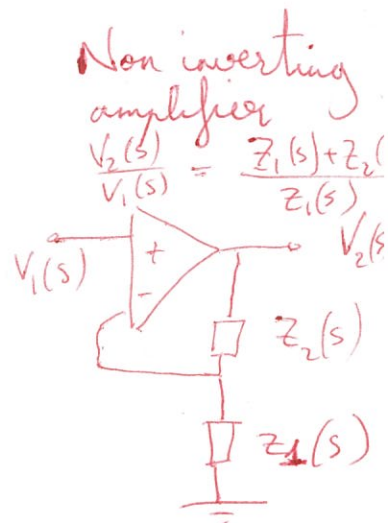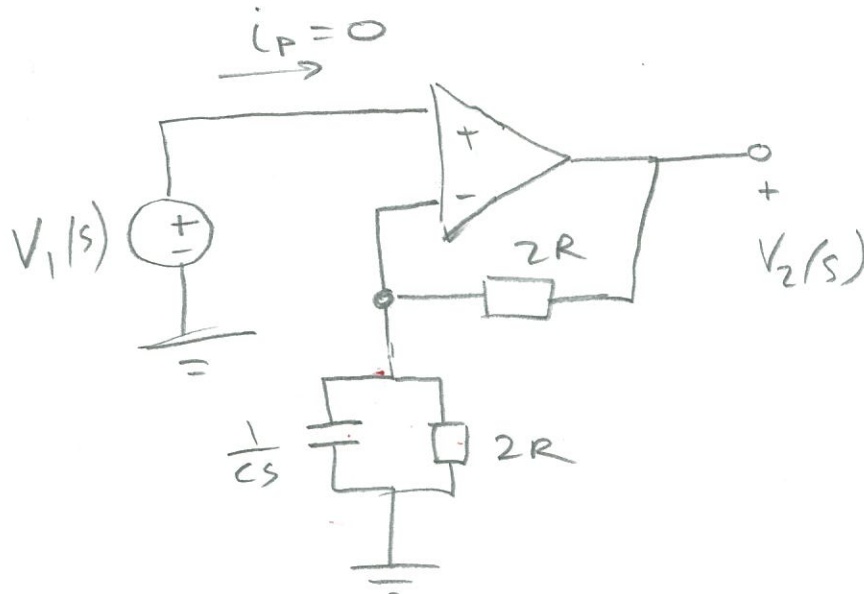

Non inverting amplifier with $Z_2(s) = 2R$ and $Z_1(s) = \frac{1}{cs + \frac{1}{2R}}$
(Mauricio's notes)

$$T_V(s) = \frac{V_2(s)}{V_1(s)} \stackrel{P.156}{=} \frac{Z_1(s) + Z_2(s)}{Z_1(s)} = 1 + \frac{Z_2(s)}{Z_1(s)}$$

$$= 1 + \frac{2R}{\frac{1}{cs + \frac{1}{2R}}} = 1 + (cs + \frac{1}{2R}) 2R$$


$$= 1 + 2RCs + 1 = 2 + 2RCs$$

This is what we've been doing with resistive circuits and we called gain.

The driving point impedance (impedance seen from the source) is ∞ because $i_P = 0$, i.e.,

$$0 = I_P(s) = \frac{V_1(s)}{Z(s)} \Rightarrow Z(s) = \infty$$

11.14

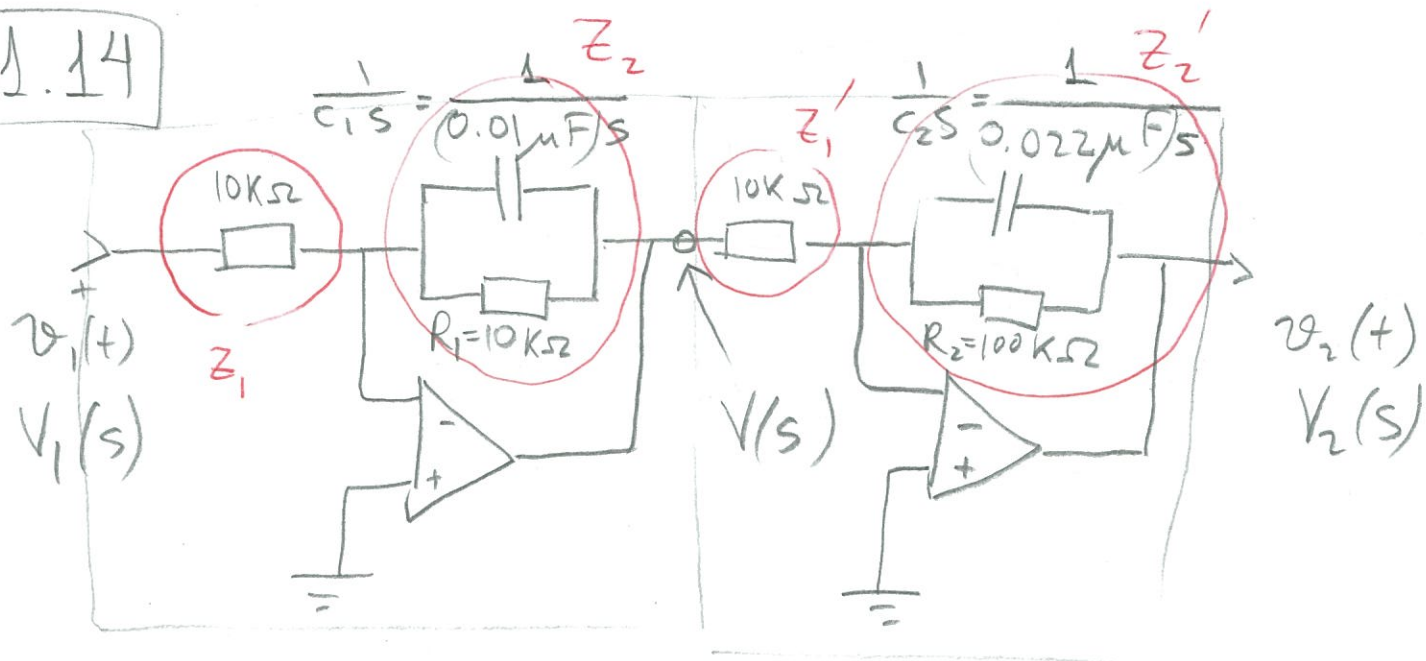

Chain rule for two inverting amplifiers

Mauricio's notes r.155

$$\frac{V(s)}{V_1(s)} = - \frac{Z_2(s)}{Z_1(s)} ; \frac{V_2(s)}{V(s)} = - \frac{Z_2'(s)}{Z_1'(s)}$$

$$T_V = \frac{V(s)}{V_1(s)} \frac{V_2(s)}{V(s)} = \left(- \frac{Z_2(s)}{Z_1(s)} \right) \left(- \frac{Z_2'(s)}{Z_1'(s)} \right)$$


$$= \frac{1}{C_1 s + \frac{1}{R_1}} \frac{1}{C_2 s + \frac{1}{R_2}} = \left(\begin{array}{l} \text{Farad} = \frac{\text{sec}}{\text{ohm}} \\ 1 \text{ mF} = \frac{\text{sec}}{\text{K}\Omega} \end{array} \right) \begin{array}{l} C_1 = 10 \text{ mF} \\ C_2 = 22 \text{ mF} \\ R_1 = 10 \text{ K}\Omega \\ R_2 = 100 \text{ K}\Omega \end{array}$$

$$= \frac{1}{100 (C_1 s + \frac{1}{R_1}) (C_2 s + \frac{1}{R_2})} = \frac{1}{\frac{100}{C_1 C_2} (s + \frac{1}{R_1 C_1}) (s + \frac{1}{C_2 R_2})}$$

Poles: $-\frac{1}{R_1 C_1} = -\frac{1}{10 \cdot 10} = \boxed{-\frac{1}{100} \frac{1}{\text{sec}}}$; $-\frac{1}{C_2 R_2} = -\frac{1}{22 \cdot 100} = \boxed{-\frac{1}{2200} \frac{1}{\text{sec}}}$

Zeros: two at ∞ .

12 6

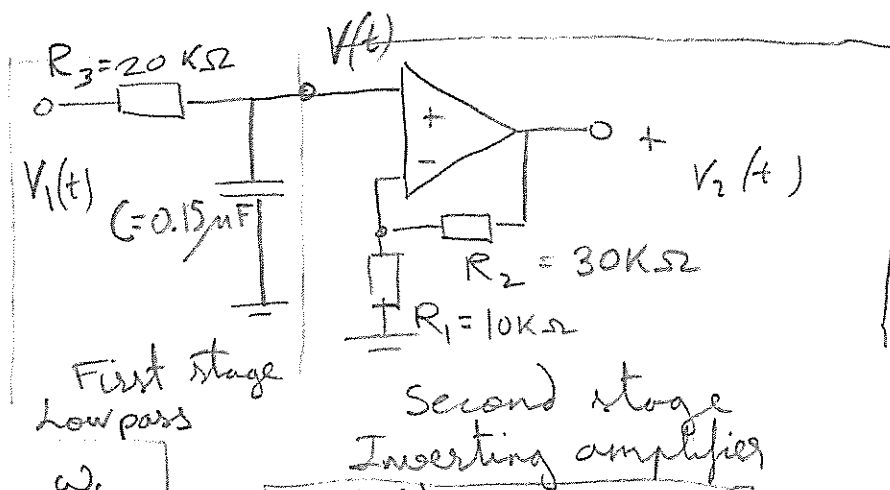

$$\frac{V(s)}{V_1(s)} = \frac{\omega_c}{\omega_c + s}$$

with $\omega_c = \frac{1}{CR_3}$

$$\frac{V_2(s)}{V(s)} = -\frac{R_2}{R_1}$$

$$T(s) = \frac{V_2(s)}{V_1(s)} = \frac{V(s)}{V_1(s)} \frac{V_2(s)}{V(s)} = \frac{\omega_c}{\omega_c + s} \left(-\frac{R_2}{R_1} \right)$$

• dc gain = $|T(0)| = \left| -\frac{R_2}{R_1} \frac{\omega_c}{\omega_c + 0} \right| = \boxed{\frac{R_2}{R_1}}$

$$|T(j\omega)| = \frac{\omega_c R_2}{R_1} \left| \frac{1}{\omega_c + j\omega} \right| = \frac{\omega_c R_2}{R_1} \frac{1}{\sqrt{\omega_c^2 + \omega^2}}$$

• infty frequency gain = $\lim_{\omega \rightarrow \infty} \frac{\omega_c R_2}{R_1} \frac{1}{\sqrt{\omega_c^2 + \omega^2}} = \boxed{0}$


• Cut off frequency = $\boxed{\omega_c}$ because this is the frequency such that $|T(j\omega_c)| = \frac{\sqrt{2}}{2} |T(0)|$

and ω_c is the cut off frequency of $\frac{\omega_c}{\omega_c + s}$ (note that $\left| \frac{\omega_c}{\omega_c + j\omega_c} \right| = \frac{1}{\sqrt{2}} = \frac{\sqrt{2}}{2}$).

• It is a low-pass filter

12.6 continued

$$\log(|T(0)|) = \log \frac{R_2}{R_1} = \log 3$$

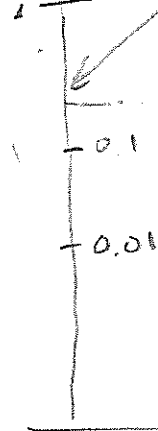

$$\omega_c = \frac{1}{CR_3} = \frac{1}{0.15 \mu F \cdot 20 K \Omega} = \frac{1}{3 \times 10^{-6} s \cdot 20 \cdot 10^3 \Omega} = \frac{1}{60 \cdot 10^{-3} s}$$

For $\alpha = 0.1, 1, 10$

$$|T(j\alpha\omega_c)| = \frac{\omega_c R_2}{R_1} \frac{1}{\sqrt{\omega_c^2 + \alpha^2 \omega_c^2}} = \frac{\omega_c R_2}{R_1} \frac{1}{\omega_c \sqrt{1 + \alpha}}$$

$$= \frac{R_2}{R_1} \frac{1}{\sqrt{1 + \alpha}} \text{ so we just need to evaluate}$$

$$\text{at } \alpha = 0.1, 1, 10 \text{ to get } \frac{R_2}{R_1} \frac{1}{\sqrt{1.1}}, \frac{R_2}{R_1} \frac{1}{\sqrt{2}}, \frac{R_2}{R_1} \frac{1}{\sqrt{11}}$$

e) Double the passband gain without changing the cutoff frequency.

$$\text{We knew that } |T(0)| = \frac{R_2}{R_1}$$


$$\text{whereas the cutoff frequency is } \omega_c = \frac{1}{CR_3}$$

$$\text{Therefore, we just need to take } \boxed{\hat{R}_2 = 2R_2}$$

$$f) \text{ Slope } \frac{R_2}{R_1} \cdot (-20 \text{ dB per decade}), \text{ so}$$

$$\text{it is } -20 \frac{R_2}{R_1} \text{ dB less} = -60 \text{ dB less.}$$

12.7

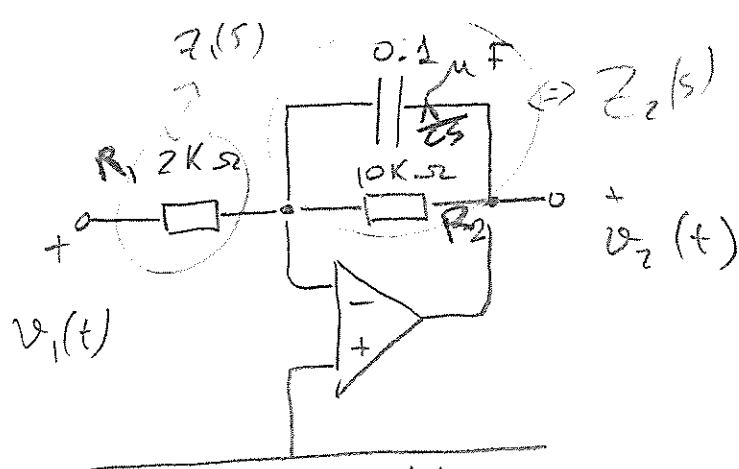

Inverting amplifier

$$\frac{V_2(s)}{V_1(s)} = \frac{Z_2(s)}{Z_1(s)} = \frac{\frac{1}{Cs + \frac{1}{R_2}}}{R_1} = \frac{1}{CR_1 s + \frac{R_1}{R_2}} =$$

multiplying and dividing by R_2





$$= \frac{1}{CR_1} \frac{1}{s + \frac{1}{CR_2}} = \frac{R_2}{R_1} \frac{1}{s + \frac{1}{CR_2}}$$

$$= \frac{R_2}{R_1} \frac{\frac{1}{CR_2}}{s + \frac{1}{CR_2}} = \frac{R_2}{R_1} \frac{\omega_c}{s + \omega_c} \quad \text{with } \omega_c = \frac{1}{CR_1}$$

This is the same as in 12.6 except for the sign and the specific numerical values.

The sign changes the phase but not $|T(j\omega)|$


12.9

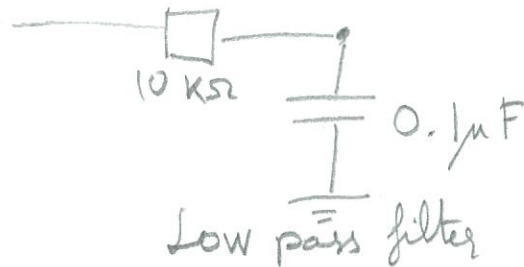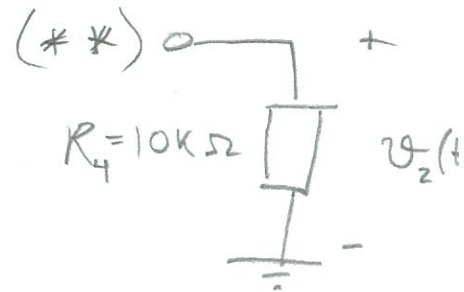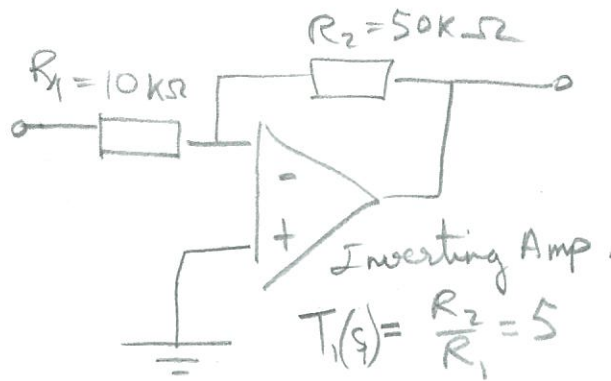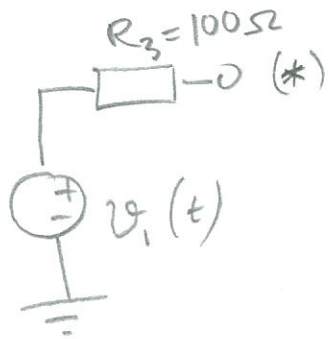

$$T_2(s) = \frac{\omega_c}{s + \omega_c} ; \omega_c = \frac{1}{R_c} = \frac{1}{0.1 \cdot 10^{-6} \frac{s}{\Omega} \cdot 10^3 \Omega} = 10^{-3} \frac{1}{s}$$


The problem is that R_4 is not ∞ (withdraws current) and R_3 is not 0 (part of the voltage $v_1(t)$ drops at R_3)

We saw in class the trick of using

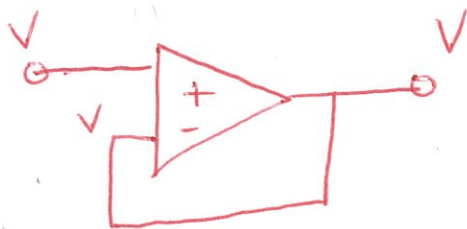

in the interfaces (*) and (**).

12.35

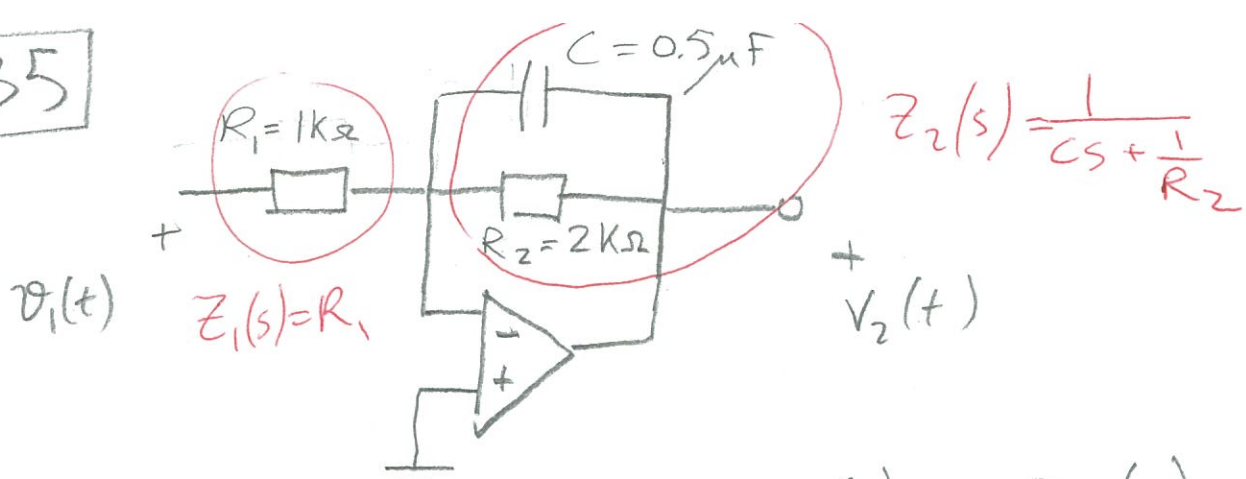

Inverting amplifier: $T(s) = \frac{V_2(s)}{V_1(s)} = -\frac{Z_2(s)}{Z_1(s)}$

$$= -\frac{\frac{1}{Cs + \frac{1}{R_2}}}{R_1} = -\frac{1}{R_1 Cs + \frac{R_1}{R_2}} = -\frac{1}{R_1 C} \frac{1}{s + \frac{1}{R_2 C}}$$

$$T(j\omega) = +\frac{1}{R_1 C} \frac{e^{i\pi}}{j\omega + \frac{1}{R_2 C}} = \frac{1}{R_1 C} \frac{e^{i\pi}}{\sqrt{\omega^2 + \frac{1}{R_2^2 C^2}}} e^{i \tan^{-1}(\frac{\omega}{1/R_2 C})}$$

$$= \frac{1}{R_1 C \sqrt{\omega^2 + \frac{1}{R_2^2 C^2}}} e^{i(\pi - \tan^{-1}(\omega R_2 C))} = |T(j\omega)| e^{i\angle T(j\omega)}$$

" $(T(j\omega))$

$$|T(j\omega)| = \frac{1}{R_1 C \sqrt{\omega^2 + \frac{1}{R_2^2 C^2}}} = \frac{1}{10^3 \times 5 \times 10^{-7} \frac{\text{sec}}{\Omega} \sqrt{\omega^2 + \left(\frac{1}{2 \times 10^3 \times 5 \times 10^{-7} \frac{\text{sec}}{\Omega}}\right)^2}}$$

FOR CONVENIENCE $\omega = \alpha \times 10^3$


$$= \frac{1}{5 \times 10^{-4} \frac{1}{\text{sec}} \sqrt{\omega^2 + 10^6 \frac{1}{\text{sec}^2}}} = \frac{2}{5 \times 10^{-4} \sqrt{\alpha^2 10^6 + 10^6}} = \frac{2}{\sqrt{1 + \alpha^2}}$$

$$\angle T(j\omega) = \pi - \tan^{-1}(\omega R_2 C) = \boxed{\pi - \tan^{-1}(\omega 10^{-3})}$$

so $v_2(t) = A \cos \omega t \Rightarrow v_{2ss} = A |T(j\omega)| \cos(\omega t + \angle T(j\omega))$

$10 \cos 500 t$	$\omega = 500 = 0.5 \times 10^3$	$10 \frac{2}{\sqrt{1+0.5^2}} \cos(\omega t + \pi - \tan^{-1}(\frac{1}{2}))$
$10 \cos 10^3 t$	$\omega = (1) \times 10^3$	$10 \frac{2}{\sqrt{2}} \cos(\omega t + \pi - \tan^{-1}(1))$
$10 \cos 10^4 t$	$\omega = (10) \times 10^3$	$10 \frac{2}{\sqrt{101}} \cos(\omega t + \pi - \tan^{-1}(10))$

11.36

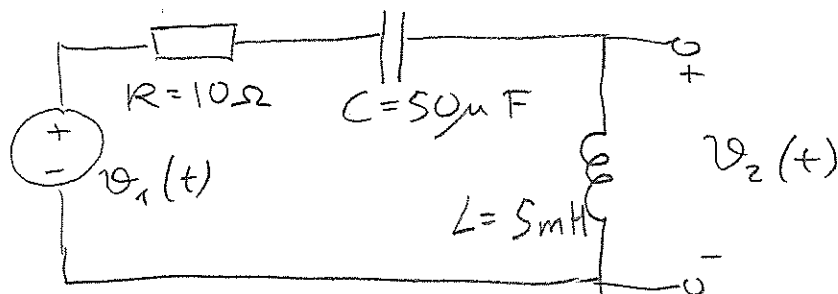

Voltage divider in s-domain

$$T(s) = \frac{V_2(s)}{V_1(s)} = \frac{Ls}{R + \frac{1}{Cs} + Ls} = \frac{LCs^2}{RCs + 1 + Lcs^2}$$

$$= \frac{s^2}{\frac{1}{LC} + \frac{R}{L}s + s^2} = \frac{s^2}{\frac{1}{5 \times 10^{-3} \times 50 \times 10^{-6}} + \frac{10}{5 \times 10^{-6}}s + s^2} = \frac{s^2}{\frac{10^8}{25} + \frac{10^7}{5}s + s^2}$$

$$= \frac{s^2}{4 \times 10^6 + 2 \times 10^6 s + s^2} \quad \text{[with poles approx. } -2 \times 10^6 \text{ and } 0]$$

$$T(j\omega) = \frac{1}{10^6} \frac{-\omega^2}{4 + 2j\omega - \frac{\omega^2}{10^6}} = \frac{1}{10^6} \frac{-\omega^2}{4 - \frac{\omega^2}{10^6} + j2\omega}$$

$$= \frac{1}{10^6} \frac{\omega^2 e^{i\pi}}{\sqrt{(4 - \frac{\omega^2}{10^6})^2 + 4\omega^2}} e^{i \tan^{-1}\left(\frac{2\omega}{4 - \frac{\omega^2}{10^6}}\right)}$$

$$\text{so } |T(j\omega)| = \frac{1}{10^6} \frac{\omega^2}{\sqrt{(4 - \frac{\omega^2}{10^6})^2 + 4\omega^2}}$$

$$\text{and } \angle T(j\omega) = \left| \pi - \tan^{-1}\left(\frac{2\omega}{4 - \frac{\omega^2}{10^6}}\right) \right|$$

$$v(t) = A \cos(\omega t) \Rightarrow A |T(j\omega)| \cos(\omega t + \angle T(j\omega))$$

$$v_1(t) = 25 \cos(2000t) \Rightarrow$$

see next page

$$v_2(t) = 25 \cos(10^4 t) \Rightarrow$$

We need to evaluate $|T(j\omega)|$ and $\angle T(j\omega)$
at $\omega = \alpha 10^3$ for $\alpha = 2, 10$.

$$T(j\alpha 10^3) = \frac{1}{10^6} \frac{\alpha^2 10^6}{\sqrt{(4-\alpha^2)^2 + 4\alpha^2 10^6}} \approx \frac{\alpha^2}{2\alpha 10^3} = \frac{\alpha}{2000}$$

$$\begin{aligned} \angle T(j\alpha 10^3) &= \pi - \tan^{-1}\left(\frac{2\alpha 10^3}{4-\alpha^2}\right) \\ &= \begin{cases} \pi - \tan^{-1}(\infty) = \pi - \frac{\pi}{2} \text{ if } \alpha = 2 \\ \pi - \tan^{-1}\left(\frac{2 \times 10 \times 10^3}{4-100}\right) \approx \pi - \tan^{-1}\left(\frac{2 \times 10^4}{-100}\right) \\ = \pi + \tan^{-1}(200) \text{ if } \alpha = 10 \end{cases} \end{aligned}$$

$$v(t) = A \cos \omega t \Rightarrow v_{ss} = A |T(j\omega)| \cos(\omega t + \angle T(j\omega))$$

$$v_1(t) = 25 \cos 2000t \Rightarrow v_{2ss}(t) = \frac{25}{1000} \cos(2000t + \pi - \frac{\pi}{2})$$

$$v_2(t) = 25 \cos 10^4 t \Rightarrow v_{2ss}(t) = \frac{25}{200} \cos(2000t + \pi + \tan^{-1}(200))$$

12.45 $T(s) = \frac{10(s+100)}{s+1}$

See next page for a shorter version.

The standard form for a Bode plot is

$$T(j\omega) = \frac{10 \times 100 \left(\frac{j\omega}{100} + 1 \right)}{j\omega + 1} = 10^3 \frac{1 + \frac{j\omega}{100}}{1 + j\omega}$$

The scale factor is $K_0 = 10^3$ and the corner

frequencies $\omega_c = 1$ (because there is a pole at -1)


and $\omega_c = 100$ (because there's a zero at -100)

At low frequency (for $\omega < 1$ because that is the first corner) we have $|T(j\omega)| \approx 10^3 \frac{1}{1} = 10^3$ so the low frequency baseline is $|T(j\omega)|_{SL} = 10^3$ for $\omega \leq 1$.

At $\omega = 1 \text{ rad/s}$, we encounter the pole -1, so the slope changes by -1 (or -20 dB/decade). The straight line gain becomes $|T(j\omega)|_{SL} = 10^3 \frac{1}{\omega}$ for $\omega \in [1, 100]$.

At $\omega = 100 \text{ rad/s}$, we encounter the zero -100, so the slope changes by $+1$ (or 20 dB/decade). I.e., the plot becomes horizontal. After this point the gain contribution, due to the factor $1 + \frac{j\omega}{100}$ is represented by the high frequency asymptote $\frac{\omega}{100}$ and $|T(j\omega)|_{SL} = 10^3 \frac{1}{\omega} \cdot \frac{\omega}{100} = 10$. See next page

$$|T(j\omega)|_{SL} = \begin{cases} 10^3 & \text{if } 0 < \omega < 1 \\ \frac{10^3}{\omega} & \text{if } 1 < \omega < 100 \\ 10 & \text{if } 100 < \omega \end{cases}$$

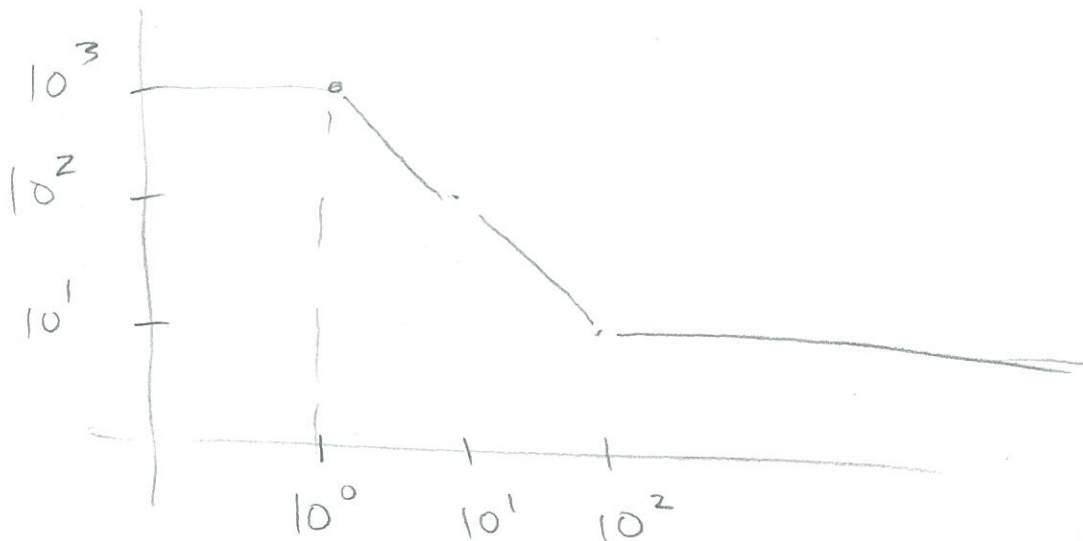

THIS IS WHAT YOU NEED TO KNOW

Alternatively, we compute

$$|T(j\omega)| = 10 \frac{|j\omega + 100|}{|j\omega + 1|} = 10 \frac{\sqrt{\omega^2 + 100^2}}{\sqrt{\omega^2 + 1}}$$

and compute limits:


$$|T(0)| = 1000$$

$$\lim_{\omega \rightarrow \infty} |T(j\omega)| = 10$$

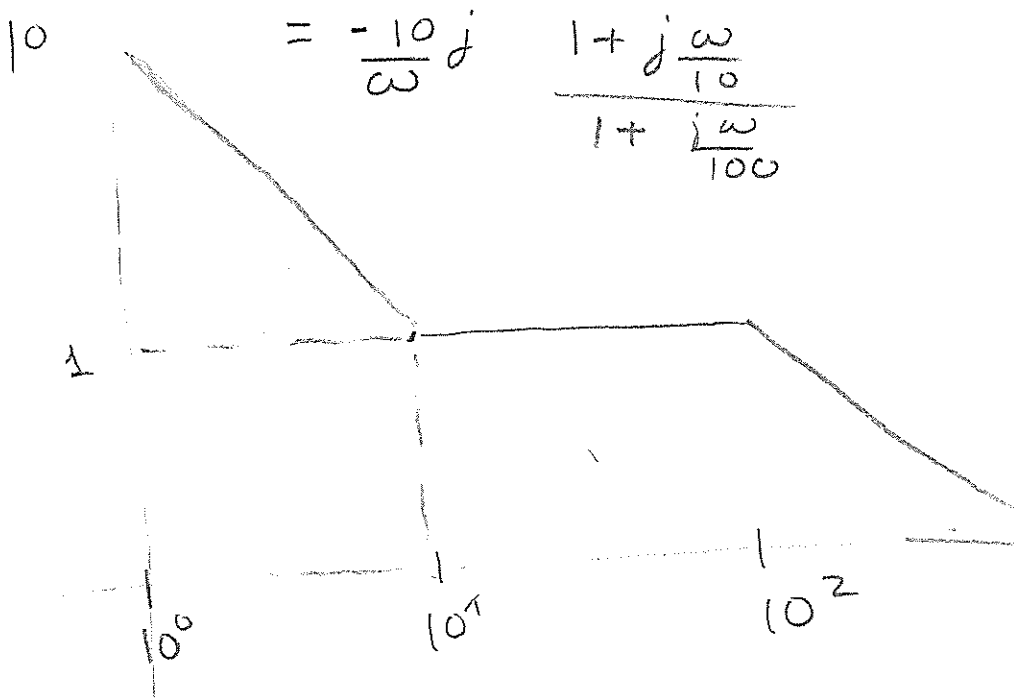12.46

$$T(s) = \frac{100(s+10)}{s(s+100)}$$

$$T(j\omega) = \frac{100 \times 10}{j\omega \times 100} \frac{(1 + j\frac{\omega}{10})}{1 + j\frac{\omega}{100}}$$



$$|T(j\omega)| = \begin{cases} \frac{10}{\omega} & \text{if } 0 < \omega < 10 \\ \frac{10}{\omega} \cdot \frac{\omega}{10} = 1 & \text{if } 10 < \omega < 100 \\ 1 / (\frac{\omega}{100}) = \frac{100}{\omega} & \text{if } 100 < \omega \end{cases}$$

Q? you can compute

$$|T(j\omega)| = 100 \frac{|j\omega + 10|}{|j\omega| |j\omega + 100|} = 100 \frac{\sqrt{\omega^2 + 10^2}}{\omega \sqrt{\omega^2 + 100^2}}$$

so $\lim_{\omega \rightarrow \infty} |T(j\omega)| = 0$ and $\lim_{\omega \rightarrow 0} |T(j\omega)| = \infty$