

MAE140 – Linear Circuits – Fall – 2019
Final, December 12th

Instructions

1. This exam is open book. You may use whatever written materials you choose, including your class notes and textbook. You may use a handheld calculator with no communication capabilities.
2. You have 170 minutes.
3. Do not forget to write your name and student number.
4. This exam has 6 questions, for a total of 60 points.

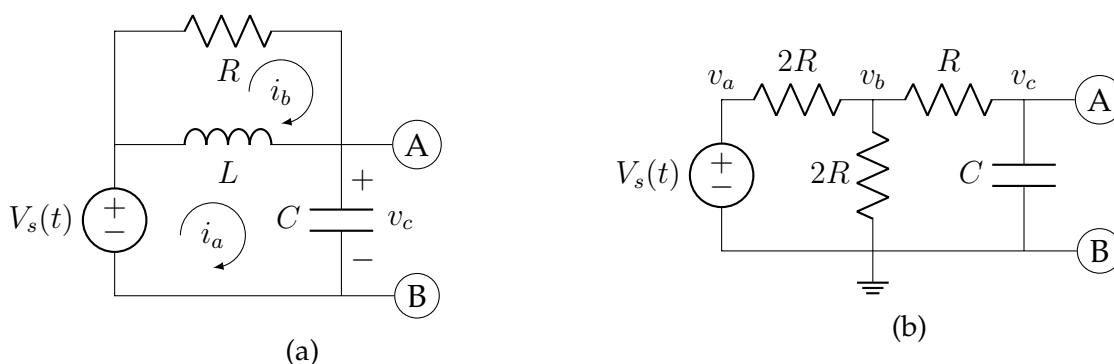


Figure 1: Circuits for Questions 1-3

1. Circuit Equivalence - Part I

Consider the circuit in Fig. 1a and answer the following questions:

- (a) (1 point) Assume zero initial conditions and convert the circuit into the s -domain.
- (b) (3 points) Calculate the s -domain open-circuit voltage at (A) and (B).
- (c) (3 points) Calculate the s -domain short-circuit current at (A) and (B).
- (d) (2 points) Calculate the equivalent impedance as seen from (A) and (B).
- (e) (1 point) Draw the s -domain Thevenin equivalent for the circuit in Fig. 1a.

2. Circuit Equivalence - Part II

Consider the circuit in Fig. 1b and answer the following questions:

- (a) (1 point) Assume zero initial conditions and convert the circuit into the s -domain.
- (b) (3 points) Calculate the s -domain open-circuit voltage at (A) and (B).
- (c) (3 points) Calculate the s -domain short-circuit current at (A) and (B).
- (d) (2 points) Calculate the equivalent impedance as seen from (A) and (B).
- (e) (1 point) Draw the s -domain Thevenin equivalent for the circuit in Fig. 1b.

3. Circuit Analysis

- (a) (4 points) Do not assume zero-initial conditions, convert the circuit in Fig. 1a to the s -domain and formulate its mesh-current equations. Express the component's initial conditions in terms of the indicated mesh-currents and voltage. Use the mesh-currents and labels provided in the figure and clearly indicate the final equations and circuit variable unknowns. Make sure your final equations only involve mesh-currents.
- (b) (5 points) Do not assume zero-initial conditions, convert the circuit in Fig. 1b to the s -domain and formulate its node-voltage equations. Express the component's initial conditions in terms of the indicated node-voltages. Use the node-voltages and labels provided in the figure and clearly indicate the final equations and circuit variable unknowns. Make sure your final equations only involve node-voltages.
- (c) (1 point) Write s -domain expressions for the voltage $\textcircled{A}$ and $\textcircled{B}$ in terms of the node voltages and mesh currents from parts (a) and (b).

4. Frequency Response

Consider the transfer-function:

$$T(s) = \frac{10s^2}{s^2 + s 200 + 10,000}$$

and answer the following questions:

- (a) (2 points) What are the poles and zeros of $T(s)$?
 - (b) (1 point) Is $T(s)$ asymptotically stable?
 - (c) (4 points) Evaluate $|T(j\omega)|$ and $\angle T(j\omega)$ at $\omega = \{0, 100, \infty\}$.
 - (d) (2 points) Sketch the functions $|T(j\omega)|$ and $\angle T(j\omega)$ for $\omega \geq 0$.
 - (e) (1 point) What type of filter is $T(s)$?
5. (10 points) **OpAmp Design**

Consider the transfer-function:

$$T(s) = \frac{10s^2}{s^2 + s 200 + 10,000}$$

from Question 4 and design a circuit using opAmps that implements $T(s)$.

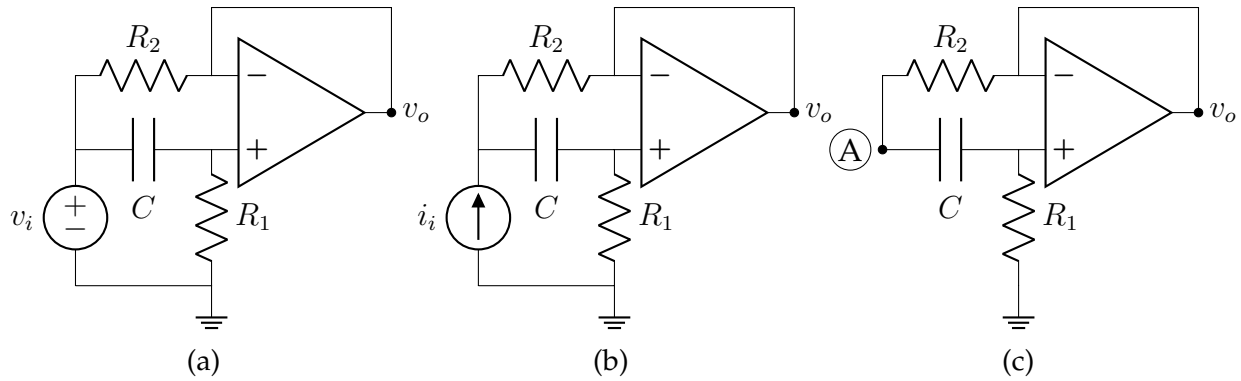


Figure 2: Circuits for Question 6

6. OpAmp Analysis

Assume zero initial-conditions for the circuits in Fig. 2 and answer the questions:

(a) (3 points) For the circuit in Fig. 2a show that

$$\frac{V_o(s)}{V_i(s)} = \frac{s}{s + \frac{1}{R_1 C}}.$$

(b) (3 points) For the circuit in Fig. 2b show that

$$\frac{V_o(s)}{I_i(s)} = \frac{s R_1}{s + \frac{1}{R_2 C}}.$$

(c) (2 points) Show that the impedance at point (A) in Fig. 2c is

$$Z(s) = R_1 \frac{s + \frac{1}{R_1 C}}{s + \frac{1}{R_2 C}}.$$

(d) (1 point) Show that

$$Z(j\omega) \approx R_2 + R_1 R_2 C j\omega$$

when $\omega \ll \frac{1}{R_2 C}$.

Hint: What is the value of

$$\frac{\frac{1}{R_2 C}}{j\omega + \frac{1}{R_2 C}}$$

when $\omega \ll \frac{1}{R_2 C}$?

(e) (1 point) Explain why the above circuit is called a “simulated inductor.”

Have a great Winter break!