

MAE140 - Linear Circuits - Fall 2019
Midterm, November 19th

Instructions

1. This exam is open book. You may use whatever written materials you choose, including your class notes and textbook. You may use a hand calculator with no communication capabilities.
2. You have 70 minutes.
3. Write your answers on your “Blue Book”.
4. Do not forget to write your name, student number, and instructor.
5. This exam has 3 questions, for a total of 23 points.

1. (6 points) OpAmp Design

Assume that sources $+V_{cc} = 12V$ and $-V_{cc} = -12V$ are available and design an opAmp circuit that implements the following operation

$$v_o = 6V + 10v_1$$

without using any voltage or current source other than v_1 and the available voltages $+V_{cc}$ and $-V_{cc}$. You can use as many opAmps as you would like.

2. (4 points) Photodetector

The circuit in Fig. 1 is used to produce a voltage in response to light. When the base of the phototransistor shown in the picture is exposed to light the transistor goes into saturation, that is it acts essentially as a short circuit. When the base is in the dark the transistor is cut, that is it is an open circuit.


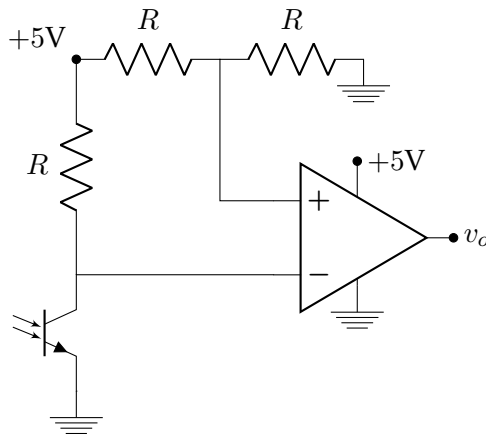
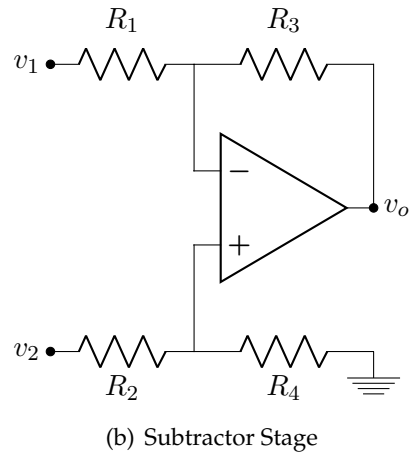


Figure 1: Phototransistor circuit

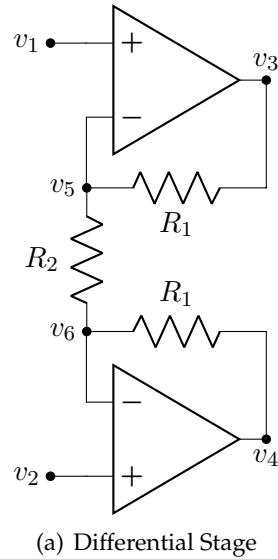Explain how the output v_o responds in the presence of a light or dark environment.



3. Instrumentation Amplifier.

In the rest of the exam you will analyze a circuit called *instrumentation amplifier*, which is made of a combination of the circuits in Figs. 2(a) and 2(b).

- (a) (5 points) Formulate node voltage analysis equations relating the voltages v_1 through v_6 in the circuit in Fig. 2(a) and use those equations to show that

$$v_3 = \left(1 + \frac{R_1}{R_2}\right) v_1 - \frac{R_1}{R_2} v_2,$$

$$v_4 = -\frac{R_1}{R_2} v_1 + \left(1 + \frac{R_1}{R_2}\right) v_2.$$

- (b) (2 points) We have shown in class that

$$v_o = \frac{R_1 + R_3}{R_1} \frac{R_4}{R_2 + R_4} v_2 - \frac{R_3}{R_1} v_1$$

for the circuit in Fig. 2(b). Show that if the circuit in Fig. 2(b) is to have a gain of the form

$$v_o = K(v_2 - v_1), \quad K > 0,$$

then

$$K = \frac{R_3}{R_1} = \frac{R_4}{R_2}.$$

- (c) (4 points) Connect the outputs v_3 and v_4 from the circuit in Fig. 2(a) to the inputs v_1 and v_2 from the circuit in Fig. 2(b). The resulting circuit is an *instrumentation amplifier*. Show that in this new circuit

$$v_o = \left(1 + 2\frac{R_1}{R_2}\right) (v_2 - v_1).$$

Clearly explain your reasoning.

- (d) (2 points) A student needs to measure a voltage out of a sensor that can be modeled as a voltage source in series with a 100Ω resistor. He intends to use either the circuit in Fig. 2(b) setup as in part (b) or the circuit you designed in part (c). Explain which circuit is better suited to this task?